

# Electronic Circuit Analysis

## UNIT - I

### Single stage and Multi stage Amplifiers

#### UNIT - I(a) : single stage Amplifiers

- ① Classification of Amplifiers
- ② Distortion in Amplifiers
- ③ Analysis of CE, CC and CB configurations with simplified Hybrid Model.
- ④ Analysis of CE Amplifier with Emitter Resistance and Emitter follower.
- ⑤ Miller's Theorem and its dual
- ⑥ Design of Single stage RC Coupled Amplifier Using BJT

#### UNIT - I(b) : Multistage Amplifiers


- ① Analysis of cascaded RC Coupled BJT amplifiers.
- ② Cascode Amplifier
- ③ Darlington Pair
- ④ Different Coupling Schemes used in Amplifiers
  - RC Coupled Amplifier
  - Transformer " "
  - Direct "

## UNIT - I (a)
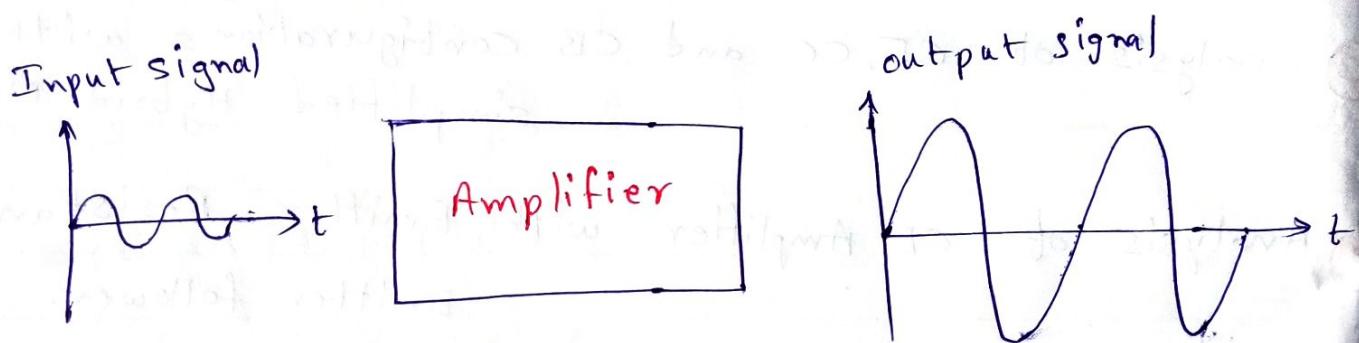
### Single stage Amplifier

Amplifier:- Amplifier is a device, which is used to amplify the applied input signal.

Amplification:- It is the process of raising the strength of a weak signal without any change in its shape along the frequency.



Example:- ① BJT (Bipolar Junction Transistor)  
② FET (Field Effect Transistor)

→ Amplifiers are used in - Essential part of Radio, TV, other communication circuit, etc.

Single stage Amplifier:- When only one Transistor with its associated circuit is used for amplifying the weak signal is known as single stage amplifier.

Multi stage Amplifier:-

An amplifier which uses

no. of stages (or) Transistors to obtain a desire amplification is known as multi stage amplifier.

### Small signal Amplifier:-

When the i/p signal is so weak as to produce a small fluctuation in the collector current compared to its operating point. This type of amplifier is known as small signal amplifier.

### Large signal Amplifier:-

When the fluctuations in the collector current is large that is beyond the linear characteristics of the amplifier. This type of amplifier is the large signal amplifier.

### Classification of Amplifiers:-

#### ① Based on Configuration

→ common Emitter Amplifier

→ " Base

→ " collector

#### ② Based on Input

→ Small signal Amplifier (**Voltage Amplifier**)

→ Large " " (**Power Amplifier**)

- ③ Based on Output
- Voltage Amplifier
  - Current "
  - Power "

- ④ Based on Frequency
- DC Amplifier (amplification from 0 Hz to 20 Hz)
  - Audio " (20 Hz - 20 KHz)
  - Video " (Amplifier up to few MHz)
  - Radio Frequency " (a few KHz to Hundreds of mHz)
  - Ultra high " " (Hundreds (or) Thousands of mHz)

- ⑤ Based on Bandwidth

- Tuned Amplifier
- Untuned "

- ⑥ Based on Stages

- single stage Amplifier
- multi "

- ⑦ Based on Coupling

- Direct coupling (DC) Amplifier
- Resistance capacitance (RC) coupled Amplifier
- Inductor - capacitor (LC) "
- Transformer coupled Amplifier

- ⑧ Based on Biasing/ Position of operating point
- class A Amplifier
  - " B " "
  - class C Amplifier
  - " AB " "

## II Distortion in Amplifier:-

The change in the o/p waveform from the i/p waveform of an amplifier is known as "distortion".

### Classification of Distortion :-

- ① Amplitude / Non-linear / Harmonic distortion
- ② Frequency distortion
- ③ Phase / Delay distortion.

### ① Amplitude / Non-linear / Harmonic distortion :-

The transistor is perfectly linear device that is the dynamic characteristics of a transistor is a straight line over the operating range [ $i_c = \beta i_b$ ]. But in practical ckt's, the dynamic characteristics is not perfectly linear. Due to such non-linearity in the dynamic char's, the waveform of the o/p voltage differs from that of the i/p signal. Such a distortion

is called "non-linear distortion" (or) "amplitude distortion".

The harmonic distortion means the presence of the frequency components in the o/p waveform, which are not present in the i/p signal. The component with freq same as the i/p signal is called fundamental freq component. The additional freq components present in the o/p signal are having freq components are called harmonic components or harmonics.

## ② Frequency Distortion:-

This type of distortion exists when the signal components of different freq's are amplified differently.

This distortion is due to the various freq dependent "reactances" (both capacitive and inductive) associated with the circuit and the active device (BJT or FET) it self.

## ③ Phase (or) Delay Distortion :-

Delay distortion is a phaseshift distortion, it results due to unusual phase shift

of signals of different frequencies.

When this distortion exists the phase angle of the gain ( $A$ ) depends upon the frequency.

### III Analysis of CE, CC and CB configurations

#### with simplified Hybrid Model :-

If  $\text{h}_{ie} R_L \ll 1$  then

the rule is satisfied

then we can proceed


for Approximate

analysis otherwise


do the exact analysis.

	CE	CC	CB
$h_i$	$1100\Omega$	$1100\Omega$	$22\Omega$
$h_{re}$	$2.5 \times 10^{-4}$	1	$3 \times 10^{-4}$
$h_{fe}$	50	-50	0.98
$h_o$	$25\text{mA/V}$	$25\text{mA/V}$	0.49

#### ① simplified CE Hybrid model :-

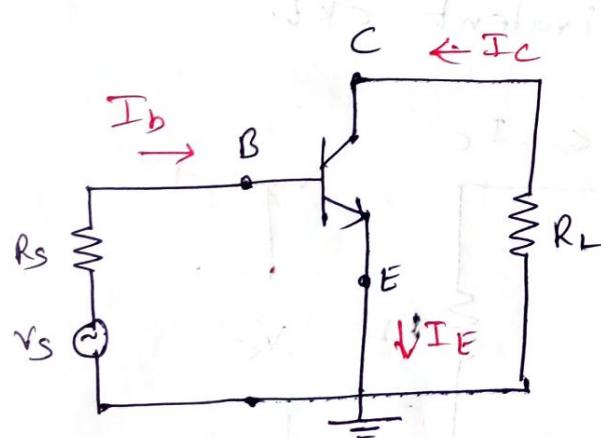

CE Transistor ckt

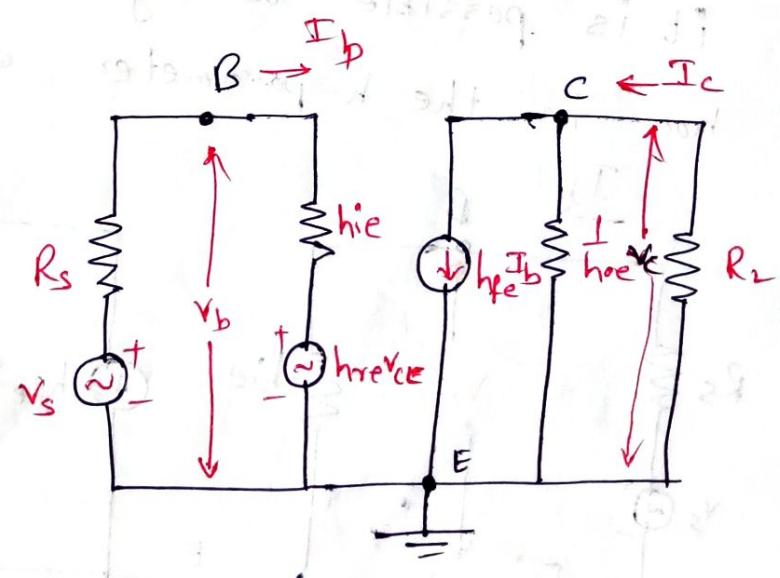

simplified CE model  
(equivalent ckt)

→ If  $\frac{1}{h_{oe}} \gg R_L \parallel R_C$ , then  $h_{oe}$  may be neglected.

→ If we neglect  $h_{oe}$  the collector current  $I_C$  is given by

$$I_C = h_{fe} I_B$$


→ Under these conditions the magnitude of the voltage of the generator in the emitter ckt

$$h_{re} |V_{CEl}| = h_{re} I_C (R_L \parallel R_C)$$

$$= h_{re} h_{fe} I_B (R_L \parallel R_C)$$

→ since  $h_{re} \cdot h_{fe} \approx 0.01$ , this voltage may be neglected in comparison with the  $h_{ie} I_B$  drop across  $h_{ie}$  provided that  $R_L \parallel R_C$  is not too large.

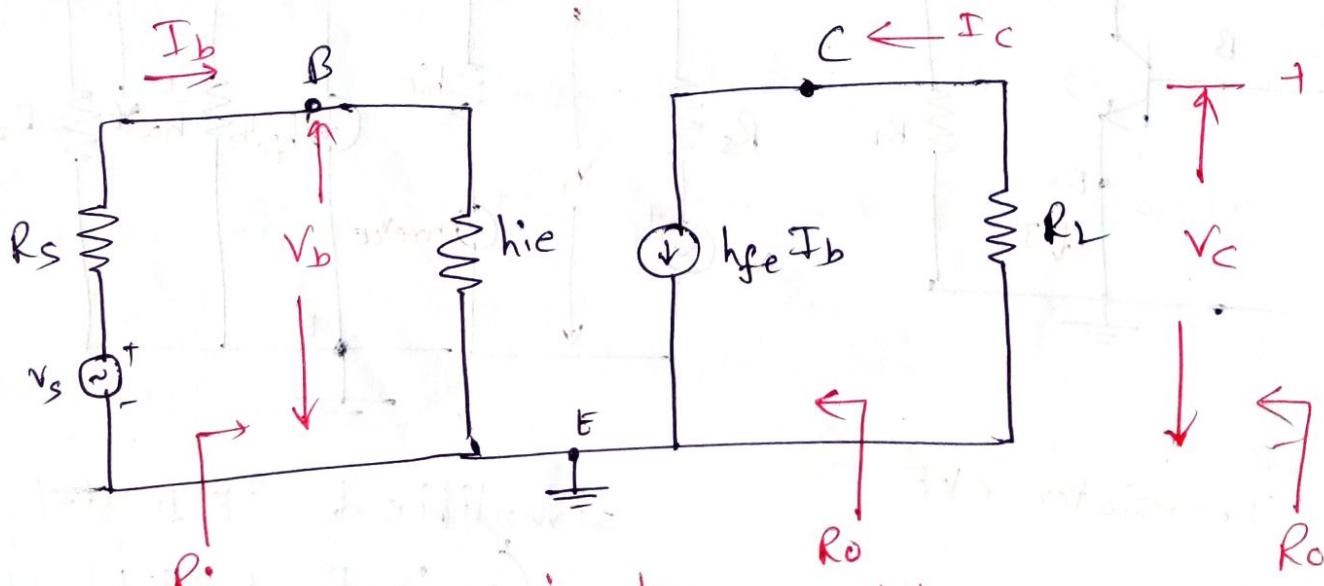→ Hence if the load resistance  $R_L \parallel R_C$  is small it is possible to neglect the parameters  $h_{re}$  &  $h_{oe}$  in the h-parameter equivalent ckt.



Approximate CE model

current gain :-  $A_i = \frac{-I_c}{I_b} = \frac{-h_{fe}}{1 + h_{oe} R_L}$

By neglecting  $h_{oe}$

$$A_i \approx -h_{fe}$$

Input Impedance :-  $R_i = h_{ie} + h_{re} A_i R_L$

By neglecting  $h_{re}$

$$R_i \approx h_{ie}$$

voltage Gain :-  $A_v = \frac{A_i R_L}{R_i}$

$$A_v = A_i \frac{R_L}{h_{ie}}$$

Output Impedance :-

$$Y_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s}$$

By neglecting  $h_{oe}$  and  $h_{re}$




$$Y_o = 0$$

$$R_o = \frac{1}{Y_o} = \frac{1}{0} = \infty$$


$$R_o' = R_o || R_L = \infty || R_L = R_L$$

$$R_o' = R_L$$

### Approximate Analysis

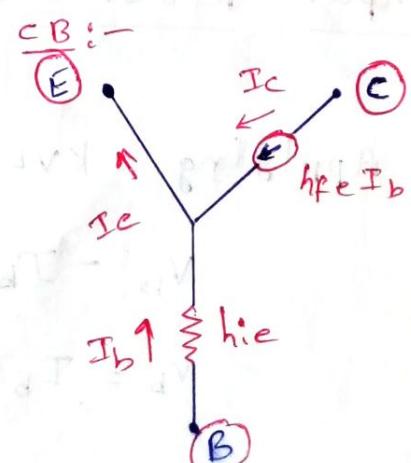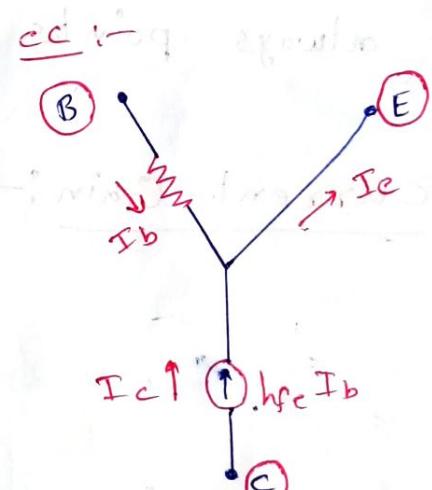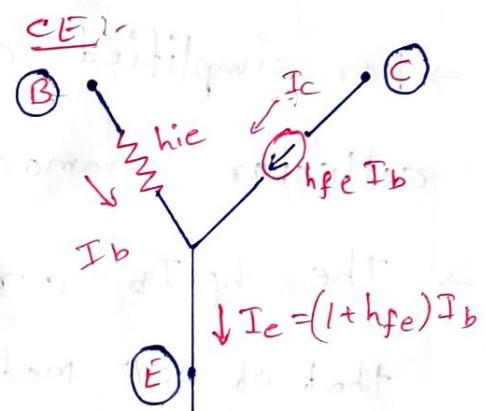

## ② simplified cc Hybrid model :-

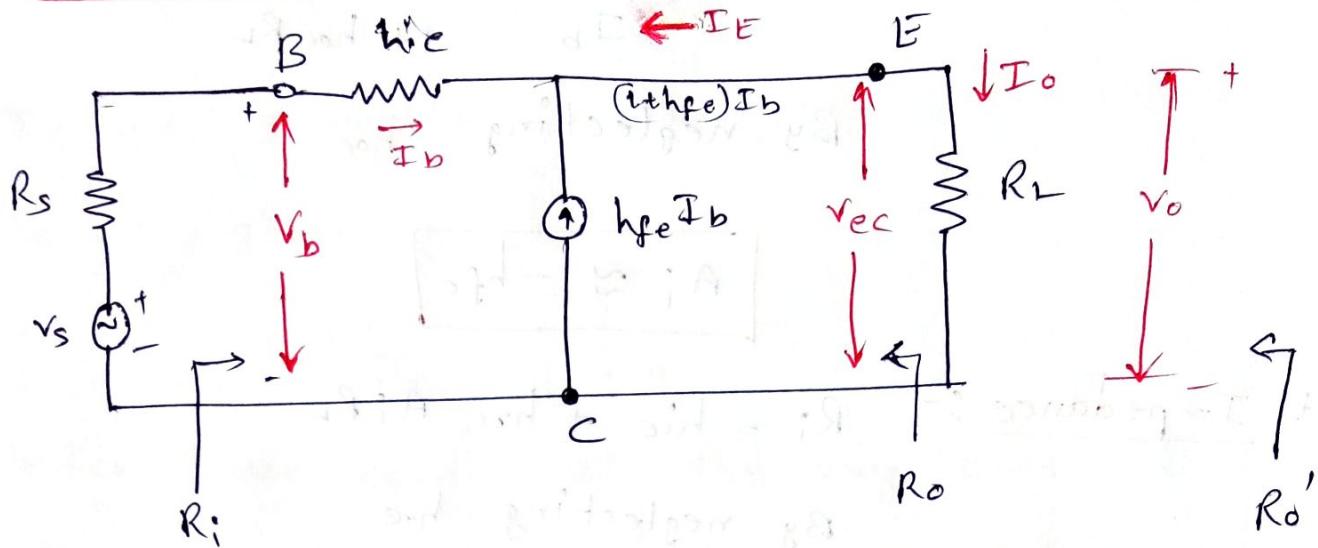

- For simplified cc model, we have to make collector common and take the o/p from emitter.
- The  $h_{FE}I_b$  current direction is now exactly opposite that of CE model because the current  $h_{FE}I_b$  always points towards emitter.

### current Gain:-

$$A_i = \frac{I_o}{I_b} = \frac{-I_e}{I_b} = \frac{(1+h_{FE})I_b}{I_b}$$

$$A_i = 1 + h_{FE}$$

Input Resistance :-  $R_i = \frac{V_b}{I_b}$

Applying KVL to the i/p ckt, we get

$$V_b - I_b h_{IE} - I_o R_L = 0$$

$$V_b = I_b h_{IE} + I_o R_L$$

$$V_b = I_b \left( h_{IE} + \frac{I_o}{I_b} R_L \right)$$

$$\frac{V_b}{I_b} = h_{ie} + \frac{I_o}{I_b} R_L$$

$$R_i = \frac{V_b}{I_b} = h_{ie} + (1+h_{fe}) R_L$$

Voltage Gain :-  $A_v = \frac{V_o}{V_b} = \frac{I_o R_L}{I_b R_i} = \frac{I_o}{I_b} \cdot \frac{R_L}{R_i}$

$$A_v = A_i \frac{R_L}{R_i}$$

Output Resistance :-  $R_o = \frac{V_o}{I_e} \Big|_{V_s=0}$

Applying KVL to the ckt, we get

$$V_s - I_b R_s - I_b h_{ie} - V_o = 0$$

$$V_o = - I_b R_s - I_b h_{ie} \quad [V_s = 0]$$

$$V_o = - I_b (R_s + h_{ie})$$

Emitter current,  $I_e = -(1+h_{fe}) I_b$


$$R_o = \frac{V_o}{I_e} = \frac{- I_b (R_s + h_{ie})}{-(1+h_{fe}) I_b}$$

$$R_o = \frac{R_s + h_{ie}}{1+h_{fe}}$$

$$R_o' = R_o || R_L$$
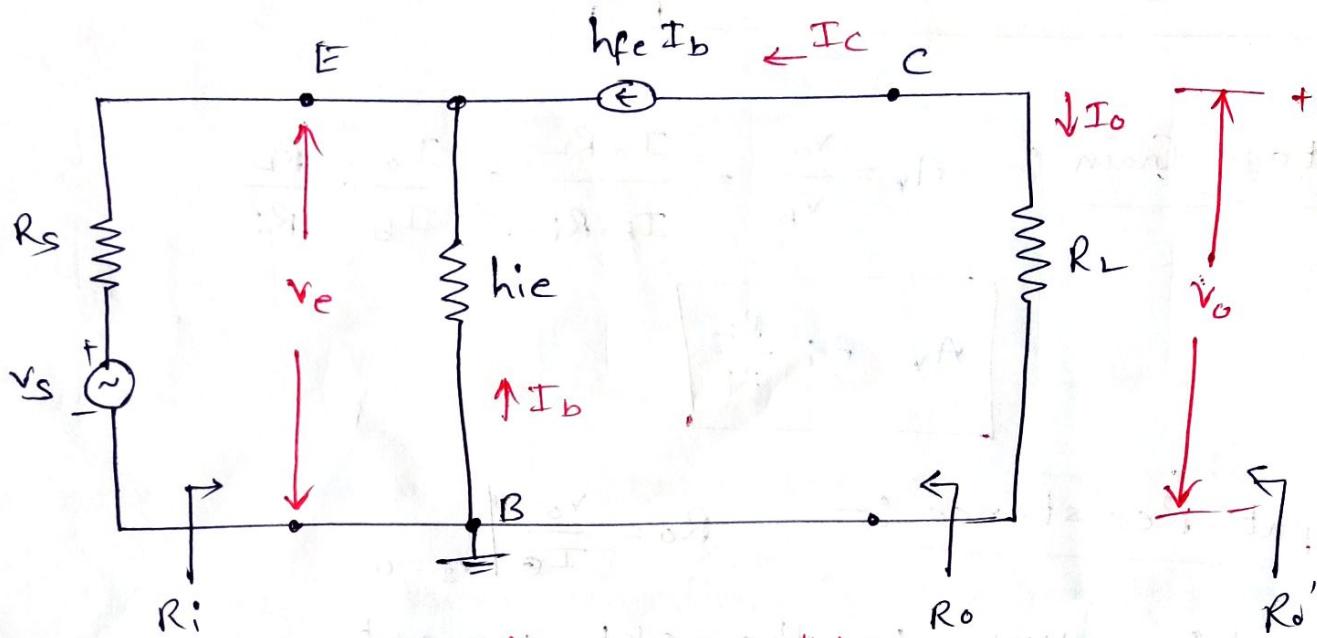
### ③ Simplified CB Hybrid Model :-

In this ckt, giving ilp to emitter, taking olp from collector & making base common.



simplifier CB model

Current Gain :-

$$A_{if} = \frac{I_o}{I_e} = \frac{-I_c}{I_e} = \frac{-hfe I_b}{(1+hfe) I_b}$$

$$A_i = \frac{hfe}{1+hfe}$$

Input Resistance :-

$$R_i = \frac{v_e}{I_e}$$

$$v_e = -hie I_b$$

$$I_e = -(1+hfe) I_b$$

$$R_i = \frac{v_e}{I_e} =$$

$$= \frac{-hie I_b}{-(1+hfe) I_b}$$

$\Rightarrow$

$$R_i = \frac{hie}{1+hfe}$$

## Voltage Gain :-

$$A_v = \frac{V_o}{V_e} = \frac{I_o R_L}{I_e R_i} = \frac{I_o}{I_e} \cdot \frac{R_L}{R_i}$$

$$A_v = A_i \cdot \frac{R_L}{R_i}$$

substituting value of  $A_i$  &  $R_i$  we get

$$A_v = \frac{h_{fe}}{1+h_{fe}} \cdot \frac{R_L}{\frac{h_{ie}}{1+h_{fe}}} = \frac{h_{fe} \cdot R_L}{h_{ie}}$$

$$A_v = \frac{h_{fe} \cdot R_L}{h_{ie}}$$

## Output Resistance :-

$$R_o = \frac{V_o}{I_c} \Big|_{v_s=0}$$

when  $v_s=0$ , the current through i/p loop  $I_b=0$ ,

hence  $I_c=0$  and  $R_o=\infty$

$$R_o' = R_{o1} || R_L = \infty || R_L = R_L$$

$$R_o' = R_L$$


Problem ①:- consider a single

stage CE amp with  $R_s=1k\Omega$ ,

$$R_1=50k, R_2=2k, R_C=2k, R_L=2k,$$


$$R_E=2k, h_{fe}=50, h_{ie}=1.1k$$
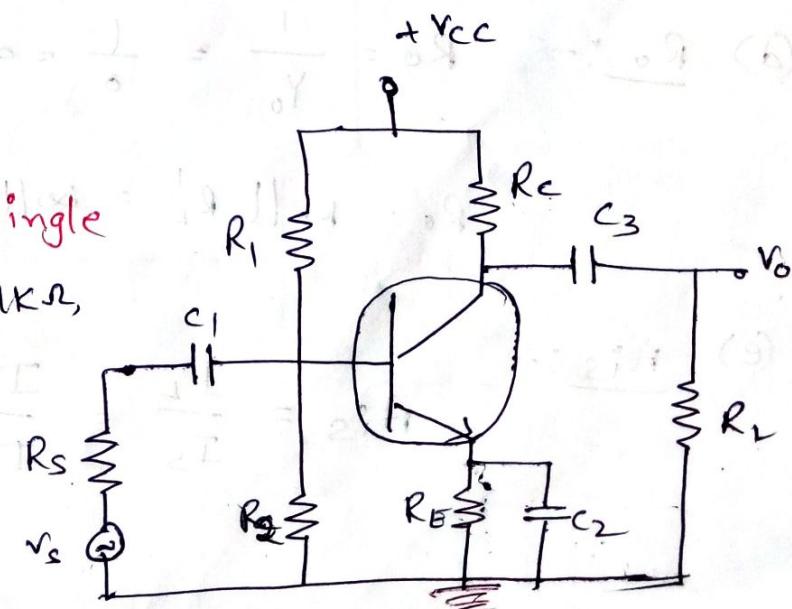
$$h_{oc}=25\mu A/V \text{ and } h_{re}=2.5 \times 10^{-4}$$



Find  $A_i$ ,  $R_i$ ,  $A_v$ ,  $R_o$ ,  $A_{is} = \frac{I_L}{I_S}$  and  $A_{vs} = \frac{V_o}{V_s}$ .

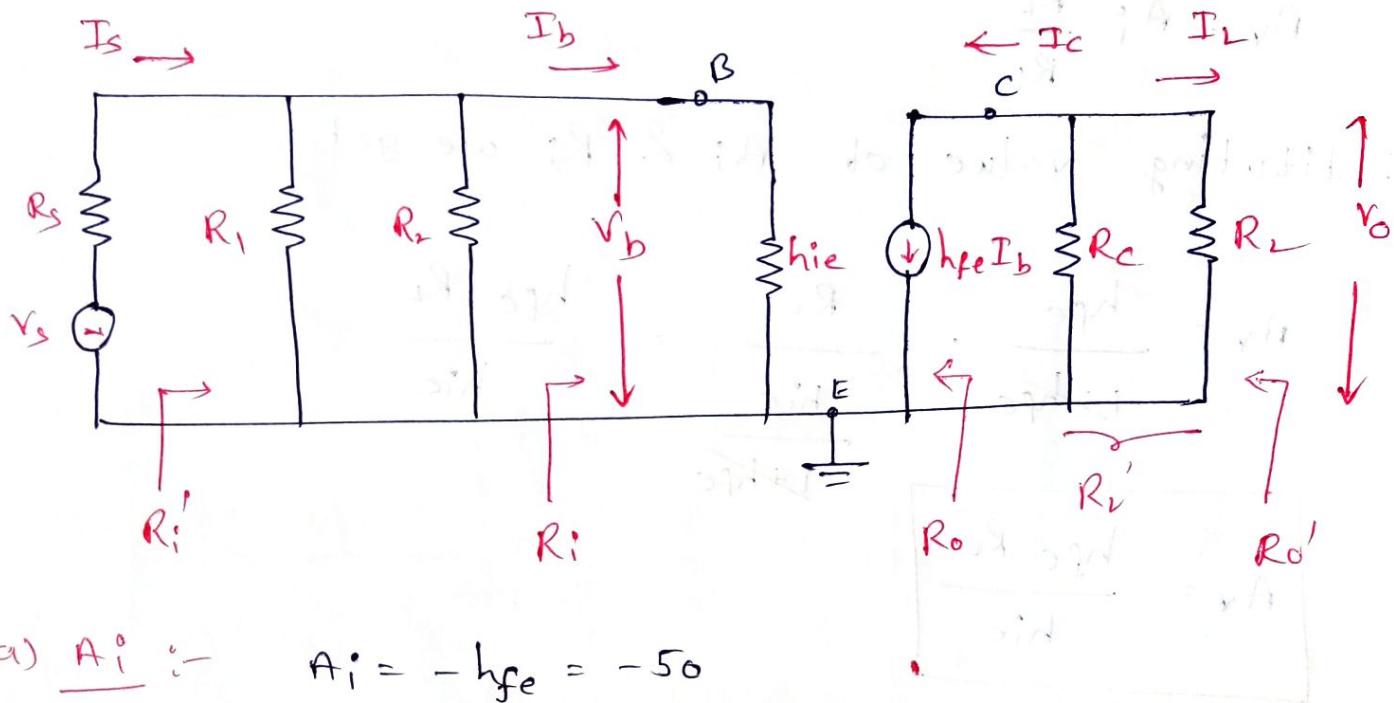Sol :- since  $h_{oe} \cdot R_k' = 25 \times 10^{-6} \times (2k \parallel 2k) = 0.025$ , which is less than 0.1, we use approximate analysis.



(a)  $A_i$  :-  $A_i = -h_{fe} = -50$

(b)  $R_i$  :-  $R_i = h_{ie} = 1.1k\Omega$

$$R_i' = h_{ic} \parallel R_1 \parallel R_2 \\ = 1.1k \parallel 50k \parallel 2k = 700\Omega$$


(c)  $A_v$  :-  $A_v = A_i = \frac{R_L'}{R_i'} = -50 \times \frac{(2k \parallel 2k)}{1.1k} = -45.45$

(d)  $R_o$  :-  $R_o = \frac{1}{Y_o} = \frac{1}{0} = \infty$


$$R_o' = R_o \parallel R_L' = \infty \parallel 2k \parallel 2k = 1k\Omega$$

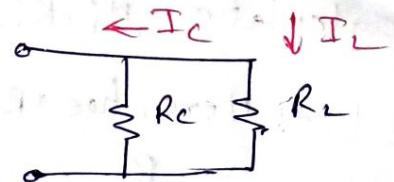(e)  $A_{is}$  :-  $A_{is} = \frac{I_L}{I_S} = \frac{I_L}{I_C} \times \frac{I_C}{I_B} \times \frac{I_B}{I_S}$

$$\frac{I_L}{I_C} = \frac{R_C}{R_C + R_L} = \frac{-2k\Omega}{2k + 2k} = -0.5$$



$$\frac{I_C}{I_B} = h_{FE} = 50$$

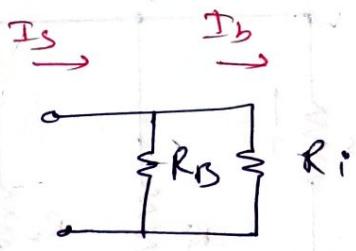

$$\frac{I_B}{I_S} = \frac{R_B}{R_B + R_i} = \frac{(50\text{k}\Omega)}{(50\text{k}\Omega) + 1\text{k}} = 0.636$$

$$\therefore A_{IS} = \frac{I_L}{I_S} = -0.5 \times 50 \times 0.636 = -15.9$$

(F) A\_{VS} :-

$$A_{VS} = \frac{V_O}{V_S} = \frac{V_O}{V_b} \times \frac{V_b}{V_S}$$

$$\frac{V_O}{V_b} = A_V = -45.45$$

$$\frac{V_b}{V_S} = \frac{R_i'}{R_i' + R_s} = \frac{700}{700 + 1\text{k}} = 0.411$$


$$\therefore A_{VS} = (-45.45) \times (0.411) = -18.71$$

Problem(2) :- A common collector ckt as shown in Fig. has the following components.


$$R_1 = 27\text{k}\Omega, R_2 = 27\text{k}\Omega$$

$$R_E = 5.6\text{k}\Omega, R_L = 47\text{k}\Omega$$

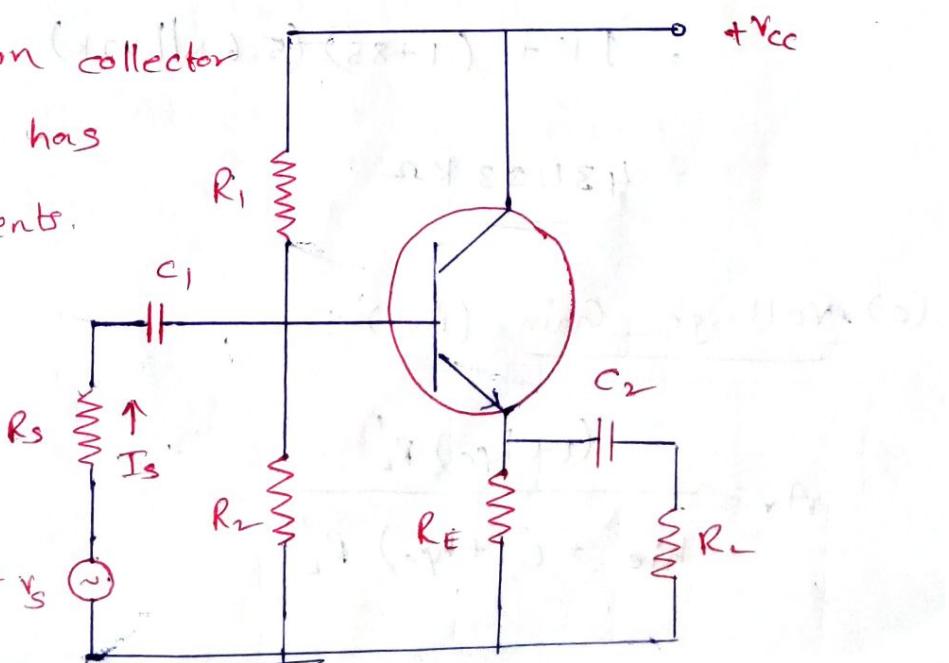$R_s = 600\Omega$ . The transistor parameters are  $\beta = 1\text{k}\Omega$ ,  $h_{FE} = 85$ , and  $h_{OE} = 2\text{mV/V}$ .



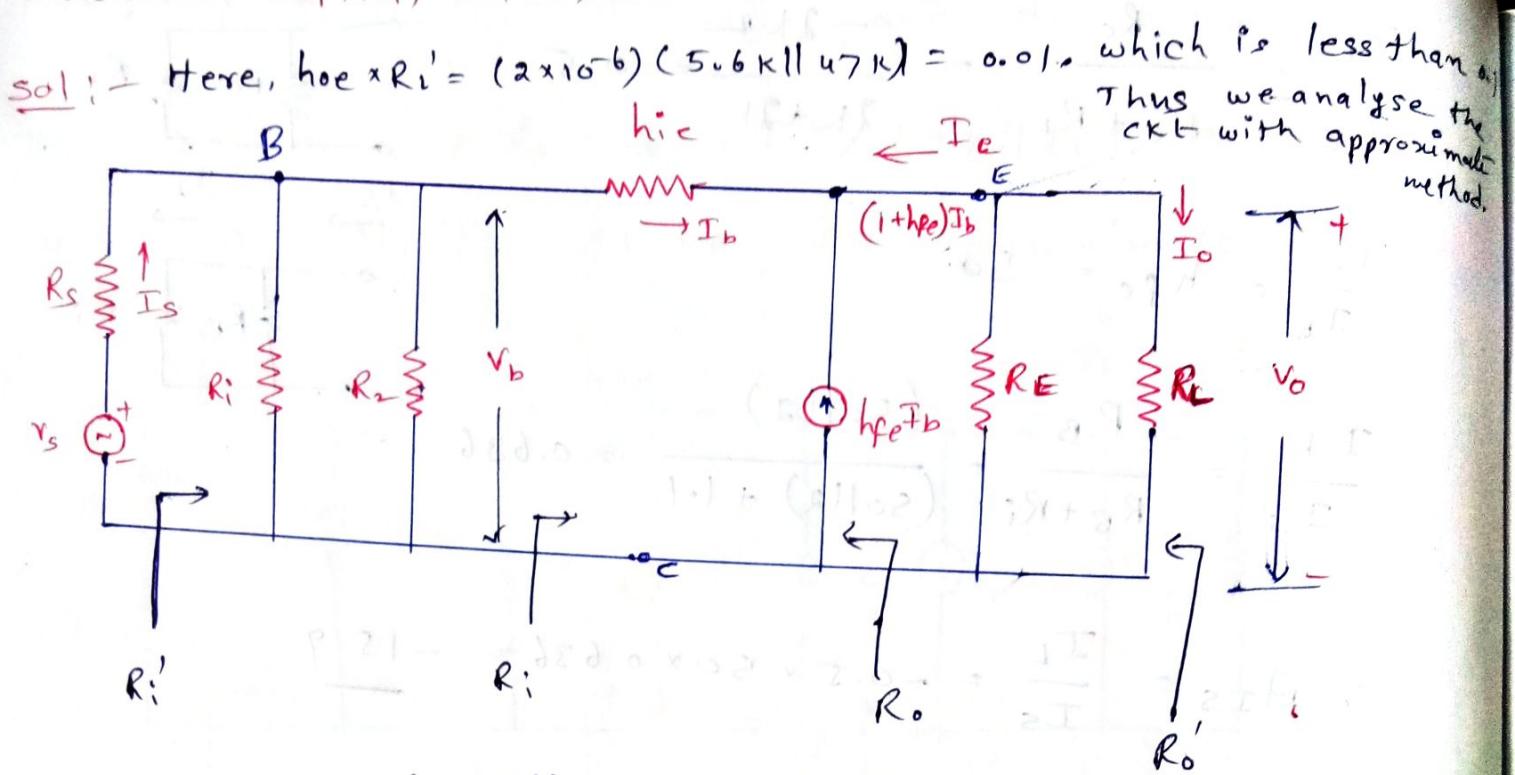Calculate  $A_i$ ,  $R_i$ ,  $A_v$ ,  $R_o$ ,  $A_{vs}$  and  $A_{is}$ .



Simplified Hybrid Model

(a) Current Gain ( $A_i$ ) :-

$$A_i = 1 + h_{fe} = 1 + 85 = 86$$

(b) Input Resistance ( $R_i$ ) :-

$$\begin{aligned} R_i &= h_{ie} + (1+h_{fe}) R_L' \\ &= h_{ie} + (1+h_{fe}) (R_E \parallel R_L) \\ &= 1 \text{ k} + (1+85)(5.6 \text{ k} \parallel 17 \text{ k}) \\ &= 431.33 \text{ k}\Omega \end{aligned}$$

(c) Voltage Gain ( $A_v$ ) :-

$$A_v = \frac{(1+h_{fe}) R_L'}{h_{ie} + (1+h_{fe}) R_L'}$$

$$= \frac{(1+h_{fe})(R_E || R_L)}{h_{ie} + (1+h_{fe})(R_E || R_L)}$$

$$= \frac{(1+85)(5.6\text{ k} || 47\text{ k})}{1\text{ k} + (1+85)(5.6\text{ k} || 47\text{ k})}$$

$$= 0.997$$

(d) Output Resistance ( $R_o$ ) :-

$$R_o = \frac{R'_i + h_{ie}}{1+h_{fe}} = \frac{(R_i || R_2 || R_s) + h_{ie}}{1+h_{fe}} = \frac{(27\text{ k} || 27\text{ k} || 600) + 1\text{ k}}{1+85} = 18.3\text{ }\Omega$$

$$R'_i = R_o || R_E || R_L = 18.3 || 5.6\text{ k} || 47\text{ k} = 18.23\text{ }\Omega$$

(e) Overall Voltage Gain ( $A_{vS}$ ) :-

$$A_{vS} = \frac{V_o}{V_S} = \frac{V_o}{V_b} \times \frac{V_b}{V_S}$$

$$\text{where, } \frac{V_o}{V_b} = A_V, \quad \frac{V_b}{V_S} = \frac{R'_i}{R'_i + R_s}$$

$$A_{vS} = A_V \cdot \frac{R'_i}{R'_i + R_s} = 0.997 \times \frac{13.09\text{ k}}{13.09\text{ k} + 600} = 0.953$$


(f) Overall Current Gain ( $A_{iS}$ ) :-

$$A_{iS} = \frac{I_o}{I_S} = \frac{I_o}{I_e} \times \frac{I_e}{I_b} \times \frac{I_b}{I_S}$$

$$\text{where, } \frac{I_o}{I_e} = \frac{-R_E}{R_E + R_L} = \frac{-5.6\text{ k}}{5.6\text{ k} + 47\text{ k}} = -0.106$$


$$\frac{I_e}{I_b} = -(1+h_{fe}) = -(1+85) = -86.$$

$$\frac{I_b}{I_S} = \frac{R_B}{R_B + R_i} = \frac{(R_i || R_L)}{(R_i || R_L) + R_i} = \frac{(27\text{ k} || 27\text{ k})}{(27\text{ k} || 27\text{ k}) + 431.93\text{ k}} = 0.03$$

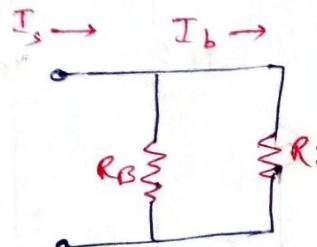

$$A_{IS} = \frac{I_o}{I_s} = \frac{I_o}{I_e} \times \frac{I_e}{I_b} \times \frac{I_b}{I_s} = (-0.106)(-86)(0.03) = \underline{\underline{0.273}}$$


Problem ③:-

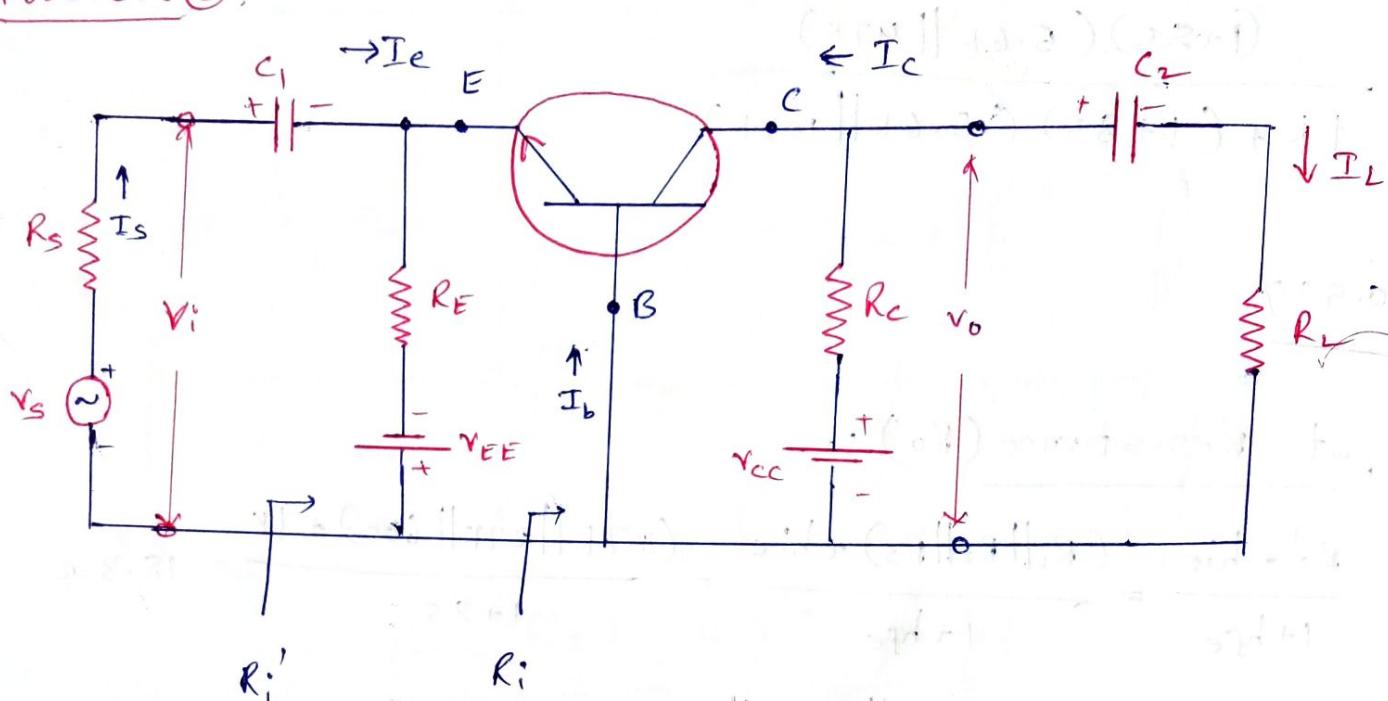

A Common Base amplifier, as shown in Fig., has the following components:  $R_s = 600\Omega$ ,  $R_c = 5.6\text{ k}\Omega$ ,  $R_E = 5.6\text{ k}\Omega$ ,  $R_L = 3.9\text{ k}\Omega$ . The transistor parameters are  $h_{ie} = 1\text{ k}\Omega$ ,  $h_{fe} = 8$  and  $h_{oe} = 2\text{ mA/V}$ . Calculate  $R_i$ ,  $R_o$ ,  $A_v$ ,  $A_i$ ,  $A_{vs}$ .

$$\text{Sol:-- Since } h_{oe} \times R_i' = h_{oe} \times (R_c || R_L) = (2 \times 10^{-6}) \times (5.6\text{ k} \parallel 3.9\text{ k}\Omega) \\ = 9.79 \times 10^{-3} = 0.00979$$

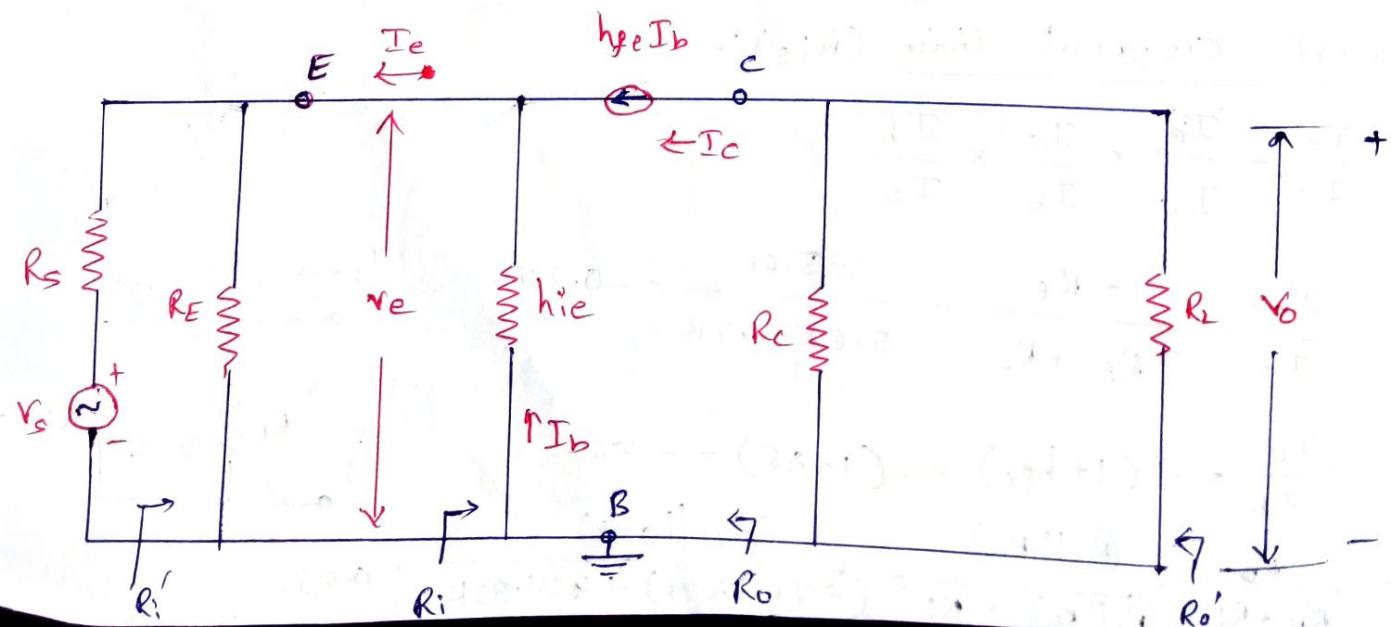which is less than 0.1, we use approximate analysis method.



(a) Current Gain ( $A_i$ ) :-  $A_i = \frac{h_{fe}}{1+h_{fe}} = \frac{85}{1+85} = 0.988$

(b) Input Resistance ( $R_i$ ) :-  $R_i = \frac{h_{ie}}{1+h_{fe}} = \frac{1K}{1+85} = 11.627\Omega$

$$R_i' = R_i \parallel R_E = 11.627 \parallel 5.6K = 11.6\Omega$$

(c) Voltage Gain ( $A_v$ ) :-  $A_v = \frac{h_{fe} R_L'}{h_{ie}} = \frac{h_{fe} \times (R_C \parallel R_L)}{h_{ie}}$

$$= \frac{85 \times (5.6K \parallel 39K)}{1K} = 416.23$$

(d) Output Resistance ( $R_o$ ) :-  $R_o = \infty$

$$R_o' = R_C \parallel R_L' = R_C \parallel R_C \parallel R_L = \infty \parallel 5.6K \parallel 39K = 4.89K\Omega$$

(e) Overall Voltage Gain ( $A_{vs}$ ) :-

$$A_{vs} = \frac{V_o}{V_s} = \frac{V_o}{V_e} \times \frac{V_e}{V_s} = A_v \times \frac{V_e}{V_s}$$

where,  $\frac{V_e}{V_s} = \frac{R_i'}{R_i' + R_S} = \frac{11.6}{11.6 + 600} = 0.0189$

$$A_{vs} = 416.23 \times 0.0189 = 7.89$$

## IV Analysis of CE Amplifier with Emitter Resistance

→ Whenever the gain provided by a single stage amplifier is not sufficient, it is necessary to cascade the no. of stages of the amplifier.

→ In such situations, it becomes important to stabilize the voltage amplification of each stage, because instability of the first stage is amplified in the next.

→ This is not desired. The simple and effective way to obtain voltage gain stabilization is to add an emitter resistance  $R_E$  to a CE stage as shown in Fig(a).


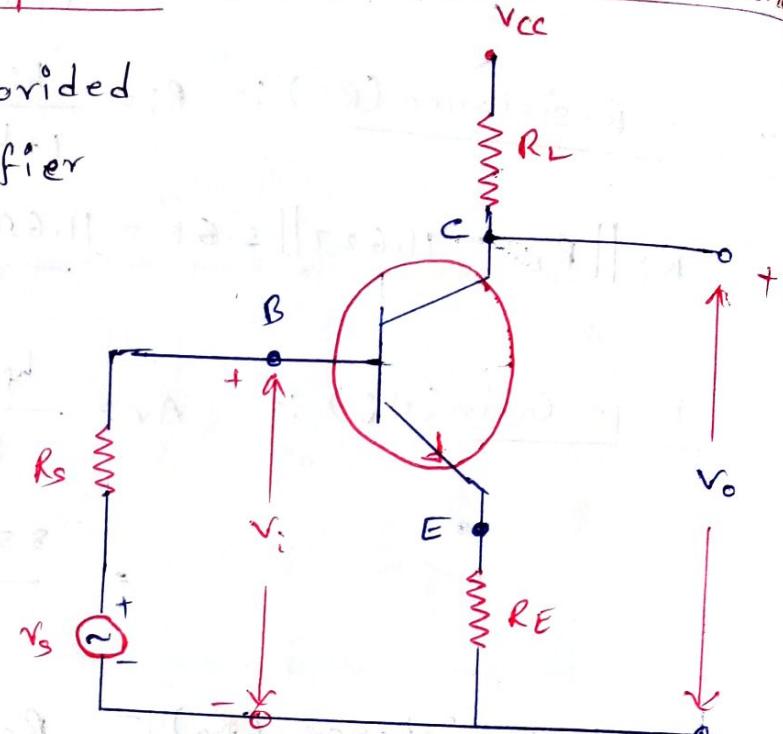


Fig.(a)

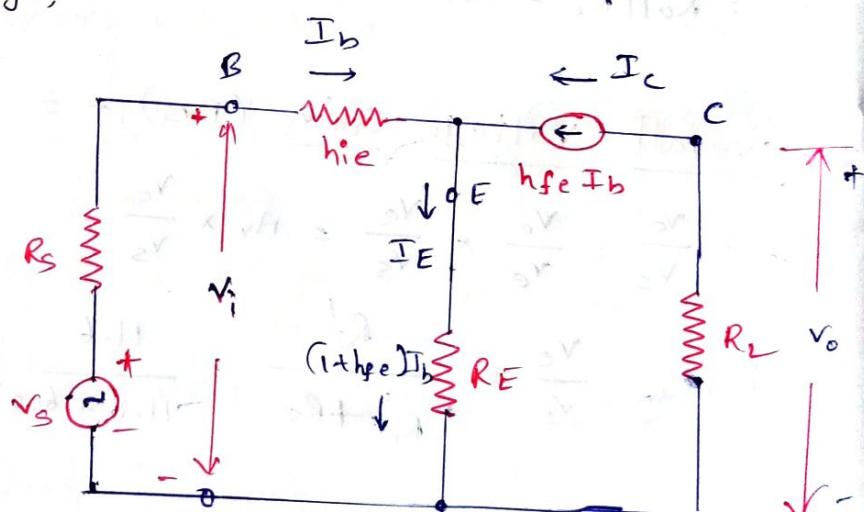

Fig(b). Approximate model for  
CE Amplifier with  $R_E$

→ The presence of emitter resistance has no. of better effects on the amplifier performance. These effects can be analysed with the help of h-parameter equivalent circuit.

## Approximate Analysis :-

An approximate analysis of the common emitter circuit with  $R_E$  can be made using approximate h-parameter equivalent circuit shown in Fig.(b).

current Gain ( $A_i$ ) :-

$$A_i = \frac{-I_c}{I_b} = -\frac{h_{fe} I_b}{I_b}$$

$$A_i = -h_{fe}$$

Input Resistance ( $R_i$ ) :-

$$R_i = \frac{V_i}{I_b} = h_{ie} + (1+h_{fe}) R_E$$

The input resistance due to factor  $(1+h_{fe}) R_E$  may be very much larger than  $h_{ie}$ . Hence an emitter resistance greatly increases the input resistance.

Voltage Gain ( $A_v$ ) :-

$$A_v = A_i \cdot \frac{R_L}{R_i} = \frac{-h_{fe} R_L}{h_{ie} + (1+h_{fe}) R_E}$$

Output Resistance ( $R_o$ ) :-

$$R_o = \frac{r_o}{I_o} \Big|_{V_s=0}$$

when  $V_s=0$ , the current through the i/p loop  $I_b=0$ , hence  $I_c$  and  $I_b$  both are zeros. Therefore  $R_o = \infty$ .

The output resistance  $R'_o$  of the stage, taking the load into account is given as,

$$R'_o = R_{out} || R_L = \infty || R_L = R_L$$

$$R'_o = R_L$$

## Emitter Follower (or) Common Collector Amplifier

→ The d.c. biasing is provided by  $R_1$ ,  $R_2$  and  $R_E$ .

→ The load resistance is capacitor coupled to the emitter terminal of the transistor.

→ When a signal is applied via to the base of the transistor,


$v_B$  is increased and decreased as the signal goes +ve and -ve respectively

$$\text{i.e., } V_E = V_B - V_{BE}$$

→ Considering  $V_{BE}$  fairly constant, we say that variation in the  $v_B$  appears at emitter and emitter voltage  $V_E$  will vary same as base voltage  $V_B$ .

→ Since the emitter is o/p terminal, it can be noted that the o/p voltage from a common collector circuit is the same as its i/p voltage.

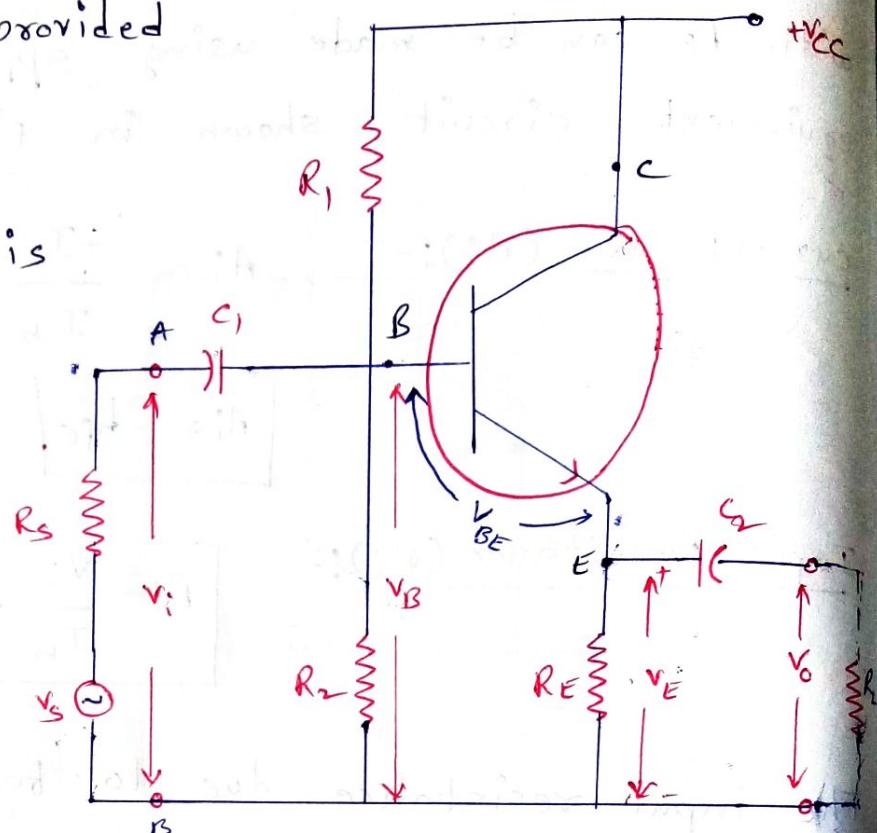→ We can say that in common collector circuit emitter terminal follows the signal voltage applied to the base. Hence it is also known as "Emitter follower"



## Miller's Theorem :-

The Miller theorem is used for converting any circuit having configuration to another configuration.

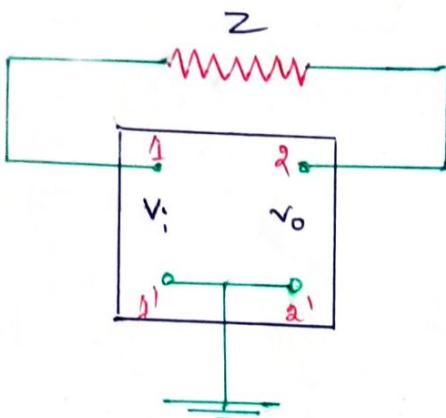


Fig.(a)

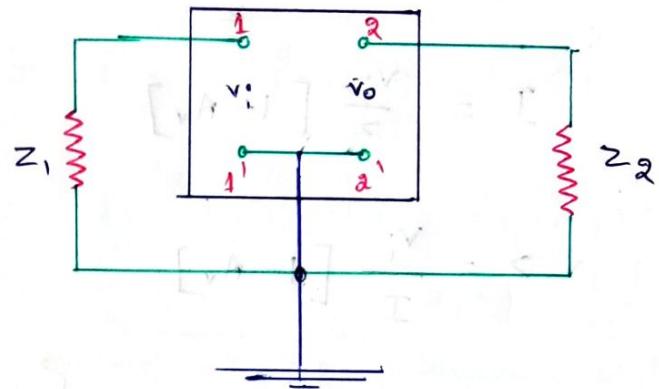


Fig.(b)

→ If  $Z$  is the impedance connected between two nodes, node 1 and node 2, it can be replaced by two separate impedances  $z_1$  and  $z_2$ .

→ Where  $z_1$  is connected b/w node 1 and ground.

→ The  $v_i$  and  $v_o$  are the voltages at the node 1 and node 2 respectively. The values of  $z_1$  and  $z_2$  can be derived from the ratio of  $v_o$  and  $v_i$ , ( $v_o/v_i$ ), denoted

$$\text{by } k = \frac{v_o}{v_i}.$$


## Proof of miller's Theorem:-

→ Miller theorem states that, the effect of resistance  $Z$  on the ilp ckt is a ratio of ilp voltage  $v_o$  to the current  $I$  which flows from the ilp to the olp.

$$\therefore z_1 = \frac{v_i}{I} \quad \text{--- (1)}$$

where,
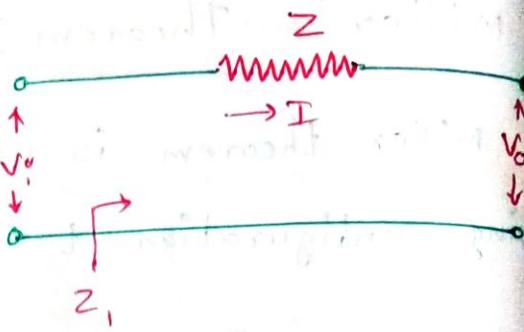
$$I = \frac{v_i - v_o}{z} = \frac{v_i \left[ 1 - \frac{v_o}{v_i} \right]}{z}$$



$$= \frac{v_i \left[ 1 - A_v \right]}{z} = \frac{v_i}{z} \left[ 1 - A_v \right]$$

$$I = \frac{v_i}{z} \left[ 1 - A_v \right]$$

$$z = \frac{v_i}{I} \left[ 1 - A_v \right]$$

$$z = z_1 \left[ 1 - A_v \right] \quad [\because \text{from eqn (1)}]$$


$$\boxed{z_1 = \frac{z}{1 - A_v} = \frac{z}{1 - K}} \quad \left[ \because \frac{v_o}{v_i} = A_v = K \right]$$



→ Miller theorem states that, the effect of resistance  $z$  on the o/p ckt is a ratio of o/p voltage  $v_o$  to the current  $I$  which flows from the o/p to the i/p.

$$\therefore z_2 = \frac{v_o}{I} \quad \text{--- (2)}$$
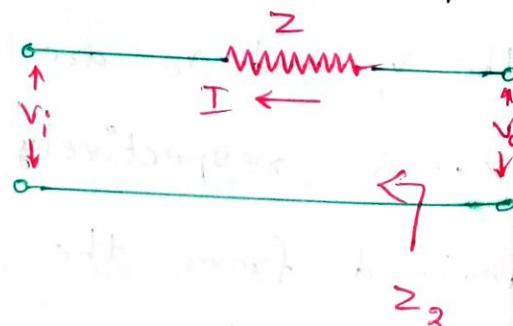
$$\text{where, } I = \frac{v_o - v_i}{z} = \frac{v_o \left[ 1 - \frac{v_i}{v_o} \right]}{z}$$



$$= \frac{v_o \left[ 1 - \frac{1}{A_v} \right]}{z} = \frac{v_o \left[ \frac{A_v - 1}{A_v} \right]}{z} = \frac{v_o}{z} \left[ \frac{A_v - 1}{A_v} \right]$$

$$I = \frac{v_o}{z} \left[ \frac{A_v - 1}{A_v} \right]$$

$$Z = \frac{V_o}{I} \left[ \frac{A_v + 1}{A_v} \right]$$

$$Z = Z_2 \left[ \frac{A_v + 1}{A_v} \right]$$

[∴ from eqn ②]

$$Z_2 = Z \cdot \frac{A_v}{A_v - 1} = Z \cdot \frac{K}{K - 1}$$

$$\left[ \because \frac{V_o}{V_i} = A_v = K \right]$$

### Dual of Miller's Theorem:-

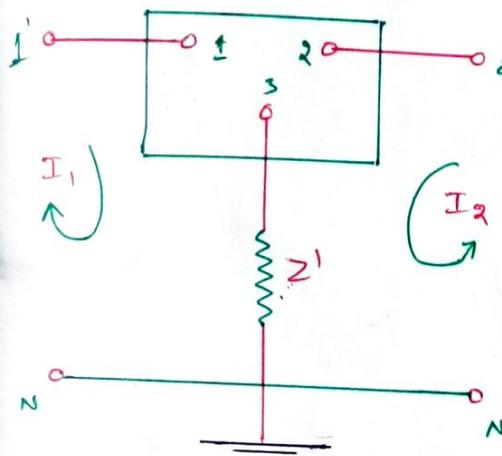


Fig. 1

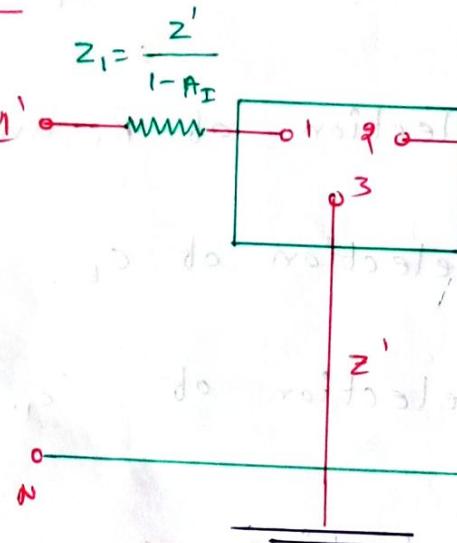


Fig. 2

- Where  $z'$  is the impedance b/w node 3 and ground N.
- According to dual of Miller's theorem,  $z'$  can be split into  $z_1$  and  $z_2$  such that  $z_1$  is placed in mesh 1 and  $z_2$  is added to mesh 2.

$$z_1 = \frac{z'}{1 - A_I}, \quad z_2 = z' \left[ \frac{A_I - 1}{A_I} \right]$$

where,  $A_I = \frac{-I_2}{I_1}$

# IV Design of single stage RC coupled Amplifier

Using BJT :-

The following steps required for amplifier design.

Step ① :- Calculate the load resistance  $R_L$ .

Step ② :- Selection of Q-point.

Step ③ :- calculate of  $R_E$ .

Step ④ :- Selection of  $R_1$  and  $R_2$ .

Step ⑤ :- selection of  $C_E$ .

Step ⑥ :- selection of  $C_{C_1}$ .

Step ⑦ :- selection  $C_{C_2}$ .

Step ⑧ :- Calculation of Power dissipation in Resistors.

## UNIT - I(b)

### Multi stage Amplifiers

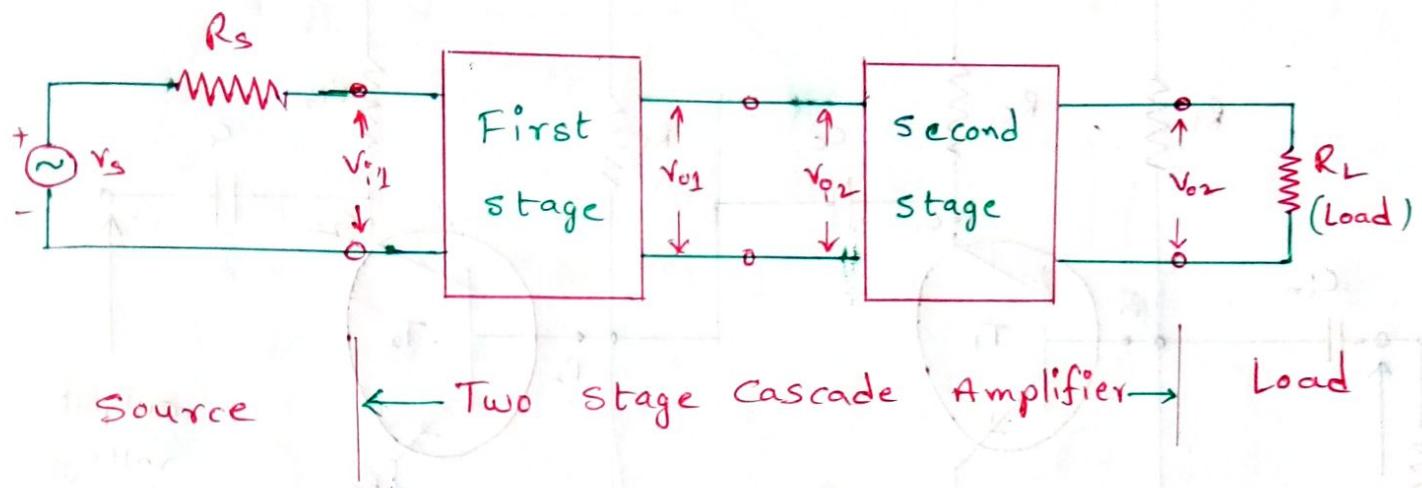


Fig 1. Multi stage Amplifier

→ A multi stage amplifier using two (or) more single stage common emitter amplifier is called as "Cascade Amplifier".

<u>1<sup>st</sup> stage</u>	<u>2<sup>nd</sup> stage</u>	<u>Amplifier Name</u>
CE	CE	cascade Amplifier
CE	CB	cascode "
CE	CC	compound "
CC	CC	parlington Pair "

Voltage Gain of Two stage Amplifier :-


From Fig-1, Overall voltage Gain,  $A_v = \frac{V_o}{V_{i1}} = \frac{V_o}{V_{i2}} \cdot \frac{V_{i2}}{V_{i1}}$

wkt.  $V_{o1} = V_{o2}$ ,  $A_v = \frac{V_o}{V_{i1}} = \frac{V_{o2}}{V_{i2}} \cdot \frac{V_{i2}}{V_{i1}} = \frac{V_{o2}}{V_{i2}} \cdot \frac{V_{o1}}{V_{i1}} = A_{v2} \cdot A_{v1}$


$$A_v = A_{v2} \times A_{v1}$$

# I Analysis of Two stage RC Coupled CE-CE cascade

Amplifier:-

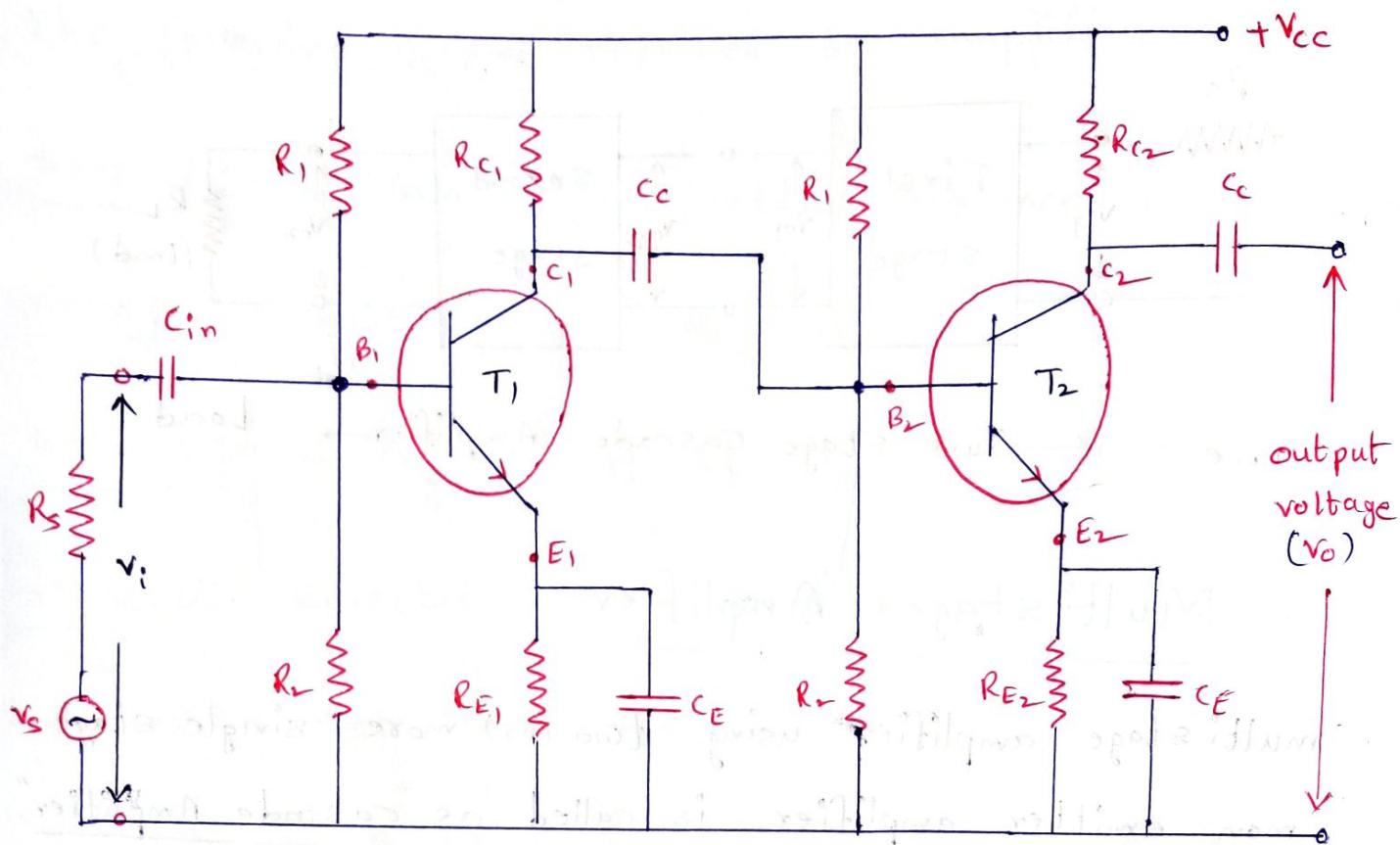

## Two stage CE-CE cascade Amplifier

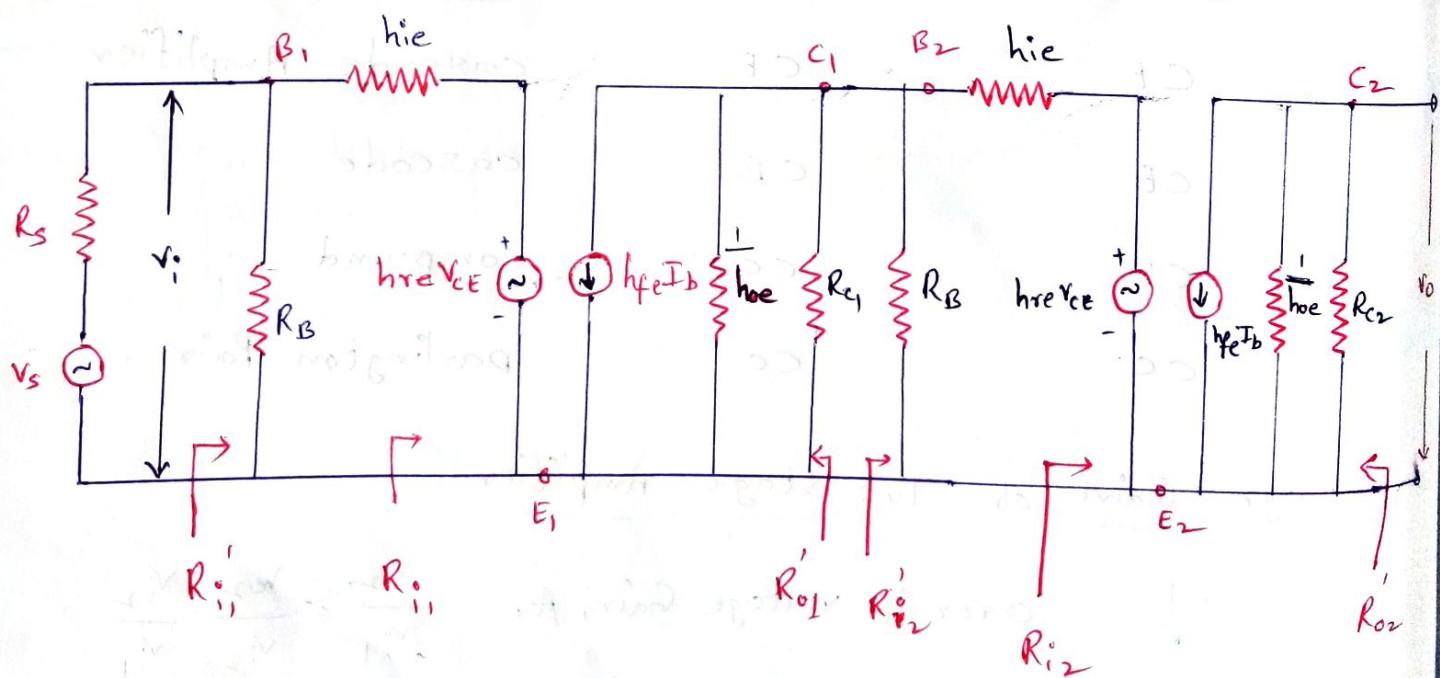

H-parameter Equivalent CRT for RC coupled Amplifier

$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

## Second Stage Analysis :-

current Gain ( $A_{i_2}$ ) :-

$$A_{i_2} = \frac{-h_{fe}}{1 + h_{oe} \cdot R_L}$$

$$= \frac{-h_{fe}}{1 + h_{oe} \cdot R_{C2}}$$

Neglecting  $h_{oe} R_{C2}$

$$\therefore A_{i_2} = -h_{fe}$$

Input Impedance ( $R_{i_2}$ ) :-

$$R'_{i_2} = R_B \parallel h_{ie}$$

since  $R_B \gg h_{ie}$ , hence neglecting  $R_B$

$$\therefore R'_{i_2} = h_{ie}$$

Voltage Gain ( $A_{v_2}$ ) :-

$$A_{v_2} = A_{i_2} \frac{R_L}{R_{i_2}}$$

$$A_{v_2} = -h_{fe} \frac{R_{C2}}{h_{ie}}$$

First stage Analysis :-

current Gain ( $A_{i_1}$ ) :-

$$A_{i_1} = -h_{fe}$$

Input Resistance ( $R_{i_1}$ ):-

$$R_{i_1} = h_{ie}$$

Voltage Gain ( $A_{v_1}$ ):-

$$A_{v_1} = A_{i_1} \frac{R_L}{R_{i_1}}$$

$R_L = R_C || R_B || h_{ie}$  and  $R_{i_1} = h_{ie}$ ; we get

$$A_{v_1} = -h_{fe} \frac{R_C || R_B || h_{ie}}{h_{ie}}$$

Overall voltage Gain ( $A_v$ ):-

$$A_v = A_{v_1} - A_{v_2}$$

Output Impedance ( $R_o$ ):-

$$R_{o_1} = R_C || h_{oe_1}$$

$$R_{o_2} = R_C || h_{oe_2}$$

Problem ①:- Using a CE-CE amplifier circuit diagram and find the voltage gain, current gain, input impedance output impedance for the ckt parameters given as

First stage

$$R_C = 10\text{ k}\Omega$$

$$R_1 = 20\text{ k}\Omega$$

$$R_2 = 200\text{ k}\Omega$$

$$R_E_1 = 10\text{ k}\Omega, R_S = 1\text{ k}\Omega$$

Second stage

$$R_C_2 = 5\text{ k}\Omega$$

$$R_1 = 50\text{ k}\Omega$$

$$R_2 = 300\text{ k}\Omega$$

$$R_E_2 = 100\text{ k}\Omega$$

Assume that

$$h_{ie} = 1.2\text{ k}\Omega$$

$$h_{re} = 2.5 \times 10^{-4}$$

$$h_{oe} = 2.5 \times 10^4 \text{ A/V}$$

$$h_{fe} = 50$$

Sol:  $h_{oe} \cdot R_L = h_{oe} \cdot R_{C2} = 2.5 \times 10^{-6} \times 5 \times 10^3 = 0.0125$

since  $h_{oe} \cdot R_L < 1$ , we can use simplified model for Analysis.

### Second Stage Analysis:

current gain,  $A_{i_2} = -h_{fe} = -50$

Input Impedance,  $R_{in} = h_{ie} = 1.2 \text{ k}\Omega$

voltage gain,  $A_{V2} = A_{i_2} \cdot \frac{R_{C2}}{h_{ie}} = -50 \times \frac{5 \times 10^3}{1.2 \times 10^3} = -208.33$

### First Stage Analysis:-

current gain,  $A_{i_1} = -h_{fe} = -50$

Input impedance,  $R_{i_1} = h_{ie} = 1.2 \text{ k}\Omega$

voltage gain,  $A_{V1} = A_{i_1} \cdot \frac{(R_{C1} \parallel R_B \parallel h_{ie})}{h_{ie}}$   
 $= -50 \times \frac{(10 \text{ k} \parallel 20 \text{ k} \parallel 200 \text{ k} \parallel 1.2 \text{ k})}{1.2 \text{ k}}$

$$[\because R_B = R_1 \parallel R_2]$$

$$= -50 \times \frac{1012.14}{1200} = -42.17$$

Overall voltage Gain,  $A_v = A_{V1} \cdot A_{V2}$


$$= (208.33) (-42.17)$$

$$A_v = 8785.27$$


Output Impedance,  $R_{o_1} = R_{C1} = 10 \text{ k}\Omega$

$$R_{o_2} = R_{C2} = 5 \text{ k}\Omega$$

## Two stage RC Coupled CE-CC Amplifier

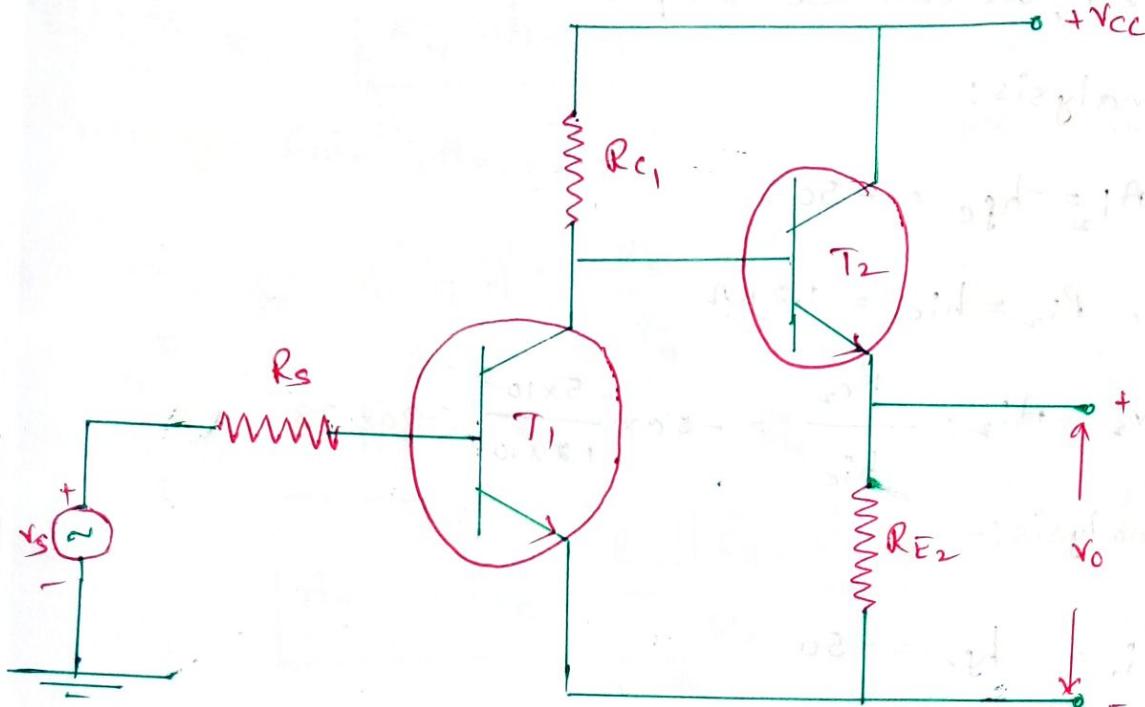
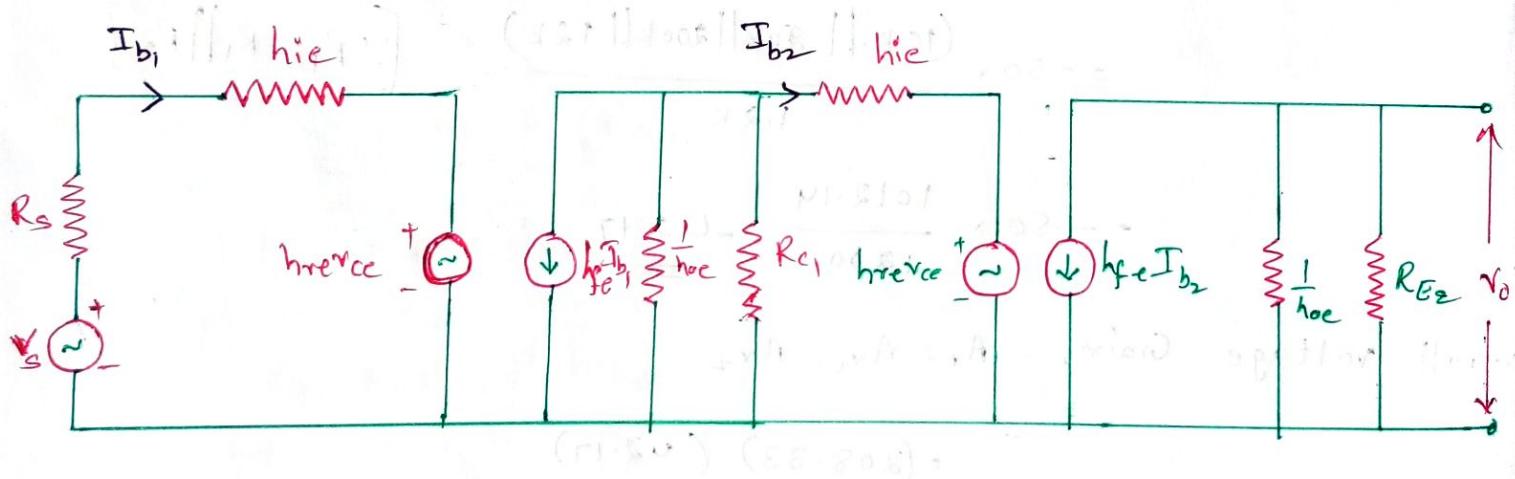
## Two stage Amplifier in CE-CC configuration



h-parameter Equivalent CKT of Two-stage Amplifier in CE-CC

## Second stage Analysis (cc stage)

current Gain ( $A_{i2}$ ) :-

$$A_{i2} = \frac{-I_{E2}}{I_{b2}} = \frac{-h_{fc}}{1 + h_{oe} \cdot R_{E2}}$$

Input Impedance ( $R_{i2}$ ) :-

$$R_{i2} = h_{ie} + h_{re} A_{i2} R_{E2}$$

Voltage Gain ( $A_{v2}$ ) :-

$$A_{v2} = \frac{V_o}{V_2} = A_{i2} \frac{R_{E2}}{R_{i2}}$$

First stage Analysis (CE stage) :-

The net load impedance  $R_L$  of first stage is obtained by

$$R_L = R_{C1} \parallel R_{i2}$$

Current Gain ( $A_{i1}$ ) :-

$$A_{i1} = \frac{-I_{C1}}{I_{B1}} = \frac{-h_{fe}}{1 + h_{oe} \cdot R_{E1}}$$

Input Impedance ( $R_{i1}$ ) :-

$$R_{i1} = h_{ie} + h_{re} A_{i1} R_L$$

Voltage Gain ( $A_{v1}$ ) :-

$$A_{v1} = \frac{V_o}{V_1} = A_{i1} \cdot \frac{R_L}{R_{i1}}$$

Output Impedance ( $R_o$ )

$$Y_{o1} = h_{oe} - \frac{h_{fe} \cdot h_{re}}{h_{ie} + R_{S1}}$$

$$R_{o1} = \frac{1}{Y_{o1}}$$

$$Y_{o2} = h_{oc} - \frac{h_{fe} \cdot h_{re}}{h_{ie} + R_{S2}}$$

$$\therefore R_{S2}' = R_{o1}'$$

$$R_{o2} = \frac{1}{Y_{o2}}$$

Problem ② :- Using a CE-CC amplifier circuit diagram, and

$R_s = 1\text{ k}\Omega$ ,  $R_c = 2\text{ k}\Omega$ ,  $R_{E_2} = 1.2\text{ k}\Omega$ . The h-parameter are  
 $h_{ie} = 1\text{ k}\Omega$ ,  $h_{fe} = 50$ ,  $h_{re} = 1 \times 10^{-4}$ ,  $h_{oe} = 10^{-4}\text{ A/V}$

$h_{ic} = 1\text{ k}\Omega$ ,  $h_{fc} = 51$ ,  $h_{rc} = 1$ , and  $h_{oc} = 10^{-4}\text{ A/V}$

compute (a) Input Impedance, (b) = output Admittance

(c) Current gain, voltage gain for individual stages

Sol:-

Second stage Analysis (CC stage) :-

$$\text{Current Gain, } A_{i_2} = \frac{-h_{fc}}{1 + h_{oc} R_{E_2}} = \frac{-51}{1 + (10^{-4} \times 1.2 \times 10^3)}$$

$$\therefore A_{i_2} = \underline{\underline{-45.54}}$$

$$\text{Input Impedance, } R_{i_2} = h_{ic} + h_{rc} A_{i_2} R_{E_2}$$

$$= (1 \times 10^3) + (1 \times 45.54 \times 1.2 \times 10^3)$$

$$\underline{\underline{R_{i_2} = 55.65\text{ k}\Omega}}$$

$$\text{Voltage Gain, } (A_{v_2}) = A_{i_2} \cdot \frac{R_{E_2}}{R_{i_2}} = 45.54 \times \frac{1.2 \times 10^3}{55.65 \times 10^3}$$

$$\therefore A_{v_2} = 0.982$$

$\underline{\underline{}}$

First stage Analysis (CE stage) :-

$$R_L(\text{or}) R_{E_1} = R_c \parallel R_{i_2} = \frac{R_c \times R_{i_2}}{R_c + R_{i_2}} = \frac{2 \times 10^3 \times 55.65 \times 10^3}{2 \times 10^3 + 55.65 \times 10^3} = 1.93\text{ k}\Omega$$

current Gain ( $A_{i_1}$ ) :-

$$A_{i_1} = \frac{-h_{fe}}{1 + h_{oe} R_E} = \frac{-50}{1 + (10^{-4} \times 1.93 \times 10^3)} = -41.67$$

Input impedance ( $R_{i_1}$ ) :-

$$R_{i_1} = h_{ie} + h_{re} A_{i_1}, R_L = 1 \times 10^3 + (10^{-4} \times 41.67 \times 1.93 \times 10^3)$$

$$= 1008 \Omega$$

Voltage Gain ( $A_{v_1}$ ) :-

$$A_{v_1} = \frac{V_2}{V_1} = A_{i_1} \cdot \frac{R_L}{R_{i_1}} = \frac{+41.67 \times 1.93 \times 10^3}{1008} = +79.78$$

output Admittance :-

$$Y_{o_1} = h_{oc} - \frac{h_{fe} \cdot h_{re}}{h_{ie} + R_S} = 10^{-4} - \frac{50 \times 10^{-4}}{(1 \times 10^3) + (1 \times 10^3)}$$

$\left[ \because \text{Assume } R_S = 1 \text{ k}\Omega \right]$

$$= 10^{-4} - 2.5 \times 10^{-7} = 9.75 \times 10^{-5} \text{ A/V}$$

$$R_{o_1} = \frac{1}{Y_{o_1}} = \frac{1}{9.75 \times 10^{-5}} = 10.26 \text{ k}\Omega$$



$$R_{S_2} (\text{or } R_{o_1}') = \frac{R_{C_1} \times R_{o_1}}{R_{C_1} + R_{o_1}} = \frac{2 \text{ k} + 10.26 \text{ k}}{2 \text{ k} + 10.26 \text{ k}} = 1.674 \text{ k}\Omega$$

$$Y_{o_2} = h_{oc} - \frac{h_{fc} \cdot h_{rc}}{h_{ie} + R_{S_2}} = 10^{-4} - \frac{51 \times 1}{1 \times 10^3 + 1.674 \times 10^3}$$

$$= 18.9 \times 10^{-4} \text{ A/V}$$

$$R_{o_2} = \frac{1}{Y_{o_2}} = \frac{1}{18.9 \times 10^{-4}} = 52.9 \Omega$$

## II Cascode Amplifier (CE-CB)

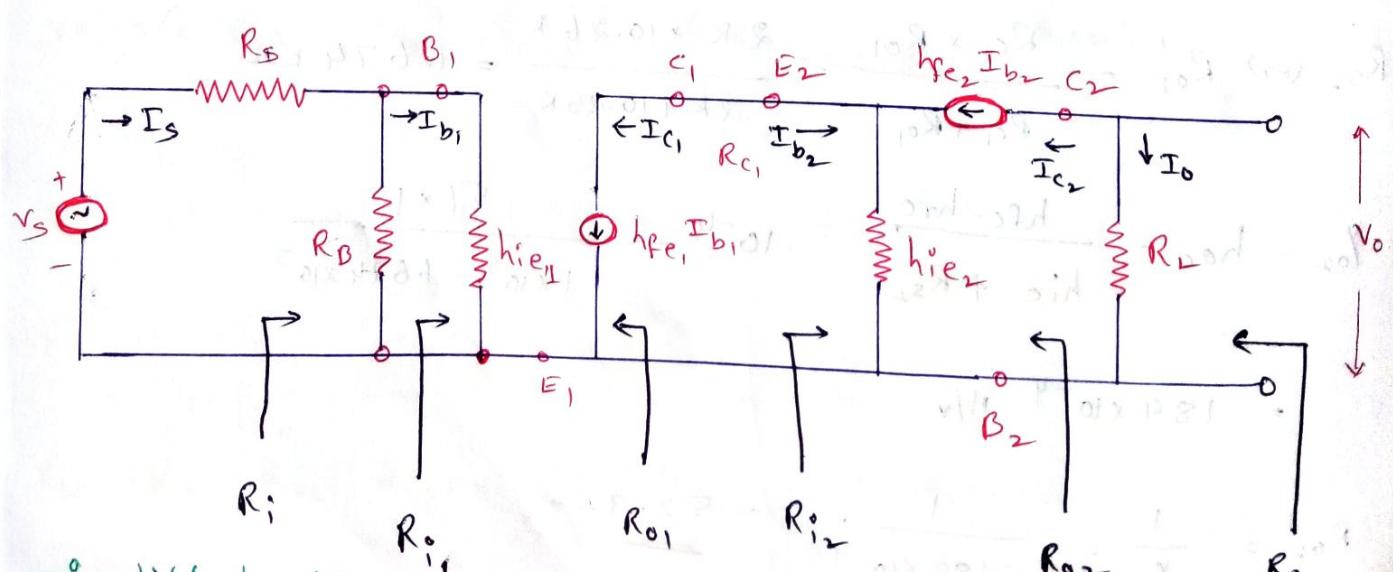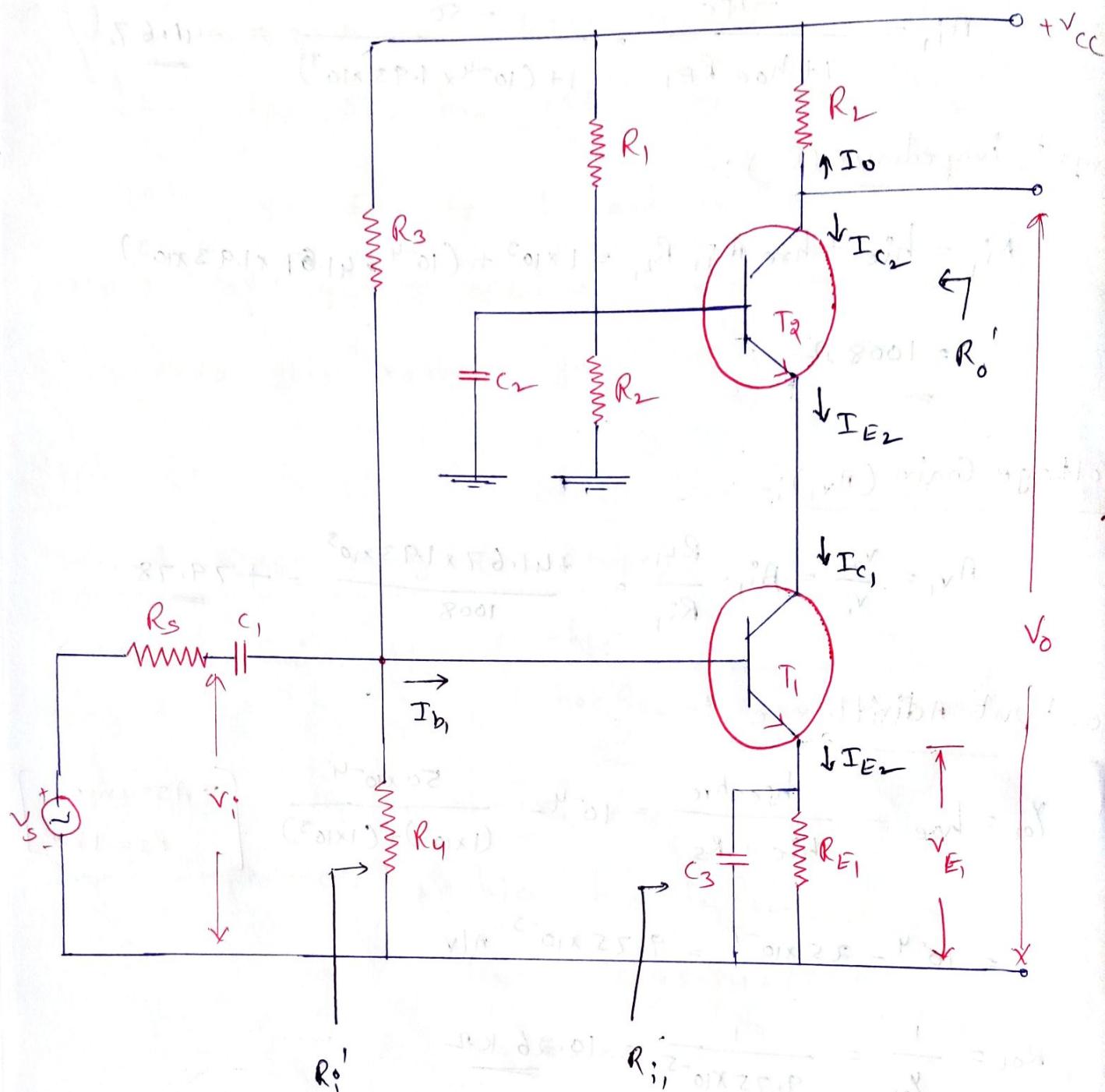

Simplified  $h$ -parameter Equivalent ckt for CE-CB Amplifier

## Second stage Analysis (CB Amplifier)

(i) Current Gain ( $A_{i2}$ ) :-

$$A_{i2} = \frac{h_{fe}}{1 + h_{fe}}$$

(ii) Input Impedance ( $R_{i2}$ ) :-

$$R_{i2} = \frac{h_{ie}}{1 + h_{fe}}$$

(iii) Voltage Gain ( $A_{v2}$ ) :-

$$A_{v2} = A_{i2} \cdot \frac{R_{L2}}{R_{i2}}$$

## First stage Analysis (CE amplifier)

(iv) Current Gain ( $A_{i1}$ ) :-  $A_{i1} = -h_{fe}$

(v) Input Impedance ( $R_{i1}$ ) :-  $R_{i1} = h_{ie}$

(vi) Voltage Gain ( $A_{v1}$ ) :-  $A_{v1} = A_{i1} \cdot \frac{R_{L1}}{R_{i1}}$

(vii) Overall Voltage Gain ( $A_v$ ) :-  $A_v = A_{v1} \times A_{v2}$

(viii) Overall Input Resistance ( $R_i$ ) :-

$$R_i = R_{i1} \parallel R_B = R_{i1} \parallel R_3 \parallel R_u$$

(ix) Overall Voltage Gain ( $A_{vs}$ ) considering Source Resistance

$$A_{vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = A_v \cdot \frac{R_i}{R_i + R_s}$$

(x) Overall Current Gain ( $A_{IS}$ ) Considering Source

Resistance :-

$$A_{IS} = \frac{I_o}{I_s} = \frac{I_o}{I_{C_2}} \times \frac{I_{C_2}}{I_{E_2}} \times \frac{I_{E_2}}{I_{C_1}} \times \frac{I_{C_1}}{I_{B_1}} \times \frac{I_{B_1}}{I_s}$$

(xi) Output Resistance ( $R_o$ ) :-

$$R_o = R_{o_2} \parallel R_L$$

Problem ③ :- Using a CE-CB amplifier circuit diagram,

and  $R_s = 1\text{ k}\Omega$ ,  $R_3 = 200\text{ k}\Omega$ ,  $R_u = 10\text{ k}\Omega$ ,  $R_L = 3\text{ k}\Omega$  and  $h_{ie} = 1.1\text{ k}\Omega$ ,  $h_{fe} = 50$ ,  $h_{re} = h_{oe} = 0$ . Find current gain, input impedance, voltage gain and output impedance.

Sol:- Analysis of second stage (CB amplifier)

(i) Current gain,  $A_{i_2} = \frac{h_{fe}}{1+h_{fe}} = \frac{50}{1+50} = 0.98$

(ii) Input Impedance,  $R_{i_2} = \frac{h_{ie}}{1+h_{fe}} = \frac{1.1\text{ k}}{1+50} = 21.56\text{ }\Omega$

(iii) Voltage gain,  $A_{v_2} = A_{i_2} \cdot \frac{R_{L_2}}{R_{i_2}} = 0.98 \times \frac{3 \times 10^3}{21.56} = 136.36$

Analysis of First Stage (CE Amplifier)

(iv) Current gain,  $A_{i_1} = -h_{fe} = -50$

(v) Input Impedance,  $R_{i_1} = h_{ie} = 1.1\text{ k}\Omega$

(vi) Voltage Gain,  $A_{v_1} = A_{i_1} \cdot \frac{R_{L_1}}{R_{i_1}} = +50 \times \frac{21.56}{1.1 \times 10^3} = +0.98$   $\therefore R_{L_1} = R_{i_1}$

(vii) overall voltage Gain,  $A_v = A_{v1} \times A_{v2} = +0.98 \times 136.36 = +133.6$

(viii) overall Input Resistance,  $R_i = R_i^o \parallel R_B = R_i^o \parallel R_3 \parallel R_4$

$$= 1.1k \parallel 200k \parallel 20k = 986.1 \Omega$$

(ix) overall voltage Gain ( $A_{vs}$ ) considering source Resistance,

$$A_{vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = A_v \times \frac{R_i}{R_i + R_s}$$

$$= +133.63 \times \frac{986.1}{986.1 + 1000} = +66.35$$

(x) Overall Current Gain ( $A_{is}$ ) Considering Source Resistance,

$$A_{is}^o = \frac{I_o}{I_s} = \frac{I_o}{I_{c2}} \times \frac{I_{c2}}{I_{e2}} \times \frac{I_{e2}}{I_{c1}} \times \frac{I_{c1}}{I_{b1}} \times \frac{I_{b1}}{I_s}$$

where,

$$\frac{I_o}{I_{c2}} = -1, \quad \frac{I_{c2}}{I_{e2}} = +A_{i2}^o, \quad \frac{I_{e2}}{I_{c1}} = +1, \quad \frac{I_{c1}}{I_{b1}} = -A_{i1}^o, \quad \frac{I_{b1}}{I_s} = \frac{R_B}{R_B + R_i^o}$$



$$A_{is}^o = -1 \times +A_{i2}^o \times +1 \times -A_{i1}^o \times \frac{R_B}{R_B + R_i^o}$$
$$= (-1) \times (+0.98) \times (+1) \times (-50) \times \frac{(200k \parallel 10k)}{(200k \parallel 10k) + 1.1k} = -43.9$$

(xi) Output Resistance ( $R_o$ ):

$$R_{o1} = \infty, \quad R_{o2} = \infty$$

$$R_o = R_{o2} \parallel R_L = \infty \parallel 3k = \underline{\underline{3k \Omega}}$$

### III Darlington Pair

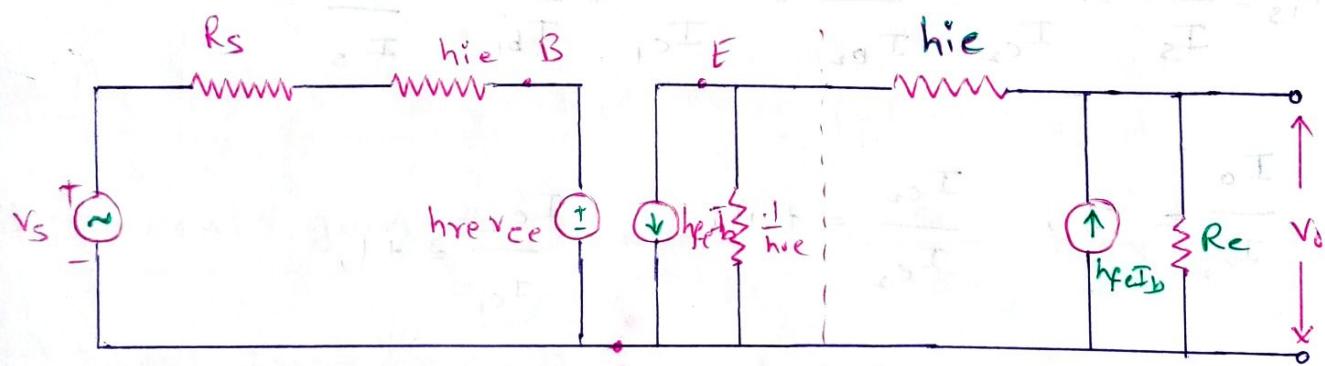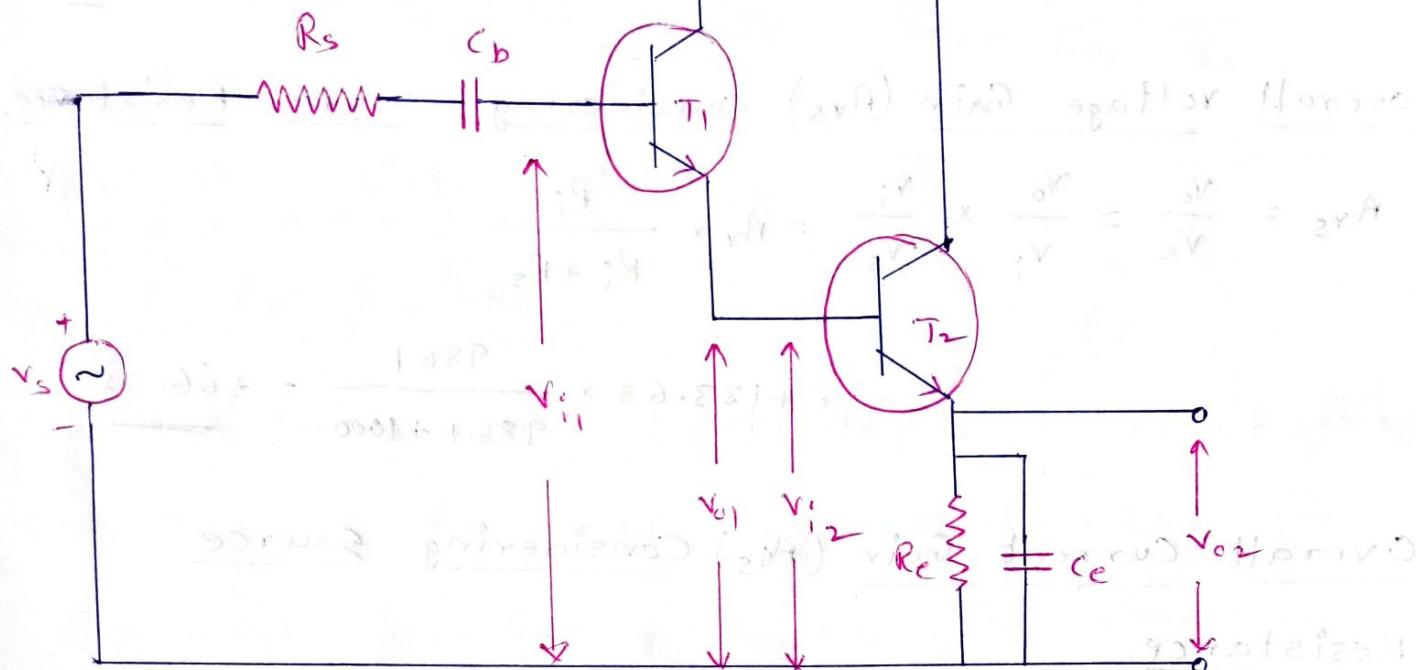

1<sup>st</sup> stage CC Exact method      2<sup>nd</sup> stage CC approximation  
method

Because  $h_{ce} \cdot R_L \ll 1$  rule not

satisfied i.e., the load resistance

1<sup>st</sup> is connected || I<sub>P</sub> resistance

or 2<sup>nd</sup> stage. I<sub>P</sub> resistance is

very high in cc.

Second stage:

(i) Current gain,  $A_{i_2} = 1 + h_{fe}$

(ii) Input Resistance,  $R_{i_2} = h_{ie} + (1 + h_{fe}) R_E$

(iii) Voltage gain,  $A_{v_2} = A_{i_2} \cdot \frac{R_L}{R_{i_2}}$  [since  $R_L = R_E$ ]

(iv) Output Resistance,  $R_{o_2} = \frac{R_s + h_{ie}}{1 + h_{fe}}$

First stage:

(v) Current gain,  $A_{i_1} = \frac{-h_{fe}}{1 + h_{oe} \cdot R_L} = \frac{-h_{fe}}{1 + h_{oe} \cdot h_{ie}}$

(vi) Input Resistance,  $R_{i_1} = h_{ie} + h_{re} \cdot A_{i_1} \cdot R_L$

(vii) Voltage gain,  $A_{v_1} = A_{i_1} \cdot \frac{R_L}{R_{i_1}}$

(viii) Output Resistance,  $R_{o_1} = \frac{1}{Y_{o_1}} = \frac{h_{re} \cdot h_{fe}}{R_s + h_{ie}}$

where,  $Y_{o_1} = h_{oe} = \frac{h_{re} \cdot h_{fe}}{R_s + h_{ie}}$

Overall,

(ix) Voltage gain,  $A_v = A_{v_1} \cdot A_{v_2}$

(x) Current gain,  $A_i = A_{i_1} \cdot A_{i_2}$

(xi) Voltage gain  $\frac{R_L}{R_{i_1}}$

Consider source resistance,  $A_{vs} = A_v \cdot \frac{R_s + R_{i_1}}{R_s + R_{i_1}}$

Problem 4 :- Find the characteristics of Darlington pair amplifier, use the standard h-parameter values i.e.,  $h_{ie} = 1\text{ k}\Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$ ,  $h_{fe} = 50$ ,  $h_{oe} = 25 \mu\text{A/V}$  and  $R_s = 3\text{k}\Omega$ ,  $R_E = 3\text{k}\Omega$ .

Sol :- Second stage : ( $R_L = R_E$ )

$$\text{Current gain, } A_{i_2} = 1 + h_{fe} = 1 + 50 = 51$$

$$\text{Input resistance, } R_{i_2}^* = h_{ie} + (1 + h_{fe}) R_E$$

$$= 1 \times 10^3 + (1 + 50) \times 3 \times 10^3 = 154 \text{ k}\Omega$$

$$\text{Voltage gain, } A_{v_2} = A_{i_2} \times \frac{R_L}{R_{i_2}} = 51 \times \frac{3 \times 10^3}{154 \times 10^3} = 0.99$$

$$\text{Output resistance, } R_{o_2} = \frac{R_s + h_{ie}}{1 + h_{fe}} = \frac{3 \times 10^3 + 1 \times 10^3}{1 + 50} = 78.43 \text{ }\Omega$$

First stage : ( $R_L = R_E$ )

$$\text{Current gain, } A_{i_1} = \frac{-h_{fe}}{1 + h_{oe} \cdot R_L} = \frac{-50}{1 + (25 \times 10^{-6} \times 3 \times 10^3)} = -46.51$$

$$\text{Input impedance, } R_{i_1}^* = h_{ie} + h_{re} \cdot A_{i_1} \cdot R_L$$

$$= 1 \times 10^3 + (2.5 \times 10^{-4} \times -46.51 \times 3 \times 10^3)$$

$$= 1.034 \text{ k}\Omega$$

$$\text{Voltage gain, } A_{v_1} = A_{i_1} \cdot \frac{R_L}{R_{i_1}^*} = (-46.51) \times \frac{3 \times 10^3}{1.034 \times 10^3} = 134.94$$

$$\text{Output resistance, } R_{o_1} = h_{oe} - \frac{h_{re} \cdot h_{fe}}{R_s + h_{ie}} = 25 \times 10^{-6} - \frac{2.5 \times 10^{-4} \times 50}{3 \times 10^3 + 1 \times 10^3}$$

$$= 25 \times 10^{-6} - 3.125 \times 10^{-6} = 21.875 \mu\text{A/V}$$

$$R_{O1} = \frac{1}{Y_{O1}} = \frac{1}{21.875 \times 10^{-6}} = 0.0457 \times 10^6 = 45.7 \times 10^3 = 45.7 \text{ k}\Omega$$


## Different Coupling Schemes Used in Amplifiers:-

① RC Coupled Amplifier

② Transformer Coupled Amplifier

③ Direct Coupled Amplifier.

### ① RC Coupled Amplifier :-

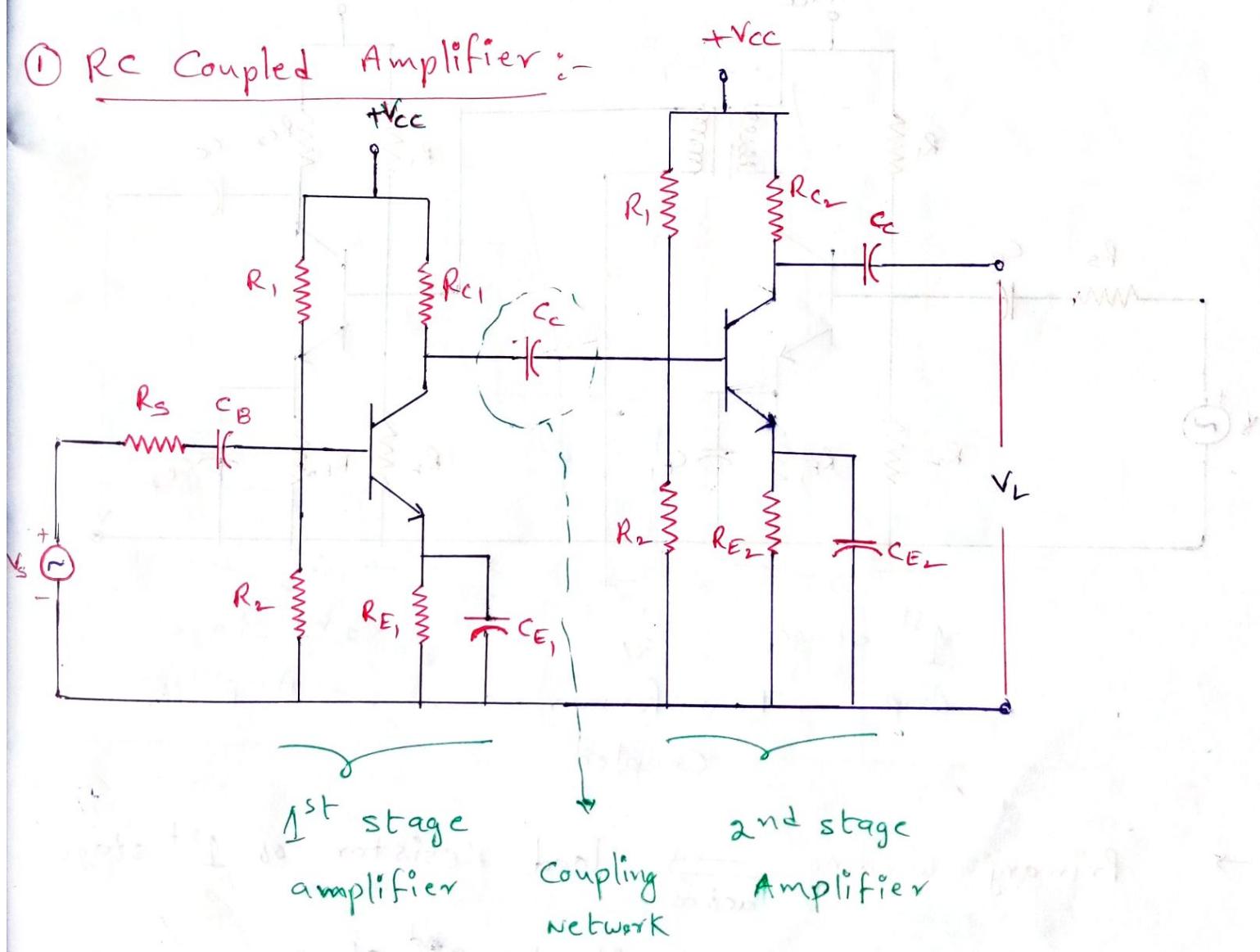


→ In this coupling network resistor and capacitor are used for overall gain. It is mostly widely used circuit.

→ It's satisfying the frequency response (or) it gives the good frequency response.

→ It is less expensive compared to other circuits.


→ It is a simple circuit.

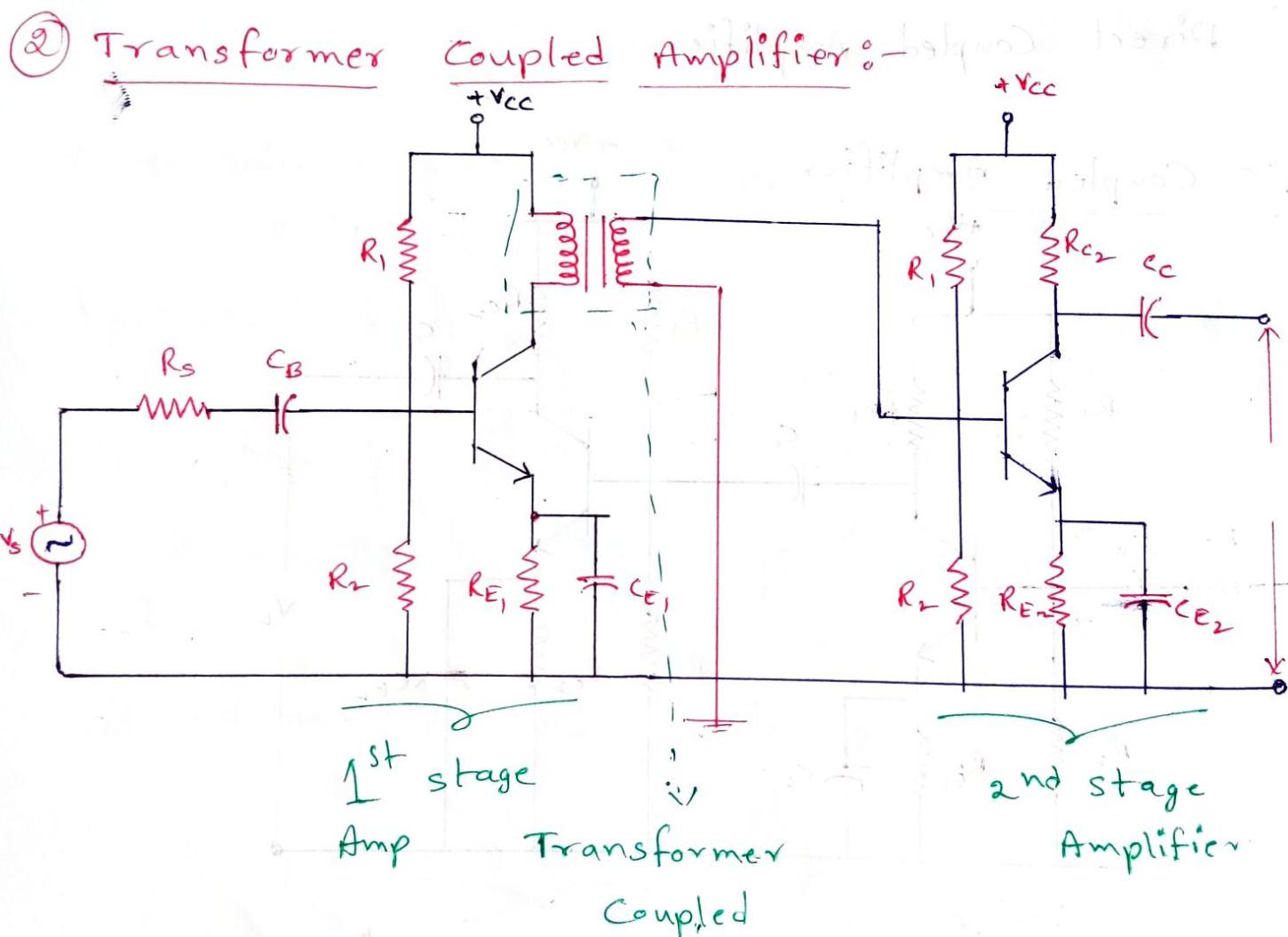

→ Primary winding  $\Rightarrow$  load Resistor of 1<sup>st</sup> stage  
acts as  
Secondary "  $\Rightarrow$  ip to 2<sup>nd</sup> stage.

- In this network, the primary winding of the transformer acts as collector resistance (or) collector load of 1<sup>st</sup> stage and the 2<sup>nd</sup> winding of the transformer acts as input of the 2<sup>nd</sup> stage and a.c. power supply.
- The transformer coupled network gives more d.c. isolation between the 2 stages.
- The transformer coupled network mostly used in power amplifier.
- It is more expensive compared to others.
- It has low frequency response.

### ③ Direct Coupled Amplifier:-

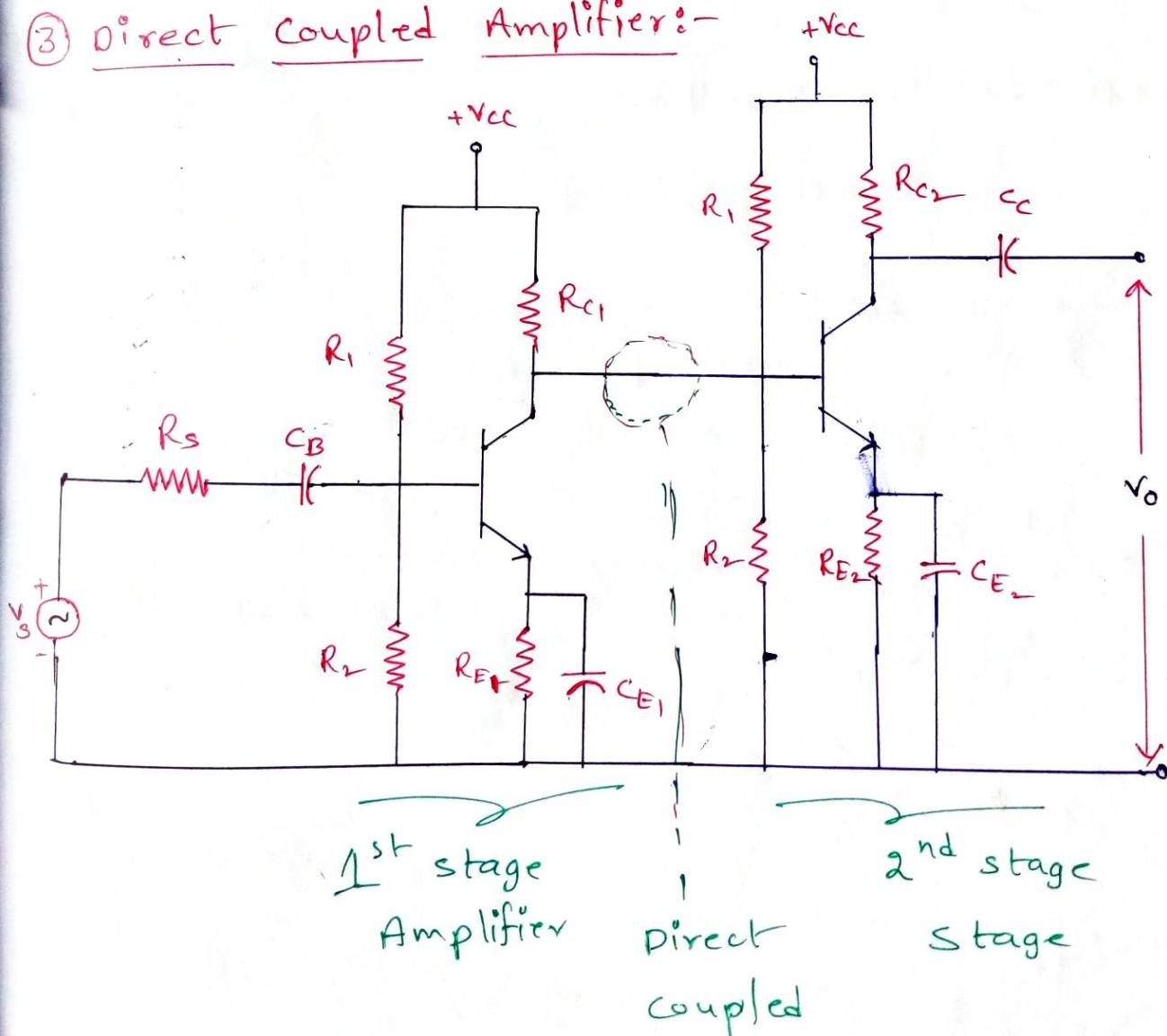

- In this coupling network, the 1<sup>st</sup> stage of the o/p is given to the i/p of the 2<sup>nd</sup> stage.
- It is less expensive coupling network.
- Low frequency response, it is not suitable for application point of view.



## UNIT-II Problems

⑥ Determine the low frequency response of CE amplifier using the following specifications

$$V_{CC} = 12V, R_C = 3k\Omega, R_E = 10k\Omega, R_i = 52k\Omega, R_2 = 12k\Omega, R_S = 600\Omega$$

$$C_b = 0.1\mu F, C_E = 10\mu F, C_o = 0.1\mu F, h_{ie} = 1.6k\Omega, h_{fe} = 49$$

Sol:-  $C_b$

$$f_{Lc_b} = \frac{1}{2\pi R_{eq} C_b}$$

$$\therefore R_{eq} = R_S + z_i$$

$$z_i' = R_B \parallel z_i$$

$$R_B = R_1 \parallel R_2 = 52k \parallel 12k = 9.75k\Omega$$

$$z_i = h_{ie} = 1.6k\Omega$$

$$z_i' = R_B \parallel z_i = 9.75k \parallel 1.6k = 1.37k\Omega$$

$$R_{eq} = 600 + 1.37k = 1.974k\Omega$$

$$f_{Lc_b} = \frac{1}{2 \times 3.14 \times 1.974 \times 10^3 \times 0.1 \times 10^{-6}} = \frac{1}{1.239 \times 10^{-3}} = 0.807 \times 10^3 = 807.1 \text{ Hz}$$

$C_E$

$$f_{Lc_e} = \frac{1}{2\pi R_{eq} C_E}$$

$$R_{eq} = R_E \parallel \left( \frac{R_s' + h_{ie}}{1 + h_{fe}} \right)$$

$$R_s' = R_S \parallel R_B$$

$$R_B = R_1 \parallel R_2 = 52k \parallel 12k = 9.75k\Omega$$

$$R_s' = R_s \parallel R_B = 600 \parallel 9.75k\Omega = 565.21\Omega$$

$$\begin{aligned} R_{eq} &= R_E \parallel \left( \frac{R_s' + h_{ie}}{1 + h_{fe}} \right) = 10k \parallel \left( \frac{565.21 + 1.6k}{1 + 49} \right) \\ &= 10k \parallel \left( \frac{2165.21}{50} \right) = 10k \parallel 43.3 \\ &= 43.11\Omega \end{aligned}$$

$$f_{Lce} = \frac{1}{2\pi R_{eq} C_e} = \frac{1}{2 \times 3.14 \times 43.11 \times 10 \times 10^{-6}} = \frac{10^6}{2707.308}$$

$$f_{Lce} = 369.37 \text{ Hz}$$

C<sub>c</sub>

$$f_{Lcc} = \frac{1}{2\pi R_{eq} C_c}$$

$$\begin{aligned} R_{eq} &= R_c + R_L = 3k + 10k\Omega \quad [ \because R_L = R_E ] \\ &= 13k\Omega \end{aligned}$$

$$f_{Lcc} = \frac{1}{2\pi R_{eq} C_c} = \frac{1}{2 \times 3.14 \times 13 \times 10^3 \times 0.1 \times 10^{-6}} = \frac{10^3}{8.164}$$

$$f_{Lc} = 122.48 \text{ Hz}$$

Lower cut-off frequency.

$$f_L = \max(f_{Lcb}, f_{Lce}, f_{Lcc})$$

$$= \max(807.1, 369.37, 122.48)$$

$f_L = 807.1 \text{ Hz}$
--------------------------

⑦ A transistor amplifier in CE configuration, in operating at high frequency with the following specifications

$$f_T = 5 \text{ MHz}, g_m = 0.05 \text{ siemens}, h_{fe} = 50, r_{bb}' = 100\Omega, R_s = 500\Omega$$

$C_C = 10 \text{ pF}$ ,  $R_L = 10 \text{ k}\Omega$ . Compute the overall voltage gain,

Upper 3dB cut-off frequency, and  $(GBW)$

Sol: Overall voltage gain,  $A_v = -h_{fe} \cdot \frac{R_L}{(R_s + h_{ie})}$

$$h_{ie} = r_{bb}' + r_{be}'$$

$$r_{be}' = \frac{h_{fe}}{g_m} = \frac{50}{0.05} = 1000\Omega$$

$$h_{ie} = 100 + 1000 = 1100\Omega$$

$$A_v = -h_{fe} \frac{R_L}{(R_s + h_{ie})} = -50 \times \frac{10 \times 10^3}{500 + 1100} = \frac{-500 \times 10^3}{1600} = -312.5$$

The Upper 3dB cut-off frequency,

$$f_H = \frac{1}{2\pi R C} = \frac{1}{2 \times 3.14 \times 10 \times 10^3 \times 10 \times 10^{-9}} = \frac{1}{6.28 \times 10^{-7}} = 0.159 \times 10^7$$

$$= 1.59 \text{ MHz}$$

Gain-Bandwidth Product ( $GBW$ ) =  $A_v \cdot f_H$

$$= -312.5 \times 1.59 \times 10^6$$

$$= \underline{\underline{496.8 \text{ MHz}}}$$

⑧ Given the following transistor measurements made at

$I_C = 10 \text{ mA}$ ,  $V_{CE} = 10 \text{ V}$  and at room temperature,  $h_{fe} = 50$ ,

$r_{ie} = 1 \text{ k}\Omega$ ,  $|A_{ie}| = 20$  at  $20 \text{ MHz}$ ,  $C_C = 3 \text{ pF}$ , Find  $f_B$ ,  $f_T$ ,

$C_E$ ,  $r_{be}$  and  $r_{bb}$ .

Sol: Given data,  $I_C = 10 \text{ mA}$ ,  $V_{CE} = 10 \text{ V}$ ,  $h_{FE} = 50$ ,  $h_{IE} = 1 \text{ k}\Omega$ ,  $|A_{ie}| = 20$  at  $20 \text{ MHz}$ ,  $C_C = 3 \text{ pF}$ ,  $V_T = 26 \text{ mV}$  (at room temp)

$$|A_{ie}| = \frac{h_{FE}}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}}$$

Squaring on both sides

$$|A_{ie}|^2 = \frac{h_{FE}^2}{1 + \left(\frac{f}{f_p}\right)^2}$$

$$1 + \left(\frac{f}{f_p}\right)^2 = \frac{h_{FE}^2}{|A_{ie}|^2}$$

$$\left(\frac{f}{f_p}\right)^2 = \left[\frac{h_{FE}}{|A_{ie}|}\right]^2 - 1$$

$$\frac{f}{f_p} = \sqrt{\left[\frac{h_{FE}}{|A_{ie}|}\right]^2 - 1}$$

$$f_p = \frac{f}{\sqrt{\left[\frac{h_{FE}}{|A_{ie}|}\right]^2 - 1}}$$

$$f_p = \frac{20 \times 10^6}{\sqrt{\left[\frac{50}{20}\right]^2 - 1}} = \frac{20 \times 10^6}{\sqrt{(2.5)^2 - 1}} = \frac{20 \times 10^6}{\sqrt{5 - 1}} = \frac{20 \times 10^6}{2.236} = 8.91 \text{ MHz}$$

$$f_T = h_{FE} \cdot f_B$$

$$= 50 \times 8.69 \times 10^6 = 173.9 \text{ MHz}$$

$$\gamma_{be}^{(o)} \gamma_{be}^{-1} = \frac{h_{FE}}{g_m}$$

$$g_m = \frac{|I_C|}{V_T} = \frac{10 \times 10^{-3}}{26 \times 10^{-3}} = 0.192 \text{ A/V}$$

$$\gamma_{be}^{-1} = \frac{h_{FE}}{g_m} \cdot \frac{50}{0.192} = 260.41 \Omega$$

$$\gamma_{bb}^{(o)} \gamma_{bb}^{-1} = h_{ie} - \gamma_{be}^{-1} = 1000 - 260.41 = 739.59 \Omega$$

$$f_T = \frac{g_m}{2\pi C_e}$$

$$\therefore C_e = \frac{g_m}{2\pi f_T} = \frac{0.192}{2 \times 3.14 \times 173.9 \times 10^6} = \frac{0.192}{1092092 \times 10^6} = 0.175 \times 10^{-3} \times$$

$$= 0.0001758 \times 10^{-6} = 0.1758 \times 10^{-3} \times 10^{-6} = 175.8 \times 10^{-12} = 175.8 \text{ pF}$$

Q) A high frequency amplifier uses a transistor which is driven from a source with  $R_s = 1 \text{ k}\Omega$ . Calculate the value of  $f_H$ ,  $A_{v\text{slow}}$  and  $A_{v\text{HIGH}}$  if  $R_L = 0$  and  $R_s = 1 \text{ k}\Omega$ . Assume typical values for hybrid  $\pi$ -parameters.

Sol:- (i) For  $R_L = 0$

$$f_H = \frac{1}{2\pi R_{eq} C_{eq}}$$

$$R_{eq} = \gamma_{b'e} \parallel (\gamma_{bb1} + R_s) ; C_{eq} = C_e + C_c (1 + g_m R_L)$$

$$(\because R_L = 0)$$

$$C_{eq} = C_e + C_c (1 + g_m(0))$$

$$= C_e + C_c (1+0)$$

$$C_{eq} = C_e + C_c$$

Assume

\* typical values.  $\gamma_{b'e} = 1\text{ k}\Omega$ ,  $\gamma_{bb1} = 100\text{ }\Omega$ ,  $h_{ie} = 1\text{ k}\Omega$

$$C_e = 1\text{ nF}, C_c = 3\text{ pF}, g_m = 50\text{ mA/V}$$

$$f_H = \frac{1}{2\pi [\gamma_{b'e} \parallel (\gamma_{bb1} + R_s)] [C_e + C_c]}$$

$$= \frac{1}{2 \times 3.14 [1\text{ k} \parallel (100 + 1\text{ k})] [1\text{ nF} + 3\text{ pF}]}$$

$$\therefore f_H = 2.95 \text{ MHz}$$

$$A_{vSLOW} = -h_{fe} \cdot \frac{R_L}{R_s + h_{ie}} = -h_{fe} \cdot \frac{0}{R_s + h_{ie}} = 0$$

$$A_{vSHIGH} = -g_m \gamma_{b'e} \cdot R_s$$

$$= \frac{R_s + \gamma_{bb1} + \gamma_{b'e}}{R_s + \gamma_{bb1} + \gamma_{b'e}}$$

$$= \frac{-50 \times 1\text{ k} \times 1\text{ k}}{1\text{ k} + 100 + 1\text{ k}} = \frac{-50 \times 1000 \times 1000}{1000 + 100 + 1000}$$

$$\underline{\underline{A_{vSHIGH} = -23.8}}$$

$$\underline{R_L = 1 \text{ k}\Omega}$$

$$f_H = \frac{1}{2\pi R_{eq} C_{eq}}$$

$$R_{eq} = r_{bb'} || (r_{bb'} + R_s) ; C_{eq} = C_e + C_C [1 + g_m R_L]$$

$$f_H = \frac{1}{2\pi [r_{bb'} || (r_{bb'} + R_s)] [C_e + C_C (1 + g_m R_L)]}$$

$$= \frac{1}{2 \times 3.14 [1k || (100 + 1k)] [100pF + 3pF (1 + 50 \times 10^{-3} \times 1 \times 10^3)]}$$

$$= \frac{1}{2 \times 3.14 \times 523.8 \times (100p + 151p)} = \frac{1}{825.655 \times 10^3 \times 10^{-12}}$$

$$= 1.21 \text{ MHz}$$

$$A_{VSLow} = -h_{fe} \cdot \frac{R_L}{R_S + h_{ie}} = -50 \times \frac{1k}{1k + 1k} = -50 \times \frac{1k}{2k}$$

$$\therefore \underline{A_{VSLow} = -25}$$

$$A_{VSHIGH} = \frac{-g_m r_{bb'} \cdot R_S}{R_S + r_{bb'} + r_{bb'}}$$

$$= \frac{-50 \times 1k \times 1k}{1k + 100 + 1k}$$

$$\therefore \underline{A_{VSHIGH} = -23.8}$$



## UNIT-II

### BJT Amplifiers - Frequency Response

#### UNIT-II(a) : BJT Amplifiers - Frequency Response

- ① Logarithms,
- ② Decibels
- ③ General Frequency considerations.
- ④ Frequency response of BJT Amplifier.
- ⑤ Analysis at low and High frequencies
- ⑥ Effect of Coupling and By pass capacitors.
- ⑦ The Hybrid-pi - Common Emitter Transistor Model
- ⑧ CE Short circuit current Gain
- ⑨ Current Gain with Resistive Load
- ⑩ Single stage CE Transistor Amplifier Response
- ⑪ Gain-Bandwidth Product
- ⑫ Emitter follower at higher frequencies.

#### UNIT-II(b) : MOS Amplifiers

- ① Basic Concepts
- ② Mos small signal model
- ③ Common Source Amplifier with Resistive load.

①

UNIT - II (a)BJT Amplifiers - Frequency Response

I Logarithms :- The analysis of amplifiers normally

extends over a wide frequency range. Use of logarithmic scale makes it comfortable plotting the response between wide limits.

→ Logarithm taken to the "base 10" is common logarithm.

Example: logarithm of a variable "a" is  $\log_{10} a$ .

→ Logarithm taken to the "base e" is natural logarithm.

Example: logarithm of a variable "a" is  $\log_e a$  (or)  $\ln a$ .

II Decibels :- Decibel is used to compare two power levels on a logarithmic basis.

→ The term "bel" is derived from the name of telephone invention, Alexander Graham Bell.

→ The unit "bel" (B) is defined relating two power levels  $P_1$  and  $P_2$  is

$$G = \log_{10} \left( \frac{P_2}{P_1} \right) \text{ bel}$$

As "bel" was found to be a large unit for measurement  
the decibel (dB) is defined where 10 decibels = 1 bel.

(2)

Hence,

$$G_{dB} = 10 \log_{10} \left( \frac{P_2}{P_1} \right) dB$$

### III General Frequency Consideration:-

#### ① Mid-band (or) Middle Frequency Range:-

In the entire midband, gain  $A$  is almost constant say at value  $A_m$  and the time delay  $\tau$  is also almost constant at value  $\tau_0$  seconds. In this midband gain is normalized to unity i.e.,  $A_m = 1$ .

#### ② Low Frequency Range:-

This frequency range lies below the midband. In low frequency range, the gain  $A$  decreases with decrease of frequency and tends to become zero at frequency  $f=0$  (o.c. signal).

→ thus in this frequency range, the amplifier behaves as a simple high pass circuit.

### ③ High Frequency Range:-

This frequency range lies above the mid-band. In high frequency range, the gain decreases with increases of frequency.

→ Thus in this frequency range, the amplifier behaves as a simple low pass circuit.

### IV Frequency Response of BJT Amplifier:- (08)

#### Single stage CE Transistor Amplifier Response

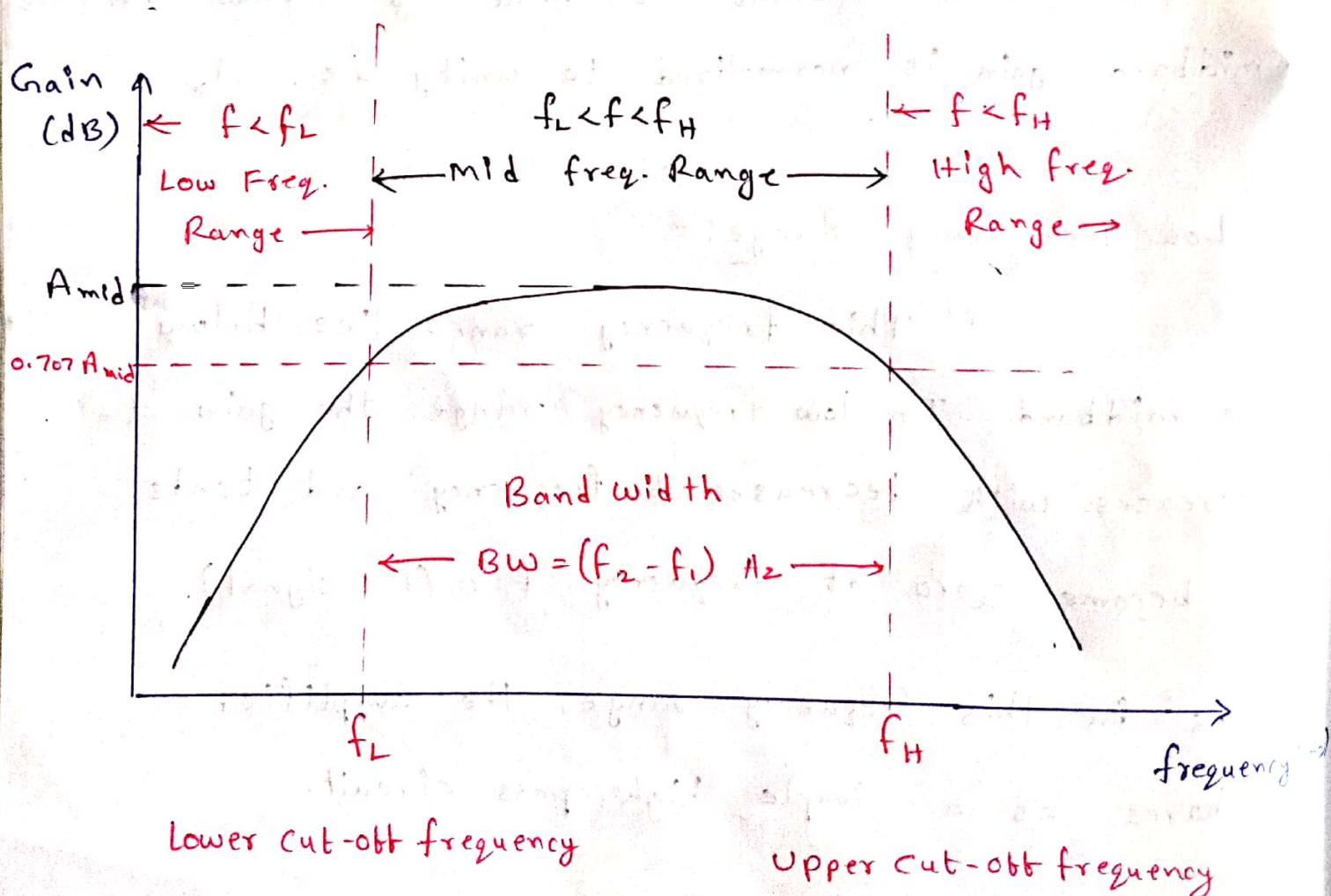


Fig. Frequency Response of RC Coupled Amplifier

→ The main aim of any amplifier should be to provide a constant amplification at any frequency (at all freq's over a selected range). This is analysed by means of a curve called frequency response curve.

→ To plot this curve, we measure the voltage gain ( $\frac{V_{out}}{V_{in}}$ ) at different frequencies (over a frequency range) and plot it with the corresponding frequency value on a semi-log graph sheet.

→ The voltage gain is measured in Decibels (dBs), whereas the frequencies are taken on log scale.

Lower cut-off frequency ( $f_L$ ) :- This is the freq at which the gain of amplifier rises to  $0.707 (or)  $\frac{1}{\sqrt{2}}$  of its midband gain. It is denoted by  $f_L$ .$

High cut-off Frequency ( $f_H$ ) :- This is the freq at which the gain of amplifier falls to  $0.707$  (or)  $\frac{1}{\sqrt{2}}$  of its midband gain. It is denoted by  $f_H$ .

Bandwidth :- The frequency range, extending from  $f_L$  to  $f_H$ , constitutes the bandwidth of the amplifier.

→ In this frequency range, the magnitude of gain remains constant,

⑤ ignoring the 3dB variation. In most cases  $f_H \gg f_L$   
Hence the bandwidth  $BW$  is given by,  
Band width ( $BW$ ) =  $f_H - f_L$   
 $\approx f_H$

### Low Frequency Response of Amplifier:-

The low freq response of the amplifier is the calculation of lower cut-off frequency of amplifier.

The lower cut-off freq. of amplifier due to  $C_b, C_o, C_e$ .


### Procedure to calculate the cut-off frequency of an Amplifier:-

- ① Draw the A.C. equivalent ckt of the given amplifier by considering all capacitors and all the sources (a.c and d.c) set equal to zero.
- ② Draw the a.c. equivalent ckt related to any one capacitor and remaining capacitors replaced by short circuit.
- ③ Calculate the equi-resistance looking across the terminals of capacitor, then the cut-off freq. due to that capacitor is


$$f_L = \frac{1}{2\pi R_{eq} C}$$

④ The cut-off freq. of the amplifier is the largest value of cut-off frequency due to  $C_b$ ,  $C_e$ ,  $C_c$ .


Example :-

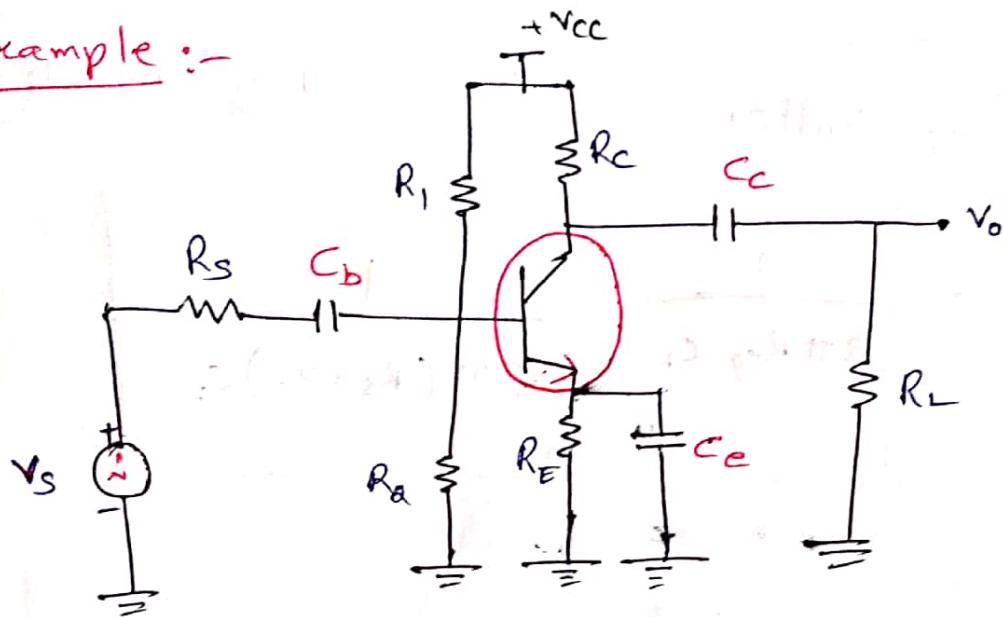


Step ① :-

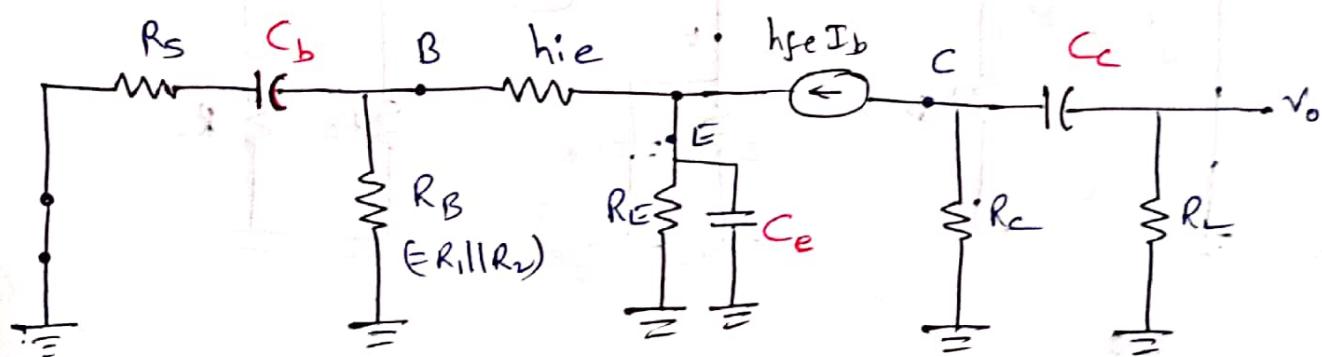

Step ② :-

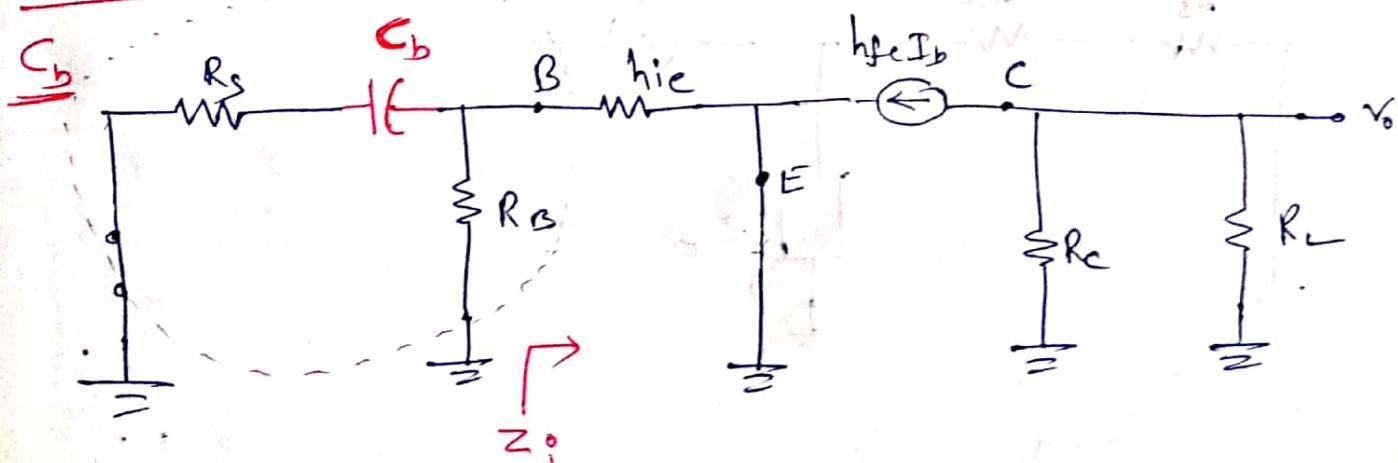


⑦ Step ③:-

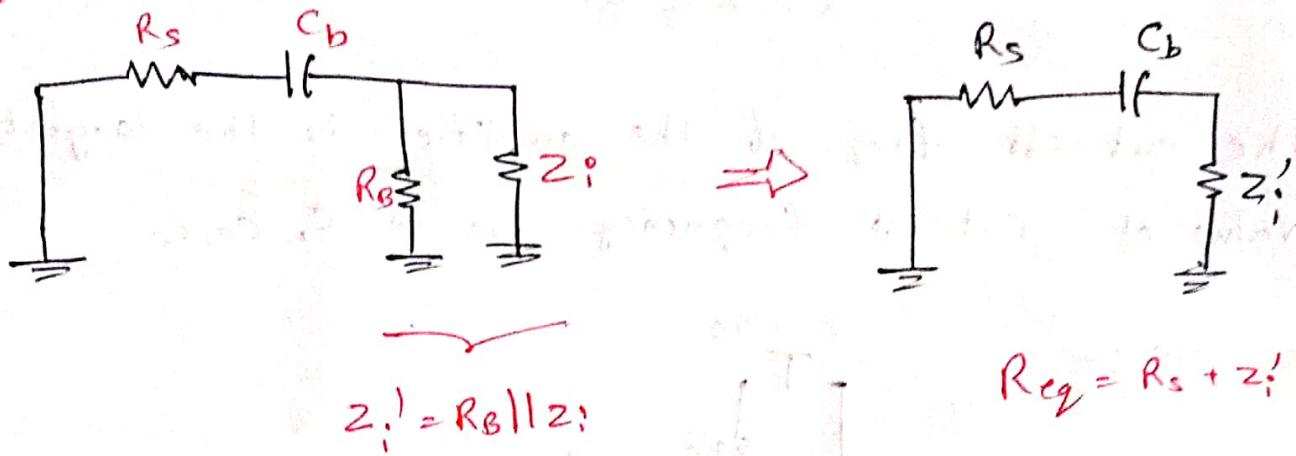


$$f_L = \frac{1}{2\pi R_{eq} C_b} = \frac{1}{2\pi (R_s + Z_i') C_b}$$


$C_e$

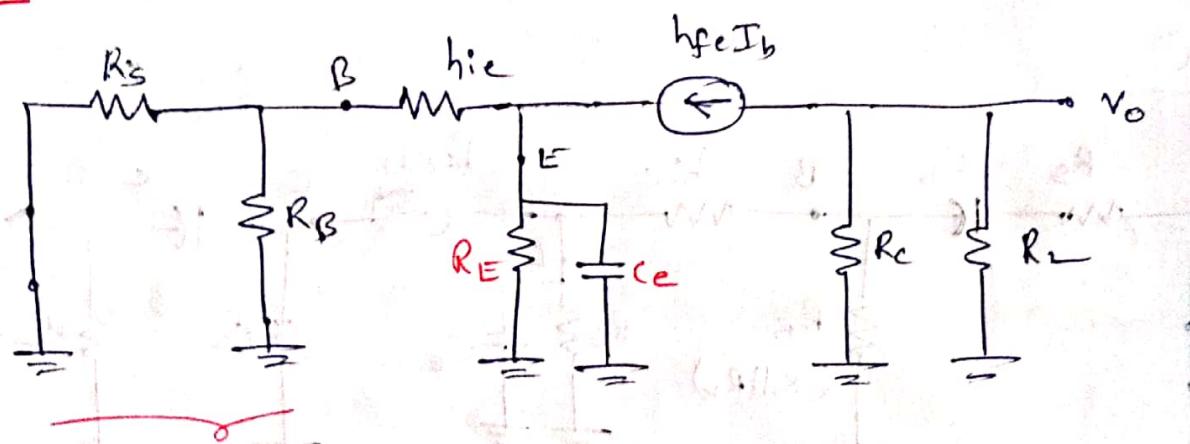

$$R_s' = R_s + R_B$$

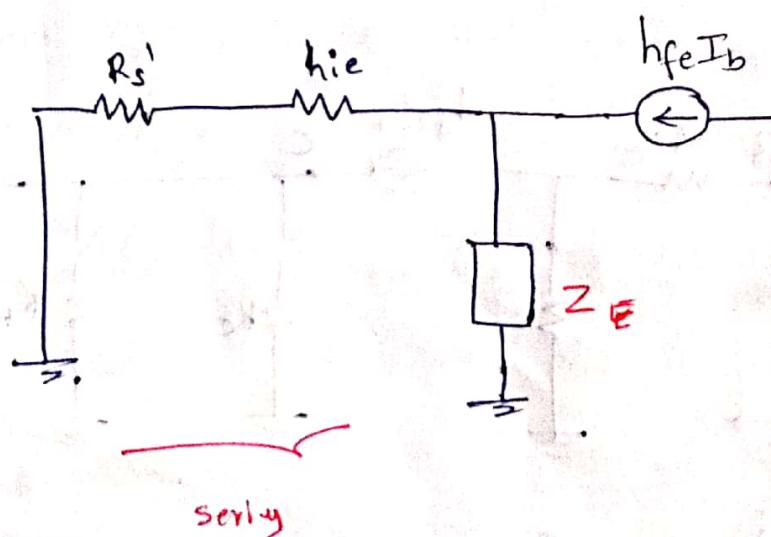

series

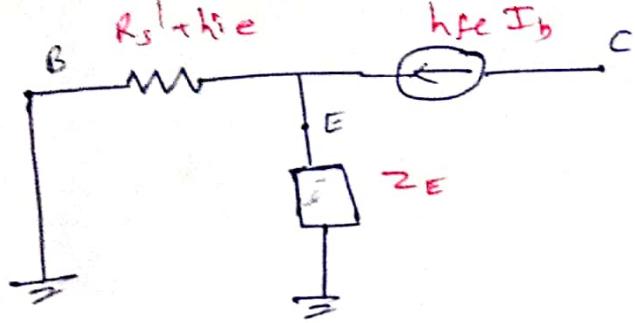


Apply KVL


$$I_b(R_s + h_{ie}) + (1 + h_{fe}) I_b Z_E = 0$$

$$I_b (1 + h_{fe}) \left[ \frac{R_s + h_{ie}}{1 + h_{fe}} + Z_E \right] = 0$$

$$\frac{R_s + h_{ie}}{1 + h_{fe}}$$

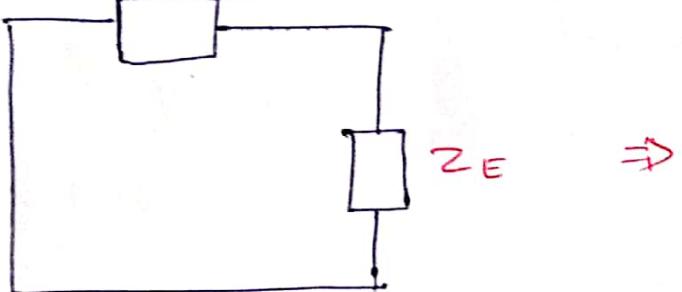


$$\frac{R_s + h_{ie}}{1 + h_{fe}}$$

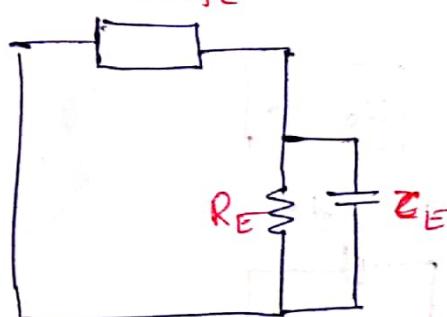

$$R_{eq} = R_E \parallel \frac{R_s + h_{ie}}{1 + h_{fe}}$$

$$f_{LCe} = \frac{1}{2\pi \left( R_E \parallel \frac{R_s + h_{ie}}{1 + h_{fe}} \right) C_e}$$

$C_C$

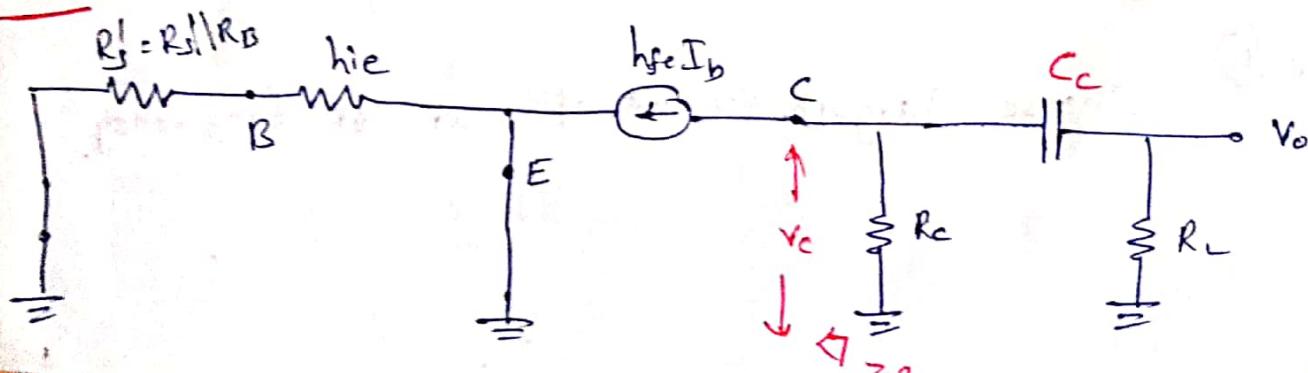

③ Apply KVL to i/p loop

$$I_b(R_s + h_{ie}) = 0$$

$$R_s + h_{ie} \neq 0, \quad I_b = 0$$


$$\therefore I_c = h_{fe} I_b$$

$$= h_{fe}(0) = 0$$

$$I_c = 0$$

$$\therefore Z_0 = \frac{V_o}{I_o} = \frac{V_o}{I_c} = \frac{V_o}{0} = \infty$$

$$Z_0 = \infty$$

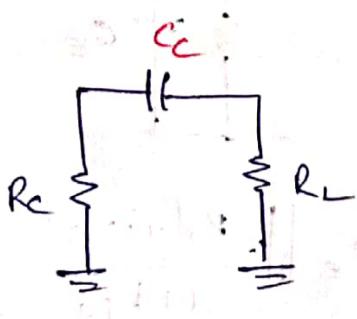

$$R_{eq} = R_c + R_L$$

$$f_{LCC} = \frac{1}{2\pi R_{eq} C_C} = \frac{1}{2\pi (R_c + R_L) C_C}$$

Step ④:-

Choose largest value of cut-off frequency.

Problem ① :-  $h_{ie} = 1 \text{ k}\Omega$ ,  $h_{fe} = 100$ ,  $R_S = R_E = 1 \text{ k}\Omega$ ,  $R_I = 16 \text{ k}\Omega$ ,  $R_A = 4 \text{ k}\Omega$ ,  $R_C = 3 \text{ k}\Omega$ ,  $R_L = 7 \text{ k}\Omega$ .  $C_b = C_c = 10 \mu\text{F}$ ,  $C_e = 100 \mu\text{F}$ .

Calculate lower-cut-off frequency of amplifier.

Sol:-

$C_b$

$$f_{Lc_b} = \frac{1}{2\pi(R_S + z_i') C_b}$$

$$\begin{aligned} z_i' &= z_i || R_B = h_{ie} || R_I || R_A \\ &= 1 \text{ k} || 16 \text{ k} || 4 \text{ k} \end{aligned}$$

$$\begin{aligned} &\left[ \text{where } z_i = h_{ie} \right] \\ &R_B = R_I || R_A \\ &= 3.2 \text{ k} \end{aligned}$$

$$f_{Lc_b} = \frac{1}{2 \times 3.14 \times (1 \times 10^3 + 0.7619 \times 10^3) \times 10 \times 10^{-6}}$$

$$f_{Lc_b} = 9.033 \text{ Hz}$$

$C_e$

$$f_{Lce} = \frac{1}{2\pi \left[ R_E || \frac{R_S' + h_{ie}}{1 + h_{fe}} \right] C_e}$$

$$R_S' = R_S || R_B = R_S || R_I || R_A = 1 \text{ k} || 16 \text{ k} || 4 \text{ k}$$

$$R_S' = 0.7619 \text{ k}\Omega$$

(11)

$$= \frac{1}{2 \times 3.14 \left[ 1K + \frac{0.7619K + 1K}{1+100} \right] \times 100 \times 10^{-6}}$$

$$f_{L_{ce}} = 92.826 \text{ Hz}$$

 $C_C$ 

$$f_{L_{cc}} = \frac{1}{2\pi(R_a + R_L)C_C}$$

$$= \frac{1}{2 \times 3.14 \times (3 \times 10^3 + 7 \times 10^3) \times 10 \times 10^{-6}}$$

$$f_{L_{cc}} = 1.59 \text{ Hz}$$

$$f_L = \max(f_{L_{cb}}, f_{L_{ce}}, f_{L_{cc}})$$

$$= \max(9.033, 92.826, 1.59)$$

$$f_L = 92.826 \text{ Hz}$$

## High Frequency Response of Amplifier:-



Calculate "Higher cut-off frequency" / Upper cut-off freq.

$$X_C = \frac{1}{2\pi f_C}$$

- At high frequencies, the h-parameters become complex in nature and varies with frequencies. So, that h-parameter model is not valid at high frequencies.
- At high freq's, Hybrid  $\pi$ -model is used.

## VII Hybrid - $\pi$ common Emitter Transistor model :-

$r_{bb}$  → Base spreading Resistance

( $r_{bb} \leq 100\Omega$  always)

$g_m$  → Transconductance

$r_{be}$  → reverse bias resistance



( $r_{be} \approx 4M\Omega$ , it is very high)

$r_{ce}$  → output resistance ( $80k\Omega$ )

$C_{be}$  → Diffusion capacitance ( $100\text{ pF}$ )

$C_{bc}$  → Transition capacitance ( $1\text{ pF}$ )

(13)

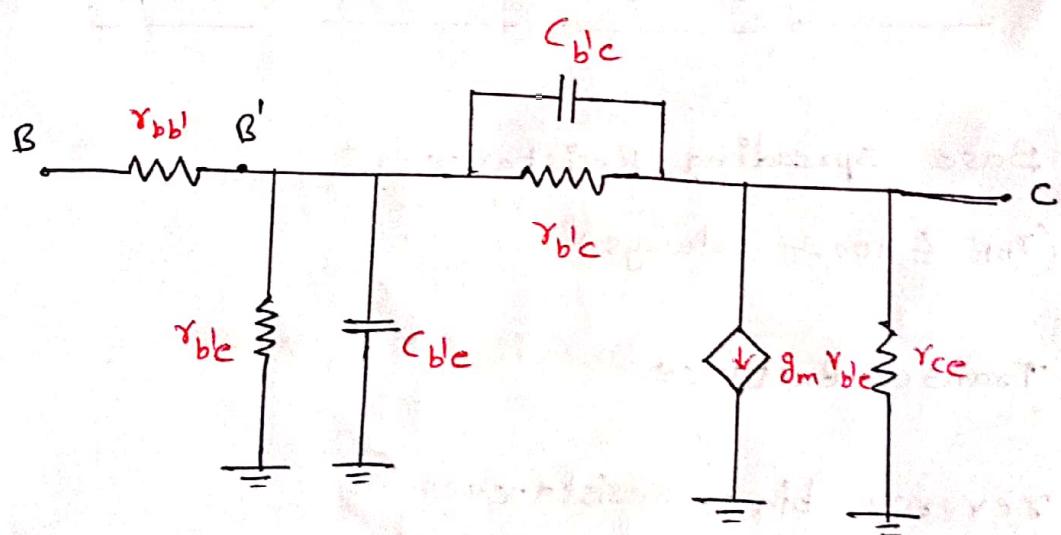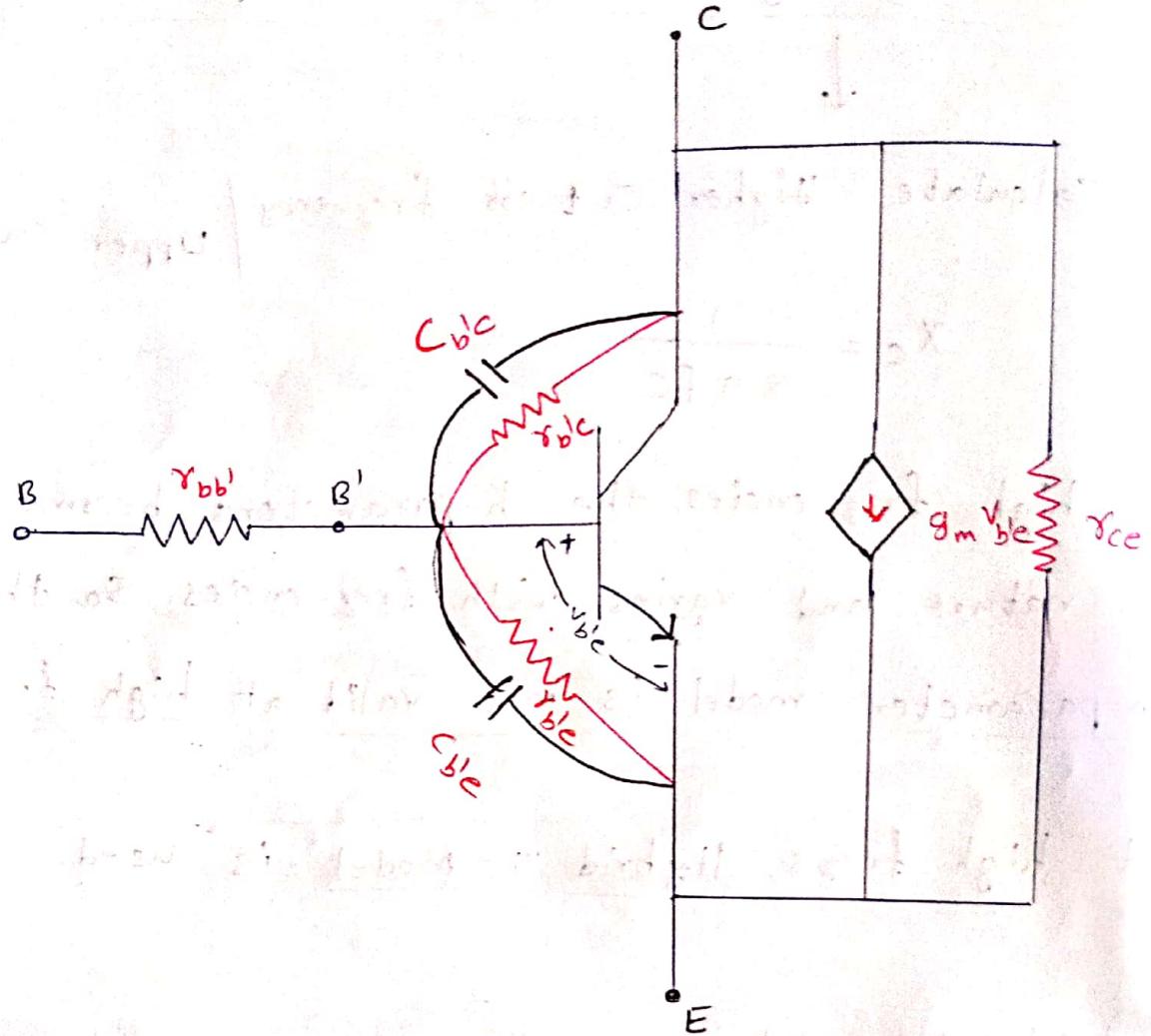

Equivalent circuit diagram.

## Notation

14

$$\gamma_{ble} \rightarrow \gamma_\pi, \gamma_{be}, \gamma_e$$

$$c_{ble} \rightarrow c_\pi, c_{be}, c_e$$

$$v_{ble} \rightarrow v_\pi, v_{be}, v_e$$

$$\gamma_{b'c} \rightarrow \gamma_u, \gamma_{bc}, \gamma_c$$

$$c_{b'c} \rightarrow c_u, c_{bc}, c_c$$



→ At low frequency, hybrid -  $\pi$  model, h-parameter model,  $\gamma_e - c_e$  model same.

→ high freq  $\xrightarrow[\text{becomes}]{}$  low freq.

at  $c_{ble} \& c_{b'c} \rightarrow$  open ckt

$\gamma_{b'c} \& \gamma_{ce} \rightarrow$  neglected (due to high value)

$$X_C \rightarrow \infty$$

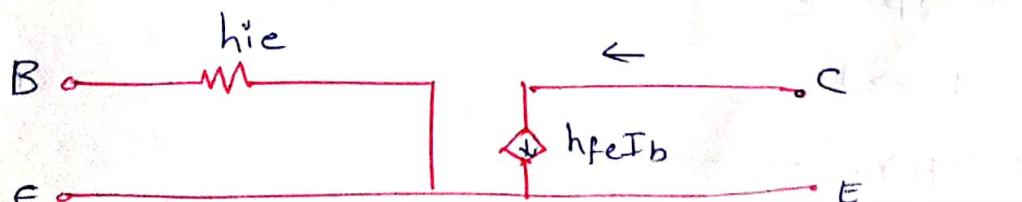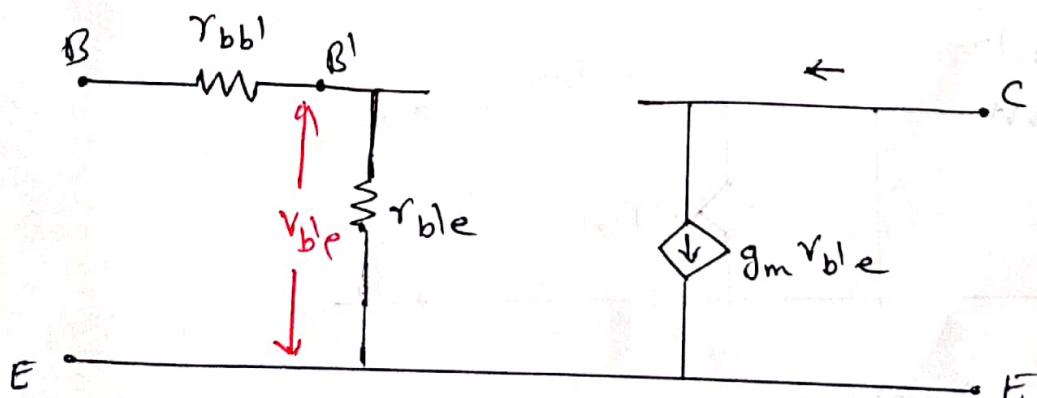

(15) compare to circuit diagram

$$I_c = h_{fe} I_b \quad I_b = g_m V_{be} \quad \text{--- } ①$$

$$I_c = \beta I_b$$

$$h_{fe} I_b = \beta I_b$$

$$\boxed{h_{fe} = \beta}$$

∴ from eqn ①,

$$h_{fe} I_b = g_m V_{be}$$


$$h_{fe} I_b = g_m I_b r_{be} \quad [\because V_{be} = I_b r_{be}]$$

$$h_{fe} = g_m r_{be}$$

$$\boxed{h_{fe} = g_m r_{be} = \beta} \quad \text{--- } ②$$

from circuits,
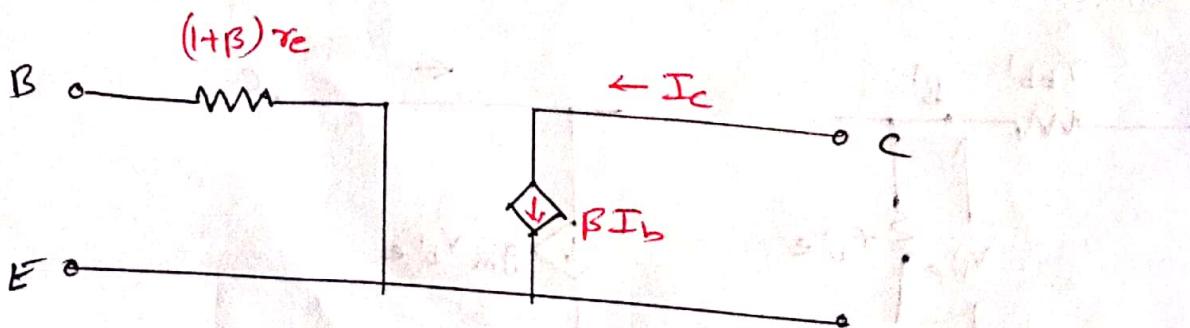
$$h_{ie} = r_{bb} + r_{be} = (1+\beta) r_e \quad [\because h_{fe} = \beta]$$



$$h_{ie} = (1+\beta) r_e$$

$$\beta \gg 1$$

$$h_{ie} \approx \beta r_e \quad \text{--- } ③$$

$\therefore$  from eqn(2),  $h_{ie} \approx g_m \gamma_{be} \gamma_e$  [  $\because \beta = g_m \gamma_{be}$  ]

$$\text{but } g_m = \frac{1}{\gamma_e}, \gamma_e = \frac{V_T}{I_C}$$

$$h_{ie} = \frac{I_C}{V_T} \cdot \gamma_{be} \cdot \frac{V_T}{I_C}$$

$$h_{ie} = \gamma_{be} = \beta \gamma_e$$

[  $\because$  from eqn(3) ]


$$h_{fe} = \beta = g_m \gamma_{be}$$


$$h_{fe} = \beta = g_m h_{ie}$$

$$h_{fe} = g_m h_{ie}$$

$$g_m = \frac{h_{fe}}{h_{ie}} \rightarrow \text{Transconductance.}$$
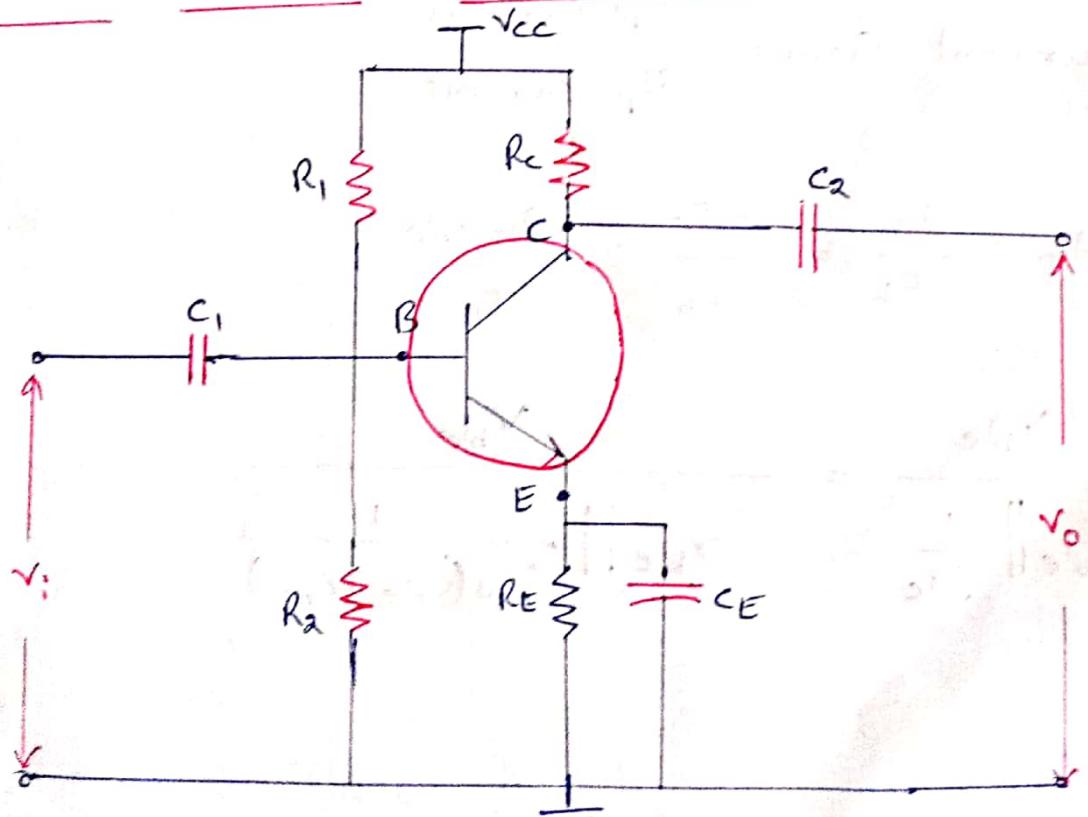
### Common Emitter Short-Circuit Chain of Amplifier:-



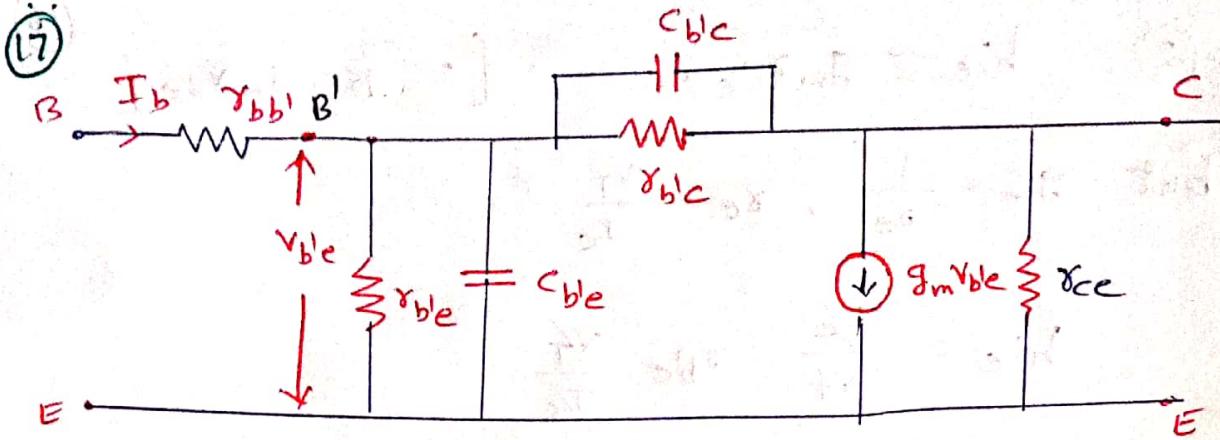


Equivalent hybrid-II model of CE Amplifier

Assumptions:

①  $r_{b'c}$  is neglected since  $r_{b'c} \gg r_{b'e}$

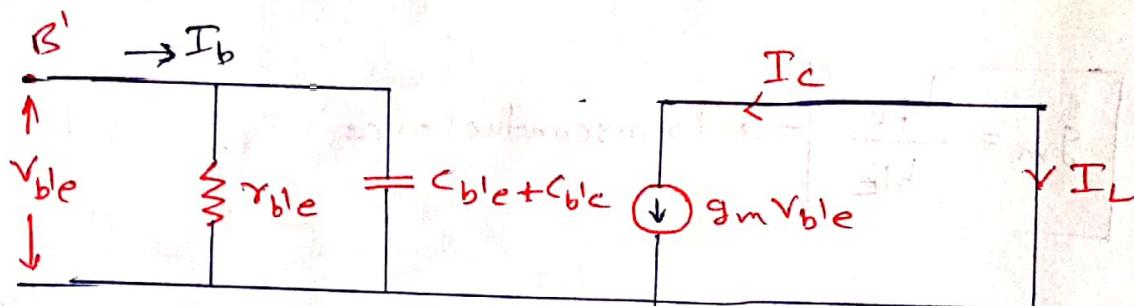②  $r_{ce}$  disappears, since it is shunt with s.c.



$$\text{Current Gain} = \frac{\text{olp current}}{\text{ilp current}}$$

$$\therefore A_I = \frac{I_L}{I_b} = \frac{-I_c}{I_b} = \frac{-g_m V_{ble}}{I_b}$$

$$I_b = \frac{V_{ble}}{r_{b'e} \parallel \frac{1}{j\omega C}} = \frac{V_{ble}}{r_{b'e} \parallel \frac{1}{j\omega (C_{ble} + C_{bc})}}$$

$$= \frac{V_{ble}}{\frac{1}{g_{ble}} + j\omega(C_{ble} + C_{b'c})} = \frac{V_{ble}}{\frac{1}{g_{ble}} + j\omega(C_{ble} + C_{b'c})}$$

$$= \frac{V_{ble}}{\frac{1}{g_{ble}} + j\omega(C_{ble} + C_{b'c})} = V_{ble} [g_{ble} + j\omega(C_{ble} + C_{b'c})]$$

$$\therefore A_I = \frac{-g_m V_{ble}}{I_b} = \frac{-g_m V_{ble}}{V_{ble} [g_{ble} + j\omega(C_{ble} + C_{b'c})]}$$

$$A_I = \frac{-g_m}{g_{ble} + j\omega(C_{ble} + C_{b'c})}$$

Dividing Numerator & Denominator by  $g_{ble}$ , we get

$$\frac{-g_m}{g_{ble}}$$

$$A_I(\omega) = \frac{\frac{g_{ble}}{g_{fe}} + \frac{j\omega(C_{ble} + C_{b'c})}{g_{ble}}}{1}$$

$$\text{but } g_m = \frac{h_{fe}}{h_{ie}} = \frac{h_{fe}}{g_{ble}} = h_{fe} \cdot g_{ble}$$

$$g_m = h_{fe} \cdot g_{ble}$$

$$\frac{g_m}{g_{ble}} = h_{fe}$$

29

$$A_I(\omega) = \frac{-h_{fe}}{1 + j\omega(C_{ble} + C_{b/c})\gamma_{ble}} \quad \text{--- (1)}$$

$\left[ \because \frac{1}{j\omega} = \gamma_{ble} \right]$

From Eqn(1), current gain is not constant, It depends on the frequency.

$$A_I(f) = \frac{-h_{fe}}{1 + j\left(\frac{f}{f_\beta}\right)}$$


where  $f_\beta = \frac{1}{2\pi\gamma_{ble}(C_{ble} + C_{b/c})}$

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_\beta}\right)^2}}$$

at  $f=0$ ,  $|A_I| = h_{fe} = \beta = 8m\gamma_{ble}$

$f=f_\beta$ ,  $|A_I| = \frac{h_{fe}}{\sqrt{2}} = 0.707 h_{fe}$

$f=\infty$ ,  $|A_I| = 0$

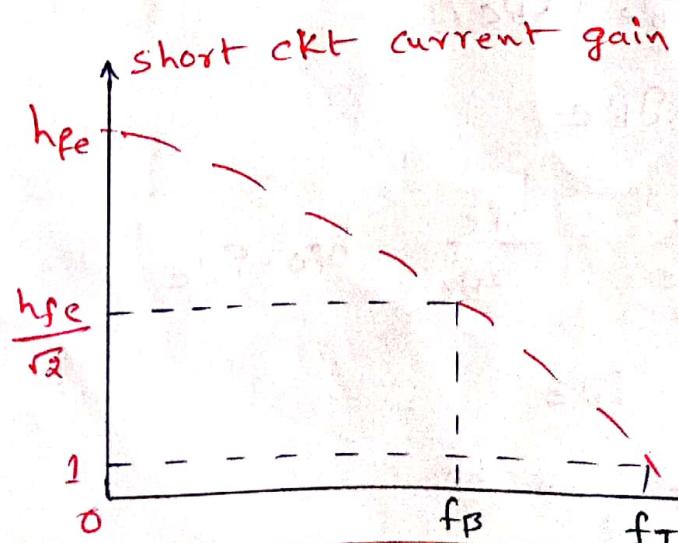


where  
 $f_\beta \rightarrow$  corner freq  
 $(\text{or})$   
 $\beta$  cut-off freq  
 $f_T \rightarrow$  Transition freq


$$f_B = \frac{1}{2\pi \gamma_{b'le} (C_{ble} + C_{b'lc})} = \frac{\gamma_{b'le}}{2\pi (C_{ble} + C_{b'lc})}$$

$$f_B = \frac{1}{h_{fe}} \left[ \frac{g_m}{2\pi (C_{ble} + C_{b'lc})} \right] \quad \left[ \gamma_{b'le} = \frac{g_m}{h_{fe}} \right]$$

Current Gain with Resistive Load :-

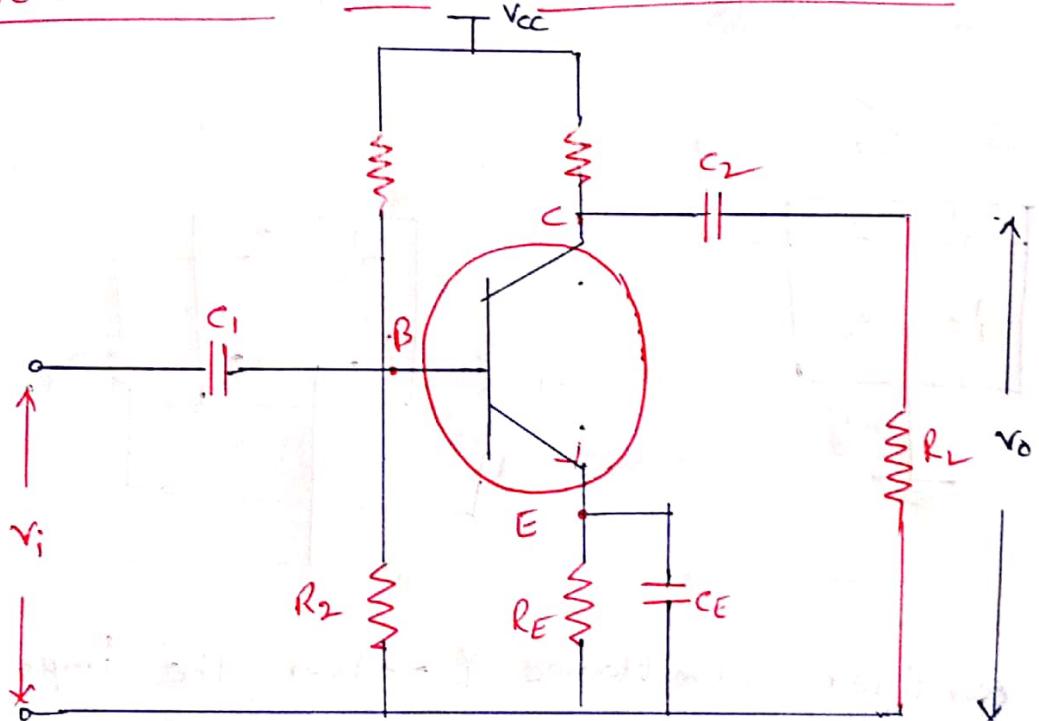

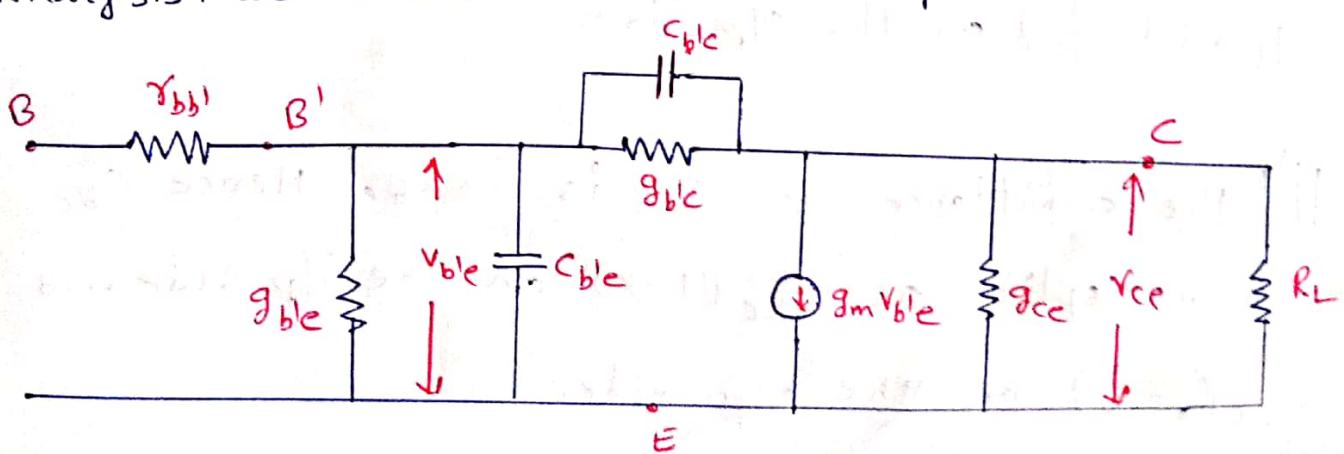
→ The Hybrid- $\pi$  model with a load resistance  $R_L$  is connected across collector & emitter terminals and To understand the analysis, we consider conductance in place of resistance.



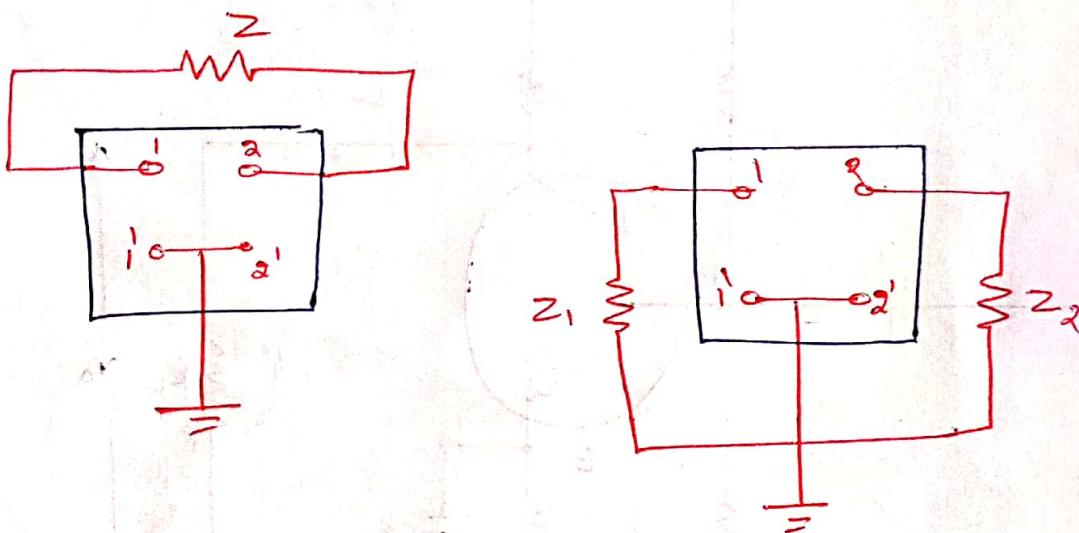(21) → The analysis get simplified by splitting the bridging elements  $C_{b'c}$  and  $g_{b'c}$  by miller theorem.


→ If an impedance  $Z$  is connected across i/p & o/p of an amplifier with gain  $K$  then it can be split into two impedances  $z_1$  and  $z_2$ .

where  $z_1 = \frac{Z}{1-K}$  and  $z_2 = \frac{Z \cdot K}{K-1}$



→ If we consider admittance  $Y$  rather the impedance  $Z$  then  $Y_1 = Y(1-K)$  and  $Y_2 = Y(1-\frac{1}{K})$ . Hence  $g_{b'c}$  can be split as  $g_{b'c}(1-K)$  on the i/p side and  $g_{b'c}(1-\frac{1}{K})$  on the o/p side.

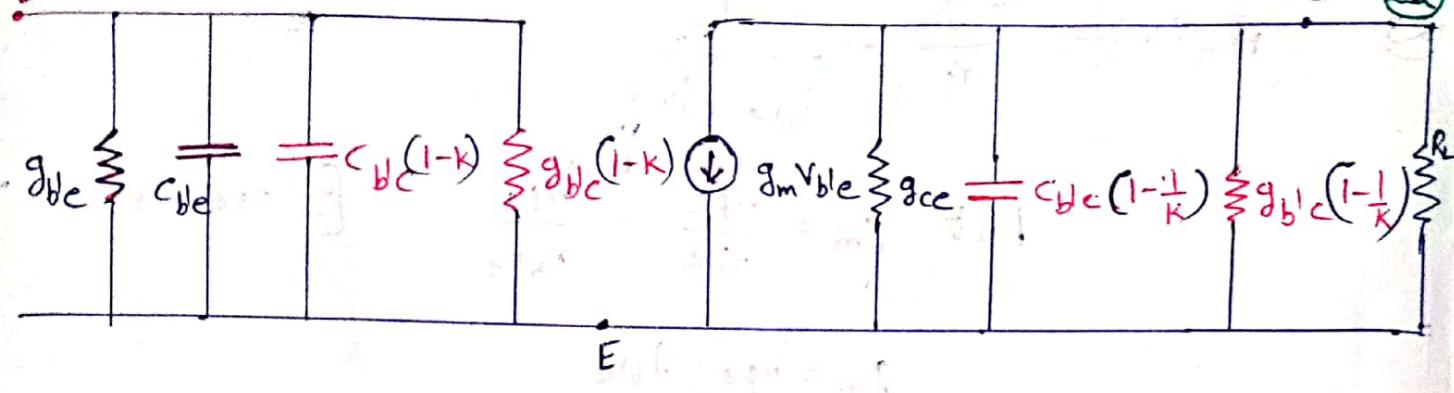→ If the admittance of  $C_{b'c}$  is  $j\omega C_{b'c}$ . Hence  $C_{b'c}$  can be split as  $C_{b'c}(1-K)$  on the i/p side and  $C_{b'c}(1-\frac{1}{K})$  on the o/p side.




→ The o/p side  $g_{ce}$ ,  $g_{b1c}(1 - \frac{1}{K})$  &  $j\omega C_{b1c}(1 - \frac{1}{K})$  are smaller than the load resistance and hence can be ignored.

$$\text{Voltage gain (K)}, \quad K = \frac{V_o}{V_i} = \frac{V_o}{V_{ble}} = \frac{I_L R_L}{V_{ble}} = \frac{-I_C R_L}{V_{ble}} = \frac{-g_m V_{ble} R_L}{V_{ble}}$$

$$K = -g_m R_L$$

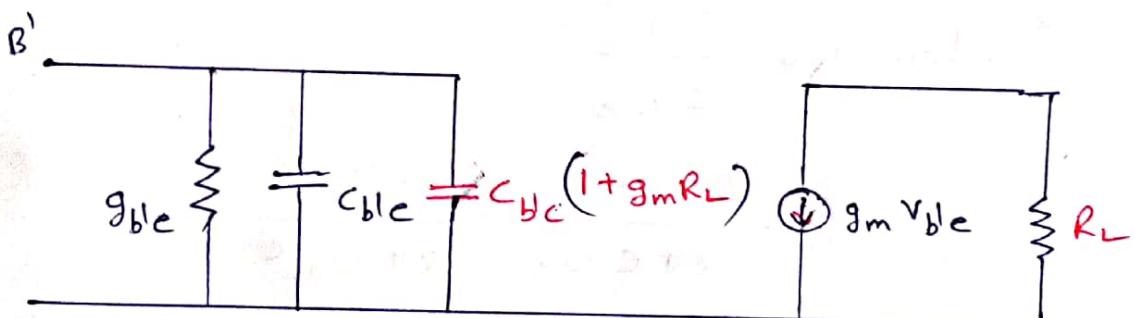→  $g_{b1c}(1-K)$  is smaller than  $g_{ble}$ , ignore  $g_{b1c}(1-K)$



Current gain ( $A_I$ ),

$$A_I = \frac{I_L}{I_i} = \frac{-g_m V_{ble}}{Y_i V_{ble}} = \frac{-g_m}{Y_i}$$

where  $Y_i = g_{ble} + j\omega [C_{ble} + C_{b1c}(1 + g_m R_L)]$

$$Y_i = g_{ble} + j\omega c$$

where,  $c = C_{ble} + C_{b1c}(1 + g_m R_L)$

$$(23) \quad A_I(\omega) = \frac{-g_m}{r_i} = \frac{-g_m}{g_{ble} + j\omega c}$$

$$\text{but } g_m = \frac{h_{fe}}{h_{ie}} = \frac{h_{fe}}{r_{ble}} \quad [ \because h_{fe} = r_{be} ]$$

$$g_m = h_{fe} \cdot g_{ble}$$

$$A_I(\omega) = \frac{-g_m}{g_{ble} + j\omega c} = \frac{h_{fe} g_{ble}}{g_{ble} + j\omega c} = \frac{-h_{fe} g_{ble}}{g_{ble} \left[ 1 + \frac{j\omega c}{g_{ble}} \right]}$$

$$= \frac{-h_{fe}}{1 + j\omega c \cdot r_{ble}}$$

$$A_I(\omega) = \frac{-h_{fe}}{1 + j\left(\frac{\omega}{\omega_H}\right)}$$

$$\text{where } \omega_H = \frac{1}{C r_{ble}}$$

$$f_H = \frac{(1)}{2\pi C r_{ble}} = \frac{1}{2\pi r_{ble} C}$$

$$\therefore A_I(\omega) = \frac{-h_{fe}}{1 + j\left(\frac{f}{f_H}\right)}$$

$$|A_I(\omega)| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

## Gain - Bandwidth Product :-

$$\begin{aligned}
 |A_{v_{\text{slow}}} f_H| &= |A_{v_{\text{so}}} f_H| = \frac{-h_{fe} \cdot R_L}{R_s + h_{ie}} \times \frac{1}{2\pi C_{eq} \cdot C_{eq}} \\
 &= \frac{-h_{fe} \cdot R_L}{R_s + h_{ie}} \times \frac{1}{2\pi C_{eq} \left[ \frac{\tau_{b'e}(\gamma_{bb} + R_s)}{\tau_{b'e} + \gamma_{bb} + R_s} \right]} \\
 &= \frac{-h_{fe} \cdot R_L}{R_s + h_{ie}} \times \frac{1}{2\pi C_{eq} \left[ \frac{\tau_{b'e}(\gamma_{bb} + R_s)}{h_{ie} + R_s} \right]} \\
 &\quad [\because h_{ie} = \tau_{b'e} + \gamma_{bb}] \\
 &= \frac{-h_{fe} \cdot R_L}{2\pi C_{eq} \left[ \tau_{b'e}(\gamma_{bb} + R_s) \right]} \\
 &= \frac{-g_m \tau_{b'e} \cdot R_L}{2\pi C_{eq} \tau_{b'e} (\gamma_{bb} + R_s)} \quad [\because h_{fe} = g_m \tau_{b'e}]
 \end{aligned}$$

$$|A_{v_{\text{so}}} \cdot f_H| = \frac{-g_m R_L}{2\pi C_{eq} (\gamma_{bb} + R_s)}$$

→ This eqn can be simplified as follow.  
where  $C_{eq} = C_e + C_c(1 + g_m R_L)$


$$\begin{aligned}
 |A_{v_{\text{so}}} \cdot f_H| &= \frac{g_m}{2\pi [C_e + C_c(1 + g_m R_L)]} \times \frac{R_L}{R_s + \gamma_{bb}} \\
 &= \frac{g_m}{2\pi [C_e + C_c(g_m R_L)]} \times \frac{R_L}{R_s + \gamma_{bb}} \quad [\because g_m R_L \gg 1] \\
 &= \frac{R_L}{R_s + \gamma_{bb}} \times \frac{2\pi f_T C_e}{2\pi [C_e + C_c(2\pi f_T C_e R_L)]} \\
 &\quad [\because g_m = 2\pi f_T C_e]
 \end{aligned}$$

Q5

$$= \frac{R_L}{R_S + r_{bbi}} \times \frac{\alpha \pi C_e f_T}{\alpha \pi C_e [1 + 2\pi f_T C_c R_L]}$$

$$\therefore |A_{vso} \times f_H| = \frac{R_L}{R_S + r_{bbi}} \times \frac{f_T}{1 + 2\pi f_T C_c R_L}$$
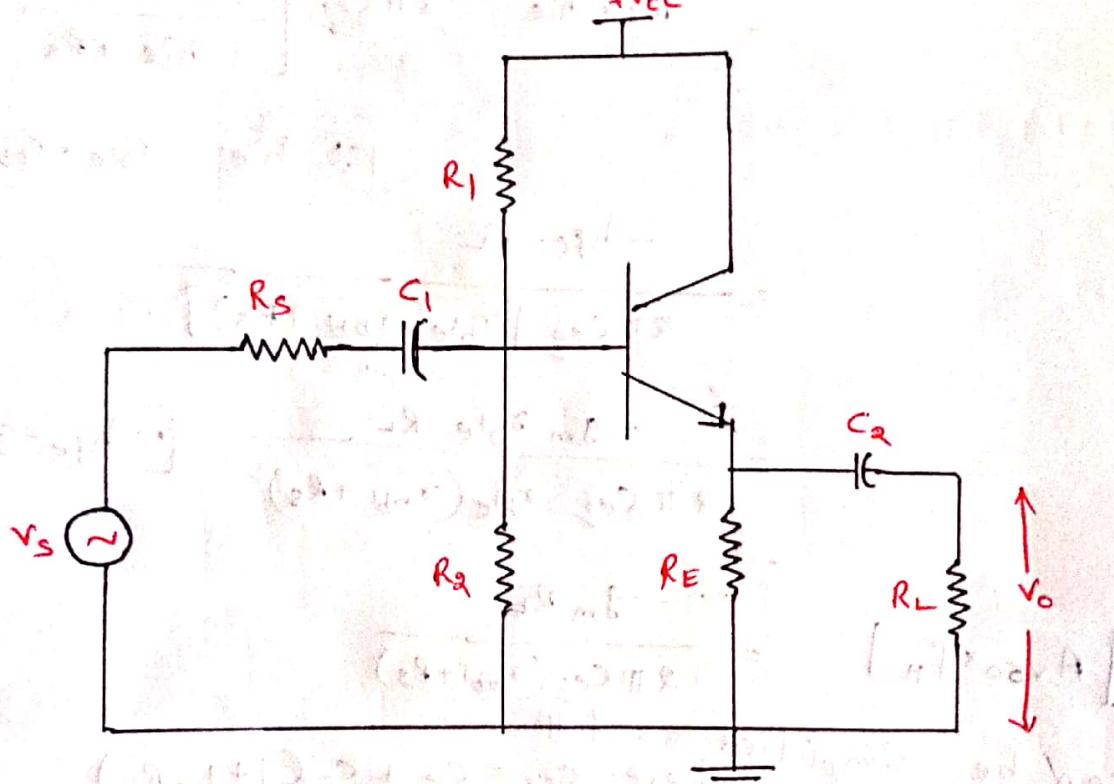
## XI. Emitter follower at high frequencies:-





→ Emitter-follower is the common collector amplifier at high frequency response.

### Procedure :-

- ① Draw the A.C. equivalent circuit of  $\pi$ -model parameter of the Transistor.
- ② All the capacitors i.e., coupling capacitors are short circuited at high frequencies.
- ③ All the A.C. and D.C. sources are made to zero.


# (26)
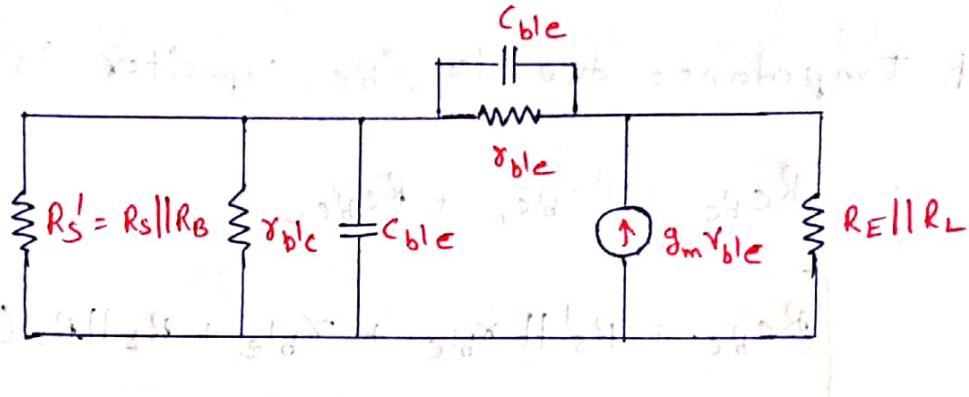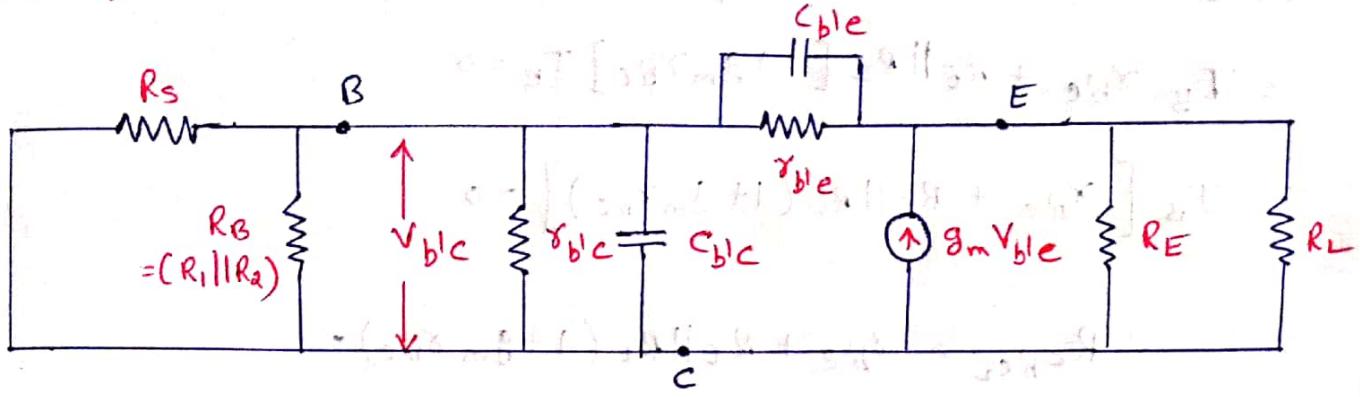
## A.C. equivalent circuit of emitter follower:



Frequency Response due to  $C_{ble}$ :

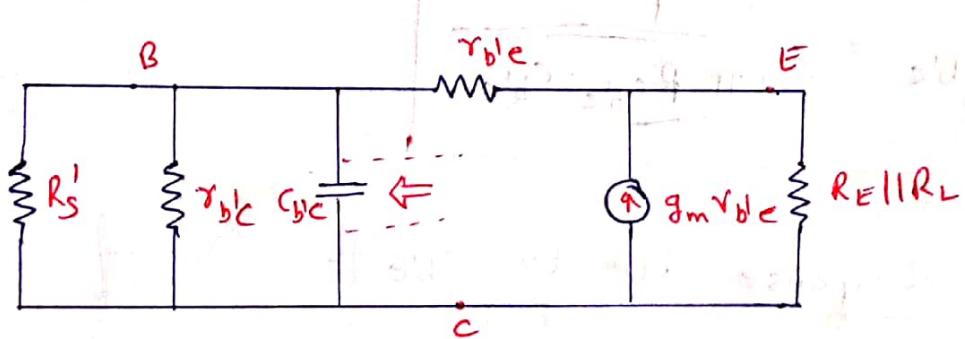Except  $C_{ble}$ , all capacitors are open circuited.



Impedance of the left side of  $C_{ble}$  capacitor

$$\text{i.e., } R_{C_{ble}} = R'_s \parallel r_{b'e}$$

Impedance of the right side of  $C_{ble}$  capacitor

$$\text{i.e., } I_E = I_B + I_C$$

$$= I_B + g_m V_{ble}$$

$$= I_B + g_m r_{b'e} I_B$$

$$I_E = I_B (1 + g_m r_{b'e})$$

(27) Apply KVL to the o/p loop

$$I_B \gamma_{ble} + R_E \parallel R_L [1 + g_m \gamma_{ble}] I_B = 0$$

$$I_B [\gamma_{ble} + R_E \parallel R_L (1 + g_m \gamma_{ble})] = 0$$

$$R_{Cble} = \gamma_{ble} + R_E \parallel R_L (1 + g_m \gamma_{ble})$$

Total Impedance due to  $C_{ble}$  capacitor is

$$R_{Cble} = R_{Cble_1} + R_{Cble_2}$$



$$R_{Cble} = R_s' \parallel \gamma_{ble} + \gamma_{ble} + R_E \parallel R_L (1 + g_m \gamma_{ble})$$

The frequency response due to  $C_{ble}$  capacitor is

$$f_{Cble} = \frac{1}{2\pi R_{Cble} C_{ble}}$$

Frequency Response due to  $C_{ble}$ :

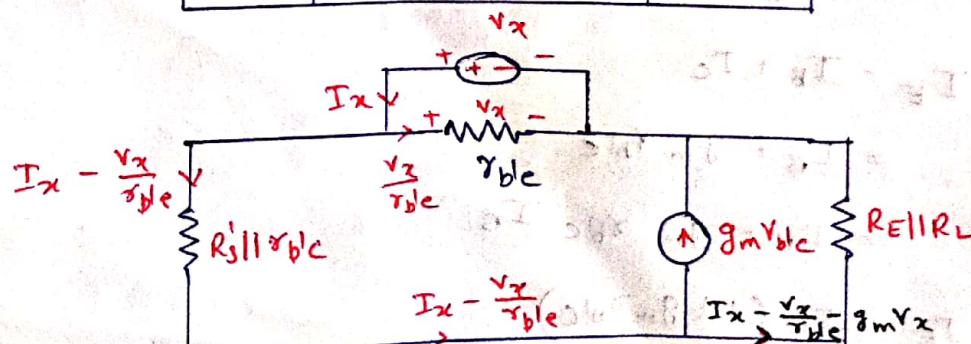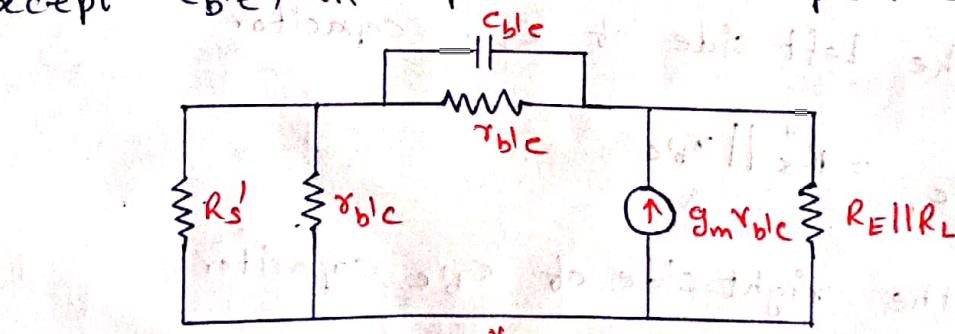Except  $C_{ble}$ , all capacitors are open circuited.



28

Apply KVL to the above ckt

$$v_x - (R_s' \parallel r_{b'e}) \left[ I_x - \frac{v_x}{r_{b'e}} \right] - (R_E \parallel R_L) \left[ I_x - \frac{v_x}{r_{b'e}} - g_m v_x \right] = 0$$

$$v_x - (R_s' \parallel r_{b'e}) I_x + (R_s' \parallel r_{b'e}) \frac{v_x}{r_{b'e}} - (R_E \parallel R_L) I_x + (R_E \parallel R_L) \frac{v_x}{r_{b'e}}$$

Left side of eqn. + (RE || RL) gm vx = 0

$$v_x + \frac{v_x}{r_{b'e}} (R_s' \parallel r_{b'e}) + \frac{v_x}{r_{b'e}} (R_E \parallel R_L) + g_m v_x (R_E \parallel R_L)$$

$$= I_x (R_s' \parallel r_{b'e}) + I_x (R_E \parallel R_L)$$

$$v_x \left[ 1 + \frac{R_s' \parallel r_{b'e}}{r_{b'e}} + \frac{R_E \parallel R_L}{r_{b'e}} + g_m (R_E \parallel R_L) \right] = I_x \left[ (R_s' \parallel r_{b'e}) + (R_E \parallel R_L) \right]$$

$$v_x \left[ \frac{R_s' \parallel r_{b'e}}{r_{b'e}} + \frac{R_E \parallel R_L}{r_{b'e}} + 1 + g_m (R_E \parallel R_L) \right] = I_x \left[ (R_s' \parallel r_{b'e}) + (R_E \parallel R_L) \right]$$

$$v_x \left[ \frac{1}{r_{b'e}} (R_s' \parallel r_{b'e} + R_E \parallel R_L) + (1 + g_m (R_E \parallel R_L)) \right] = I_x \left[ R_s' \parallel r_{b'e} + R_E \parallel R_L \right]$$

$$\frac{I_x}{v_x} = \frac{1}{r_{b'e}} \frac{R_s' \parallel r_{b'e} + R_E \parallel R_L}{R_s' \parallel r_{b'e} + R_E \parallel R_L} + \frac{1 + g_m (R_E \parallel R_L)}{R_s' \parallel r_{b'e} + R_E \parallel R_L}$$

$$\boxed{\frac{I_x}{v_x} = \frac{1}{r_{b'e}} + \frac{1 + g_m (R_E \parallel R_L)}{R_s' \parallel r_{b'e} + R_E \parallel R_L}}$$

$$\boxed{R_{C_{b'e}} = \frac{v_x}{I_x}}$$

Frequency Response due to  $C_{b'e}$  capacitor is

$$\boxed{f_{C_{b'e}} = \frac{1}{2\pi R_{C_{b'e}} \cdot C_{b'e}}}$$



①

## UNIT - II (b)

### Mos. Amplifiers


#### I Basic Concept:-


FET is a device in which the current flowing in the conduction region is controlled by o/p electric field, so it is called

Field Effect Transistor (FET)

→ In BJT → o/p current is controlled by o/p current.

In FET → o/p voltage.

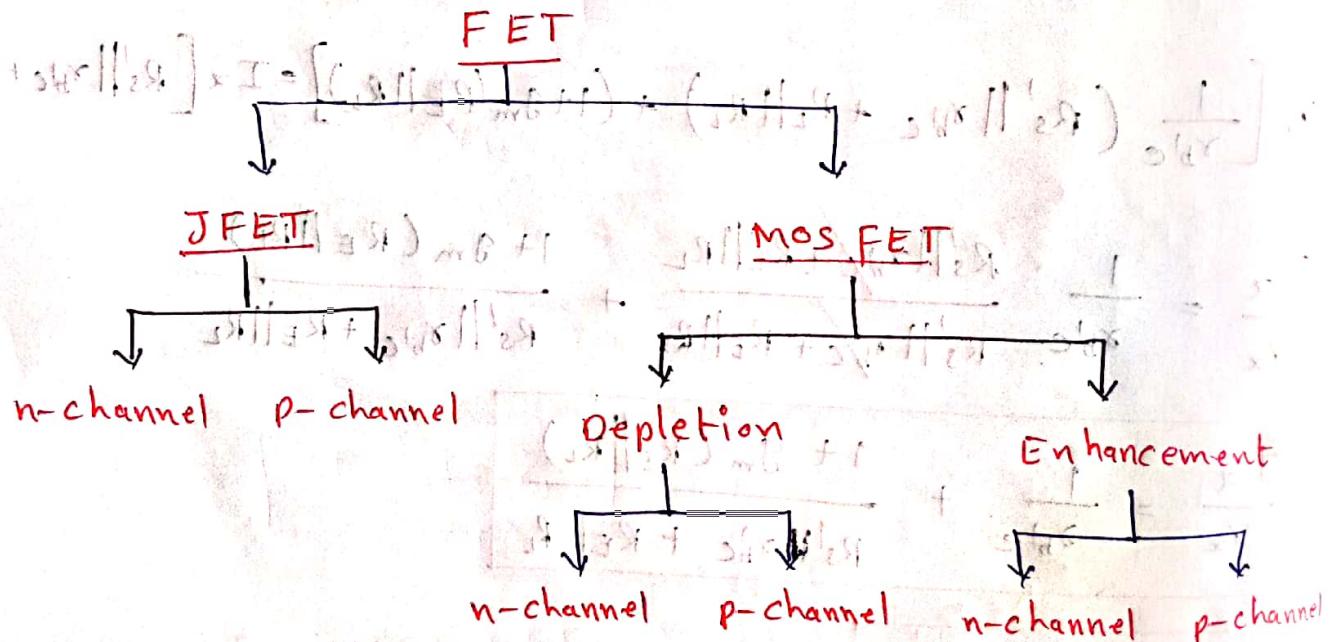

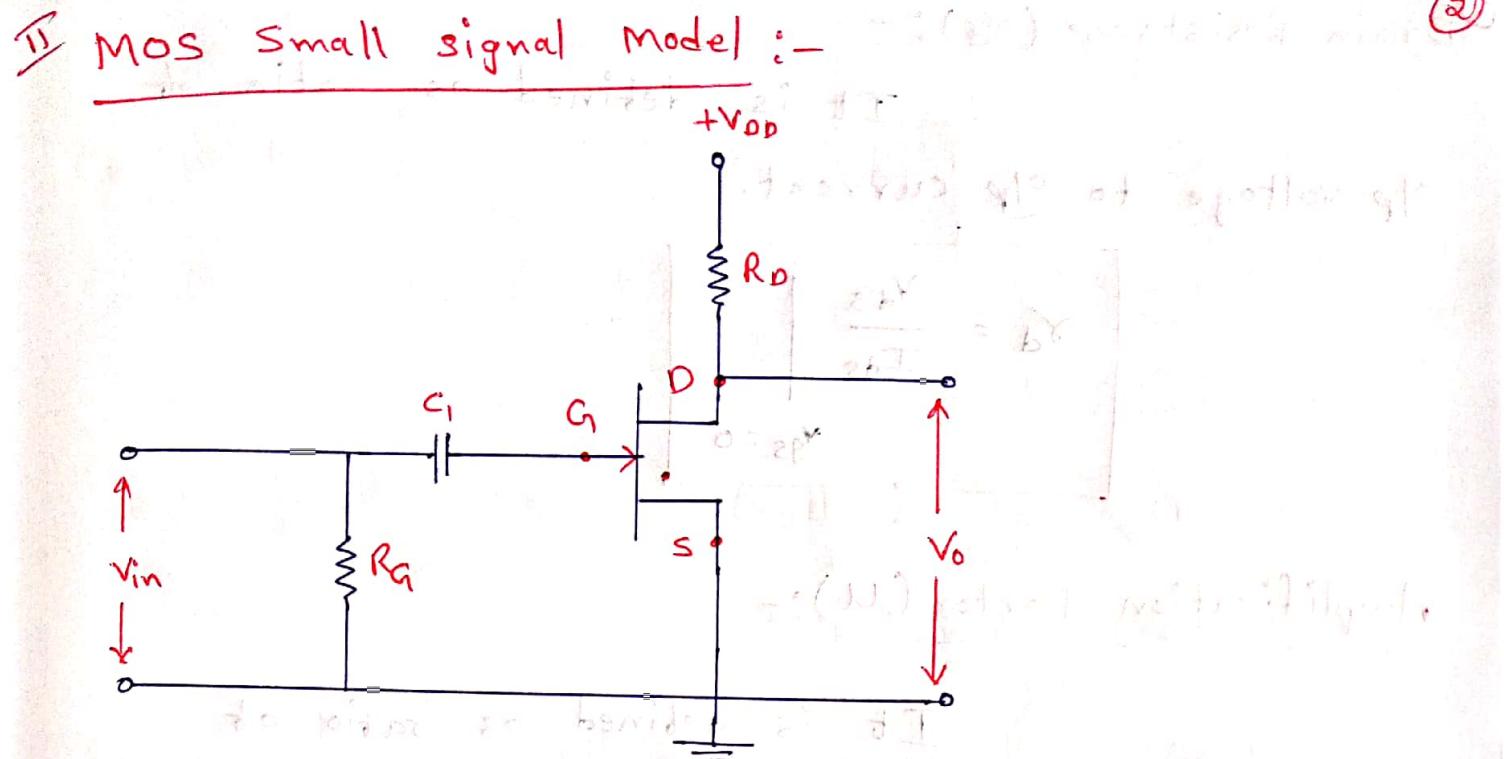

$$R_G = \frac{V_G}{I_G}$$

Theoretical


$$I_G \approx 0$$

$$R_G = \frac{V_G}{0} = \infty \text{ (open circuit)}$$

Practical

$$I_G = 10^{-9}$$
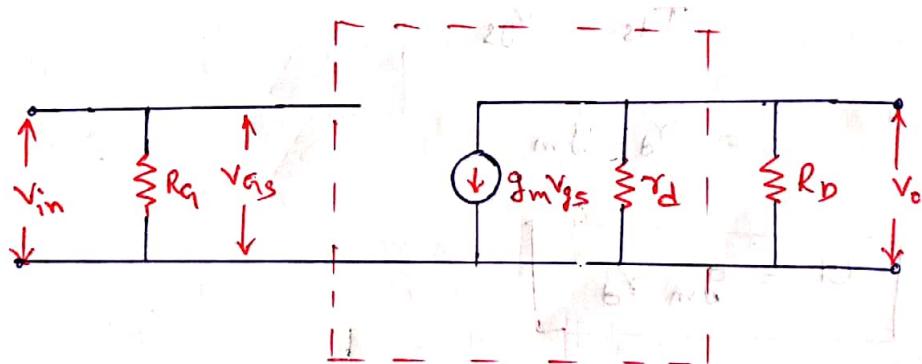
$$R_G = \frac{V_G}{10^{-9}} = 1000 \text{ M}\Omega$$



FET Parameters :-

Transconductance ( $g_m$ ) :- It is defined as the ratio of o/p current to i/p voltage.

$$g_m = \frac{I_{ds}}{V_{gs}} \quad |_{V_{ds}=0}$$

### ③ Drain Resistance ( $\gamma_d$ ):-

It is defined as ratio of o/p voltage to o/p current.

$$\boxed{\gamma_d = \frac{V_{ds}}{I_{ds}} \quad | \quad V_{gs} = 0}$$

### Amplification Factor ( $M$ ):-

It is defined as ratio of o/p voltage to i/p voltage.



$$M = \frac{V_{ds}}{V_{gs}} \quad | \quad I_{ds} = 0$$

$$\begin{aligned} M &= \frac{V_{ds}}{V_{gs}} \cdot \frac{I_{ds}}{I_{ds}} \\ &= \gamma_d \cdot g_m \end{aligned}$$

$$\boxed{M = g_m \gamma_d}$$
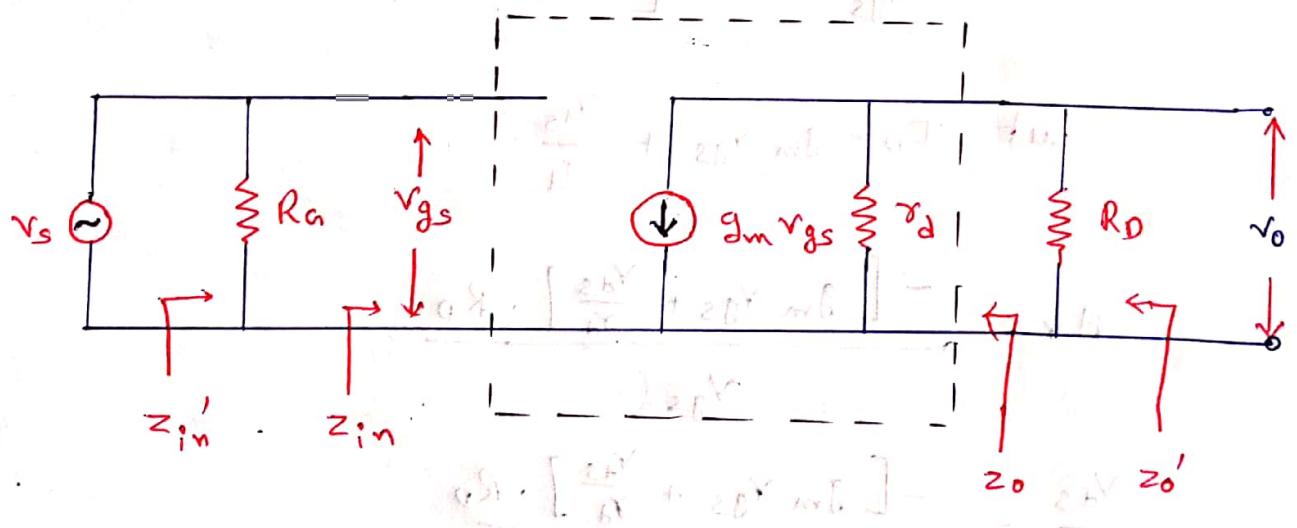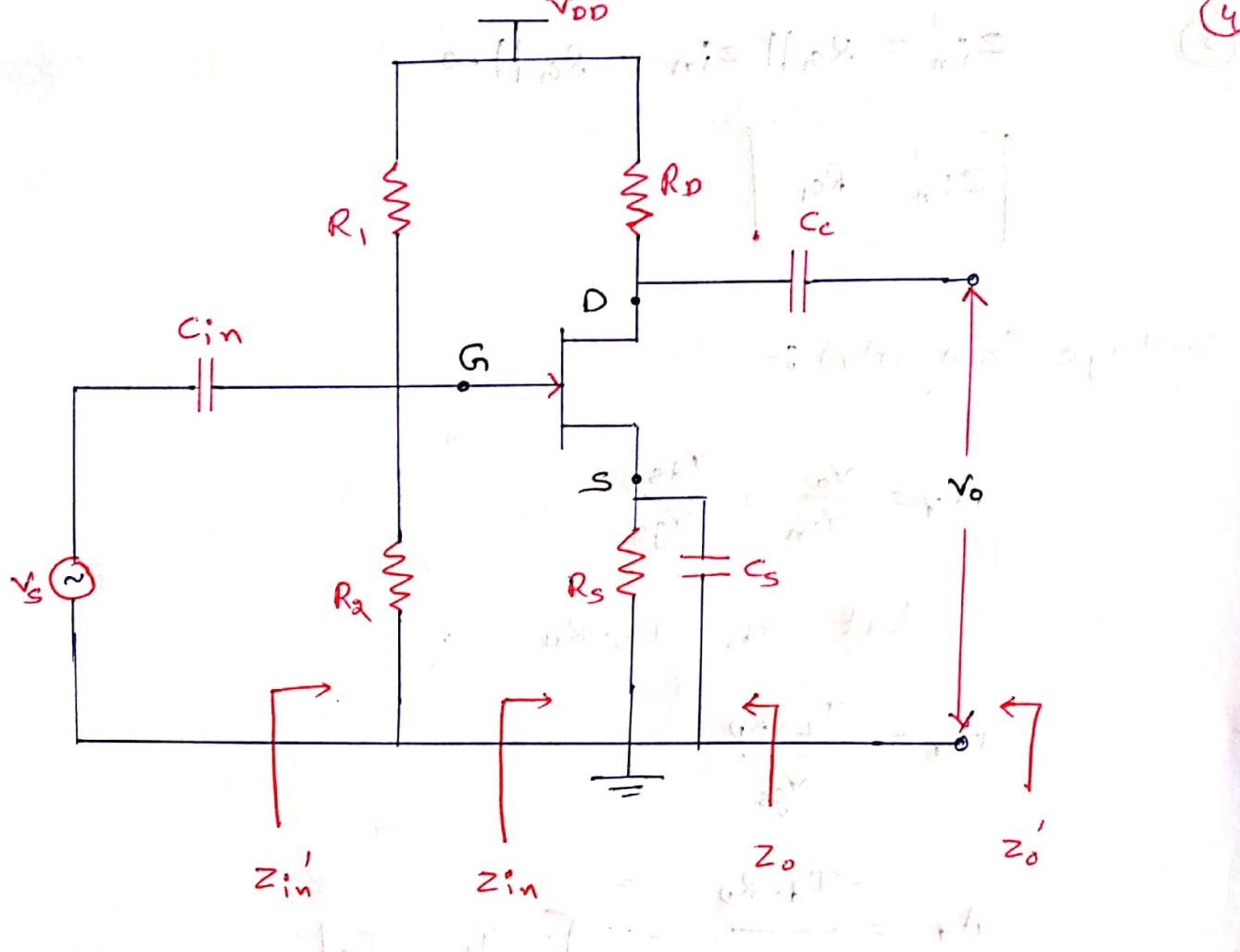
### IV Common Source FET Amplifier:-

The i/p current is very low value nA or pA i.e., negligible that's why FET device is not used for current amplification purpose.



Input Impedance ( $z_{in}$ ) :-

$$z_{in} = \frac{V_g}{I_g} R_i \left[ \frac{2^f}{R_i} + 2^f \text{ mho} \right] = 2^f \text{ mho}$$

but  $I_g = 0$

$$z_{in} = \frac{V_g}{0} \text{ mho}$$

$\boxed{z_{in} = \infty \text{ mho}}$

(5)

$$Z_{in}' = R_a \parallel Z_{in} = R_a \parallel \infty$$

$$Z_{in}' = R_a$$

Voltage Gain (Av) :-

$$A_v = \frac{V_o}{V_{in}} = \frac{V_{ds}}{V_{gs}}$$

$$\text{but } V_{ds} = I_L \cdot R_D$$

$$A_v = - \frac{I_L \cdot R_D}{V_{gs}}$$

$$A_v = - \frac{-I_D \cdot R_D}{V_{gs}} \quad [ \because I_L = -I_D ]$$

$$\text{but } I_D = g_m V_{gs} + \frac{V_{ds}}{r_d}$$

$$A_v = - \frac{-[g_m V_{gs} + \frac{V_{ds}}{r_d}] \cdot R_D}{V_{gs}}$$

$$\frac{V_{ds}}{V_{gs}} = - \frac{-[g_m V_{gs} + \frac{V_{ds}}{r_d}] \cdot R_D}{V_{gs}}$$

$$V_{ds} = - \left[ g_m V_{gs} + \frac{V_{ds}}{r_d} \right] \cdot R_D$$

$$V_{ds} = -g_m V_{gs} R_D - \frac{V_{ds}}{r_d} \cdot R_D$$

$$V_{ds} + \frac{V_{ds}}{r_d} R_D = -g_m V_{gs} R_D$$

$$V_{ds} \left(1 + \frac{R_D}{\gamma_d}\right) = -g_m V_{gs} R_D$$

$$\frac{V_{ds}}{V_{gs}} \left(1 + \frac{R_D}{\gamma_d}\right) = -g_m R_D$$

$$\frac{V_{ds}}{V_{gs}} = \frac{-g_m R_D}{\left(1 + \frac{R_D}{\gamma_d}\right)}$$

$$= \frac{-g_m R_D}{\left(\frac{\gamma_d + R_D}{\gamma_d}\right)}$$

$$= \frac{-g_m \cdot \gamma_d \cdot R_D}{\gamma_d + R_D}$$

$$= -g_m \cdot \left( \frac{\gamma_d \cdot R_D}{\gamma_d + R_D} \right)$$

$$A_V = \frac{V_{ds}}{V_{gs}} = -g_m \cdot (\gamma_d || R_D)$$

Output Impedance ( $Z_o$ ):-

$$Z_o = \frac{V_{ds}}{I_{ds}} \quad \Bigg|_{V_{gs}=0}$$

$$\text{but } I_{ds} = g_m V_{gs} + \frac{V_{ds}}{R_s}$$

$$\text{where } V_{gs} = 0$$

$$I_{ds} = 0 + \frac{V_{ds}}{\gamma_d} = \frac{V_{ds}}{\gamma_d}$$

(7)

$$I_{ds} = \frac{V_{ds}}{\gamma_d}$$

$$I_{ds} \cdot \gamma_d = V_{ds}$$

$$\gamma_d = \frac{V_{ds}}{I_{ds}}$$

$$\therefore Z_0 = \frac{\gamma_{ds}}{I_{ds}} = \gamma_d$$

$$Z_0' = \gamma_d \parallel R_D$$



## UNIT - III (a)

### Feedback Amplifier

#### Syllabus

- ① Concepts of Feedback
- ② Classification of Feedback Amplifiers.
- ③ General characteristic of Negative Feedback Amplifier
- ④ Effect of Feedback on Amplifier characteristics
  - Voltage series feedback Configuration
  - " shunt "
  - Current series "
  - " shunt "
- ⑤ Illustrative Problems.

#### Introduction :-

Feedback plays an important role in almost all electronic circuits.

→ Feedback is process whereby a portion of the op signal of the amplifier is fed back to the ip of the amplifier.

→ The feedback signal can be either voltage or current, being applied in series or shunt respectively with the i/p signal.

→ The path over which the feedback is applied is the feedback loop.


## (1) Concept of Feedback:-

Feedback is nothing but a simple passive network which is used to improve the performance of amplifiers.


→ It is a process in which a part of the o/p voltage is taken and mixed with i/p. This technique is two methods as follows

① Negative Feedback

② Positive Feedback

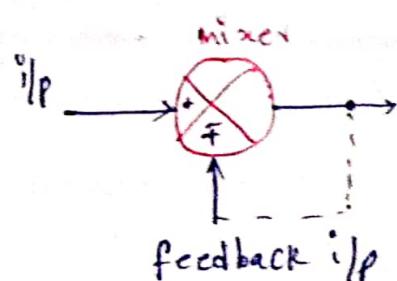

## ① Negative Feedback:-

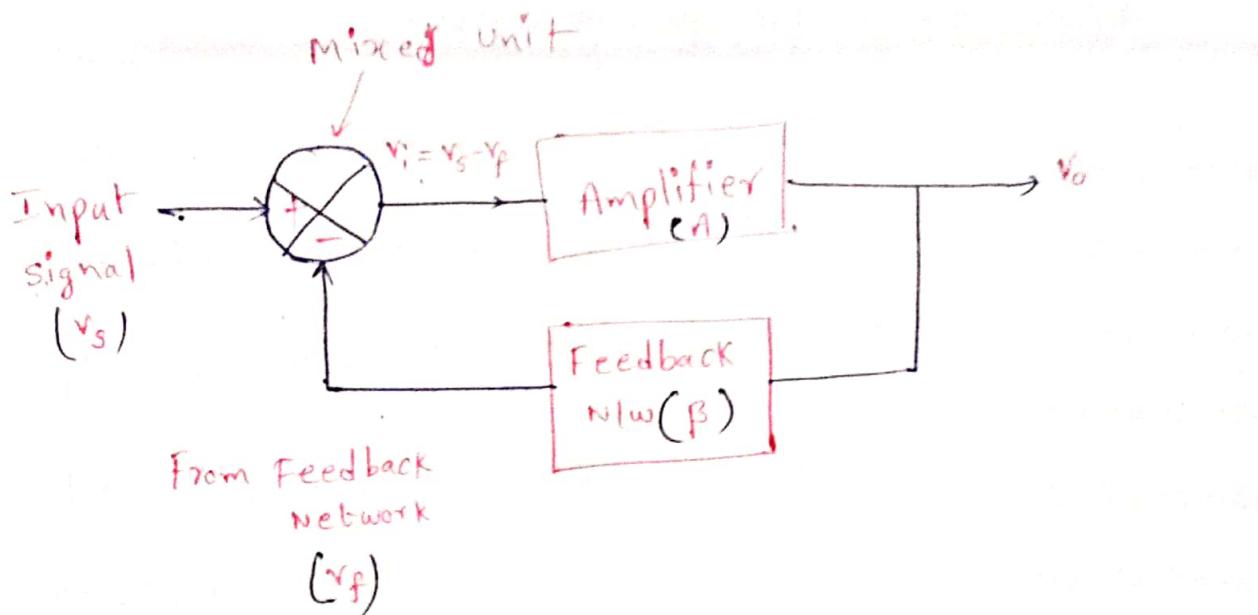

→ The feedback voltage  $v_f$  was opposite phase to the i/p voltage  $v_s$ , thereby the resultant input voltage  $v_i$  to the amplifier became the difference of the external i/p voltage  $v_s$  and the feedback voltage  $v_f$ ,

$$\text{i.e., } v_i = v_s - v_f$$

→ The resultant i/p to the amplifier is reduced the o/p of the amplifier also reduce voltage.


In otherwards, the gain of the amplifier reduce because of the feedback. This type of feedback is known 've feedback (or) degenerative feedback.'

## ② Positive Feedback :-

Another one possibility exists in feedback is called positive feedback. That is the feedback voltage can be in the same phase as the external input voltage.

In this case, the effective input to the amplifier is increased obviously,

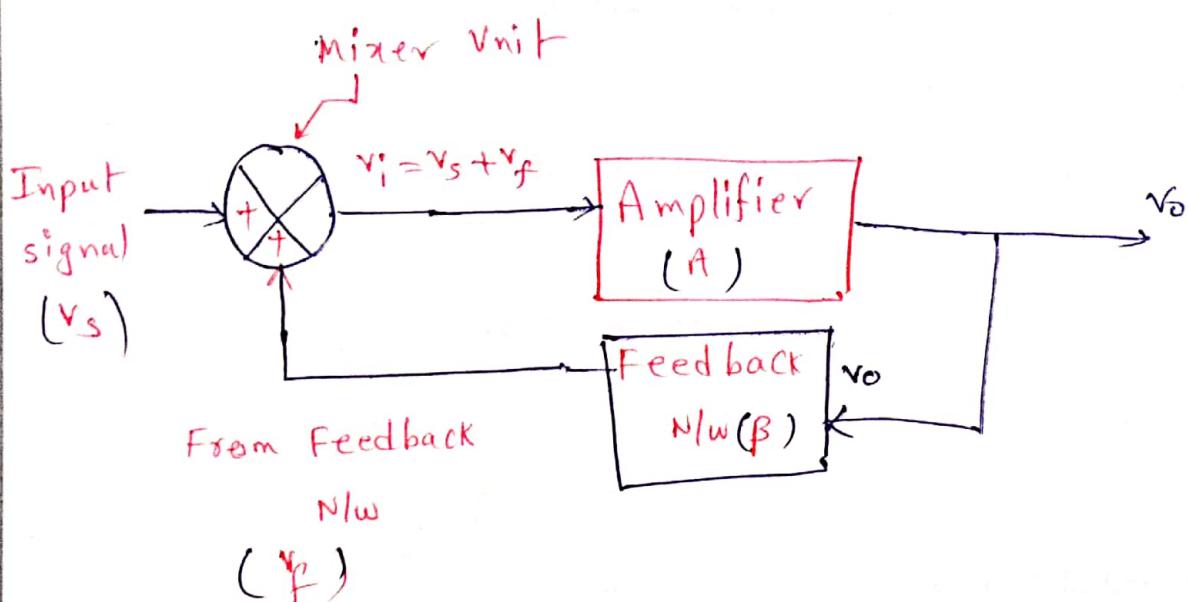Hence the gain of the amplifier increases.




→ Even though the gain of the amplifier is increased in this method, But

① It brings more distortion

② Poor gain instability
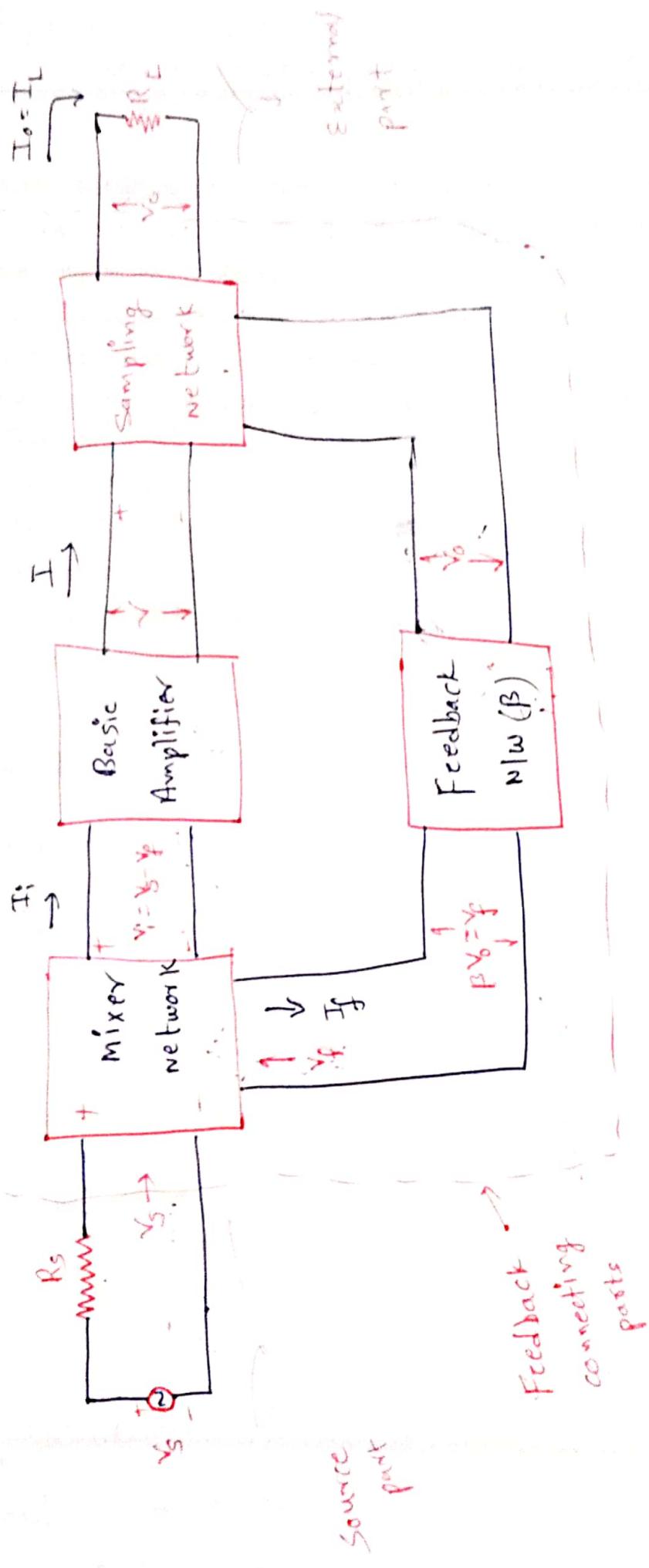
## Block diagram of Feedback Amplifier :-



Block diagram of feedback amplifier consisting of the following parts.

(1) Signal Source

(2) Mixer Block



(3) Amplifier Block

(4) Feedback Network Block

(5) Sampling Block
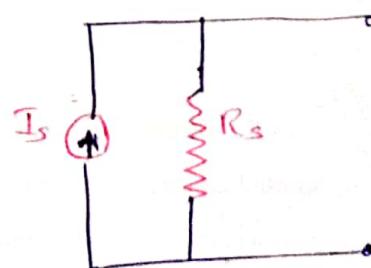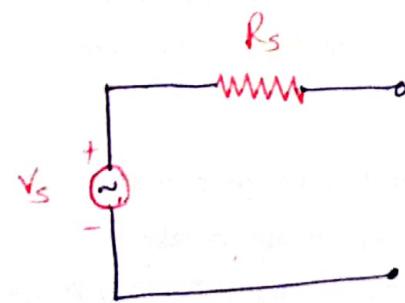
### (1) Signal Source :-

→ The signal source is either a voltage or a current source depending on the type of amplifier as classified.



fig(a). Thevenin's representation  
of voltage source

(b) Norton's Representation  
of current source

→ A voltage source is represented by a signal source  $V_s$  in series with a source resistance  $R_s$ , commonly known as Thevenin's representation.

A current source represented by a signal source  $I_s$  in parallel with a source resistance  $R_s$ , commonly known as Norton's representation.


### (a) Mixer (or) Comparator Block:-

- Mixer block is used to combine the source signal with the signal from feedback network.
- There are two types


(a) shunt mixing

(b) series "

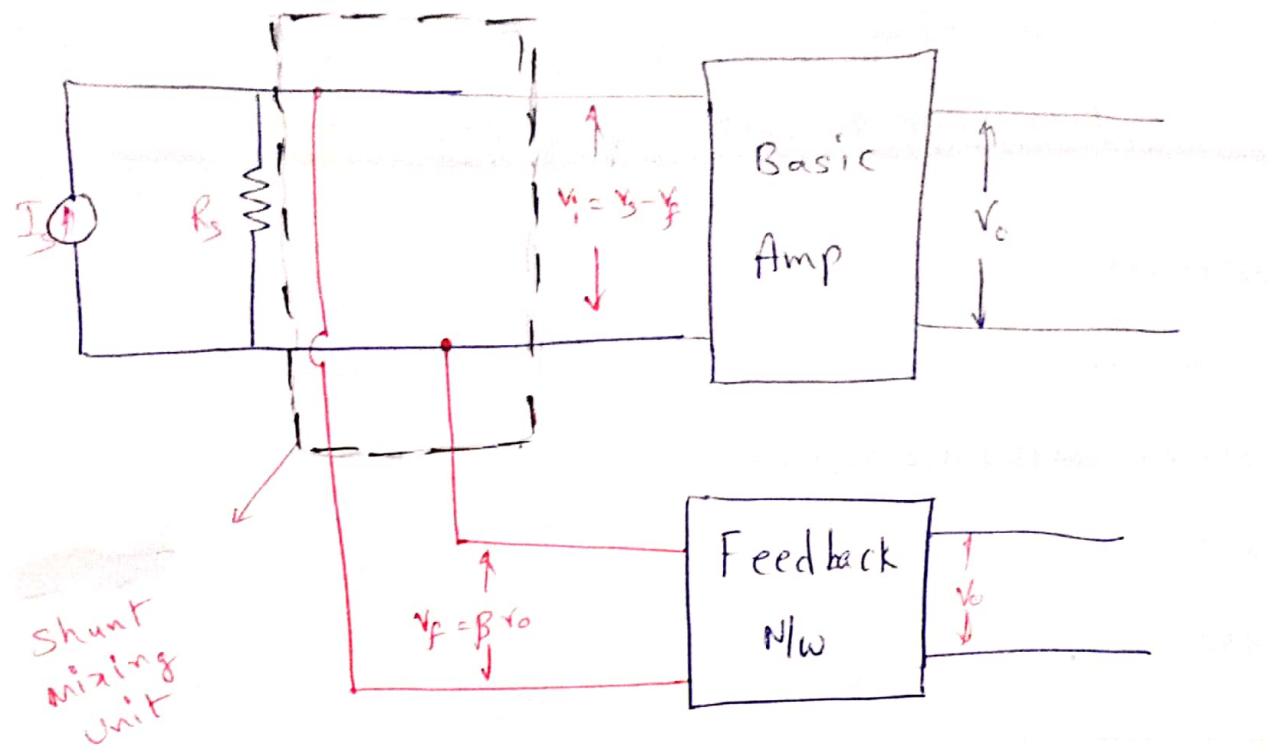(a) Shunt mixing:- When the signal source and the feedback signal are both currents, then shunt mixing is used.




### (b) series mixing:-

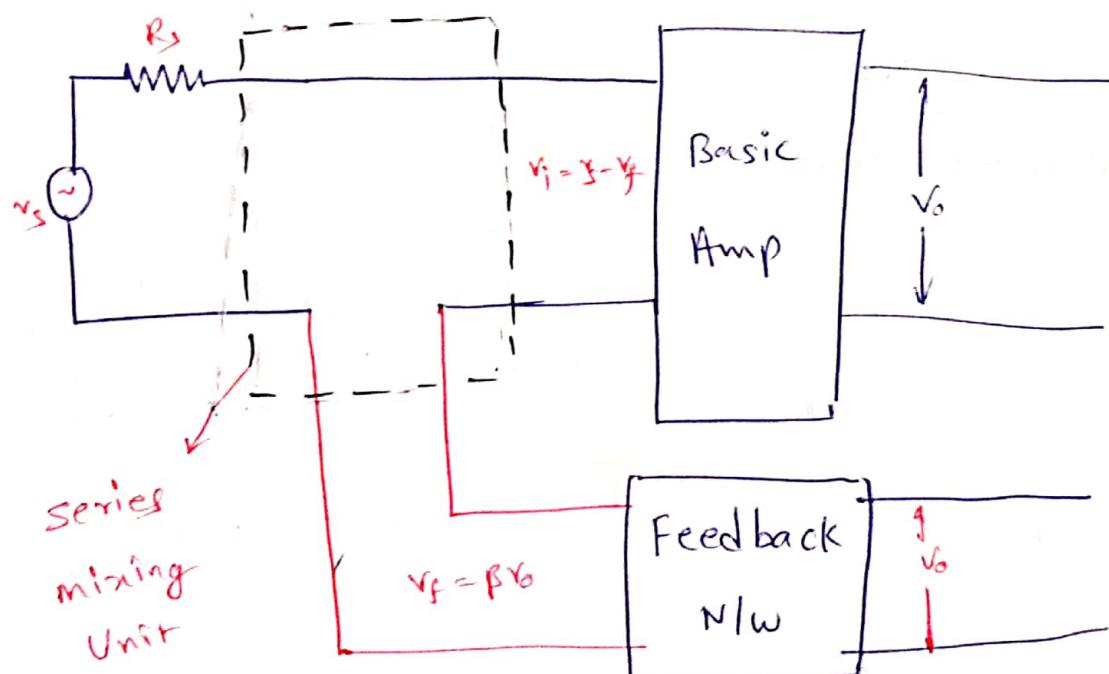

→ When the signal source and the feedback signal are both voltages, then series mixing is used.

③ Amplifier Block :- The forward gain of

amplifier block is defined as

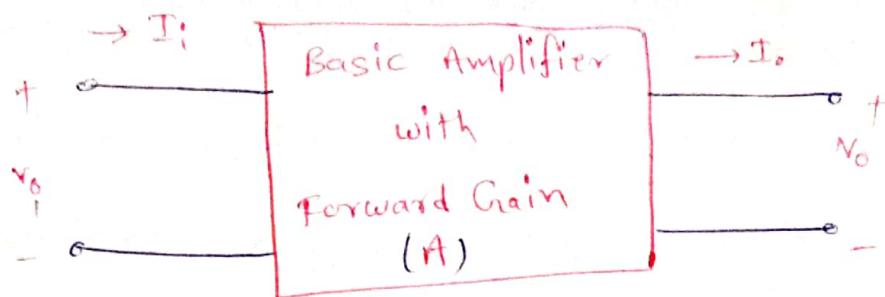

The ratio of o/p signal to the i/p signal and the amplifier gain depends on the type of amplifier.

$$\frac{v_o}{v_i} = A_v = \text{Voltage Amplification (or) Voltage Gain}$$

$$\frac{i_o}{i_i} = A_I = \text{current ratio (or) Current Gain}$$

$$\frac{v_o}{i_i} = R_m = \text{Trans resistance}$$

$$\frac{i_o}{v_i} = G_m = \text{Transconductance.}$$


Transfer gain of Basic  
 $\rightarrow A_v, A_I, R_m, G_m$  — "Amplifier without feedback"

$A_{v_f}, A_{I_f}, R_{m_f}, G_{m_f}$  — "with "
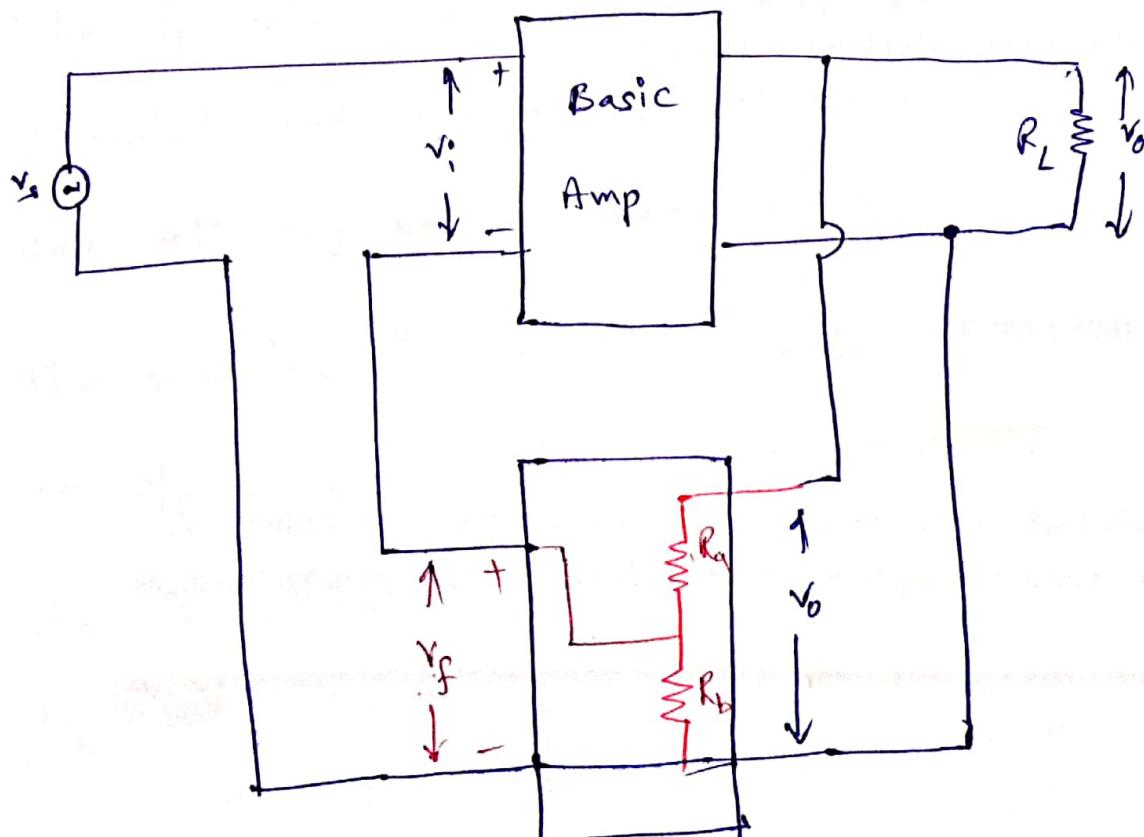
#### ④ Feedback Network Block:

- This is a passive two-port n/w configured using passive elements such as resistors, inductors and capacitors. The feedback n/w is simply a resistive n/w.
- The ratio of the o/p signal to the i/p signal of the feedback n/w is called feedback factor ( $\beta$ ) feedback ratio.

$$\rightarrow \beta \text{ lies b/w } 0 \text{ to } 1 \quad [v_f = \beta v_o]$$



Voltage sampling and Series mixing Configuration

Applying voltage-divider rule, we get

$$V_f = \frac{R_b}{R_a + R_b} \cdot V_o$$

$$\frac{V_f}{V_o} = \frac{R_b}{R_a + R_b}$$

By Def.,  $V_f = \beta V_o \Rightarrow \beta = \frac{V_f}{V_o}$

$$\boxed{\beta = \frac{V_f}{V_o} = \frac{R_b}{R_a + R_b}}$$

### ⑤ Sampling Block :-

→ The o/p voltage or current may be sampled and either o/p voltage or current may be returned to i/p.


→ The sampling is generally referred to o/p stage of the feedback amplifier.

→ The sampling can be divided into two basic types.

① voltage sampler


② current sampler.

### (1) Voltage sampler :-

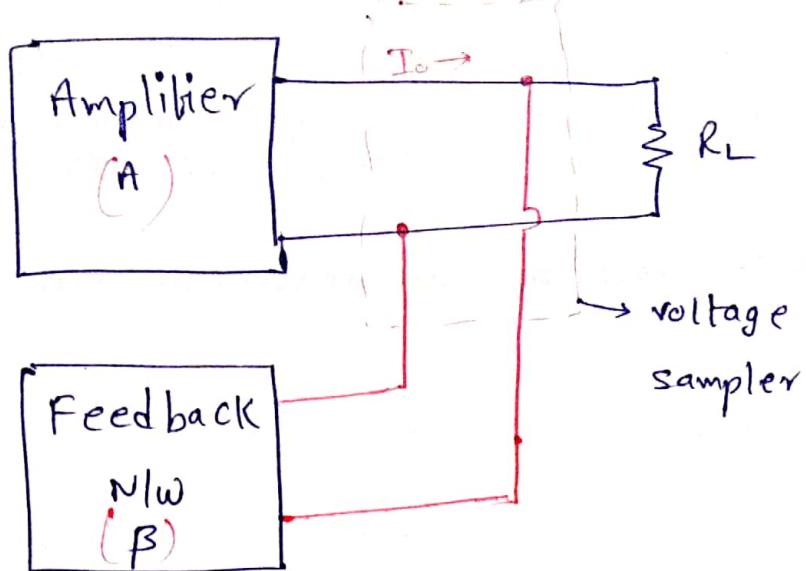

→ The feedback  $Nlw$  is connected across (parallel to) the o/p load ( $R_L$ ).

### (2) Current Sampler:-

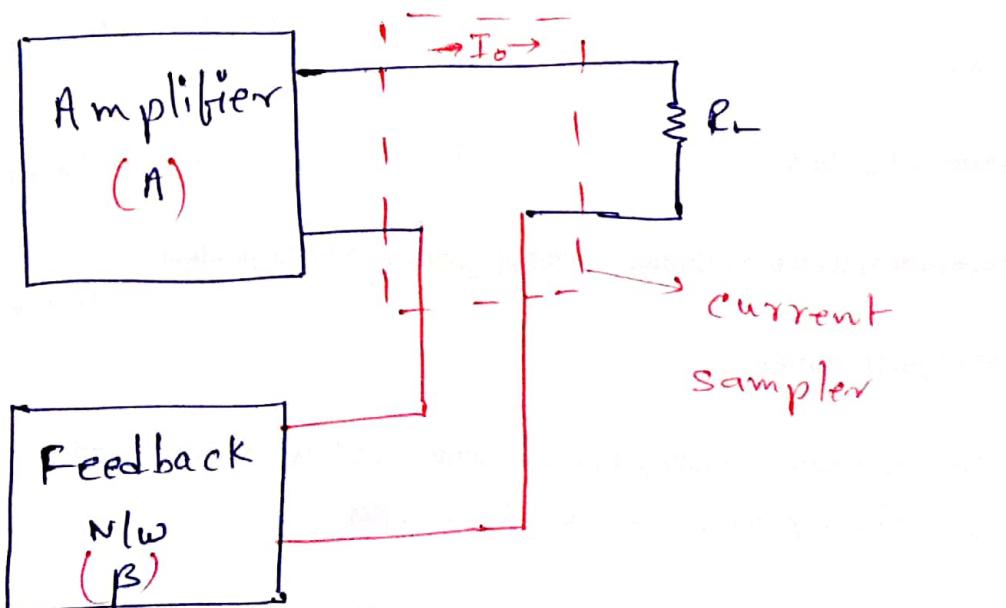


→ The feedback  $Nlw$  is connected in series with the o/p load resistor  $R_L$ .


## ② Classification of Feedback Amplifier:-

- Two types of sampling either current or voltage of two types mixer block i.e., either shunt or series mixer.
- Thus, with two types of sampling and two types of mixer, there could be four amplifiers topologies.
- Four types of feedback amplifiers are
  - ① Voltage - Series Feedback (Voltage Amplifier)
  - ② Voltage-shunt Feedback (Transresistance)
  - ③ Current - series Feedback (Transconductance)
  - ④ current - shunt Feedback (Current Amplifier)

series

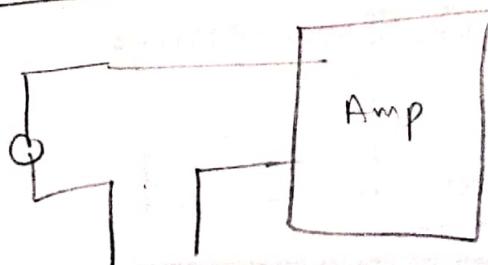


voltage sampler

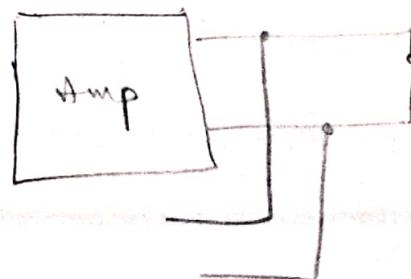


Shunt




Current sampler

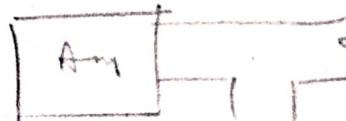


## ① Voltage series feed back :-

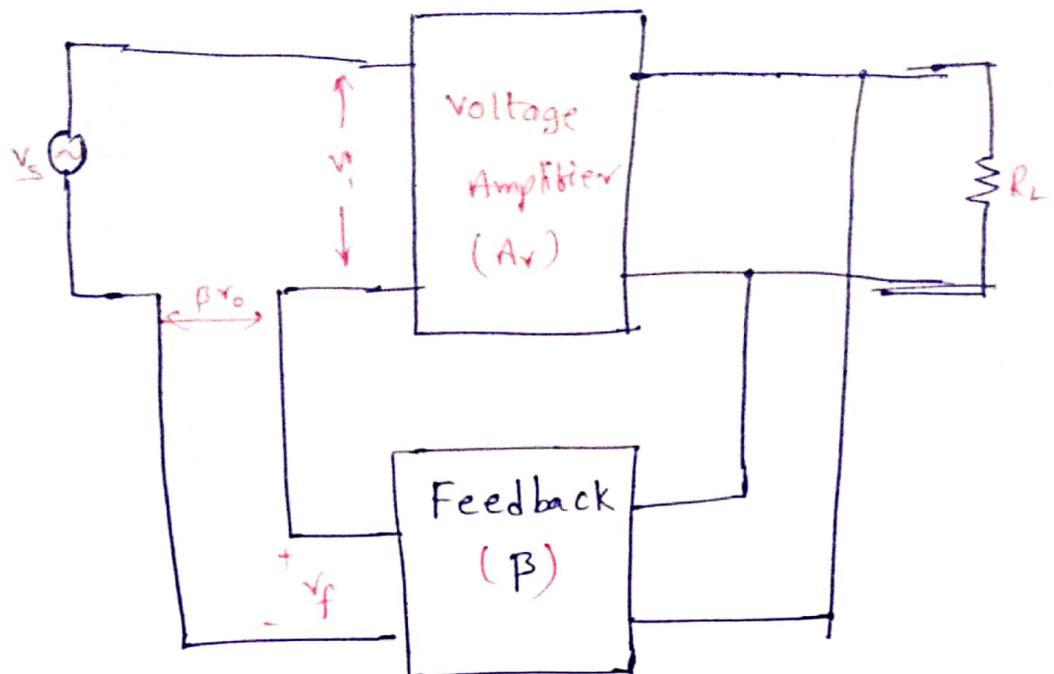


## ② Voltage shunt Feedback :-

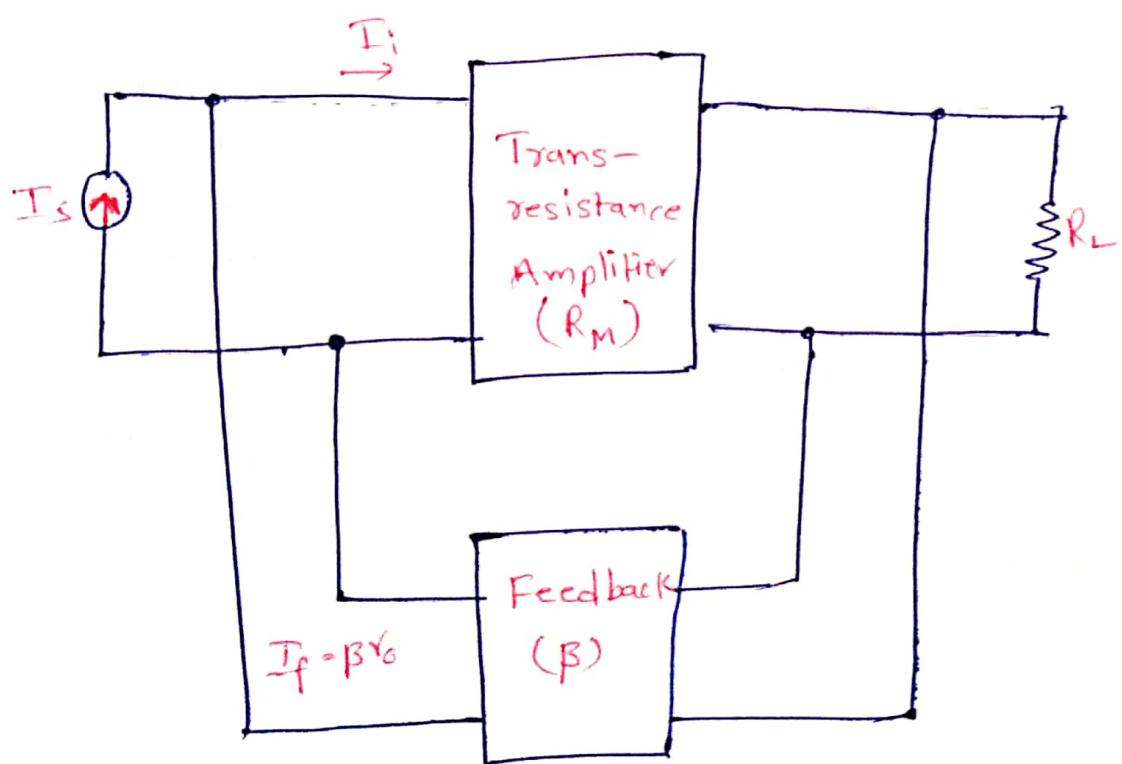

### ③ Current series Feedback :-

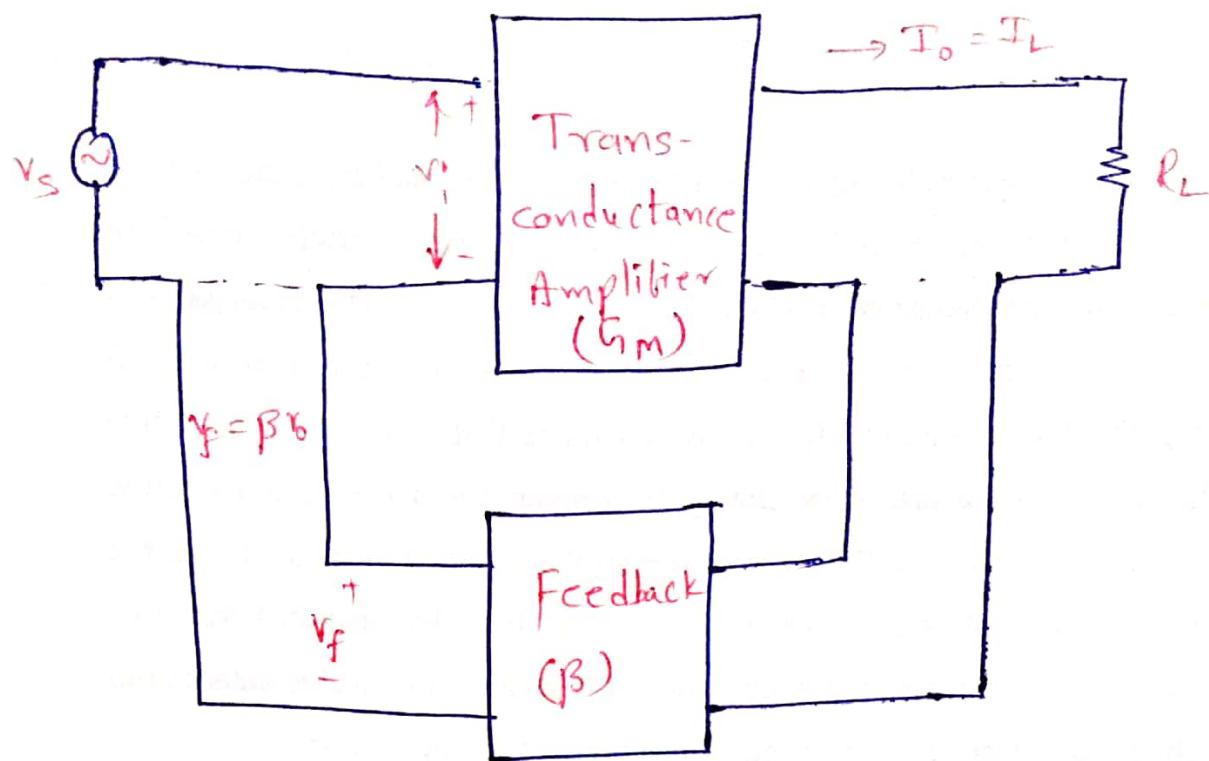

### ④ Current shunt Feedback :-

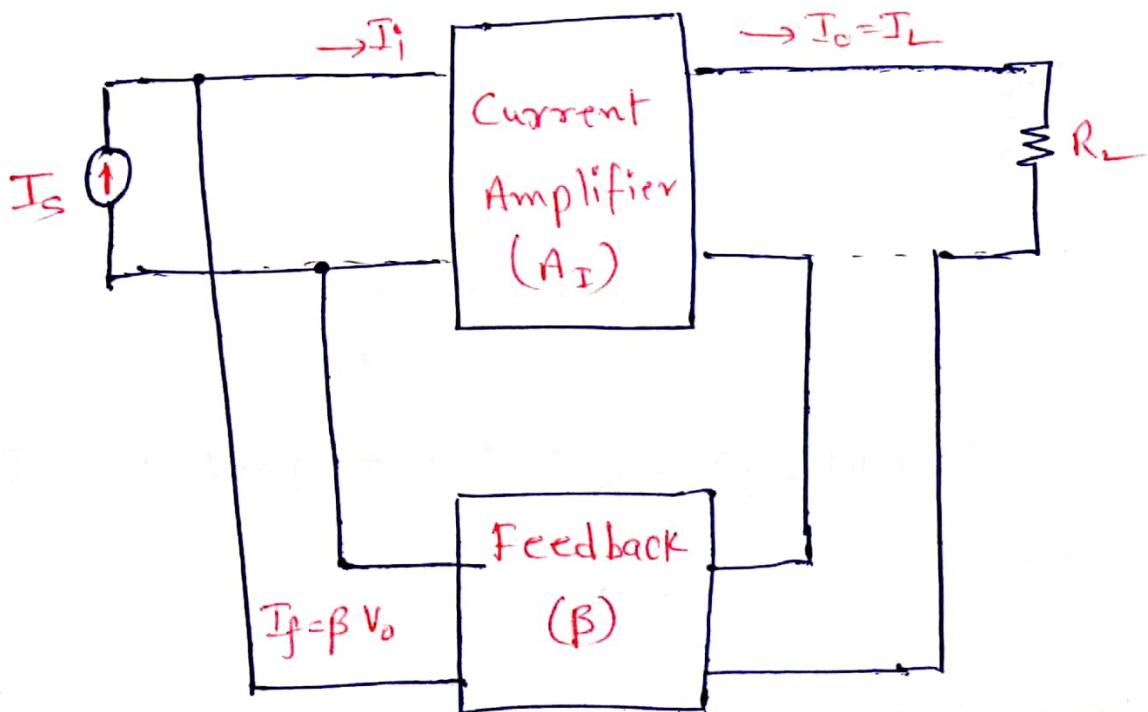


### ③ General characteristics of Negative Feedback

Amplifier:-

- ① Stability of Gain
- ② Reduction in forward gain
- ③ Reduction in non-linear distortion
- ④ change in Input Impedance
- ⑤ change in output Impedance
- ⑥ Increase in Bandwidth
- ⑦ Reduction in noise.

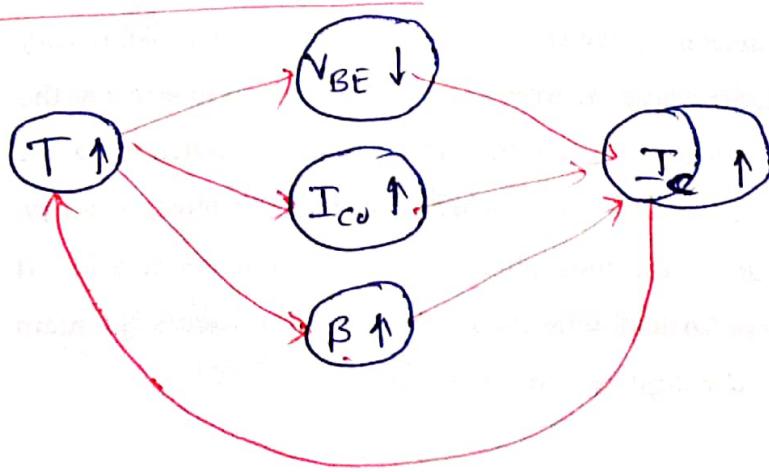① stability of Gain :- Depending on  $\beta$  value.



$$A_f = \frac{A}{1 + \beta A}$$

Eg1.  $A = 20, \beta = 0.1$

$$A_f = \frac{A}{1+\beta A} = \frac{20}{1+(0.1)20} = \frac{20}{3} = 6.66$$

at  $\beta = 0.2$

$$A_f = \frac{A}{1+\beta A} = \frac{20}{1+(0.2)20} = \frac{20}{5} = 4$$

## ② Reduction in forward Gain :-

$$A_f = \frac{A}{1+\beta A}$$

where,  $A_f$  = forward Gain

due to  $(1+\beta A)$  value

Eg1.  $A = 20, 1+\beta A = 1.2$

$$A_f = \frac{A}{1+\beta A} = \frac{20}{1.2} = 16.66$$

$A = 20, 1+\beta A = 0.6$

$$A_f = \frac{A}{1+\beta A} = \frac{20}{0.6} = 33.33$$

$$(1+\beta A) \uparrow \rightarrow A_f \downarrow$$

$\downarrow \qquad \qquad \qquad \uparrow$

### ③ Reduction in non-linear distortion:-

Net distortion = original distortion + distorted o/p

$$D_f = D - A\beta D_f \quad \text{where } -ve \rightarrow \text{o/p is off phase}$$

$$D_f + A\beta D_f = D$$

$$(1 + A\beta) D_f = D$$

$$D_f = \frac{D}{1 + A\beta}$$

### ④ Change in input impedance:-

$$Z_{if} > Z_i$$


↓

Due to -ve feedback,  $v_f$  is in opposite polarity with respect to  $v_s$  and hence  $I_i$  with -ve Feedback is less than with FB.


series →	$Z_{if} > Z_i$
shunt →	$Z_{if} < Z_i$

### ⑤ Change in output Impedance:-

depends on nature of sampling

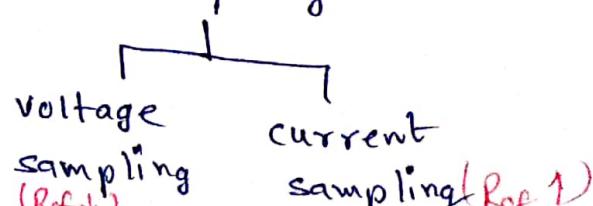

## ⑥ Increase in Bandwidth :-

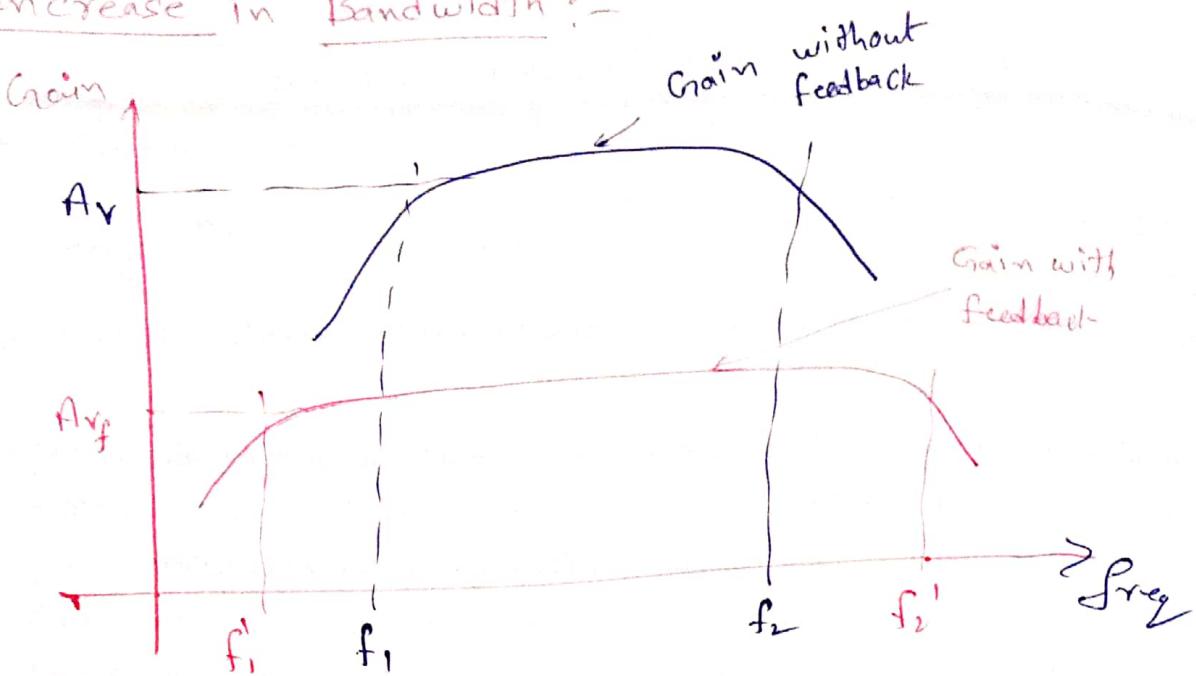

$$(B \cdot \omega)_f = f_2' - f_1' \quad (B \cdot \omega) = f_2 - f_1$$

$$(B \cdot \omega)_f > (B \cdot \omega)$$

$$f_2' > f_2, \quad f_1' > f_1$$

## ⑦ Reduction in noise :-


$$N_f = \frac{N}{1 + \beta}$$

#### ④ Effect of Feedback on Amplifier Characteristics :

- The three most important basic char's of amplifiers are gain, input impedance and output impedance.
- This is four types of feedback.

- ① Voltage-series feedback amplifier
- ② " shunt " "
- ③ current Series "
- ④ " Shunt "
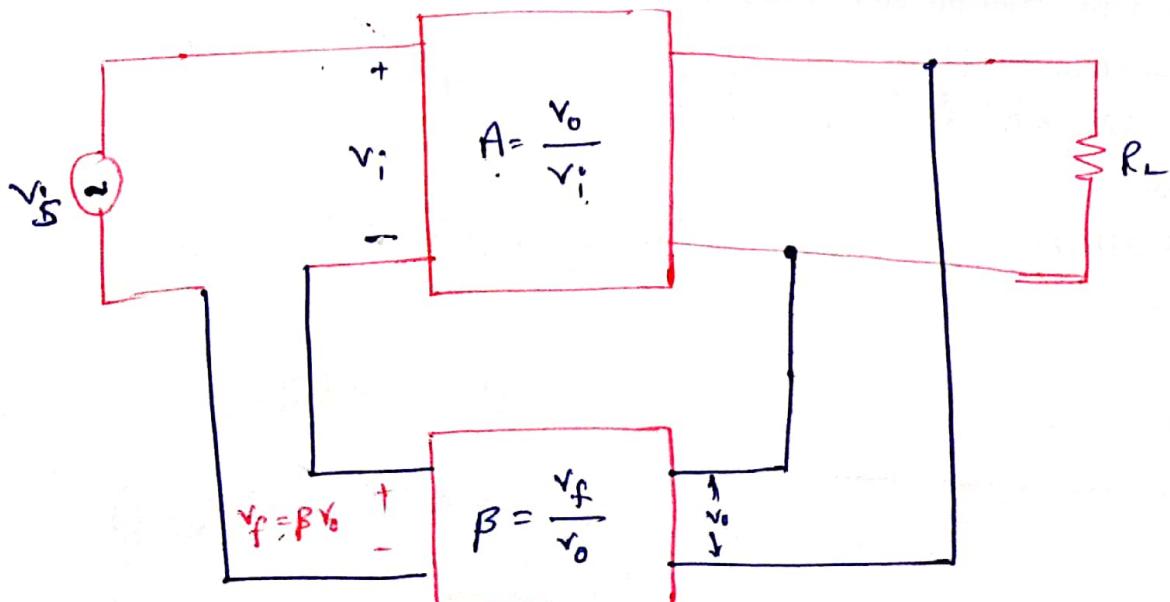
#### ① Voltage - Series Feedback Amplifier :-



(i) Gain :- If there is no Feedback ( $v_f = 0$ ),  
the voltage gain of amp. stage is

$$A = \frac{V_o}{V_i} \quad \text{--- } ①$$

If a feedback signal ( $v_f$ ) is connected  
in series with the i/p. then

$$V_i = V_s - v_f \quad \text{--- } ②$$

since  $V_o = A V_i$  [ $\because$  from eqn ①]

$$= A(V_s - v_f) \quad [\because \text{from eqn } ②]$$

$$= A V_s - A v_f$$

$$= A V_s - A(\beta v_f) \quad [\because \beta = \frac{v_f}{V_o} \Rightarrow v_f = \beta V_o]$$

$$\therefore V_o = A V_s - \beta A V_o$$

$$V_o + \beta A V_o = A V_s$$


$$(1 + \beta A) V_o = A V_s$$

$$\boxed{A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A}} \quad \text{--- } ③$$

→ Eqn ③ shows that the gain with Feedback is  
the amplifier gain reduced by the factor  $(1 + \beta A)$

### (ii) Input Impedance :-

Input Impedance without FB is given by

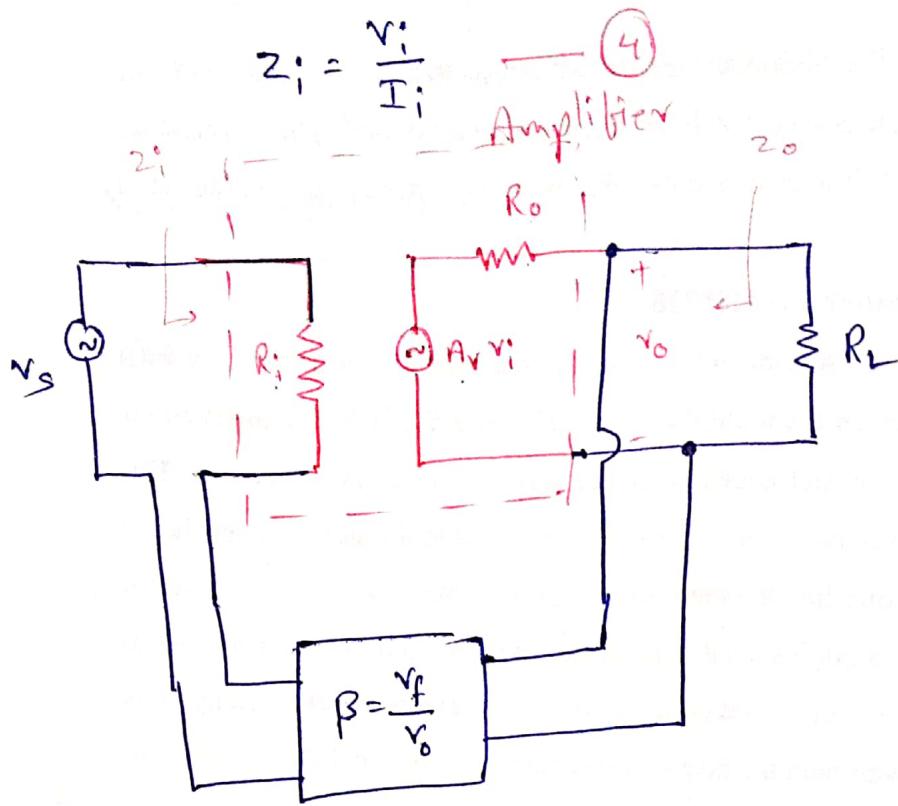

I/p imp with FB is defined as

$$Z_{if} = \frac{V_s}{I_i}$$

$$\text{From Fig., } V_i = V_s - V_f$$

$$= V_s - (\beta V_o) \quad \left[ \because \beta = \frac{V_f}{V_o} \right]$$

$$\text{But } V_o = A V_i \quad \left[ \because \text{from eqn (1)} \right]$$

$$V_i = V_s - \beta (A V_i)$$

$$V_i + \beta A V_i = V_s$$

$$V_s = V_i + \beta A V_i$$

$$V_s = V_i (1 + \beta A)$$

$$V_s = (1 + \beta A) V_i$$

$$\text{From Eqn (4), } Z_i = \frac{V_i}{I_i}$$

$$\Rightarrow V_i = Z_i I_i$$

$$V_s = (1 + \beta A) Z_i I_i$$

$$\frac{V_s}{I_i} = Z_i (1 + \beta A)$$

$$Z_{if} = \frac{V_s}{I_i} = Z_i (1 + \beta A) \quad \boxed{\text{--- (6)}}$$


→ From Eqn (6) it is clear that input imp. of voltage series f $\beta$  Amp increases by a factor of  $(1 + \beta A)$ .

### (iii) Output Impedance :-

④ The o/p imp. is computed by following two steps as

① voltage source ( $V_s$ ) is replaced by s.c.

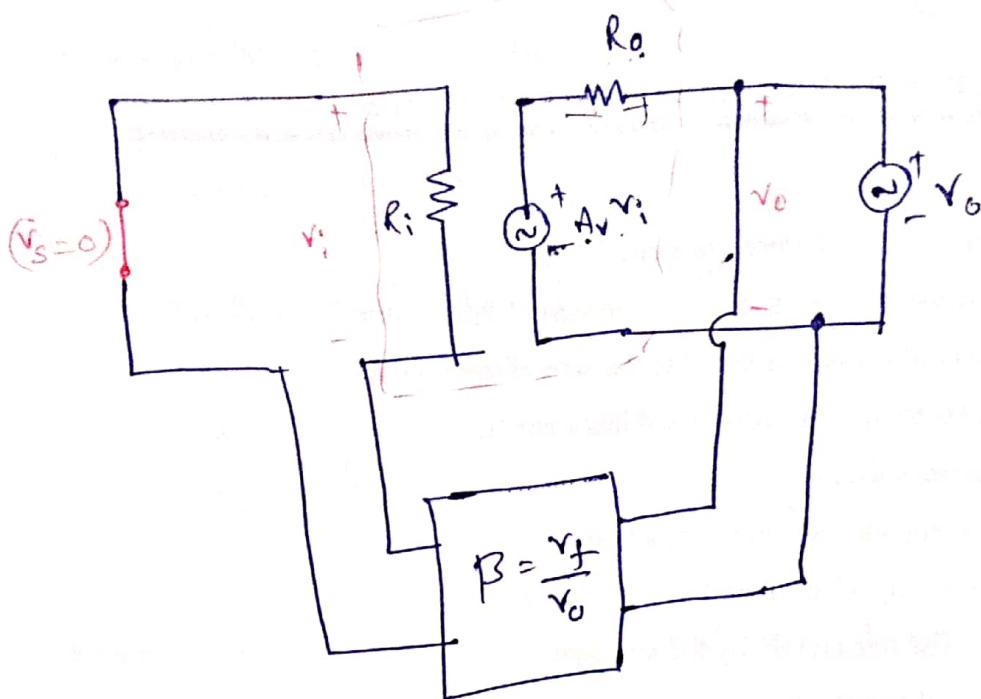② Load resistance ( $R_L$ ) " " " " " voltage source ( $V$ ).



o/p imp. is defined as

$$Z_{\text{o/f}} = \frac{V_o}{I_o}$$

Applying KVL to o/p ckt, we get

$$Av_i + I_o r_o - v_f = 0 \quad \text{--- (1)}$$

Applying KVL to i/p ckt, we get

$$v_i = v_s - v_f$$

$$= 0 - v_f$$

$$\therefore v_i = -v_f$$

$$\text{but } v_f = \beta v_o$$

$$\therefore v_i = -\beta v_o$$

substituting \$v\_i\$ value in eqn(1), we get

$$A(-\beta v_o) + I_o r_o - v_o = 0$$

$$-\beta A V_o + I_o R_o - r_o = 0$$


$$I_o R_o = V_o + \beta A V_o$$

$$I_o R_o = V_o (1 + \beta A)$$

$$Z_{of} = \frac{V_o}{I_o} = \frac{R_o}{(1 + \beta A)}$$

→ Hence, it is clear that, output Impedance of voltage series feedback amplifier gets reduced by a factor  $(1 + \beta A)$ .

## ② Voltage - shunt Feedback Amplifier

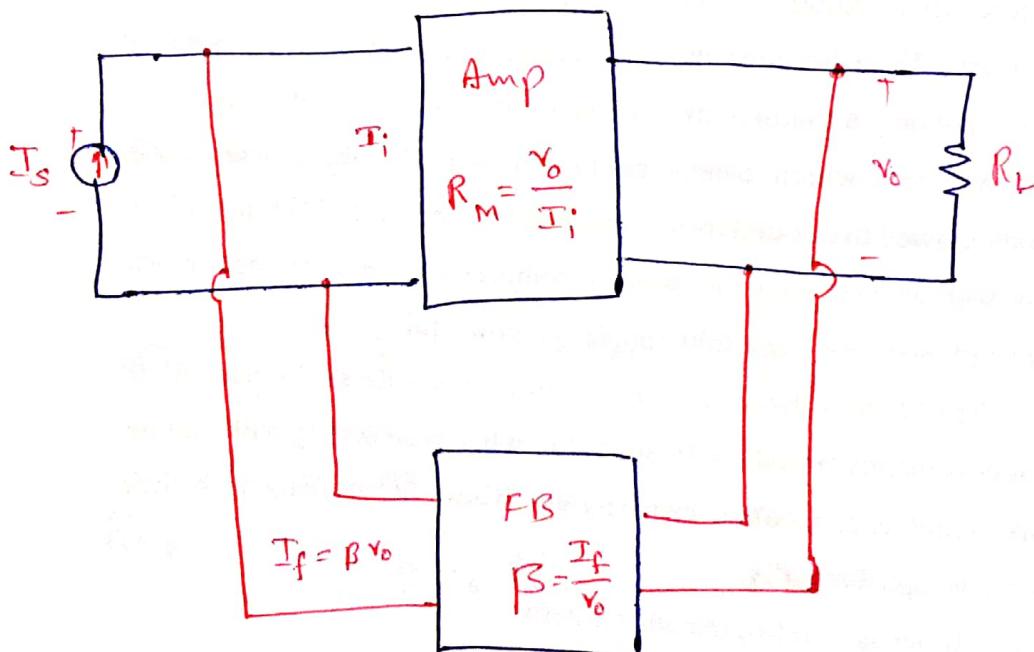

Gain :- Consider there is no feedback.

$$R_m = \frac{r_o}{I_i}$$

If a feedback signal ( $I_f$ ) is connected in shunt with  $I_i$  then

$$I_i = I_s - I_f$$

$$I_s = I_i + I_f$$

Gain of an amplifier is defined by

$$R_{mf} = \frac{V_o}{I_s}$$

$$= \frac{V_o}{I_i + I_f}$$

$$\text{But } I_f = \beta V_o \quad \left[ \because \beta = \frac{I_f}{V_o} \right]$$

$$R_{mf} = \frac{V_o}{I_i + \beta V_o}$$

$$\text{But } V_o = R_m I_i \quad \left[ R_m = \frac{V_o}{I_i} \right]$$


$$R_{mf} = \frac{R_m I_i}{I_i + \beta R_m I_i}$$

$$= \frac{R_m I_i}{I_i (1 + \beta R_m)}$$

$$R_{mf} = \frac{R_m}{1 + \beta R_m}$$

→ Hence, for voltage shunt feedback amplifier,  
gain gets reduced by a factor of  $(1 + \beta R_m)$ .

(ii) Input Impedance :-

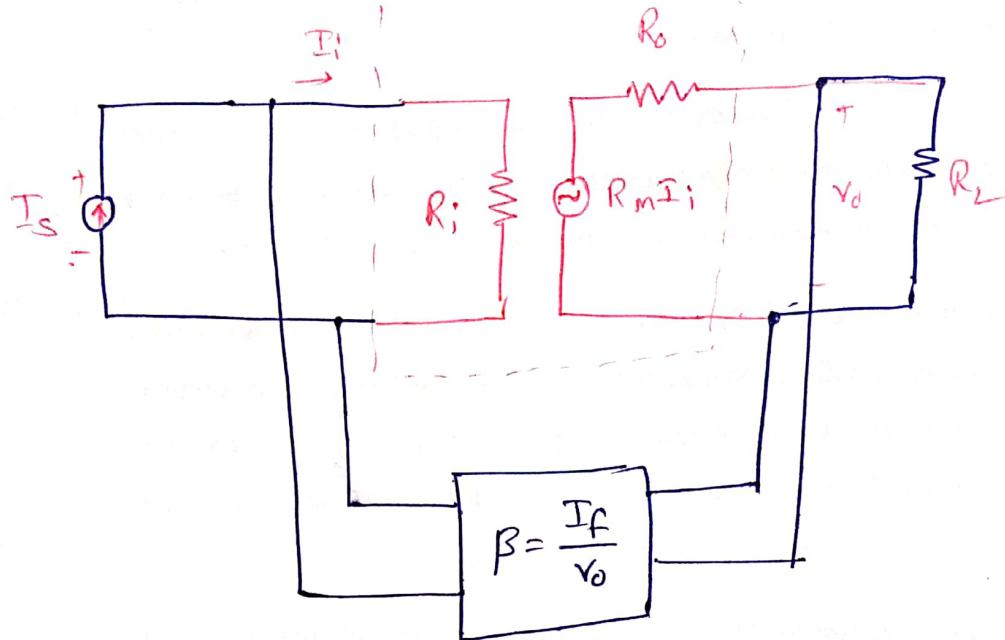

The input impedance without feedback is

$$Z_i = \frac{V_i}{I_i}$$

The input impedance with Feedback is

$$Z_{if} = \frac{V_i}{I_s}$$

$$= \frac{V_i}{I_i + I_f} \quad [ \because I_s = I_i + I_f ]$$

$$= \frac{V_i}{I_i + \beta V_o} \quad [ \because \beta = \frac{I_f}{V_o} ]$$

$$= \frac{V_i / I_i}{I_i / I_i + \beta V_o / I_i} \quad \text{--- (10)}$$

$$\text{since } \frac{V_o}{I_i} = Z_i, \quad \frac{V_o}{I_f} = R_m \quad \rightarrow (11)$$


substituting eqn (11) in (10), we get

$$Z_{if} = \frac{Z_i}{1 + \beta R_m} \quad \rightarrow (12)$$

Hence, for voltage shunt feedback amplifier input impedances gets reduced by a factor  $(1 + \beta R_m)$ .
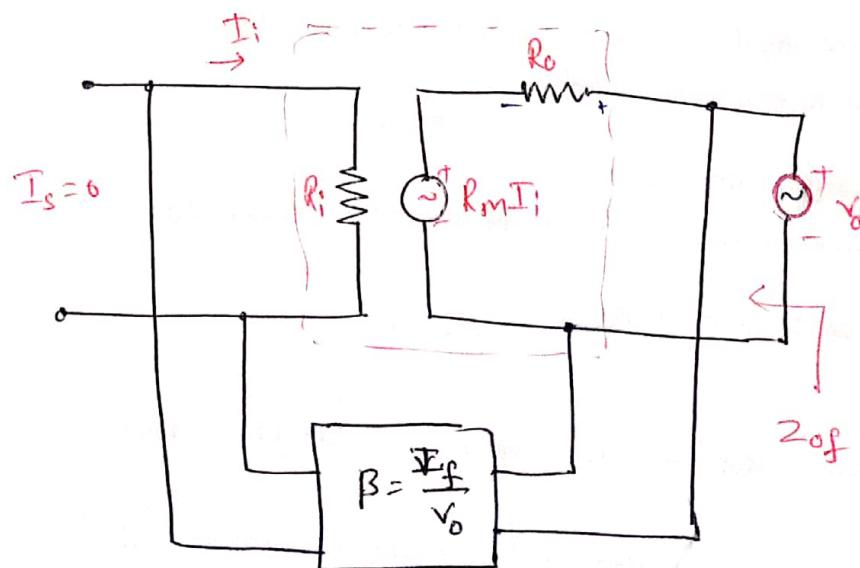
### (iii) Output Impedance :-

- ① Replacing current source with o.c.
- ② Replacing load resistance by voltage source.



Applying KVL at i/p ckt.

$$I_i + I_f = 0$$

$$I_i = -\beta f$$

$$\text{But } I_f < \beta V_o \quad \left[ \because \beta = \frac{I_f}{V_o} \right]$$

$$I_i = -\beta V_o$$

Applying KVL at output ckt,

$$R_m I_i + R_o I_o - V_o = 0 \quad \text{--- (13)}$$

substituting  $I_i$  value in Eqn (13), we get

$$R_m (-\beta V_o) + R_o I_o - V_o = 0$$

$$-\beta R_m V_o + R_o I_o - V_o = 0$$

$$R_o I_o = V_o + \beta R_m V_o \quad \text{--- (14)}$$

$$R_o I_o = V_o (1 + \beta R_m)$$


$$\frac{R_o}{1 + \beta R_m} = \frac{V_o}{I_o}$$

$$\frac{V_o}{I_o} = \frac{R_o}{1 + \beta R_m}$$

$$Z_{of} = \frac{V_o}{I_o} = \frac{R_o}{(1 + \beta R_m)}$$

→ Hence, output impedance of voltage-shunt feedback amplifier gets reduced by a factor  $(1 + \beta R_m)$ .
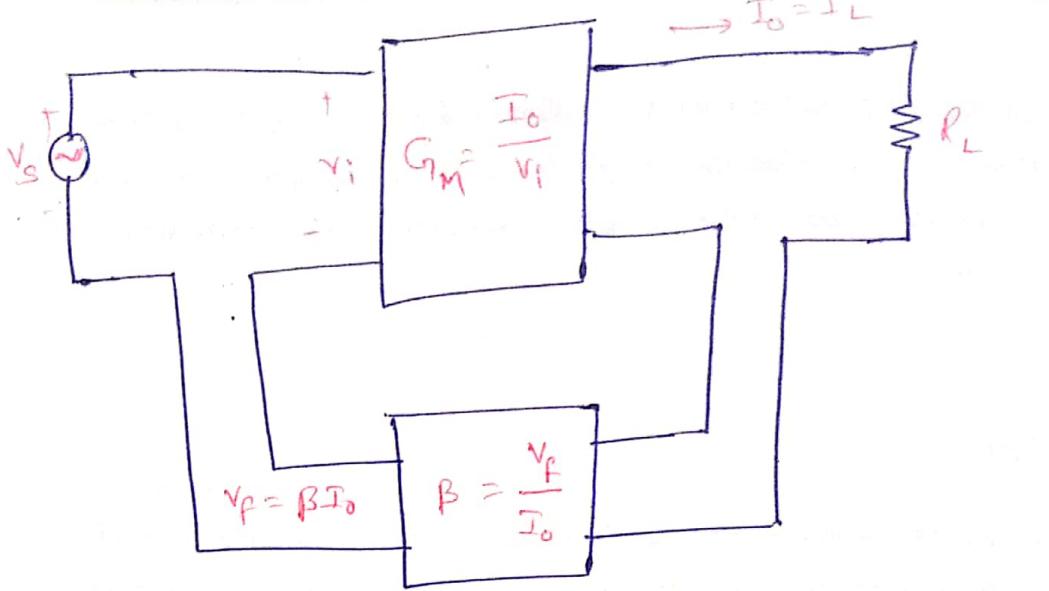
### ③ Current Series Feedback Amplifier :-



(i) Gain :-

The gain of the Amplifier without feedback is

$$G_m = \frac{I_o}{V_i}$$

The gain with feedback is

$$G_{mf} = \frac{I_o}{V_s}$$

$$\text{From Fig. } V_s = v_i + v_f$$

$$\text{But } \beta = \frac{V_f}{I_o} \Rightarrow V_f = \beta I_o$$

$$V_s = v_i + \beta I_o$$

$$G_{mf} = \frac{I_o}{v_i + \beta I_o}$$

From fig.,  $G_m = \frac{I_o}{V_i} \Rightarrow I_o = G_m V_i$

$$\therefore G_{mf} = \frac{G_m V_i}{V_i + \beta G_m V_i}$$

$$= \frac{G_m V_i}{V_i (1 + \beta G_m)}$$


$$G_{mf} = \frac{G_m}{1 + \beta G_m}$$

→ Gain of current series Feedback Amplifier gets reduced by a factor  $(1 + \beta G_m)$ .
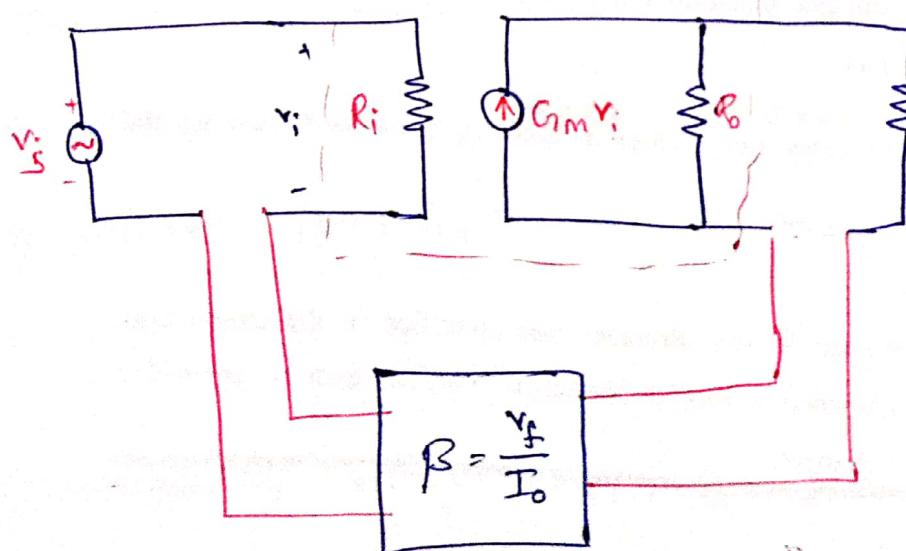
## (ii) Input Impedance :-

Input impedance without feedback is

$$Z_i = \frac{V_i}{I_i} \quad \text{Amplifier}$$



Op amp with FB is

$$Z_{if} = \frac{V_s}{I_s} = \frac{V_s}{I_i}$$

$$\text{But } V_s = V_i + V_f = V_i + \beta I_o \quad \left[ \because \beta = \frac{V_f}{I_o} \right]$$

$$Z_{if} = \frac{V_i + \beta I_o}{I_i}$$

$$= \frac{V_i + \beta G_m V_i}{I_i} \quad \left[ \because G_m = \frac{I_o}{V_i} \right]$$
$$\Rightarrow I_o = G_m I_i$$

$$= \frac{V_i}{I_i} + \frac{\beta G_m V_i}{I_i}$$

$$\text{But } \frac{V_i}{I_i} = Z_i$$

$$Z_{if} = Z_i + \beta G_m Z_i$$


$$Z_{if} = Z_i (1 + \beta G_m) \quad \rightarrow (17)$$

→ Input Impedance of a current series  
Feedback amplifier gets increased by  
a factor  $(1 + \beta G_m)$ .

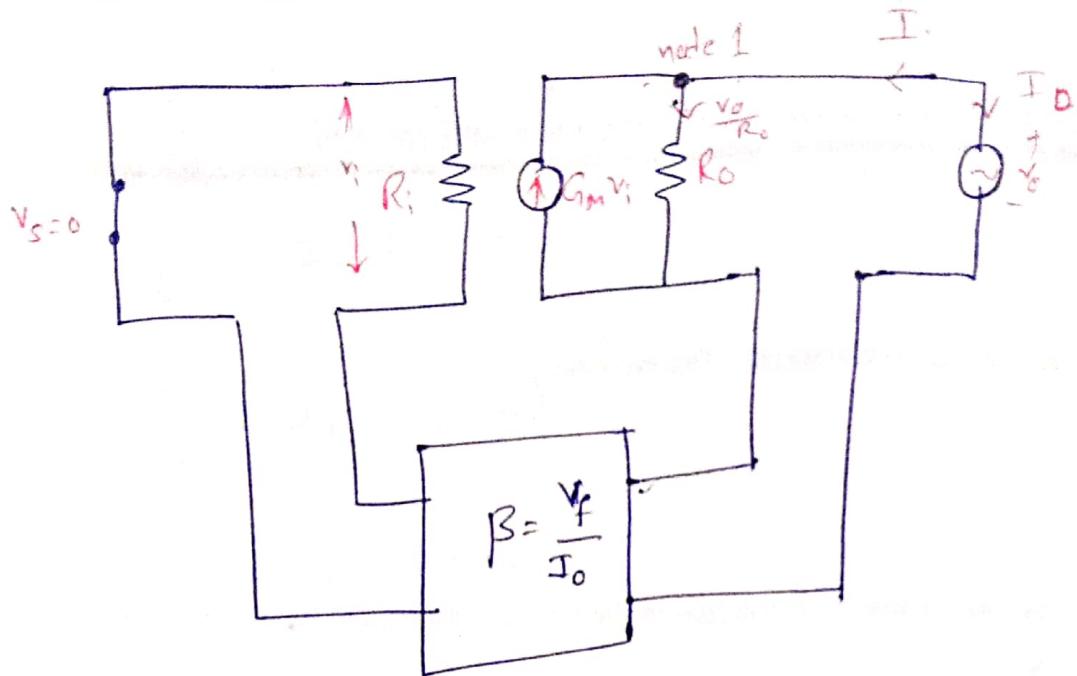(iii) Output Impedance :-

① Replacing voltage source ( $V_s$ ) with s.c.

② " Load resistance with voltage  
source.



Applying KVL at i/p ckt, we get

$$[ \because v_i = v_s - v_f ]$$

$$v_i = 0 - v_f$$

$$v_i = -v_f$$

$$\text{But } \beta = \frac{v_f}{I_0} \Rightarrow v_f = \beta I_0$$

$$v_i = -\beta I_0$$

Applying KCL at node ① of the o/p ckt, we get

$$G_m v_i + I - \frac{v_o}{Z_o} = 0 \quad [\because Z_o = R_o] \quad \text{--- (18)}$$

Substituting  $v_i$  value in Eqn (18), we get

$$G_m (-\beta I_0) + I - \frac{v_o}{Z_o} = 0$$

$$\text{From Fig. } I = -I_0$$

$$G_m (\beta I) + I - \frac{v_o}{Z_o} = 0$$

$$\frac{V_o}{Z_o} = G_m \beta I + I$$


$$\frac{V_o}{Z_o} = I(1 + \beta G_m)$$

$$\frac{V_o}{I} = Z_o (1 + \beta G_m)$$

$$Z_{of} = Z_o (1 + \beta G_m)$$

→ Output Impedance of current series Feedback amplifier gets increased by a factor  $(1 + \beta G_m)$
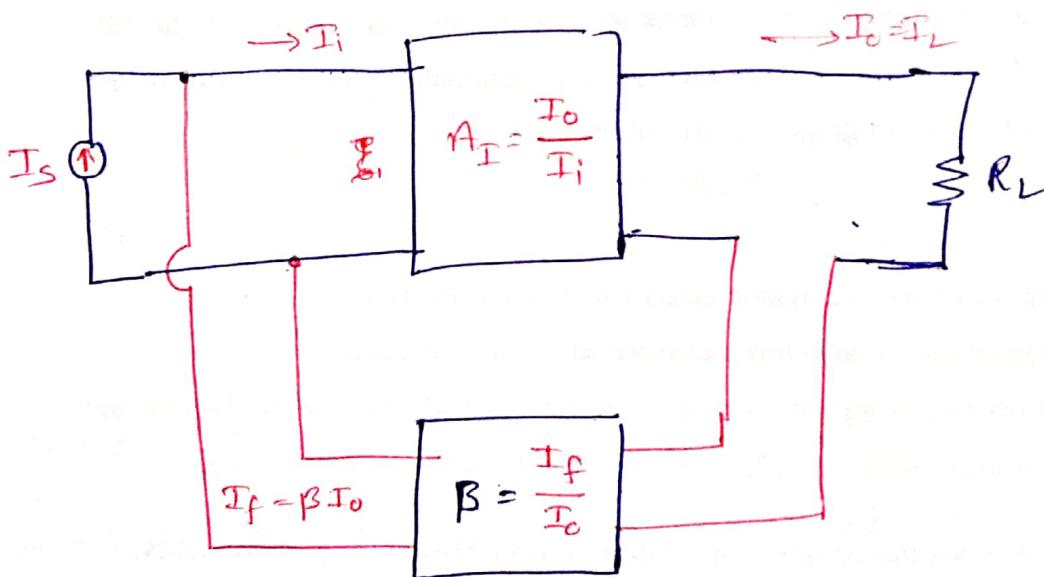
#### ④ Current shunt Feedback Amplifier:-



##### (i) Gain :-

Gain without Feedback is

$$A_I = \frac{I_o}{I_i}$$

Gain with Feedback is

$$A_{If} = \frac{I_o}{I_s}$$

But  $A_I = \frac{I_o}{I_i} \Rightarrow I_o = A_I I_i$

and  $I_s = I_i + I_f$

$$= I_i + \beta I_o \quad \left[ \because \beta = \frac{I_f}{I_o} \right]$$

$$\Rightarrow I_f = \beta I_o$$

$$A_{If} = \frac{I_o}{I_s} = \frac{I_o}{I_i + \beta I_o}$$

Dividing numerator & denominator by  $I_i$ :

$$A_{If} = \frac{I_o/I_i}{I_i/I_i + \beta I_o/I_i}$$

$$A_{If} = \frac{A_I}{1 + \beta A_I}$$

$$\left[ \because A_I = \frac{I_o}{I_i} \right]$$

→ Hence, current gain of Current Shunt Feedback amplifier gets reduced by a factor  $(1 + \beta A_I)$ .

(ii) Input Impedance :-

Input impedance without feedback

$$Z_i = \frac{V_i}{I_i}$$

Input Impedance with feedback is

$$Z_{if} = \frac{V_i}{I_s}$$

But  $I_s = I_i + I_f$

$$= I_i + \beta I_o \quad \left[ \because \beta = \frac{I_f}{I_o} \right]$$

$$Z_{if} = \frac{V_i}{I_i + \beta I_o}$$

Divide numerator & denominator by  $I_i$

$$Z_{if} = \frac{\frac{V_i}{I_i}}{\frac{I_i}{I_i} + \beta \frac{I_o}{I_i}}$$

since  $Z_i = \frac{V_i}{I_i}$ ,  $A_I = \frac{I_o}{I_i}$


$$Z_{if} = \boxed{\frac{Z_i}{1 + \beta A_I}} \quad (20)$$

→ Input impedance of current shunt feedback amplifier gets reduced by a factor  $(1 + \beta A_I)$ .

(iii) Output Impedance :-

① Replacing current source by o.c

② Load resistance by voltage source.

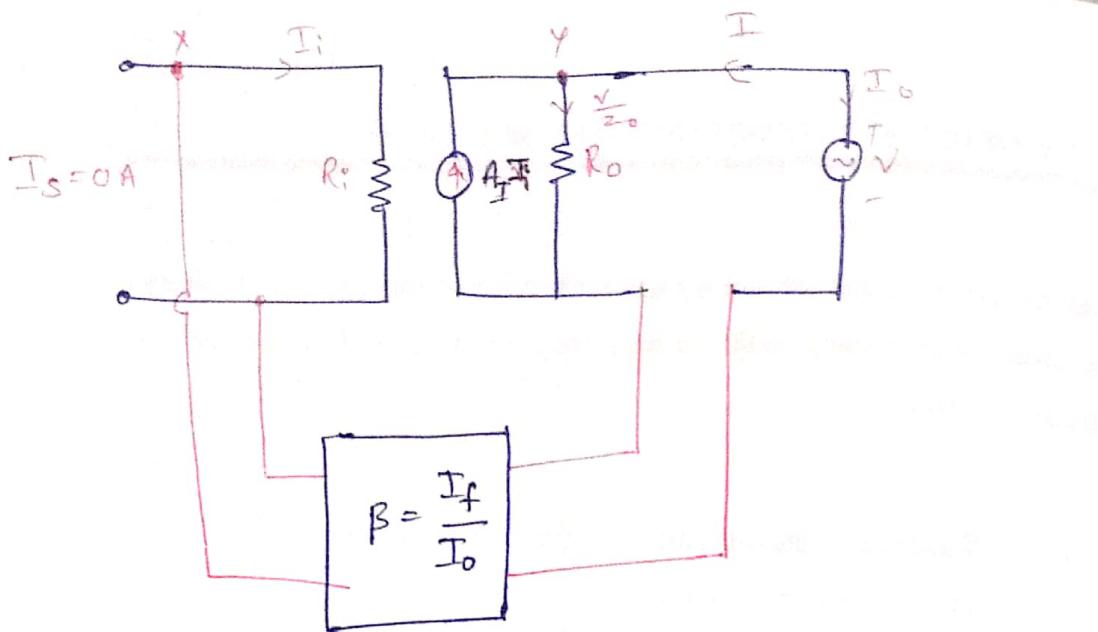

Applying KCL at node X, we get

$$I_i + I_f = 0$$

$$I_i = -I_f$$

$$\text{But } \beta = \frac{I_f}{I_o} \Rightarrow I_f = \beta I_o$$

$$I_i = -\beta I_o$$

Applying KCL at node Y, we get

$$A_I I_i + I - \frac{V}{Z_0} = 0 \quad \text{--- (21)}$$

Substituting  $I_i = -\beta I_o$  in eqn (21), we get

$$A_I (-\beta I_o) + I - \frac{V}{Z_0} = 0$$

From Fig. output ckt,  $I = -I_o$

$$A_I (\beta I_o) + I - \frac{V}{Z_0} = 0$$

$$\frac{V}{Z_0} = I + A_I (\beta I_o)$$

$$\frac{V}{Z_0} = I (1 + \beta A_I)$$

$$\frac{V}{I} = Z_0 (1 + \beta A_I)$$

$$Z_{of} = \frac{V}{I} = Z_0 (1 + \beta A_I) \quad \text{--- (22)}$$

→ Output impedance of voltage shunt feedback amplifier increases by a factor  $(1 + \beta A_I)$ .

## Problems :-

① A voltage - series negative feedback amplifier has a voltage gain without feedback of  $A = 500$ , input resistance,  $R_i = 3\text{ k}\Omega$ , output resistance  $R_o = 20\text{ k}\Omega$ , and feedback ratio  $\beta = 0.01$ . Calculate the voltage Gain ( $A_{rf}$ ), input resistance ( $R_{if}$ ) and output resistance ( $R_{of}$ ) of the amplifier with feedback.

Sol: Given  $A = 500$ ,  $R_i = 3\text{ k}\Omega$ ,  $R_o = 20\text{ k}\Omega$ ,  $\beta = 0.01$

voltage Gain,

$$A_{rf} = \frac{A}{1 + \beta A}$$

$$= \frac{500}{1 + (0.01 \times 500)} = \frac{500}{1 + 5} = \frac{500}{6} = 83.33$$

$$\boxed{A_{rf} = 83.33}$$

Input Impedance,  $Z_{if} = Z_i (1 + \beta A)$

$$(or) R_{if} = R_i (1 + \beta A)$$

$$= 3 \times 10^3 (1 + (0.01 \times 500))$$

$$= 3 \times 10^3 (1 + 5)$$

$$= 3 \times 10^3 (6) = 18 \times 10^3$$

$$\boxed{R_{if} = 18 \text{ k}\Omega}$$

$$(iii) \text{ output impedance, } Z_{of} = \frac{Z_o}{1 + \beta A}$$

$$(or) R_{of} = \frac{R_o}{1 + \beta A}$$

$$= \frac{20 \times 10^3}{1 + (0.01 \times 500)}$$

$$= \frac{20 \times 10^3}{1 + 5}$$

$$= \frac{20 \times 10^3}{6} = 3.33 \times 10^3$$

$R_{of} = 3.33 \text{ K}\Omega$

② A voltage shunt negative feedback amplifier has a proportionality constant ( $R_m$ ) = 300, input impedance  $Z_i = 2 \text{ k}\Omega$ , output impedance  $Z_o = 20 \text{ k}\Omega$ , and feedback ratio  $\beta = 0.05$ .

Calculate  $R_{mf}$ ,  $Z_{if}$  &  $Z_{of}$  of the amplifier with feedback.

Sol: Given  $R_m = 300$ ,  $Z_i = 2 \text{ k}\Omega$ ,  $Z_o = 20 \text{ k}\Omega$ , &  $\beta = 0.05$

$$R_{mf} = \frac{R_m}{1 + \beta R_m}$$

$$= \frac{300}{1 + (0.05 \times 300)} = \frac{300}{1 + 15} = \frac{300}{16} = 18.75$$

$R_{mf} = 18.75$

$$Z_{if} = \frac{Z_i}{1 + \beta R_m}$$

$$= \frac{2 \times 10^3}{1 + (0.05 \times 300)} = \frac{2 \times 10^3}{1 + 15} = \frac{2000}{16} = 125$$

$$\boxed{Z_{if} = 125 \Omega}$$

$$Z_{of} = \frac{Z_o}{1 + \beta R_m}$$

$$= \frac{20 \times 10^3}{1 + (0.05 \times 300)} = \frac{20 \times 10^3}{1 + 15} = \frac{20,000}{16} = 1250$$

$$\boxed{Z_{of} = 1.25 \text{ k}\Omega}$$

③ A current series feedback amplifier has a proportionality factor ( $G_M$ ) = 500, input impedance  $Z_i = 3 \text{ k}\Omega$ , output Impedance  $Z_o = 30 \text{ k}\Omega$  and feedback ratio  $\beta = 0.01$ . Calculate  $G_{mf}$ ,  $Z_{if}$  &  $Z_{of}$ .

Sol 1 - Given,  $G_M = 500$ ,  $Z_i = 3 \text{ k}\Omega$ ,  $Z_o = 30 \text{ k}\Omega$ , &  $\beta = 0.01$

$$G_{mf} = \frac{G_M}{1 + \beta G_M}$$

$$= \frac{500}{1 + (0.01 \times 500)} = \frac{500}{1 + 5} = \frac{500}{6} = 83.33$$

$$\boxed{G_{mf} = 83.33}$$

$$Z_{if} = Z_i (1 + \beta G_M)$$

$$= 3 \times 10^3 (1 + (0.01 \times 500)) = 3 \times 10^3 (1 + 5) = 3 \times 10^3 (6) = 18 \times 10^3$$

$$\boxed{Z_{if} = 18 \text{ k}\Omega}$$

$$Z_{of} = Z_o(1 + \beta A_I)$$

$$= 30 \times 10^3 (1 + (0.05 \times 100)) = 30 \times 10^3 (1 + 5) = 30 \times 10^3 (6) = 180 \times 10^3$$

$$\boxed{Z_{of} = 180 \text{ k}\Omega}$$

④ A current-shunt feedback amplifier has a current gain  $A_I = 100$ , input impedance  $Z_i = 2 \text{ k}\Omega$ , output impedance  $Z_o = 15 \text{ k}\Omega$ . and feedback ratio  $\beta = 0.05$ . Calculate  $A_{If}$ ,  $Z_{if}$  and  $Z_{of}$ ?

Sol: - Given,  $A_I = 100$ ,  $Z_i = 2 \text{ k}\Omega$ ,  $Z_o = 15 \text{ k}\Omega$  &  $\beta = 0.05$

$$A_{If} = \frac{A_I}{1 + \beta A_I}$$

$$= \frac{100}{1 + (0.05 \times 100)} = \frac{100}{1 + 5} = \frac{100}{6} = 16.66$$

$$\boxed{A_{If} = 16.66}$$

$$Z_{if} = \frac{Z_i}{1 + \beta A_I}$$

$$= \frac{2 \times 10^3}{1 + (0.05 \times 100)} = \frac{2 \times 10^3}{1 + 5} = \frac{2000}{6} = 333.33$$

$$\boxed{Z_{if} = 333.33 \Omega}$$

$$Z_{of} = Z_o(1 + \beta A_I)$$

$$= 15 \times 10^3 (1 + (0.05 \times 100)) = 15 \times 10^3 (1 + 5) = 15 \times 10^3 (6)$$

$$= 90 \times 10^3$$

$$\boxed{Z_{of} = 90 \text{ k}\Omega}$$

## Problems :-

(5) An amplifier voltage gain with feedback is 100. If the gain without feedback changes by 20% and the gain with feedback should not vary more than 2% determine the values of open loop gain A and feedback ratio  $\beta$ .

Sol) Given  $A_f = 100$

$$\frac{dA_f}{A_f} = 2\% = 0.02$$

$$\frac{dA}{A} = 20\% = 0.2$$

$$A = ?$$

$$\beta = ?$$

$$A_f = \frac{A}{(1 + \beta A)}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \cdot \frac{1}{(1 + \beta A)}$$

$$0.02 = 0.2 \cdot \frac{1}{(1 + \beta A)}$$

$$\frac{0.02}{0.2} = \frac{1}{(1 + \beta A)}$$

$$\frac{1}{(1 + \beta A)} = \frac{0.02}{0.2}$$

$$\frac{1}{(1 + \beta A)} = \frac{1}{10}$$

$$(1 + \beta A) = 10$$

$$\frac{0.02}{0.2} = \frac{2}{100} \times \frac{10}{2} = \frac{1}{10}$$

The gain with feedback is given by

$$A_f = \frac{A}{(1 + \beta A)}$$

$$100 = \frac{A}{10}$$

$$A = 100 \times 10 = 1000$$

$$\therefore \boxed{A = 1000}$$

$$1 + \beta A = 10$$

$$\beta A = 10 - 1$$

$$A\beta = 9$$

$$\beta = \frac{9}{A} = \frac{9}{1000} = 0.009$$

$$\boxed{\beta = 0.009}$$

- ⑥ The overall gain of a multistage amplifier is 100. When negative feedback is applied, the gain reduces to 10. Find the fraction of the output that is feedback to the input.

Sol: Given,  $A = 100$ ,  $A_f = 10$ ,  $\beta = ?$

wkT  $A_f = \frac{A}{1 + A\beta}$

$$10 = \frac{100}{1 + 100\beta}$$

$$1 + 100\beta = \frac{100}{10}$$

$$1 + 100\beta = 10$$

$$100\beta = 10 - 1$$

$$100\beta = 9$$

$$\boxed{\beta = \frac{9}{100} = 0.09}$$

7) A negative feedback amplifier has  $A=100$ ,  $\beta=0.04$  and  $V_s = 50\text{mV}$ . Find,

- (i) Gain with feedback
- (ii) output voltage
- (iii) Feedback factor
- (iv) Feedback voltage

Sol:- Given  $A=100$ ,  $\beta=0.04$  &  $V_s = 50\text{mV}$ .

(i) Gain with feedback,

$$A_f = \frac{A}{1+n\beta}$$

$$= \frac{100}{1 + (100 \times 0.04)} = \frac{100}{1+4} = \frac{100}{5} = 20$$

$$\boxed{A_f = 20}$$

(ii) output voltage,

$$A_f = \frac{V_o}{V_s}$$

$$\therefore V_o = A_f \times V_s$$

$$= 20 \times 50 \times 10^{-3}$$

$$= 1000 \times 10^{-3} = 1$$

$$\boxed{V_o = 1\text{V}}$$

(iii) Feedback factor,

$$A\beta = 100 \times 0.04 = \underline{\underline{4}}$$

(iv) Feedback Voltage,

$$\beta V_o = 0.04 \times 1 = \underline{\underline{0.04V}}$$

Q) with a negative feedback, an amplifier gives an output of 10V with an input of 0.25V, when the feedback is removed, it requires 0.25V input for the same output. Calculate (i) Gain without feedback  
(ii) Feedback fraction  $\beta$ .

Sol:- (i) Gain without feedback,

$$A = \frac{\text{o/p voltage}}{\text{i/p voltage}}$$

$$= \frac{10}{0.25} = \frac{10 \times 100}{25} = \underline{\underline{40}}$$

$$\boxed{A = 40}$$

(ii)

$$A_f = \frac{A}{1 + A\beta}$$

$$A_f = \frac{\text{o/p voltage with feedback}}{\text{i/p voltage with feedback}}$$

$$= \frac{10}{0.5} = \frac{10 \times 10^2}{\$} = 20$$

$$\therefore A_f = 20$$

$$\therefore A_f = \frac{A}{1 + n\beta}$$

$$20 = \frac{40}{1 + (40\beta)}$$

$$1 + 40\beta = \frac{40}{20}$$

$$1 + 40\beta = 2$$

$$40\beta = 2 - 1$$


$$40\beta = 1$$

$$\beta = \frac{1}{40} = 0.025$$

$\boxed{\beta = 0.025}$
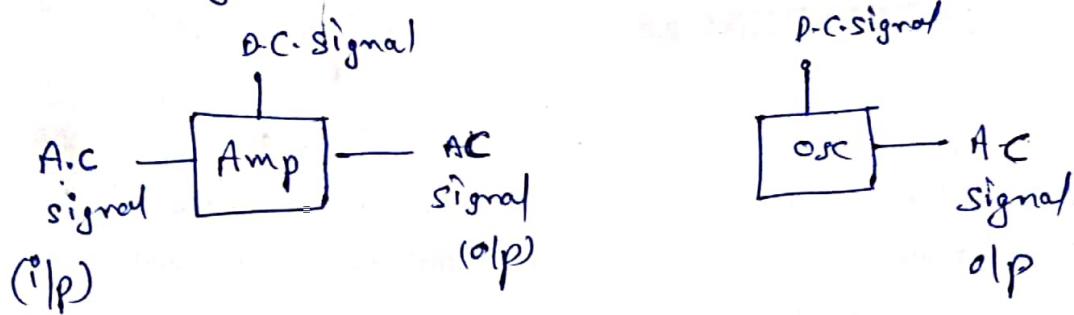
## UNIT- III (b) - Oscillators

Def: - Oscillator is an electronic ckt. which generates an a.c. o/p signal without requesting any externally applied i/p signal.



→ Oscillator works on the Principle of +ve FB.

Applications: - Radio, Television Receivers etc


+ve FB	-ve FB
<p>① When the FB is applied such that it is <u>in phase</u> with the original i/p signal then it is called +ve FB.</p>	<p>① When the FB is applied such that it is <u>out of phase</u> with the original i/p signal then it is called -ve FB.</p>
<p>② It is regenerative (or) direct FB</p>	<p>② It is degenerative (or) inverse FB.</p>
<p>③ It increases the gain of the amplifier</p> $A_f = \frac{A}{1 - A\beta}$	<p>③ It decreases the gain of the amplifier</p> $A_f = \frac{A}{1 + A\beta}$

- |  |  |
|--|--|
| ④ It makes the amplifier <u>unstable</u> . | ⑥ It makes the amplifier <u>stable</u> .   |
| ⑤ It reduces the B.W.                      | ⑤ It increases the B.W.                    |
| ⑥ It is used in the oscillators.           | ⑥ It is used in the small signal Amplifier |

## I) Classification of oscillators :-

- ① RC oscillators
  - (a) RC Phase shift oscillator
  - (b) Wien-Bridge "
- ② LC oscillators
  - (a) Hartley oscillator
  - (b) Colpitt's "
- ③ crystal oscillators
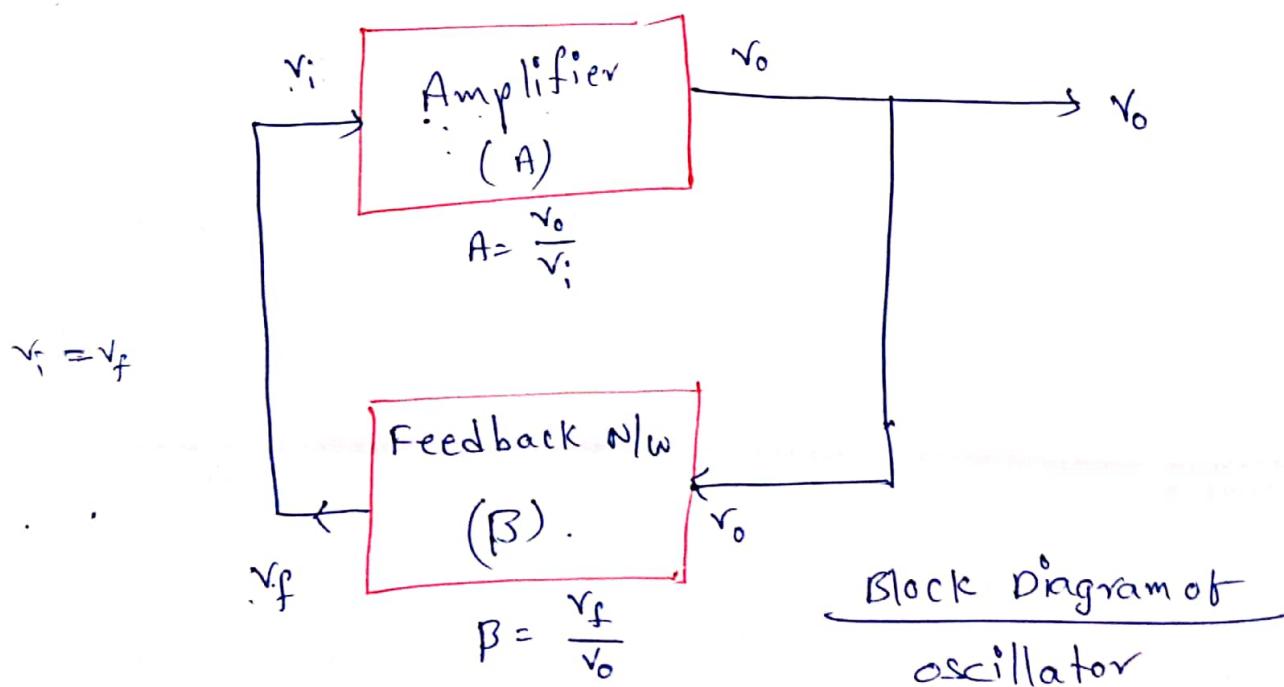
## II Conditions for oscillations / Barkhausen Criterion:-



$$\text{Def. of Amp. } A = \frac{V_o}{V_i}$$

$$\therefore V_o = A \cdot V_i \quad \text{--- (1)}$$

$$\text{Def. of FB Ratio, } \beta = \frac{V_f}{V_o}$$

$$V_o = \frac{V_f}{\beta} \quad \text{--- (2)}$$

Substituting Eqn(2) in (1), we get

$$\frac{V_f}{\beta} = A \cdot V_i$$

$$\text{But } V_i = V_f$$

$$\frac{V_i}{\beta} = A \cancel{V_i}$$

$$A\beta = 1$$

$$A\beta = 1 + j0$$

$$\therefore |A\beta| = 1, \angle A\beta = 0^\circ \leftrightarrow 360^\circ$$


→ The magnitude of loop gain  $|A\beta| = 1$  &  
Total phase of the loop is  $0^\circ$  or  $360^\circ$ .

These two conditions are called as

"Barkhausen Criteria Conditions"

①  $|A\beta| > 1$ ,


Damped Exponential  
Rise oscillations.

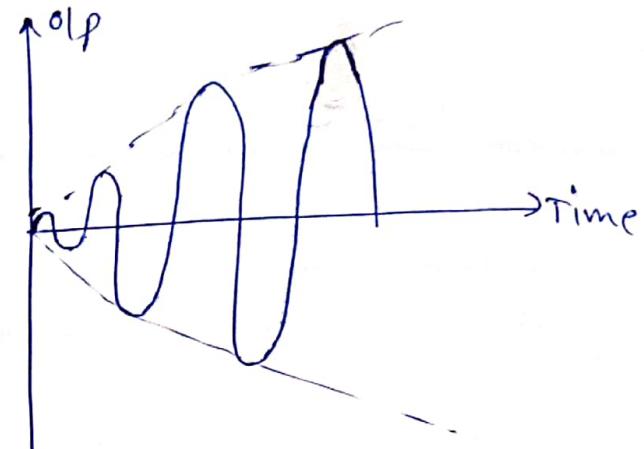

Growing type of oscillations

②  $|A\beta| < 1$


Damped Exponential  
Decay oscillations.

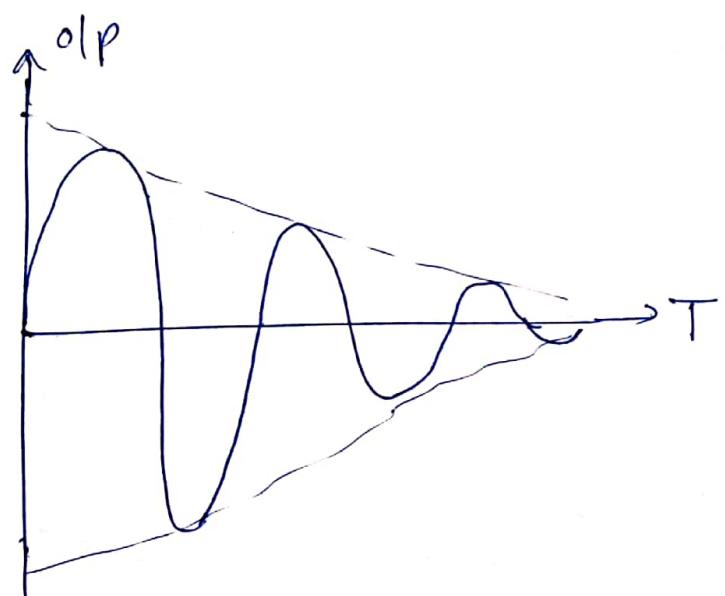

Exponentially Decay of  
oscillations



③  $|A\beta| = 1$

Undamped oscillations

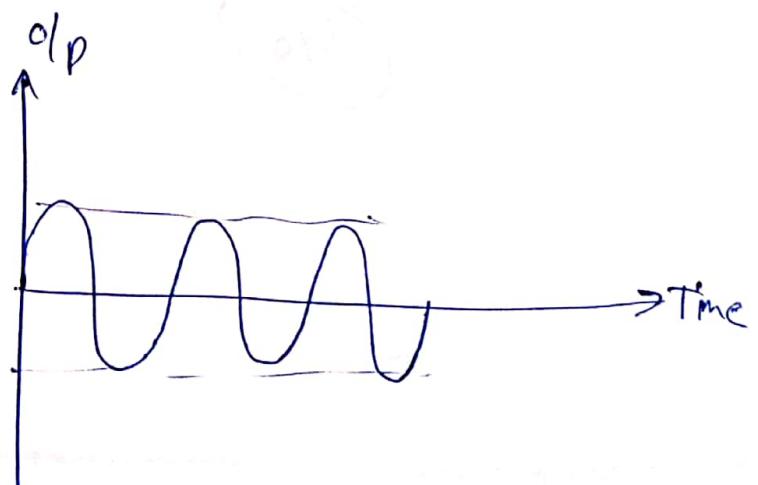

Sustained Oscillations.


## I(a) R C Phase shift oscillator :-

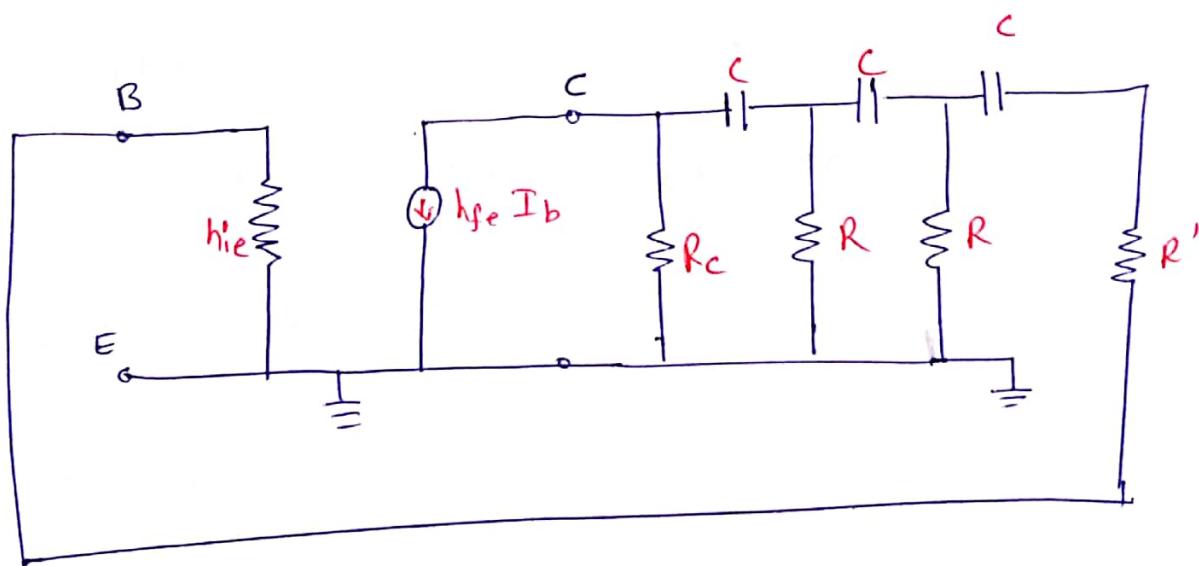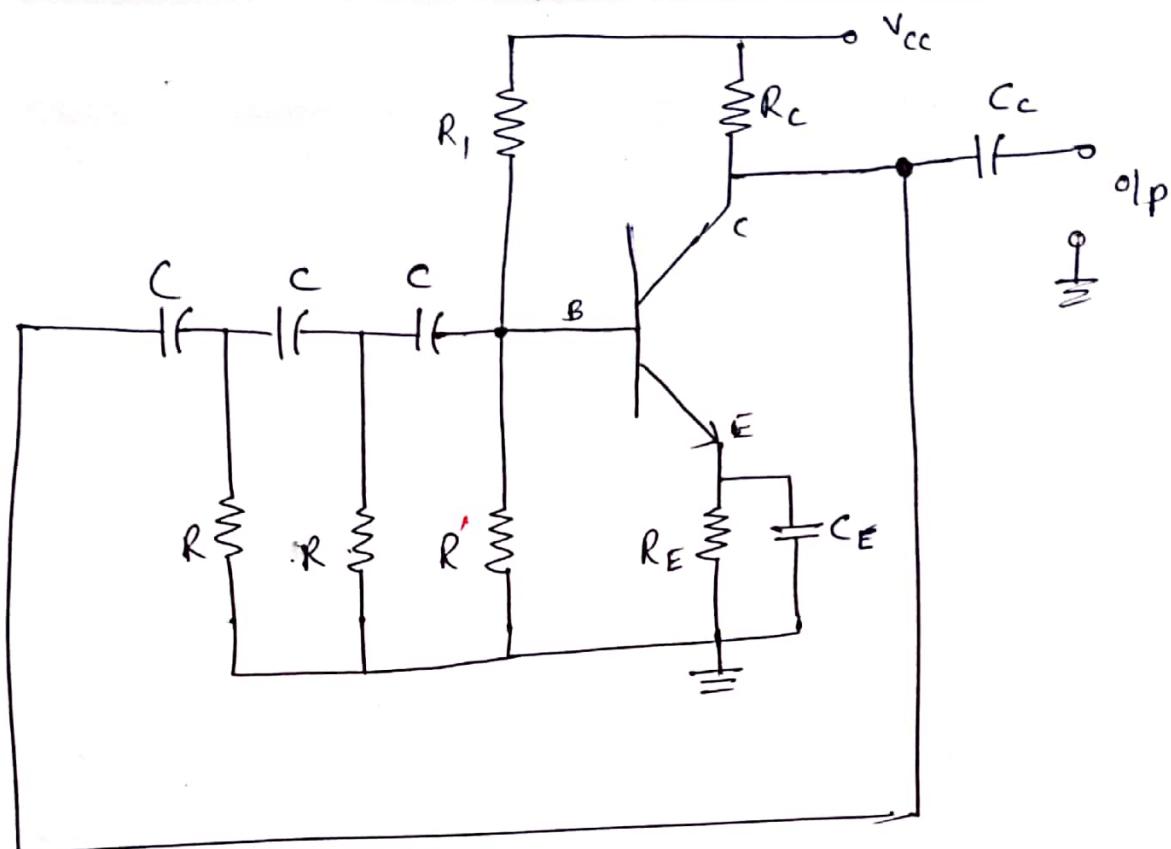

Now, we can replace  $h_{ie} + R'$  as  $R$  ||  $r$  replacing the current source ( $h_{fe} I_b$ ) by its equivalent voltage source. Assume the ratio of the resistance  $R_C$  to  $R$  be  $k$ .

$$K = \frac{R_c}{R}$$

$$\therefore R_c = KR$$

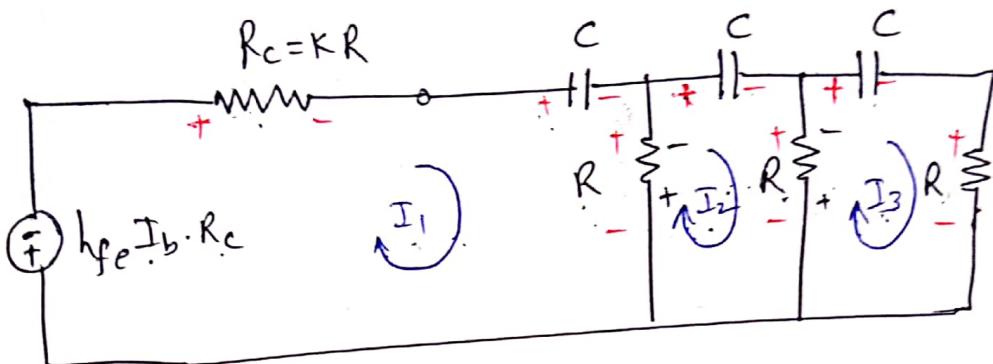

Apply KVL for loop 1

$$-R_c I_1 - \frac{1}{j\omega C} I_1 - RI_1 + I_2 R - h_{fe} I_b R_c = 0$$

$$\text{but } R_c = KR, \quad j\omega = s$$

$$-I_1 KR - \frac{1}{sc} I_1 - RI_1 + I_2 R - h_{fe} I_b R_c = 0$$

$$-I_1 \left[ KR + \frac{1}{sc} + R \right] + I_2 R = h_{fe} I_b R_c$$

$$- \left[ I_1 \left[ (K+1)R + \frac{1}{sc} \right] - I_2 R \right] = h_{fe} I_b R_c$$

$$I_1 \left[ (K+1)R + \frac{1}{sc} \right] - I_2 R = -h_{fe} I_b R_c \quad \textcircled{1}$$

Loop 2

$$-\frac{1}{j\omega C} I_2 - RI_2 + RI_3 - RI_2 + RI_1 = 0$$

$$I_1 R - I_2 \left[ \frac{1}{j\omega C} + R + R \right] - I_3 R = 0$$

$$I_1 R - I_2 \left[ 2R + \frac{1}{sc} \right] + I_3 R = 0 \quad \text{---(2)}$$

Loop 3 :-

$$-\frac{1}{j\omega c} I_3 - R I_3 - R I_3 + R I_2 = 0$$

$$I_2 R - I_3 \left[ R + R + \frac{1}{j\omega c} \right] = 0$$

$$I_2 R - I_3 \left[ 2R + \frac{1}{j\omega c} \right] = 0$$

$$I_2 R - I_3 \left[ 2R + \frac{1}{sc} \right] = 0 \quad \text{---(3)}$$

Using Cramer's Rule to solve for  $I_3$

$$D = \begin{vmatrix} (k+1)R + \frac{1}{sc} & -R & 0 \\ R & -\left[ 2R + \frac{1}{sc} \right] & R \\ 0 & R & -\left[ 2R + \frac{1}{sc} \right] \end{vmatrix}$$

To solve above matrix, we get

$$D = s^3 c^3 R^3 [3k+1] + s^2 c^2 R^2 [4k+6] + scR [5k+1] + 1$$

$$D_3 = \begin{vmatrix} (K+1)R + \frac{1}{sc} & -R & -h_{fe} I_b R_c \\ R & -\left[ 2R + \frac{1}{sc} \right] & 0 \\ 0 & R & 0 \end{vmatrix}$$

$$= -h_{fe} I_b R_c [R^2 - 0]$$

$$= -h_{fe} I_b (KR) R^2$$

$$D_3 = -KR^3 h_{fe} I_b \quad \text{--- (4)}$$

$$\therefore I_3 = \frac{D_3}{D}$$

$$I_3 = \frac{-KR^3 h_{fe} I_b s^3 c^3}{s^3 c^3 R^3 [3K+1] + s^2 c^2 R^2 [4K+6] + sc R [5K+1] + 1} \quad \text{--- (5)}$$

where,  $I_3 \rightarrow$  o/p current of the feedback amplifier

$I_b \rightarrow$  i/p " " " " " amplifier

$I_3 = h_{fe} I_b \rightarrow$  i/p current of the feedback amplifier

$$A = \frac{\text{o/p of amplifier ckt}}{\text{i/p to amplifier ckt}} = \frac{I_3}{I_b} = h_{fe}$$

$$\beta = \frac{\text{olp of feedback ckt}}{\text{olp to feedback ckt}} = \frac{I_3}{h_{fe} I_b}$$

$$A\beta = h_{fe} \times \frac{I_3}{h_{fe} I_b} = \frac{I_3}{I_b} \quad \text{--- (6)}$$

$$A\beta = \frac{-KR^3 h_{fe} s^3 c^3}{s^3 c^3 R^3 [3K+1] + s^2 c^2 R^2 [4K+6] + s c R [5K+1] + 1} \quad \text{--- (7)}$$

Substituting  $s = j\omega$ ,  $s^2 = -\omega^2$ ,  $s^3 = j\omega^3$  in the  
 $= -\omega^2 \quad = -j\omega^3$

Eqn (7), we get

$$A\beta = \frac{-KR^3 h_{fe} (-j\omega^3) c^3}{-j\omega^3 c^3 R^3 [3K+1] - \omega^2 c^2 R^2 [4K+6] + j\omega c R [5K+1] + 1}$$

Separating the Real & Imaginary parts in  
 the denominator, we get

$$A\beta = \frac{j\omega^3 KR^3 c^3 h_{fe}}{[-\omega^2 c^2 R^2 [4K+6]] - j\omega [\omega^2 c^3 R^3 [3K+1] - cR(5K+1)]}$$

Dividing numerator and denominator by

$$j\omega^3 R^3 c^3$$

$$A\beta = \frac{K_{hfe}}{\left[ \frac{1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2}{j\omega^3 R^3 C^3} \right] - \left[ \frac{j\omega(3K\omega^2 R^3 C^3 + \omega^2 R^3 C^5 - 5R^2 C^2)}{j\omega^3 R^3 C^3} \right]}$$

but  $\frac{1}{j} = -j$

$$A\beta = \frac{K_{hfe}}{-j \left[ \frac{1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2}{\omega^3 R^3 C^3} \right] - \left[ \frac{3K\omega^3 R^3 C^3 + \omega^3 R^3 C^5 - 5\omega^2 R^2 C^2 - K\omega R^2 C}{\omega^3 R^3 C^3} \right]}$$

$$= \frac{K_{hfe}}{-j \left[ \frac{1}{\omega^3 R^3 C^3} - \frac{4K\omega^2 C^2 R^2}{\omega^3 R^3 C^3} - \frac{6\omega^2 C^2 R^2}{\omega^3 R^3 C^3} \right] - \left[ \frac{3K\omega^3 R^3 C^3}{\omega^3 R^3 C^3} + \frac{\omega^3 R^3 C^5}{\omega^3 R^3 C^3} - \frac{5\omega^2 R^2 C^2}{\omega^3 R^3 C^3} - \frac{K\omega R^2 C}{\omega^3 R^3 C^3} \right]}$$

$$= \frac{K_{hfe}}{-j \left[ \frac{1}{\omega^3 R^3 C^3} - \frac{4K}{\omega R^2 C^2} - \frac{6}{\omega R^2 C^2} \right] - \left[ 3K + 1 - \frac{5}{\omega^2 R^2 C^2} - \frac{K}{\omega^2 R^2 C^2} \right]}$$

$$\frac{1}{\omega R^2 C^2} = \alpha$$

$$\therefore A\beta = \frac{K_{hfe}}{-j[\alpha^3 - 4K\alpha - 6\alpha] - [3K + 1 - 5\alpha^2 - K\alpha^2]}$$

$$A\beta = \frac{K_{lfe}}{-[3K+1 - 5\alpha^2 - K\alpha^2] - j[\alpha^3 - 4K\alpha - 6\alpha]}$$

$\therefore$  Two condition's ( $A\beta = 0^\circ$ ,  $|A\beta| = 1$ )

$\therefore$  The imaginary part is equal to  
due to  $\angle A\beta = 0^\circ$

$$\alpha^3 - 4K\alpha - 6\alpha = 0$$

$$\alpha(\alpha^2 - 4K - 6) = 0$$

$$\alpha^2 - 4K - 6 = 0, \alpha = 0 \quad (\because \text{neglect})$$

$$\alpha^2 = 4K + 6$$

$$\alpha = \sqrt{4K + 6}$$

$$\text{but } \alpha = \frac{1}{\omega RC}$$

$$\frac{1}{\omega RC} = \sqrt{4K + 6}$$

$$\omega RC = \frac{1}{\sqrt{4K + 6}}$$

$$\omega = \frac{1}{RC \sqrt{4K + 6}}$$

$$\text{since } \omega = 2\pi f$$

$$2\pi f = \frac{1}{RC \sqrt{UK+6}}$$

$$f = \frac{1}{2\pi RC \sqrt{UK+6}}$$


Advantages :-

- ① It doesn't require transformers or inductors.
- ② It can be used to produce very low frequency.
- ③ The circuit provides good frequency stability.

Disadvantages :-

- ① It is difficult for the ckt to start oscillations as the feedback is generally small.
- ② The ckt gives small o/p.
- ③ The three capacitors or resistors should be changed simultaneously change the frequency of oscillation and it is difficult to control the amplitude of oscillation without affecting the frequency of oscillation.

## Q6) Wien-Bridge Oscillator :-

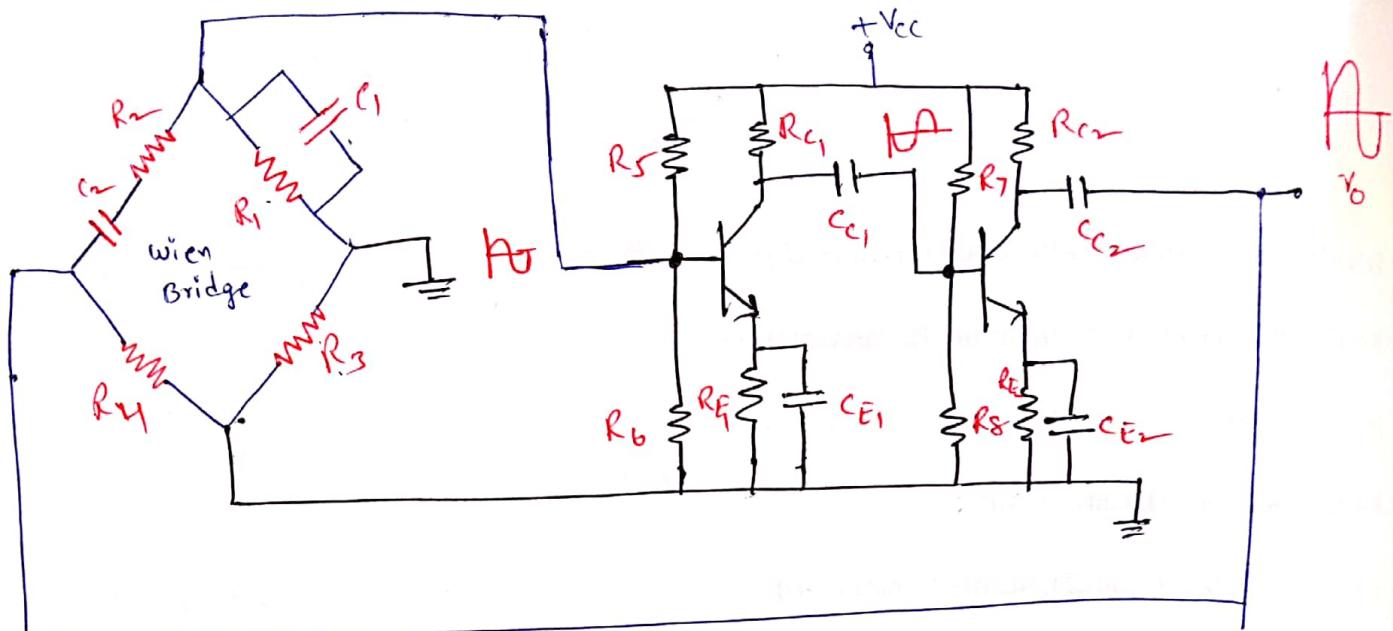

From Fig.,

$$z_1 = R_1 \text{ parallel with } C_1 (R_1 \parallel C_1)$$

$$z_2 = R_2 \text{ series with } C_2 (R_2 + C_2)$$

$$z_3 = R_3$$

$$z_4 = R_4$$

The wien bridge must be in Balance mode

$$\text{i.e. } z_1 z_4 = z_2 z_3 \quad \text{--- } ①$$

$$\therefore \frac{z_4}{z_3} = \frac{z_2}{z_1}$$

As  $\omega kT$ ,

$$z_1 = R_1 \parallel C_1 = R_1 \parallel \frac{1}{j\omega C_1}$$

$$Z_1 = \frac{R_1 \cdot \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} = \frac{\frac{R_1}{j\omega C_1}}{\frac{j\omega R_1 C_1 + 1}{j\omega C_1}}$$

$$Z_1 = \frac{R_1}{1 + j\omega R_1 C_1} \quad \text{--- (2)}$$

$$Z_2 = R_2 + C_2 = R_2 + \frac{1}{j\omega C_2} \quad \text{--- (3)}$$

$$Z_3 = R_3 \quad \text{--- (4)}$$

$$Z_4 = R_4 \quad \text{--- (5)}$$

Substituting eqn's (2), (3), (4) & (5) in (1), we get

$$Z_1 Z_4 = Z_2 Z_3$$

$$\frac{R_1}{1 + j\omega R_1 C_1} \cdot R_4 = \left( R_2 + \frac{1}{j\omega C_2} \right) \cdot R_3$$

$$\frac{R_1 R_4}{R_3} = \left( 1 + j\omega R_1 C_1 \right) \left( R_2 + \frac{1}{j\omega C_2} \right)$$

$$\frac{R_1 R_4}{R_3} = R_2 + \frac{1}{j\omega C_2} + j\omega R_1 R_2 C_1 + \frac{R_1 C_1}{C_2}$$

$$-\frac{R_1 R_4}{R_3} + R_2 + \frac{R_1 C_1}{C_2} + j\omega R_1 R_2 C_1 + \frac{1}{j\omega C_2} = 0 \quad \text{--- (6)}$$

*Real part*                    *Imaginary part*

To get the frequency of oscillations, equate  
the imaginary part to zero for  $0^\circ$  phase shift

From eqn ⑥,

$$j\omega R_1 R_2 C_1 + \frac{1}{j\omega C_2} = 0$$

$$j\omega R_1 R_2 C_1 - \frac{j}{\omega C_2} = 0 \quad [\because \frac{1}{j} = -j]$$

$$\cancel{j\omega R_1 R_2 C_1} = \frac{j}{\omega C_2}$$

$$\omega R_1 R_2 C_1 = \frac{1}{\omega C_2}$$

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\text{but } \omega = 2\pi f$$

$$2\pi f = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

7

This is the frequency of sustained oscillations.

→ If  $R_1 = R_2 = R$  and  $C_1 = C_2 = C$  then

$$f = \frac{1}{2\pi \sqrt{R \cdot R \cdot C \cdot C}}$$

$$= \frac{1}{2\pi \sqrt{R^2 C^2}}$$

$$f = \frac{1}{2\pi R C} \quad \boxed{8}$$

For changing the frequency, we must change  
R & C values.

Conditions for maximum Oscillations :

To get the maximum oscillations,  
we equate the Real part to zero in Eqn(6)

$$\frac{-R_1 R_y}{R_3} + R_2 + \frac{R_1 C_1}{C_2} = 0$$

$$\frac{R_1 R_y}{R_3} = R_2 + \frac{R_1 C_1}{C_2}$$

$$\frac{R_y}{R_3} = \frac{R_2}{R_1} + \frac{C_1}{C_2}$$

If  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$  then

$$\frac{R_y}{R_3} = \frac{R}{R} + \frac{C}{C}$$

$$\frac{R_y}{R_3} = 1+1$$

$$\frac{R_y}{R_3} = 2$$

$$R_y = 2R_3 \quad \text{--- (7)}$$

### Advantages :-

- ① This gives good frequency stability.
- ② Overall gain is high because of two Transistors
- ③ It produces a very good sinewave o/p.
- ④ Frequency of oscillations can be changed.
- ⑤ By replacing  $R_y$  with a thermistor, amplitude stability of oscillator o/p voltage can be increased.


### Disadvantages :-

- ① It cannot generate very high frequencies.
- ② It requires two transistors & large no. of components.


## Applications:-

- ① Audio Frequency range.
- ② low frequency of oscillations.
- ③ For laboratory purpose.
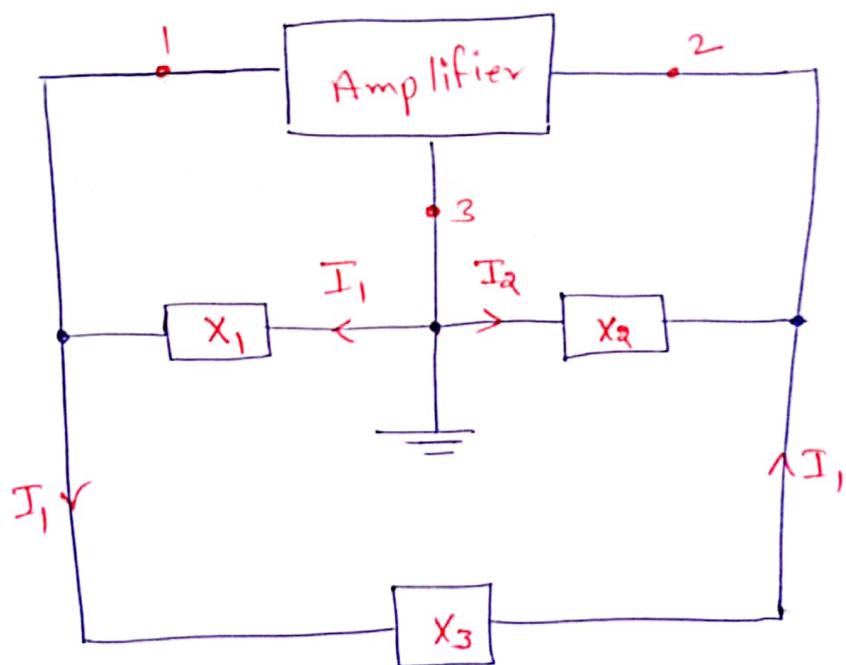
## Generalized Analysis of LC oscillators :-



General form of an oscillator

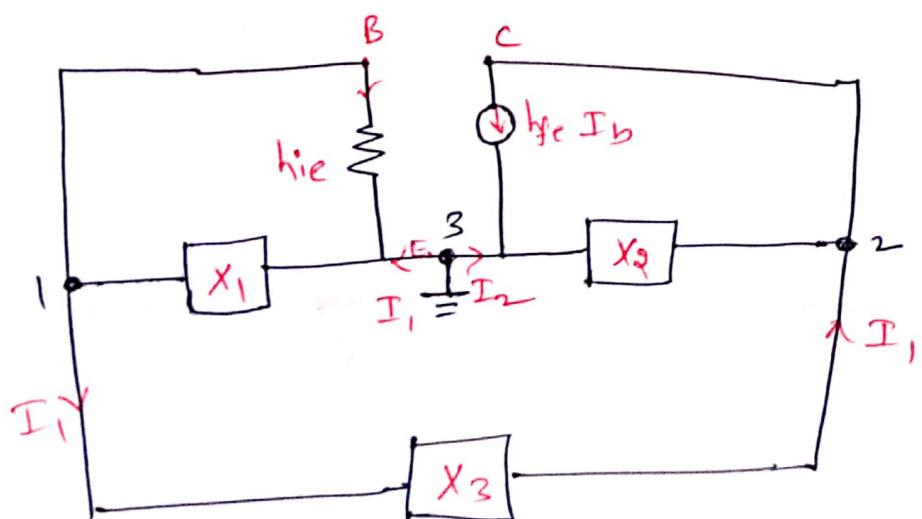

Any of the active devices such as vacuum tube, Transistor, FET and operational amplifier (op-amp) may be used in the amplifier section.

→  $X_1$ ,  $X_2$  and  $X_3$  are reactive elements constituting the feedback tank circuit which determines the frequency of oscillation.

→ Here,  $X_1$  and  $X_2$  serve as an ac voltage divider for the o/p voltage and feedback signal. Therefore, the voltage across  $X_1$  is the feedback signal. The frequency of oscillation of the LC oscillator is

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$


→ The inductive (or) Capacitive reactances are represented by  $X_1$ ,  $X_2$  and  $X_3$ . The o/p terminals are 2 and 3, and i/p terminals are 1 and 3.

∴ Final equation,

$$h_{ie}(X_1 + X_2 + X_3) + X_1 X_2 (1 + h_{fe}) + X_1 X_3 = 0$$

Oscillator	Reactive Components	
Hartley	$X_1 = X_2 = L$	$X_3 = C$
Colpitts	$X_1 = X_2 = C$	$X_3 = L$

## Hartley Oscillator :-

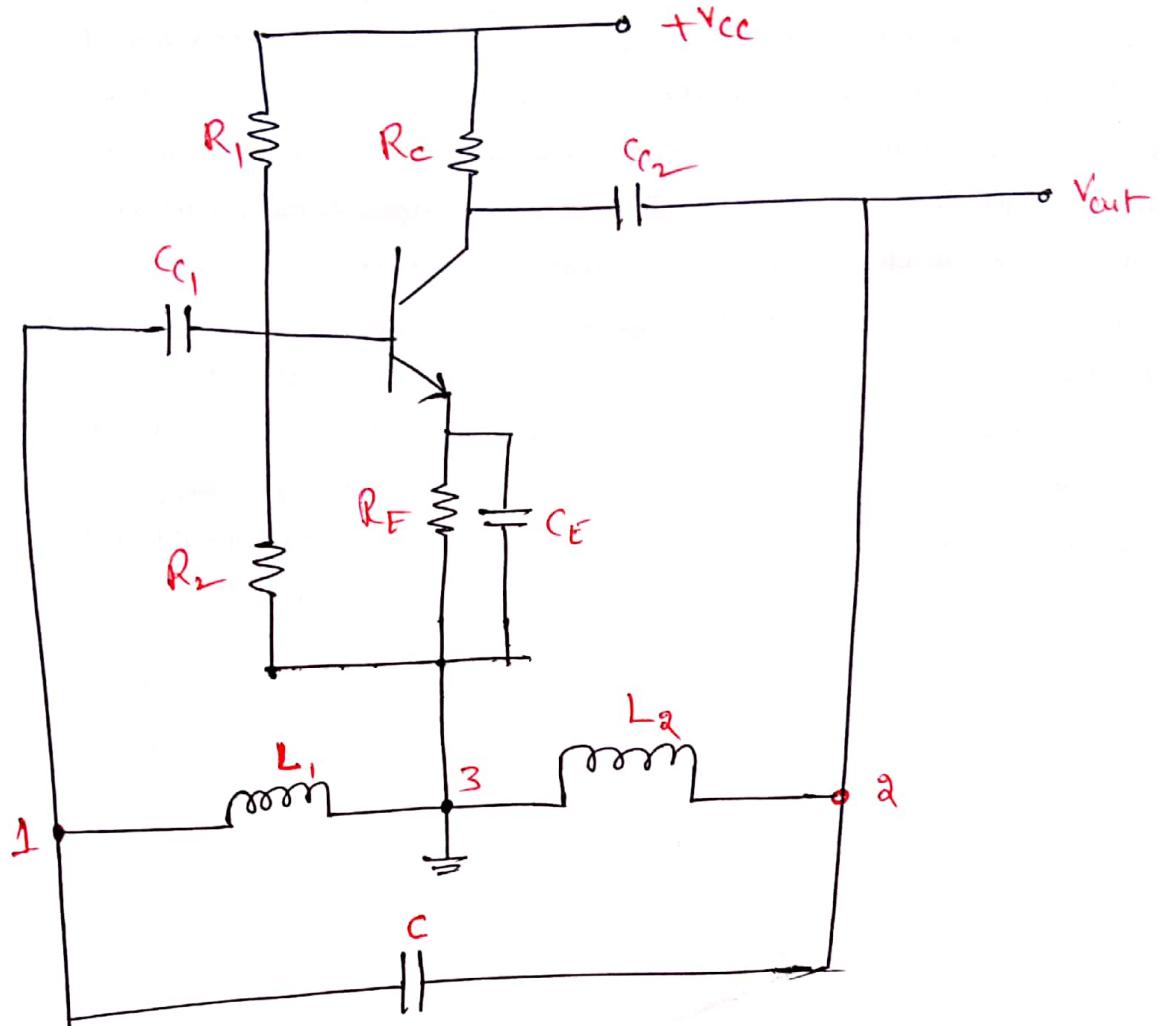

Analysis of Hartley Oscillator:-

$X_1 \quad \left. \begin{matrix} X_1 \\ X_2 \end{matrix} \right\}$  Inductive Reactances

$X_3 \rightarrow$  Capacitive "

$M \rightarrow$  Mutual Inductance b/w Inductors.

$$X_1 = j\omega L_1 + j\omega M$$

$$X_2 = j\omega L_2 + j\omega M$$

$$X_3 = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

Substituting these values in General Eqn

$$h_{ie}(X_1 + X_2 + X_3) + X_1 X_2 (1 + h_{fe}) + X_1 X_3 = 0$$

$$h_{ie} \left[ (j\omega L_1 + j\omega M) + (j\omega L_2 + j\omega M) + \left( -\frac{j}{\omega C} \right) \right]$$

$$+ (j\omega L_1 + j\omega M)(j\omega L_2 + j\omega M)(1 + h_{fe})$$

$$+ (j\omega L_1 + j\omega M) \left( -\frac{j}{\omega C} \right) = 0$$

$$h_{ie} \left[ j\omega L_1 + j\omega L_2 + 2j\omega M - \frac{j}{\omega C} \right]$$

$$+ j\omega(L_1 + M) j\omega(L_2 + M) (1 + h_{fe})$$

$$+ j\omega(L_1 + M) \left( -\frac{j}{\omega C} \right) = 0$$

$$j\omega h_{ie} \left[ L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right] - \omega^2 (L_1 + M)(L_2 + M)(1 + h_{fe}) + \frac{L_1 + M}{C} = 0$$

$$\underbrace{j\omega h_{ie} \left[ L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right]}_{\text{Imaginary part}} - \underbrace{\omega^2 (L_1 + M) \left[ (L_2 + M)(1 + h_{fe}) - \frac{1}{\omega^2 C} \right]}_{\text{Real part}} = 0$$

Equating the Imaginary Part equal to zero, we get

$$\text{while } \left[ L_1 + L_2 + 2m - \frac{1}{\omega^2 C} \right] = 0$$

$$L_1 + L_2 + 2m - \frac{1}{\omega^2 C} = 0 \quad [\because \text{while} \neq 0]$$

$$L_1 + L_2 + 2m = \frac{1}{\omega^2 C}$$

$$\omega^2 C = \frac{1}{L_1 + L_2 + 2m}$$

$$\omega^2 = \frac{1}{(L_1 + L_2 + 2m)C}$$

$$\omega = \frac{1}{\sqrt{(L_1 + L_2 + 2m)C}}$$

$$\therefore f = \frac{1}{2\pi \sqrt{(L_1 + L_2 + 2m)C}} \quad [\because \omega = 2\pi f] \quad \text{--- (3)}$$

Condition for Sustained Oscillations :-

Equating Real part equal to zero, we get

$$-\omega^2(L_1 + m) \left[ (L_2 + m)(1 + h_{fe}) - \frac{1}{\omega^2 C} \right] = 0$$

$$\omega^2(L_1 + m) \neq 0, \quad (L_2 + m)(1 + h_{fe}) - \frac{1}{\omega^2 C} = 0$$

$$(L_2 + m)(1 + h_{fe}) = \frac{1}{\omega^2 C}$$

$$(1 + h_{fe}) = \frac{1}{\omega^2 c (L_a + M)}$$

But  $\omega^2 c = \frac{1}{L_1 + L_a + 2M}$

$$(1 + h_{fe}) = \frac{1}{\frac{1}{L_1 + L_a + 2M} \cdot (L_a + M)}$$

$$= \frac{L_1 + L_a + 2M}{L_a + M}$$

$$= \frac{L_1 + L_a + M + M}{L_a + M}$$


$$= \frac{(L_1 + M) + (L_a + M)}{(L_a + M)}$$

$$= \frac{L_1 + M}{L_a + M} + \frac{L_a + M}{L_a + M}$$

~~$1 + h_{fe} = \frac{L_1 + M}{L_a + M} + 1$~~

$$h_{fe} = \frac{L_1 + M}{L_a + M}$$

## Colpitt's oscillator :-

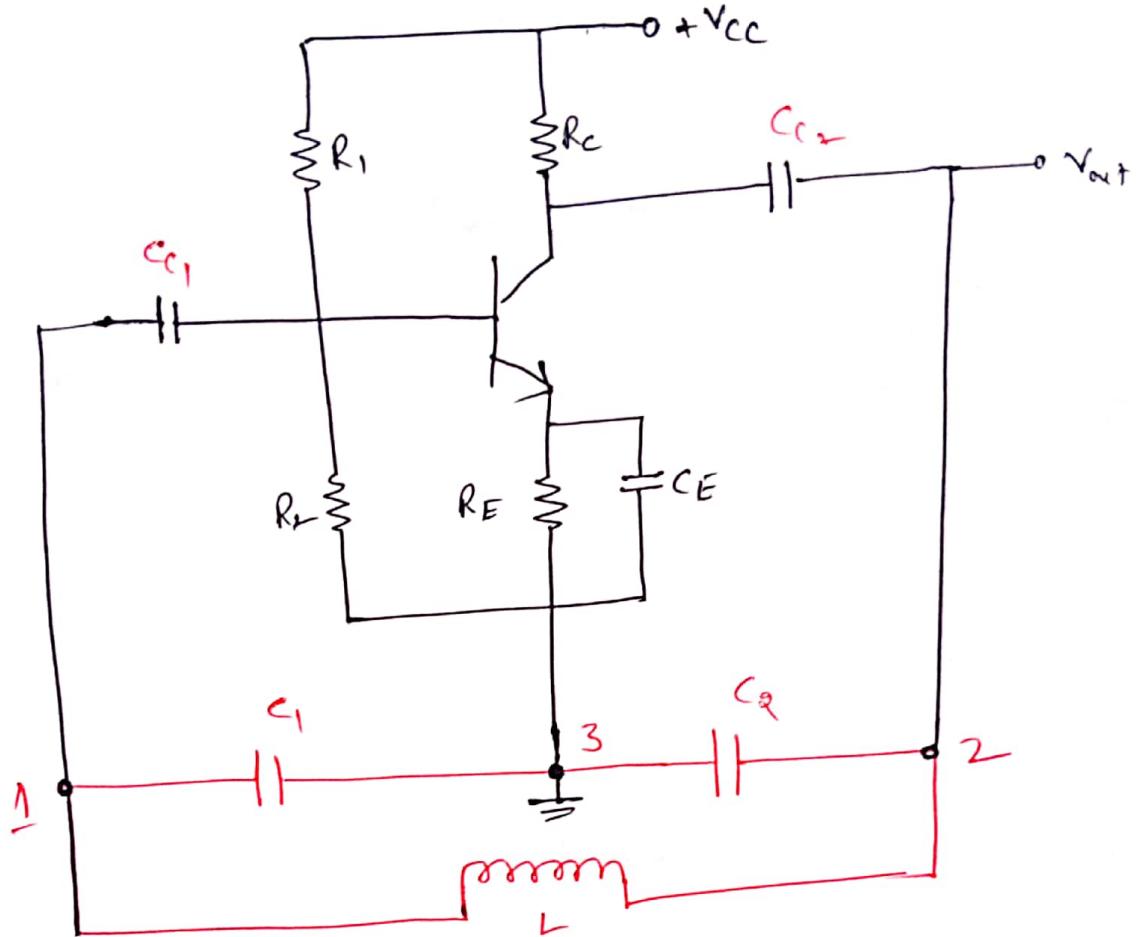

## Analysis of Colpitt's Oscillator :-

The General eqn of the oscillator is given by

$$h_{ie}(x_1 + x_2 + x_3) + x_1 x_2 (1 + h_{fe}) + x_1 x_3 = 0$$

$$x_1 = \frac{1}{j\omega C_1} = \frac{-j}{\omega C_1}$$

$$x_2 = \frac{1}{j\omega C_2} = \frac{-j}{\omega C_2}$$

$$x_3 = j\omega L$$

Substituting  $x_1, x_2$  &  $x_3$  value in General eqn,  
we get

$$h_{ie} \left[ \frac{-j}{\omega C_1} - \frac{j}{\omega C_2} + j\omega L \right] + \left( \frac{-j}{\omega C_1} \right) \left( \frac{-j}{\omega C_2} \right) (1+h_{fe}) + \left( \frac{-j}{\omega C_1} \right) (j\omega L) = 0$$

$$-jh_{ie} \left[ \frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right] + \left[ \frac{-(1+h_{fe})}{\omega^2 C_1 C_2} \right] + \frac{L}{C_1} = 0$$

$$\underbrace{j h_{ie} \left[ \frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right]}_{\text{Imaginary part}} + \underbrace{\left[ \frac{1+h_{fe}}{\omega^2 C_1 C_2} \right] - \frac{L}{C_1}}_{\text{Real part}} = 0 \quad \text{Eqn(2)}$$

Imaginary part

Real part

Equating the Imaginary Part of Eqn(2)  
equal to zero, we get

$$h_{ie} \left[ \frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right] = 0$$

$$h_{ie} \neq 0 \quad \frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L = 0$$

$$\frac{1}{\omega C_1} + \frac{1}{\omega C_2} = \omega L$$

$$\frac{C_2 + C_1}{\omega C_1 C_2} = \omega L$$

$$\frac{C_2 + C_1}{L C_1 C_2} = \omega^2$$

$$\omega^2 = \frac{C_1 + C_2}{L C_1 C_2}$$

$$\omega^2 = \frac{1}{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}$$

$$\omega = \sqrt{\frac{1}{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

$$f = \frac{1}{2\pi \sqrt{\frac{1}{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}}$$

$\left[ \because \omega = 2\pi f \right]$

③

Condition for Sustained Oscillation :-

It can be obtained by equating the coefficient of Real part of Eqn ② equal to zero, we get

$$\frac{1 + h_{fe}}{\omega^2 C_1 C_2} - \frac{L}{C_1} = 0$$

$$\frac{1 + h_{fe}}{\omega^2 C_1 C_2} = \frac{L}{C_1}$$

$$1 + h_{fe} = \omega^2 L C_2$$

But  $\omega^2 = \frac{1}{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)} = \frac{C_1 + C_2}{L C_1 C_2}$

$$1 + h_{fe} = \frac{C_1 + C_2}{L C_1 C_2} \times \cancel{L C_2}$$

$$1 + h_{fe} = \frac{C_1 + C_2}{C_1}$$

$$= \cancel{\frac{C_1}{C_1}} + \frac{C_2}{C_1}$$

$$1 + h_{fe} = 1 + \frac{C_2}{C_1}$$



$$h_{fe} = \frac{C_2}{C_1}$$

### Crystal Oscillator :-

→ A crystal oscillator is basically a tuned circuit using a piezoelectric crystal as a resonant tank circuit.

→ The crystal (usually - Quartz) has a great stability in holding constant at whatever frequency the crystal is originally cut to operate crystal oscillator are used whenever great stability is required.

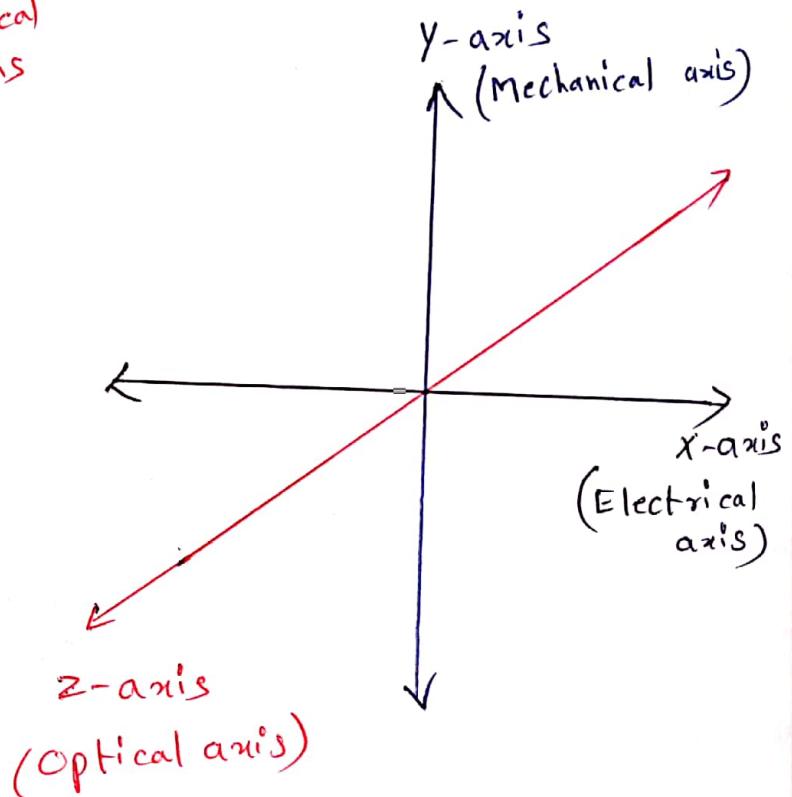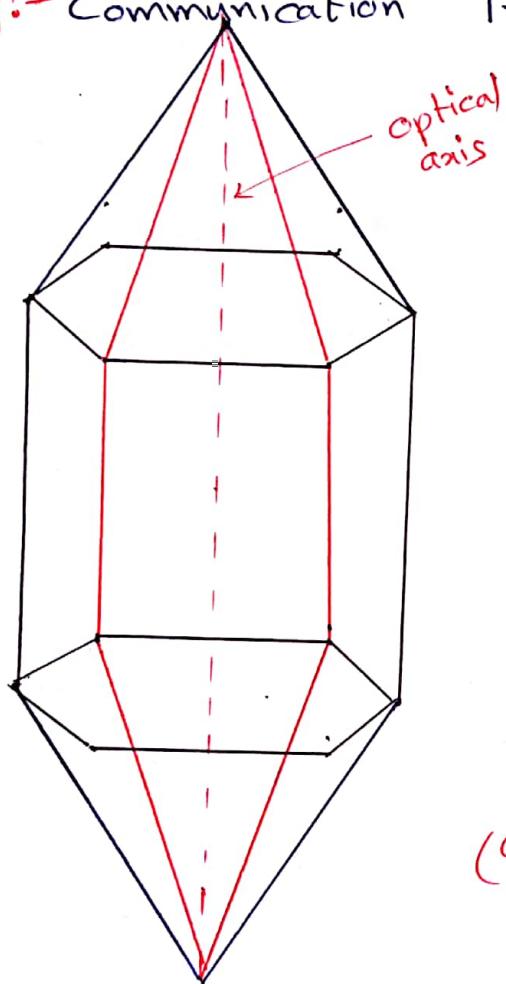Eg:- Communication Transmitter and Receivers.




Circuit of crystal :-

case(i): When the crystal is not Vibrating

→ It is equivalent to capacitance ( $C_m$ )

because it has two metal plates

separated by dielectric this capacitance

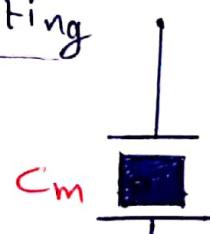


Fig(a). Crystal

is known as Mounting Capacitance ( $C_m$ ).

Case(ii): When the crystal  
is vibrating:

It is equivalent to  
R-L-C Series ckt. Therefore,  
the Equivalent ckt of a  
vibrating crystal is  
R-L-C series ckt

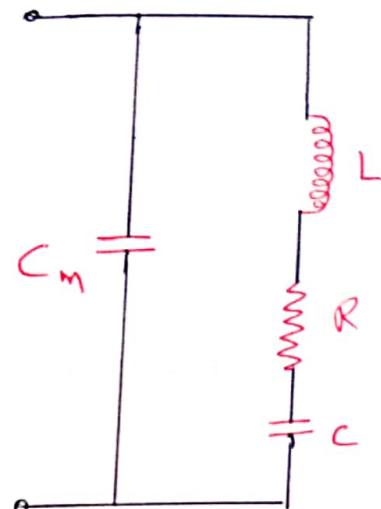shunted by the mounting capacitance ( $C_m$ ).



Fig(b). Equivalent ckt

Two Types of Frequency:-

① Series Resonant Frequency ( $f_s$ ):

$$X_L + X_C = 0$$

$$j\omega L + \frac{1}{j\omega C} = 0$$

$$j\omega L - \frac{j}{\omega C} = 0 \quad \left[ \because \frac{1}{j} = -j \right]$$

$$\cancel{j}\omega L = \frac{\cancel{j}}{\omega C}$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}} \quad [\because \omega = 2\pi f]$$

## ② Parallel Resonant frequency ( $f_p$ ) :-

$$X_L + X_C + X_{cm} = 0$$

$$X_L + X_C = -X_{cm}$$

$$j\omega L + \frac{1}{j\omega C} = \frac{-1}{j\omega C_m}$$

$$j\omega L - \frac{j}{\omega C} = \frac{j}{\omega C_m}$$

$$\cancel{j}\left(\omega L - \frac{1}{\omega C}\right) = \frac{\cancel{j}}{\omega C_m}$$

$$\omega L - \frac{1}{\omega C} = \frac{1}{\omega C_m}$$

$$\omega L = \frac{1}{\omega C} + \frac{1}{\omega C_m}$$

$$= \frac{1}{\omega} \left[ \frac{1}{C} + \frac{1}{C_m} \right]$$

$$\omega_L = \frac{1}{\sqrt{\omega}} \left[ \frac{C + C_m}{CC_m} \right]$$

$$\omega^2 L = \frac{C + C_m}{CC_m}$$

$$\omega^2 = \frac{C + C_m}{LCC_m}$$


$$\omega = \sqrt{\frac{C + C_m}{LCC_m}}$$

$$f_p = \frac{1}{2\pi} \sqrt{\frac{C + C_m}{LCC_m}}$$

(or)

$$f_p = \frac{1}{2\pi} \sqrt{\frac{LCC_m}{C + C_m}}$$

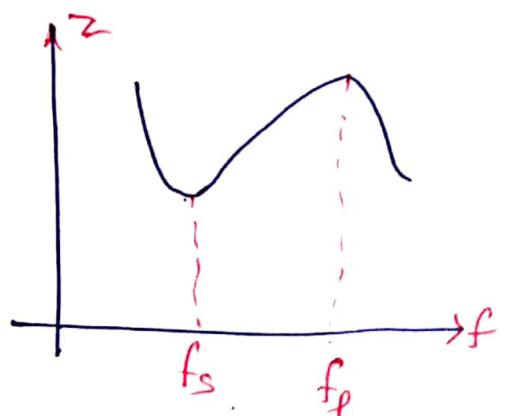→ At this frequency  
 Crystal offers a very  
 high impedance to  
 external circuit.



## Advantages :-

- ① They have a high order of frequency stability.
- ② The Quality factor ( $Q$ ) of the crystal is very high.

## Disadvantages :-

- ① They are easily damaged & consequently can only be used in low power circuits.
- ② The Frequency of oscillations can't be changed.

## Stability of oscillations :- Two types

① Frequency stability

② Amplitude stability

### ① Frequency stability :-

The freq. stability of an oscillator is a measure of its ability

to maintain the required freq as indicating exactness as possible over as long time interval.

→ The following are the factors, which contribute to the change in freq. stability

(i) change in Operating Point → due to Temp.

(ii) Variation in Temperature →  $R, L, C$  are Temp.-depend.

(iii) Due to Power Supply → Supply is Poor


(iv) Change in op. load.

## ② Amplitude stability:-

$A \rightarrow$  Amplifier

Transfer gain

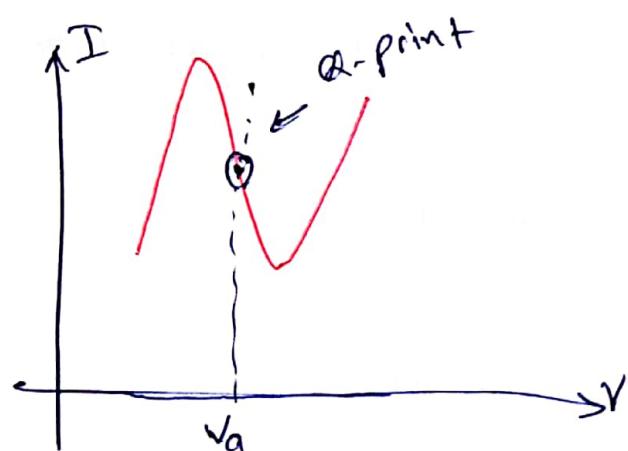$B \rightarrow$  Feedback  
network factor



At oscillator frequency,

If  $|AB| = 1$ , The feedback signal connected to i/p terminals, the removal of the external

generator will make no difference.

If  $|AB| < 1$ ,

The removal of the external generator will result in a stopping of oscillations.

If  $|AB| > 1$ ,

The amplitude of the oscillations will continue to increase without limit.

## UNIT - IV

### Large Signal Amplifiers

#### Concept of Large Signal Amplification:-

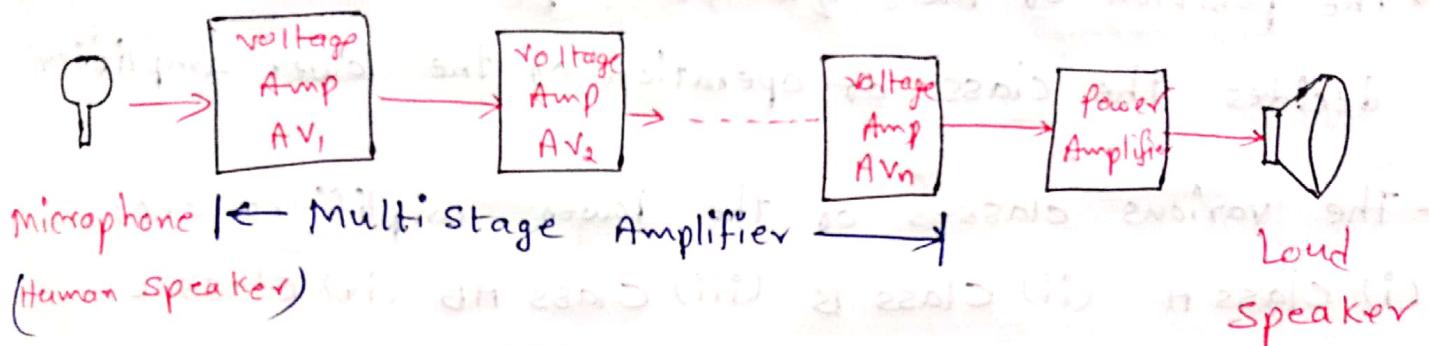


Fig. Block Diagram of Public Address System

The main aim is to develop





sufficient power hence the voltage gain is not important, in the last stage. Such a stage, which develops and feeds sufficient power to the load handling the large signals is called "Large Signal Amplifier" (or) "Power Amplifier".

#### Applications :-

- ① Public Address system
- ② Radio Receivers
- ③ Tape Players
- ④ Driving Servometer in industrial Control System.
- ⑤ T.V. Receivers
- ⑥ Cathode Ray Tubes (CRT's)

## Classification of Large Signal Amplifiers :-


- For an amplifier, a quiescent operating point ( $\alpha$ -Point) is fixed by selecting the proper d.c. biasing to the transistors used.
- The position of the quiescent point on the load line decides the class of operation of the Power amplifier.
- The various classes of the Power amplifiers are:
  - (i) Class A    (ii) Class B    (iii) Class AB    (iv) Class C.

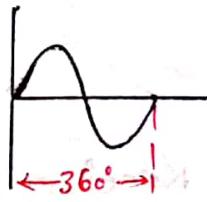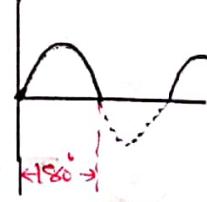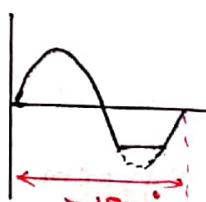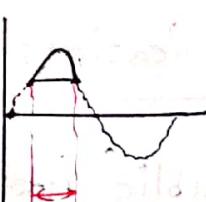SN	Class	A	B	AB	C
①	Operating cycle	$360^\circ$	$180^\circ$	$180^\circ$ to $360^\circ$	Less than $180^\circ$
②	Position of $\alpha$ -point on load line	Centre of load line	Above x-axis but below the centre of load line	Above x-axis but below the centre of load line	Below x-axis
③	Efficiency	Poor (25% to 50%)	Better (78.5%)	Higher than A but less than B (50 to 78.5%)	High
④	Nature of o/p current wave form				
⑤	Distortion	Absent No distortion	Present More than class A	Present	Highest
⑥	Power dissipation in Tr's	very high	Low	Moderate	Very low

## Class - A Large Signal Amplifiers :- It is two types

- ① Series-fed (or) Directly coupled class A Power Amp
- ② Transformer - Coupled class A power amplifiers.
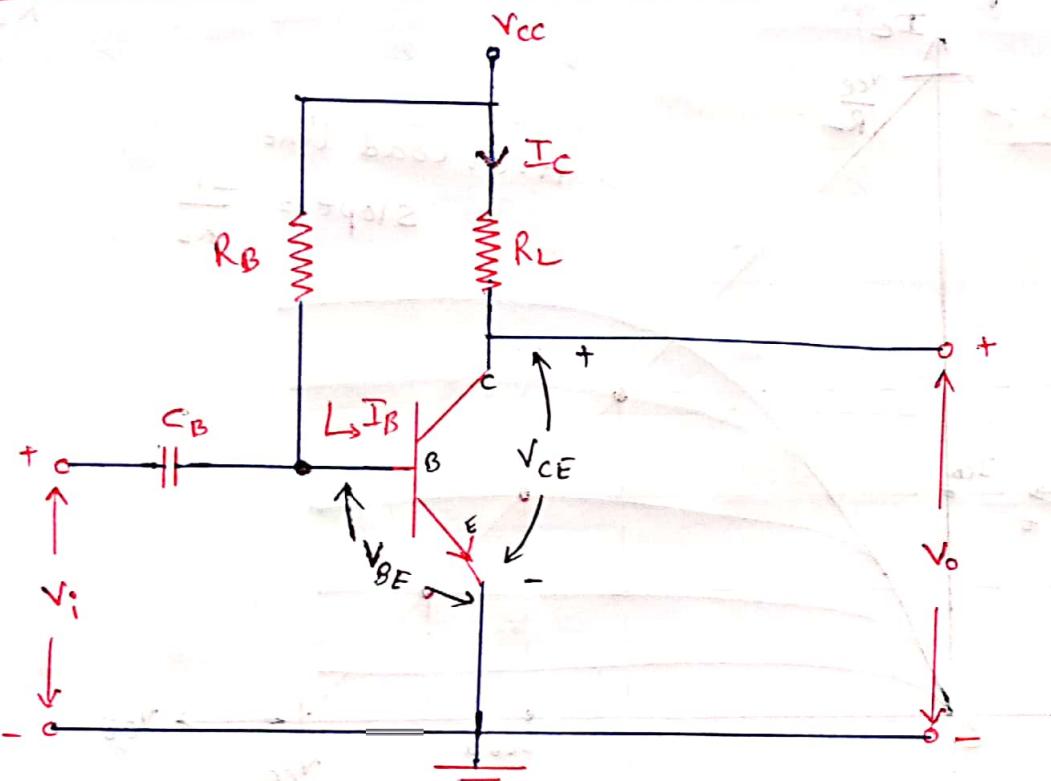
### ① Series-fed (or) Directly coupled class A Power Amp:-



#### D.C. Analysis :-

Applying KVL to the collector-emitter ckt, we have

$$V_{cc} = I_c R_L + V_{ce}$$

$$I_c R_L = V_{cc} - V_{ce}$$

$$I_c = \frac{V_{cc} - V_{ce}}{R_L}$$

$$= \frac{V_{cc}}{R_L} - \frac{V_{ce}}{R_L}$$

$$= -\frac{V_{ce}}{R_L} + \frac{V_{cc}}{R_L}$$

$$= \frac{-V_{CE}}{R_L} + \frac{V_{CC}}{R_L}$$

$$\therefore I_C = \left[ -\frac{1}{R_L} \right] V_{CE} + \frac{V_{CC}}{R_L}$$

The slope of the D.C. load line is  $\left[ -\frac{1}{R_L} \right]$  and the intercept on the current axis is  $\frac{V_{CC}}{R_L}$ .

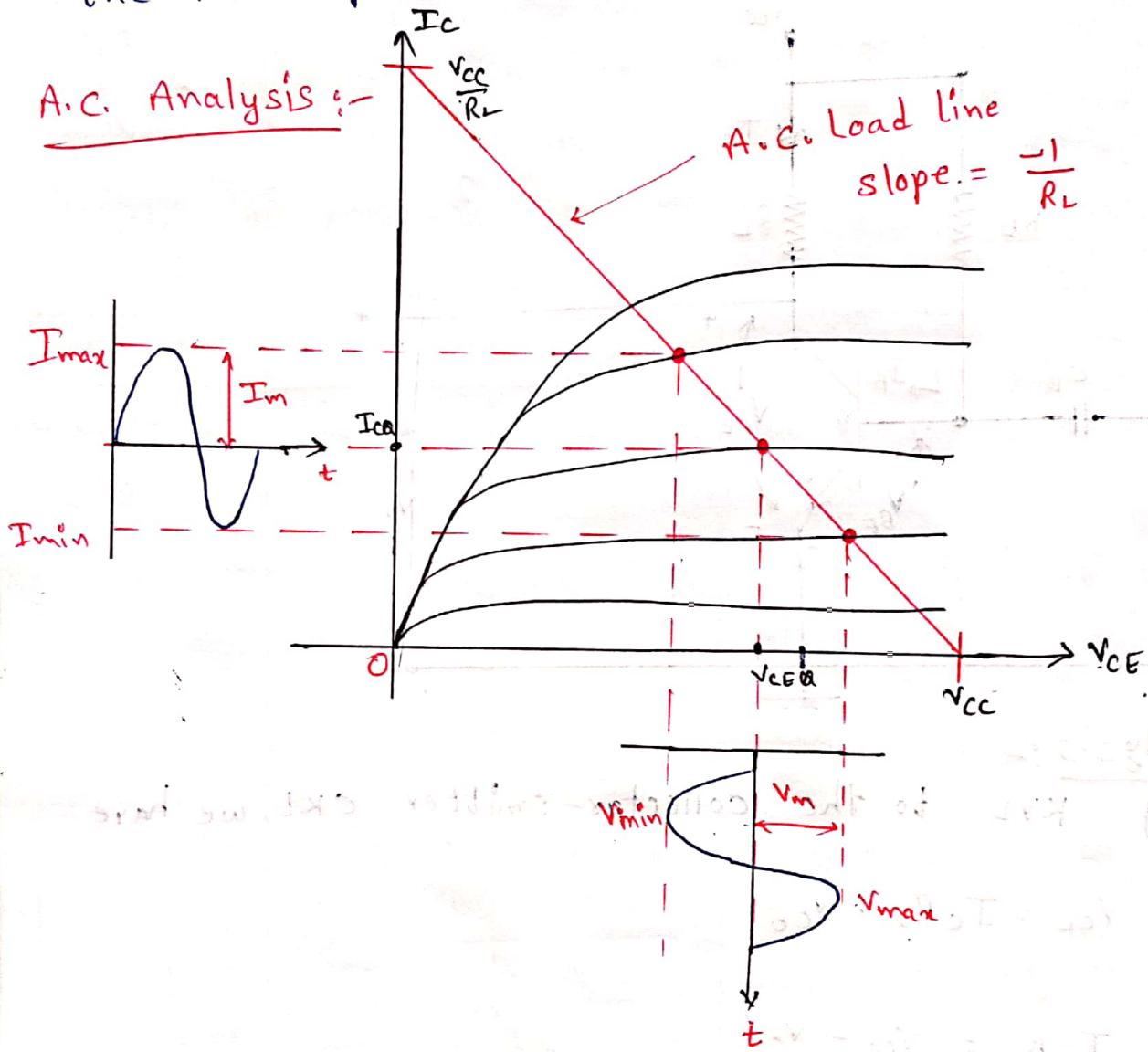


Fig. o/p voltage & current of the Series-Fed  
class A Power Amplifier

0 and  $\frac{V_{CC}}{R_L}$  for Output Current

0 and  $V_{CE}$  for " Voltage

$$\text{D.C. Power Input, } P_{in(DC)} = V_{cc} \cdot I_{cQ} \quad \text{--- (1)}$$

$$\text{A.C. Power Output, } P_{out(A-C)} = V_{rms} \cdot I_{rms} \quad \text{--- (2)}$$

$$\text{But } V_{rms} = \frac{V_m}{\sqrt{2}}, \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P_{out(A-C)} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$\therefore P_{out(A-C)} = \frac{V_m \cdot I_m}{2} \quad \text{--- (3)}$$

From Fig.,

$$V_{max} - V_{min} = 2V_m$$

$$V_m = \frac{V_{max} - V_{min}}{2}$$

$$\text{Hence } I_m = \frac{I_{max} - I_{min}}{2}$$

Substituting  $V_m$  &  $I_m$  values in eqn (3), we get

$$P_{out(A-C)} = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{2}$$

$$P_{out(A-C)} = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8} \quad \text{--- (4)}$$

Efficiency :-

$$\eta = \frac{\text{A.C. Power Delivered to the Load } P_{out(A-C)}}{\text{Total Power Drawn from D.C. supply } P_{in(DC)}}$$

$$\% \eta = \frac{P_{out}(A.C)}{P_{in}(D.C.)} \times 100 \quad \text{--- (5)}$$

Substituting eqn's (1) & (4) in eqn (5), we get

$$\% \eta = \frac{\frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8} \times 100}{V_{cc} \cdot I_{ca}} \quad \text{--- (6)}$$

$$\% \eta = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8 V_{cc} \cdot I_{ca}} \times 100 \quad \text{--- (6)}$$

### Maximum Power and Efficiency

$$V_{max} = V_{CEC}(\text{peak-to-peak}) = V_{cc}, \quad V_{min} = 0 \quad \text{--- (7)}$$

$$I_{max} = I_{CEC}(\text{peak-to-peak}) = \frac{V_{cc}}{R_L}, \quad I_{min} = 0$$

$$\begin{aligned} P_{out}(A.C.),_{\max} &= \frac{1}{8} \cdot V_{cc} \cdot \frac{V_{cc}}{R_L} = \\ &= \frac{V_{cc}^2}{8 R_L} \quad \left[ \text{from eqn (4)} \right] \end{aligned} \quad \text{--- (8)}$$

$$\begin{aligned} P_{in}(D.C.),_{\max} &= \frac{V_{cc} \cdot I_{ca}}{2} \\ &= \frac{V_{cc} \times V_{cc}/R_L}{2} \quad \left[ \because I_{ca} = \frac{V_{cc}}{R_L} \right] \end{aligned}$$

$$= \frac{V_{cc}^2}{2 R_L} \quad \text{--- (9)}$$

substituting eqn's ⑧ & ⑨ in ⑤, we get

$$\% \eta_{\max} = \frac{P_{\text{out(A.C.)}, \max}}{P_{\text{in(A.C.)}, \max}} \times 100 = \frac{\frac{V_{CC}^2 / 8 R_E}{4}}{\frac{V_{CC}^2 / 2 R_E}{4}} \times 100 = \frac{1}{4} \times 100$$

$$\boxed{\% \eta_{\max} = 25\%}$$

### maximum Efficiency of Class A Power Amplifier.

Note:- Power Dissipation:- D.C. power dissipation without

a.c. P/p signal is the maximum power dissipation.

$$P_{DQ(\max)} = V_{CC} \cdot I_{CQ}$$

### Advantages:

- ① The circuit is simple to design and to implement.
- ② The load is connected directly in the Collector circuit hence the o/p transformer is not necessary.  
This makes the circuit cheaper.
- ③ Less no. of components required as load is directly coupled.
- ④ No coupling element is required.

## Disadvantages :-

- ① The load resistance is directly connected in collector and carries the quiescent collector current. This causes considerable wastage of power.
- ② Power dissipation is more. Hence power dissipation arrangements like heat sink are essential.
- ③ The efficiency is very poor, due to large dissipation.

## ② Transformer - Coupled Class A Power Amplifier:-

→ One of the serious drawback of Series-fed Power amplifier was impedance mismatch.  
 → To overcome this problem, we go for "Transformer Coupled class A power amplifier".

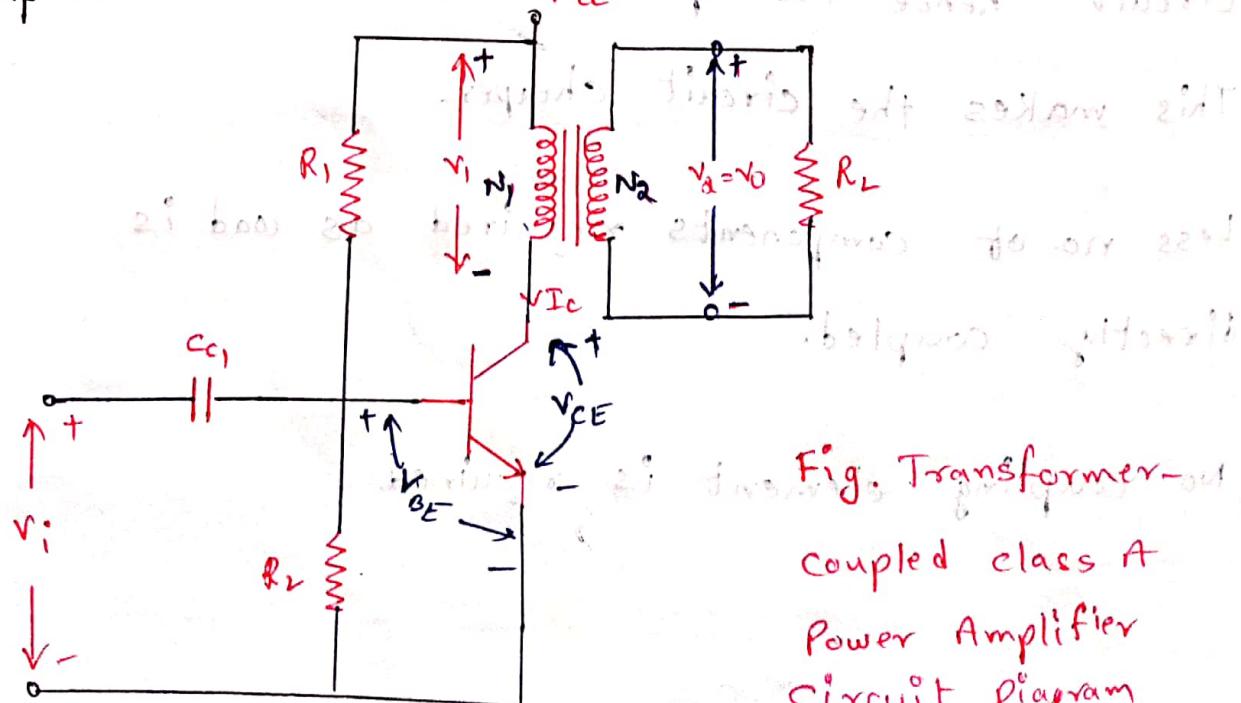


Fig. Transformer-coupled class A Power Amplifier Circuit Diagram

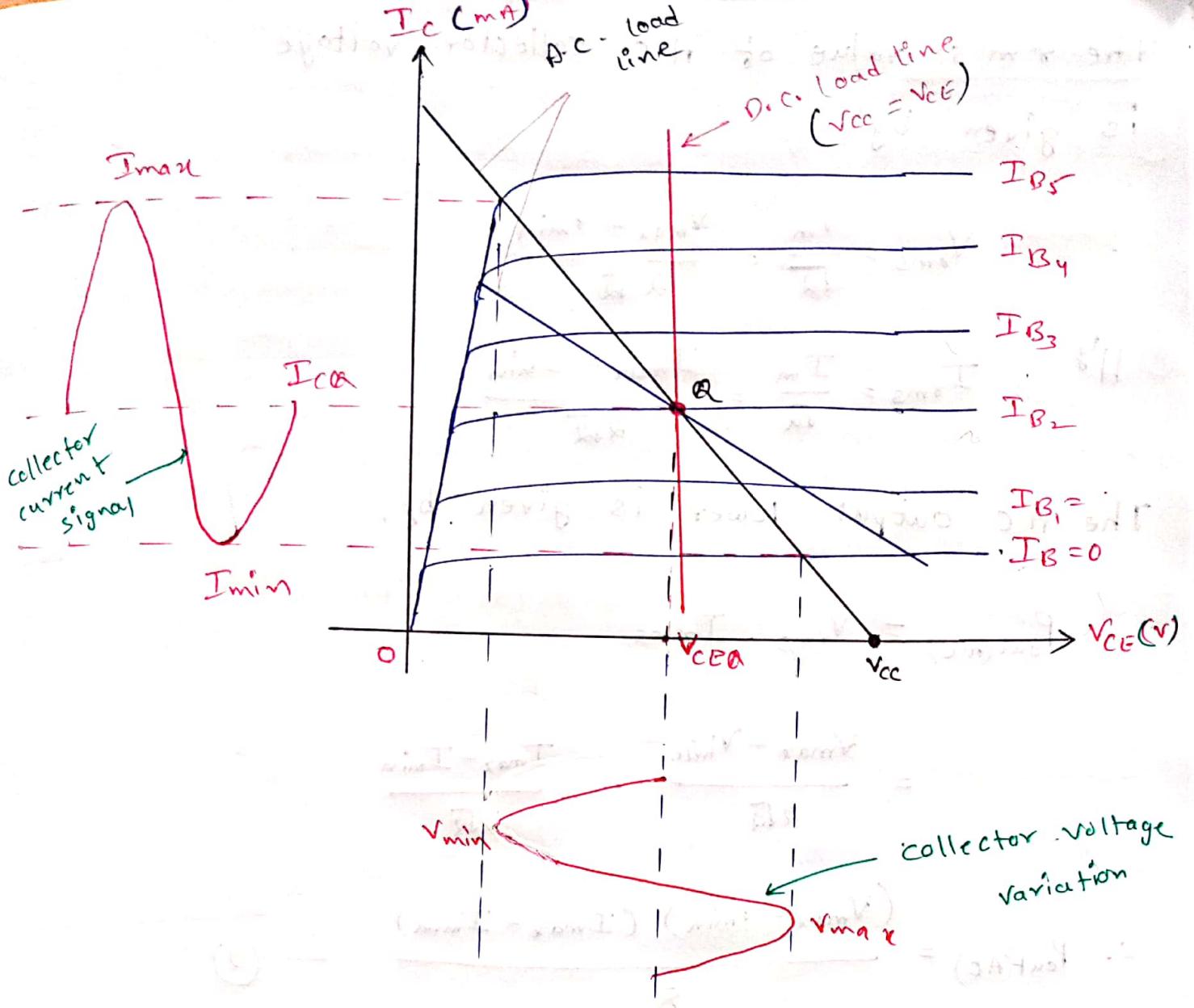


Fig. Collector characteristics of a Power Amplifier

Maximum Efficiency :- %  $\eta = \frac{P_{out(A-C)}}{P_{in(D-C)}} \times 100$  ————— (1)

From Fig. the maximum value of sine wave output voltage is,

$$V_m = \frac{V_{max} - V_{min}}{2} \quad \text{and} \quad I_c = I_{CQ}$$

The r.m.s. value of A.C. collector voltage is given by,

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{V_{max} - V_{min}}{2\sqrt{2}}$$

11'8

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{I_{max} - I_{min}}{2\sqrt{2}}$$

The A.C. output Power is given by,

$$P_{out(A.C)} = V_{rms} \cdot I_{rms}$$

$$= \frac{V_{max} - V_{min}}{2\sqrt{2}} \cdot \frac{I_{max} - I_{min}}{2\sqrt{2}}$$

$$\therefore P_{out(A.C)} = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8}$$
(2)

The Power supplied to the circuit is given by,

$$P_{in(A.C)} = V_{cc} \cdot I_{cc}$$
(3)

Substituting eqn's (2) & (3) in (1), we get

$$\% \gamma = \frac{P_{out(A.C)}}{P_{in(A.C)}} \times 100$$

$$= \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{V_{cc} \cdot I_{cc}} \times 100$$

$$\% \eta = \frac{(\text{V}_{\text{max}} - \text{V}_{\text{min}})(\text{I}_{\text{max}} - \text{I}_{\text{min}})}{8 \text{ V}_{\text{cc}} \text{ I}_{\text{ca}}} \times 100 \quad \text{(4)}$$

The maximum Efficiency will be obtained,

when  $\text{V}_{\text{min}}=0$ ,  $\text{I}_{\text{min}}=0$ ,  $\text{V}_{\text{max}}=2\text{V}_{\text{cc}}$  and

$\text{I}_{\text{max}}=2 \text{ I}_{\text{ca}}$  substituting these values

in eqn (4), we get

$$\% \eta = \frac{(2\text{V}_{\text{cc}} - 0)(2\text{I}_{\text{ca}} - 0)}{8 \text{ V}_{\text{cc}} \text{ I}_{\text{ca}}} \times 100$$

$$= \frac{2\text{V}_{\text{cc}} \times 2\text{I}_{\text{ca}}}{8 \text{ V}_{\text{cc}} \cdot \text{I}_{\text{ca}}} \times 100 \quad 50$$

$$\boxed{\% \eta = 50 \%}$$

Maximum Efficiency of Transformer Coupled class A power amplifier

Note:- Power Dissipation,

$$P_D = \text{V}_{\text{CEA}} \cdot \text{I}_C$$

## Advantages:-

- ① It provides increased efficiency over the series fed (or) Directly coupled class A P.A.
- ② The transformer coupled amplifier is easily converted in to a type of amplifier that is used extensively in communications.
- ③ It provides a higher voltage gain.

## Disadvantages :-

- ① Harmonic distortion is high.
- ② As load resistance is connected directly in the output circuit of the power stage, the power is wasted.
- ③ Frequency response is poor and it is expensive.

# Comparision of Series-fed and Transformer

(14)

## Coupled class-A Amplifier :-

<u>Series - Fed</u>	<u>Transformer Coupled</u>
① The series-fed class-A amplifier, there is no transformer.	① Transformer is used in the circuit of transformer coupled class-A amplifier.
② Maximum efficiency is 25%.	② Maximum efficiency is 50%.
③ There is a D.C. Power drop across $R_L$ .	③ D.c. drop across the primary of the transformer is negligible
④ simple to design & implement.	④ Complicated to design.
⑤ The o/p impedance is high hence can not be used for low impedance.	⑤ Low impedance matching is possible due to transformer.
⑥ Load resistance carries the $I_{CQ}$ hence considerable wastage of power.	⑥ The $I_{CQ}$ flows through primary of transformer which has zero d.c. resistance. Hence power wastage is small.
⑦ Less no. of components are required.	⑦ More no. of components required
⑧ The circuit is not heavier, bulkier and costlier.	⑧ The transformer makes the circuit heavier, bulkier and costlier.
⑨ The freq. response is better.	⑨ The freq. response is poor.

### III Class-B Power Amplifier :-

class-B large signal amplifiers, the Q-point is located on cut-off point (on X-axis). Hence, the transistor conducts current for only one-half of the signal cycle.

→ To obtain output for full cycle of signal, it is necessary to use two transistors. and each conducts on opposite half of the cycles, the combined operation provides full cycle of output signal.

→ since one part of the circuit pushes the signal high during one half-cycle and the other part pulls the signal low during the other half-cycle.

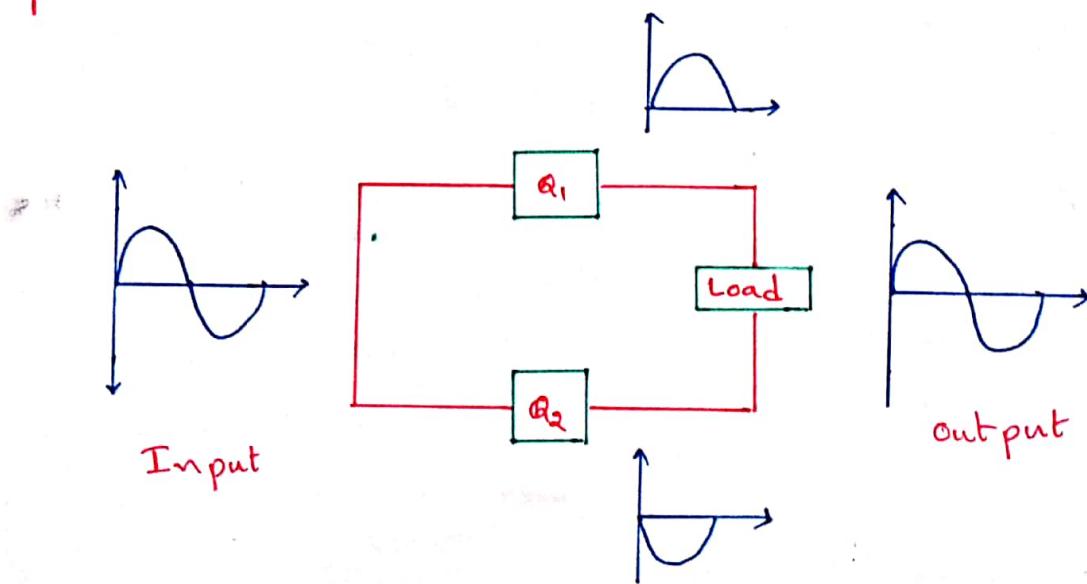


Fig.11. Basic Operation Diagram (Push Pull operation)

(15)

An A.C. input signal is applied to the push-pull circuit, with each half operating on alternate half cycle, the load then receive a signal for the full A.C. cycle.

→ The power transistor used in the push-pull circuit are capable of delivering the desired power to the load and the class-B operation of these transistors provides greater efficiency than was possible using a single transistor in class-A operation.

→ Depending on the types of two transistor configuration used, there are two configurations of class-B amplifier (i.e., NPN (or) PNP) are available as follows,

### When both Transistors

① Same Type

i.e., NPN (or) PNP

### Amplifier Name

"Push-Pull" class-B Power Amplifier.


② Different Type

i.e., PNP & NPN (or) NPN & PNP

### "Complementary Symmetry"

class-B Power Amplifier.

# ① Push Pull Class-B Power Amplifier:-

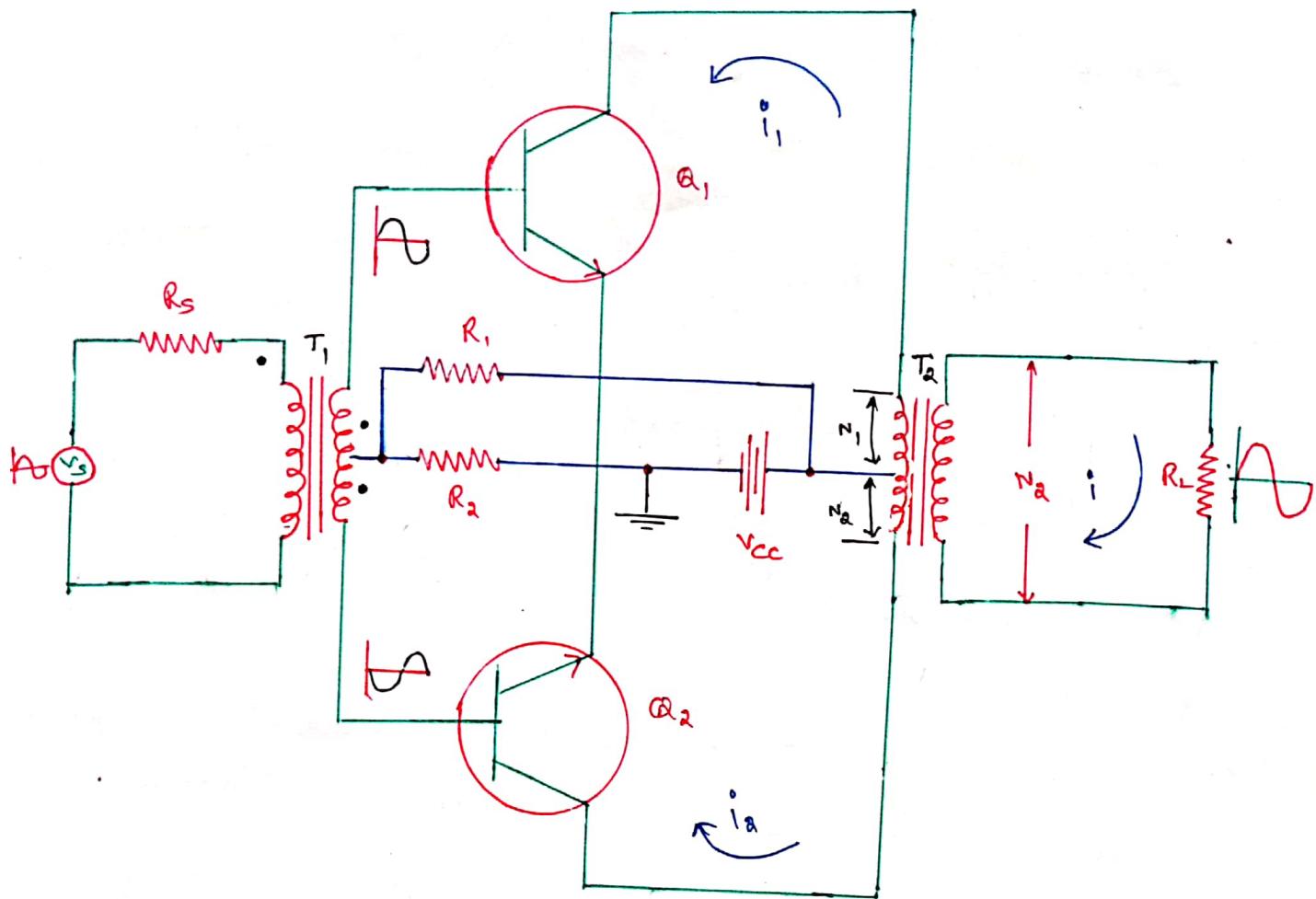

Phase - splitting  
Input Transformer

Push-Pull ckt  
connection

Push-Pull  
o/p Transformer

Load

Fig. 12. Transformer - Coupled class-B Push-Pull Amplifier

Amp (ifier)

(16)

The circuit consists of two center tapped transformers  $T_1$  and  $T_2$  and two identical transistors  $Q_1$  and  $Q_2$ .

→ The input transformer is also known as phase splitter, which provides opposite polarity signals to the inputs of transistors  $Q_1$  and  $Q_2$ . The output transformer  $T_2$  couples the A.C. output signal to the load from collector.

### Power Relations:-

The A.C. output power in a class-B amplifier is developed only during one-half cycle of the input signal.

The effective load resistance is given by,

$$R_L' = \left[ \frac{N_1}{N_2} \right]^2 R_L$$

### i) D.C. Power Input :-

The D.C. power is given by

$$P_i = 2 I_{D.C.} V_{cc}$$

→ indicate Two transistors used since,

$$I_{D.C.} = \frac{I_m}{\pi}, \quad P_i = \frac{2 I_m V_{cc}}{\pi}$$

### (ii) A.C. Power Output :-

The output of transistor  $Q_2$  is a series of sine loop pulses that are  $180^\circ$  out of phase with those of transistor  $Q_1$ .

→ The load current, which is proportional to the difference between the two collector currents, is therefore a perfect sine wave.

→ The output power is given by,

$$P_o = \frac{V_m I_m}{2} = \frac{I_m}{2} (V_{cc} - V_{min})$$

$$\therefore V_m = V_{cc} - V_{min}$$

### (iii) Power Dissipation :-

The power dissipation  $P_D$  in both transistors is the difference between the A.C. power output and D.C. power input.

$$P_D = P_{D.C.} - P_{A.C.}$$

$$= \frac{2 V_{cc} I_m}{\pi} - \frac{V_m I_m}{2}$$

$$P_D = \frac{2 V_{cc} V_m}{\pi R_L'} - \frac{V_m^2}{2 R_L'} \quad \left[ \because I_m = \frac{V_m}{R_L'} \right]$$

— ①

This equation shows that the collector dissipation (17) is zero under at two conditions,

1) When no signal is used ( $v_m = 0$ )

$$2) \text{When } \frac{2}{\pi} v_{cc} \frac{v_m}{R_L'} = \frac{v_m^2}{2 R_L'}$$

**Maximum Power Dissipation:**

The condition for maximum power dissipation can be found by differentiating Eqn ① w.r.t  $v_m$  and equating to zero.

$$\frac{d P_D}{d v_m} = \frac{d}{d v_m} \left[ \frac{2 v_{cc} \cdot v_m}{\pi R_L'} - \frac{v_m^2}{2 R_L'} \right] = 0$$

$$\frac{2 v_{cc}}{\pi R_L'} \frac{d}{d v_m} (v_m) - \frac{1}{2 R_L'} \frac{d}{d v_m} (v_m^2) = 0$$

$$\frac{2 v_{cc}}{\pi R_L'} - \frac{2 v_m}{2 R_L'} = 0$$

$$\frac{v_m}{R_L'} = \frac{2 v_{cc}}{\pi R_L'}$$

$$v_m = \frac{2}{\pi} \cdot v_{cc} \quad \text{--- (2)}$$

Substituting Eqn (2) in Eqn ①, we get

$$P_{D,\max} = \frac{2}{\pi} \frac{v_{cc}}{R_L'} \left( \frac{2}{\pi} v_{cc} \right) - \left( \frac{2}{\pi} v_{cc} \right)^2 \times \frac{1}{2 R_L'}$$

$$= \frac{4V_{cc}^2}{\pi^2 R_L'} - \frac{2V_{cc}^2}{\pi^2 R_L'}$$

$$P_{o,\max} = \frac{2}{\pi^2} \frac{V_{cc}^2}{R_L'} \quad \text{--- (3)}$$

For maximum efficiency,  $V_m = V_{cc}$ , hence the power dissipation is not maximum when the efficiency is maximum.

→ Maximum output A.c. Power is

$$P_{o,\max} = \frac{V_m^2}{2R_L'}$$

when,  $V_m = V_{cc}$

$$\therefore P_{o,\max} = \frac{V_{cc}^2}{2R_L'} \quad \text{--- (4)}$$

Using eqns ④ & ③ can be written as

$$P_{o,\max} = \frac{4}{\pi^2} \left( \frac{V_{cc}^2}{2R_L'} \right)$$

$$P_{o,\max} = \frac{4}{\pi^2} P_{o,\max}$$

$$\therefore P_{o,\max} = 0.4 P_{o,\max}$$

→ The maximum power is dissipated by both the transistors and therefore the maximum power dissipation per  $T_r$  is  $\frac{P_{o,\max}}{2}$ .

$$\therefore P_{o,\max} \text{ per Transistor} = \frac{4}{\pi^2} \frac{P_{o,\max}}{2}$$

$$\frac{8}{\pi^2} P_{o,\max} = 0.2 P_{o,\max}$$

Example :- 10W maximum power is to be delivered from a class-B push-pull amplifier to the load, then power dissipation rating of each transistor should be  $0.2 \times 10W = 2W$ .

#### (iv) Conversion Efficiency :-

The conversion efficiency of an active device is its ability to convert the D.C. power supply to A.C. power supply.

$$\eta \% = \frac{\text{Signal Power Delivered to load}}{\text{D.C. Power Supplied to output circuit}} \times 100$$

$$\begin{aligned} \% \eta &= \frac{P_{o(A-C)}}{P_{in(D-C)}} = \frac{I_m (V_{cc} - V_{min})}{2 \times 2 \times \frac{I_m V_{cc}}{\pi}} \times 100 \\ &= \frac{\pi}{4} \left[ 1 - \frac{V_{min}}{V_{cc}} \right] \times 100 \end{aligned}$$

since,  $V_{min} \ll V_{cc}$

$$\% \eta = \frac{\pi}{4} \times 100 = 0.785 \times 100$$

$\% \eta = 78.5 \%$

## Advantages :-

- ① The efficiency is much higher than class-A operation.
- ② If the input signal is absent, there is no power dissipation.
- ③ Due to push-pull connection all even harmonics are cancelled. thus, it reduces the harmonic distortion.
- ④ Due to the transformer, it provides impedance matching.
- ⑤ Due to the centre tapped transformer being used, ripple present due to the supply eliminated.

## Disadvantages :-

- ① Two centre tapped transformers are needed.
- ② The transformers make the circuit bulky and costly.
- ③ Frequency response is poor.
- ④ Supply voltage  $V_{cc}$  should have good regulation. since, if  $V_{cc}$  changes the Q-point changes. Therefore, transistor may not be at cut-off.

## ② Complementary - Symmetry Class-B Push-Pull Amplifier

- The standard class-B push-pull amplifier requires a centre tapped transformer, as only one transistor will conduct for  $180^\circ$ . So, if two transistors were to be conducted for complete  $360^\circ$ , there should be centre tapped transformer (or) there should be a phase inverter circuit.
- The need of centre tapped transformer (or) phase inverter circuit can be eliminated by the use of complementary symmetry circuit which needs only one phase.
- The complementary means the circuit uses two identical transistors, but one is NPN and the other is PNP.
- The symmetry means the biasing resistors connected in both transistors are equal. As a result of this emitter base junction of each transistors is biased with the same voltage.
- The main requirement of complementary symmetry circuit is a pair of closely matched transistors.
- Since, it is a class-B operation the Q-point is at cut-off i.e., emitter and base are shorted (or)  
 $V_{EB} = 0$ .

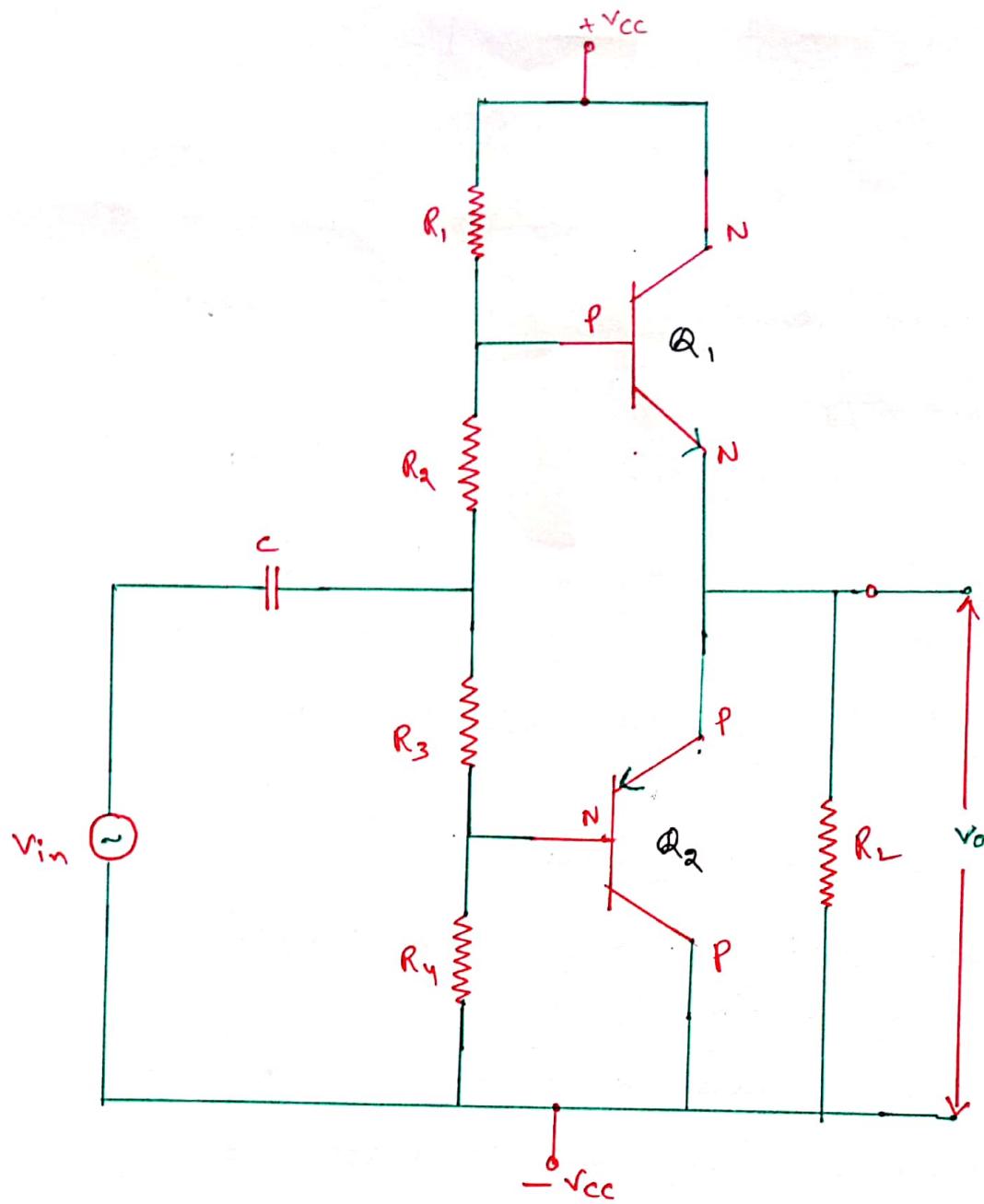


Fig.13. Complementary Symmetry Class - B

Power Amplifier

Circuit Operation :-

When the input signal is +ve i.e., during the positive half cycle of A.C. input the base to emitter voltage of both transistors becomes positive.

- (20)
- At this condition, only N-P-N transistor conducts, while the P-N-P transistor doesn't conduct. During this process, only positive half-cycle current flows through  $R_L$ .
  - During the negative half-cycle of A.C. input only the PNP transistor conducts N-P-N transistor is OFF and the negative half-cycle current flows through  $R_L$ .
  - Since, when the output is tapped across  $R_L$ , we get a complete amplified waveform of the input signal.
  - It may be noted that the amplifier circuit has a unity gain, because of the emitter follower configuration.
  - The use of split supply in the circuit gives us an advantage that the D.C. component of output voltage can be made to zero. Thus, only A.C. component of the power is available at the output, hence no need of coupling capacitor in the output.
  - As there is no D.C. current through  $R_L$ , hence an electromagnetic load such as a loud speaker can be connected directly without coupling capacitor.
  - The main disadvantage of this circuit is that they need to use two power supplies.

→ Secondly, the transistor will not conduct till the input signal magnitude exceeds the cut-in voltage

v<sub>i</sub>. Therefore, a type of distortion called crossover distortion will be present as

shown in Fig.14.

### Analysis:-

#### (i) Input DC Power:-

$$P_{idc} = P_{dc}(T_1 \text{ ON}) + P_{dc}(T_2 \text{ ON})$$

$$= \frac{V_{cc}}{2} I_1 + \frac{V_{cc}}{2} I_2$$

$$= \frac{V_{cc}}{2} (I_1 + I_2)$$

Let,  $I_1 = I_2 = \frac{I_m}{\pi}$  because the current flows only half cycle period.

$$\therefore P_{idc} = \frac{V_{cc}}{2} \left( \frac{I_m}{\pi} + \frac{I_m}{\pi} \right)$$

$$= \frac{V_{cc} I_m}{\pi}$$

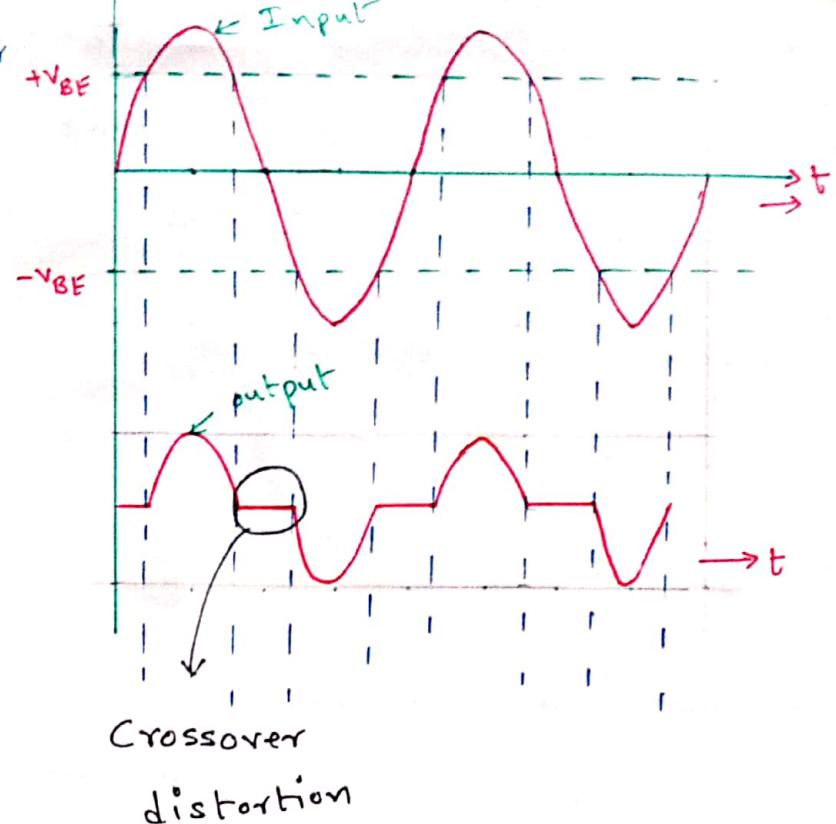


Fig.14. Crossover Distortion

(ii) Output AC Power :-

$$P_{oac} = V_{rms} I_{rms} (T_1 \text{ ON}) + V_{rms} I_{rms} (T_2 \text{ ON})$$

$$= I_{1rms}^2 R_L + I_{2rms}^2 R_L$$

we know,  $I_{1rms} = \frac{I_m}{\sqrt{2}}$

$$\begin{aligned} \therefore P_{oac} &= \frac{I_m^2}{2} R_L + \frac{I_m^2}{2} R_L \\ &= I_m^2 \cdot R_L = \frac{V_{cc}^2}{8 R_L} \end{aligned}$$

where,  $I_m = \frac{V_{cc}}{2 R_L}$

$$P_{idc} = \frac{V_{cc} I_m}{\pi} = \frac{V_{cc}^2}{2 \pi R_L}$$

(iii) Efficiency :-

$$\eta_o = \frac{P_{oac}}{P_{idc}}$$

$$\begin{aligned} &\frac{V_{cc}^2}{8 R_L} \\ &= \frac{V_{cc}^2}{2 \pi R_L} \end{aligned}$$

$$\% \eta = \frac{\pi}{4} \times 100$$

$$\boxed{\% \eta = 78.54 \%}$$

#### (iv) Power Dissipation :-

Power dissipated by the transistor (collector dissipation)

$$P_D = P_{Idc} - P_{oac}$$

$$= \frac{V_{cc}^2}{2\pi R_L} - \frac{V_{cc}^2}{8R_L}$$

$$= \frac{V_{cc}^2}{R_L} \left( \frac{1}{2\pi} - \frac{1}{8} \right)$$

$$P_D = \frac{0.034 V_{cc}^2}{R_L}$$

#### Advantages :-

- ① Due to absence of transformer, the weight, size and cost is less.
- ② Frequency response is good.
- ③ Due to common collector configuration, impedance matching is possible.

#### Disadvantages :-

- ① It produces the crossover distortion.
- ② Proper matching of transistors are required (which is difficult to get practically).

## Distortion in Power Amplifiers :-

The purpose of an amplifier is to boost up the voltage (or) power level of a signal. During this process the wave shape of the signal should not change. If the wave shape of the output is not an exact replica of the wave shape of the input, we say that distortion has been introduced by the amplifier.

→ An ideal amplifier will amplify a signal without changing its wave shape at all frequencies. Such an amplifier faithfully amplifies the signal and we say it has a good fidelity, such an amplifier is called **Hi-Fi** (High Fidelity) amplifier.

→ The change in the output waveform from the <sup>input</sup> waveform of an amplifier is known as "distortion."

### ① Harmonic Distortion :-

The distortion caused by the presence of frequencies that are not present in the input signal.

→ There are two types      ① Even-order  
                                  ② Odd-order

### Even - order

① If the frequencies of the distortion are 2, 4, 6, etc., times the fundamental frequency.

② These are caused by the

(i) Permanently magnetized magnetic head.

(ii) Faulty circuits.

(iii) Asymmetrical (or) Unbalanced bias signals.

### Odd- order

① If the frequencies of the distortion are 3, 5, 7, etc., times the fundamental frequency.

② These are caused by the magnetic tape itself.

## ② Cross over Distortion :-

(23)

This is caused by non-linearity of the input characteristic of the transistors.



Transistors do not turn on at zero volt applied to the emitter junction but only when the emitter junction is forward biased by the cut-in voltage  $V_T = 0.3V$  for Ge and  $0.7V$  for Si.

Elimination of cross over distortion :- By using class-AB

amplifier we can eliminate the crossover distortion.

In class-AB amplifier, we always maintain the base voltage equal to ' $V_T$ ', so that, when the input is applied to the transistor, it conducts instantly and reproduces the input signal without any crossover distortion.

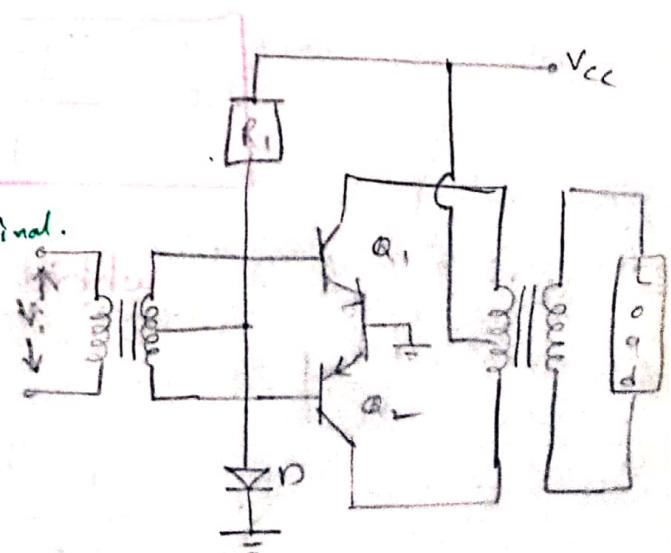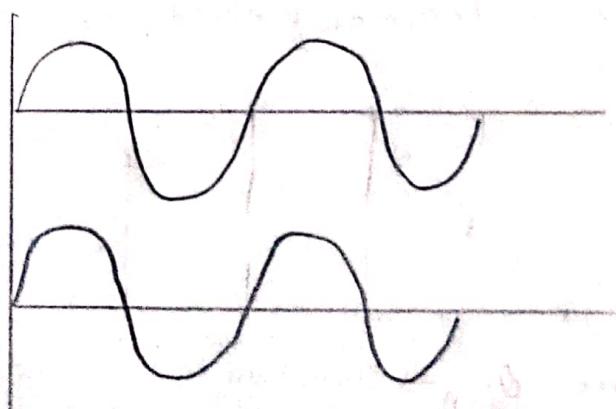→ To maintain the two transistors at  $V_T$ , we add/connect a diode between the base of the tr Q<sub>2</sub> & ground terminal.



A class-AB power amp.

## Thermal stability :-

Collector current,  $I_c = \beta I_o + (\beta + 1) I_{CBO}$

PN Junction,  $I_{o2} = I_{o1} \times 2^{\frac{(T_2 - T_1)}{10}}$

Let  $T_2 = T_1 + 10$

$T_2 - T_1 = 10$

$$I_{o2} = I_{o1} \times 2^{\frac{10}{10}}$$

$$= I_{o1} \cdot 2^1$$

$$\therefore I_{o2} = 2I_{o1}$$

∴ For every  $10^\circ\text{C}$  raise in Temp  $\Rightarrow$  current becomes double

$$T \uparrow I_{CBO} \uparrow I_c \uparrow P_d \uparrow \text{Jun Temp} \uparrow I_{CBO} \uparrow$$

**Conclusion:-** Collector current increases with increase Temperature.


→ If we maintain proper biasing & stability of transistor, then collector current should be in proper limit. The conditions satisfied then this concept we called thermal stability.

## Heat sinks:-


Heat sinks are relatively larger, usually black metallic conducting device and it is placed at the surface area.

→ Many type of heat sinks exist, depending upon the shape and size.


## Examples:-

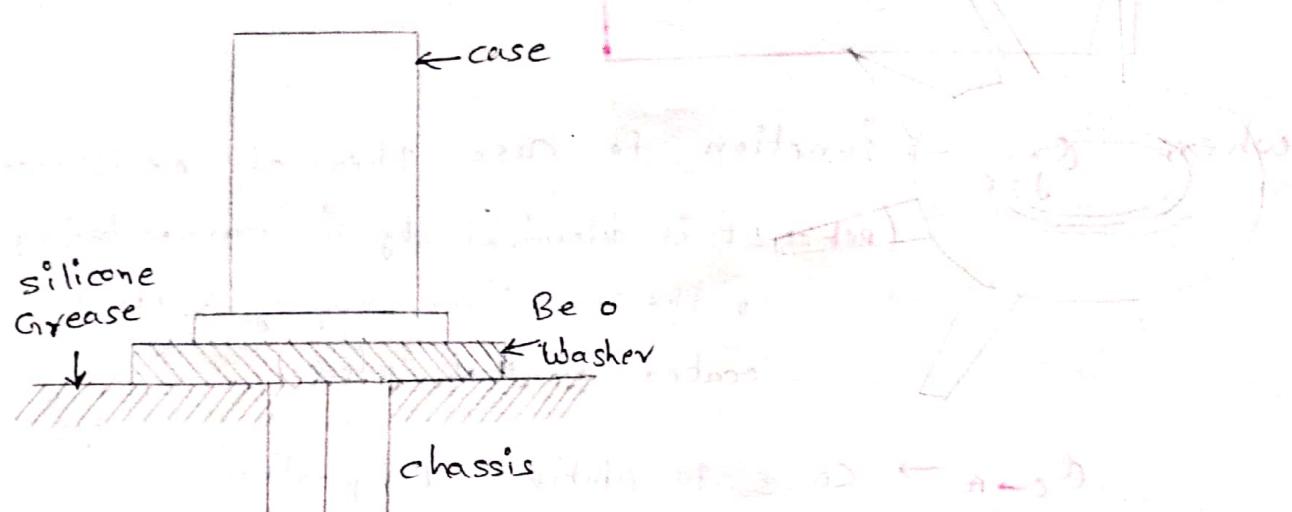

## Power transistor Heat sink

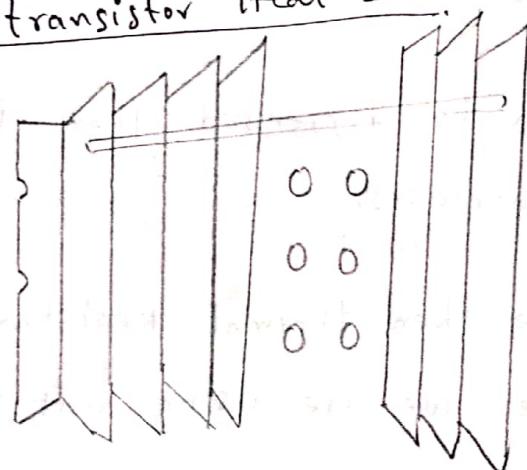

→ 24ms fast

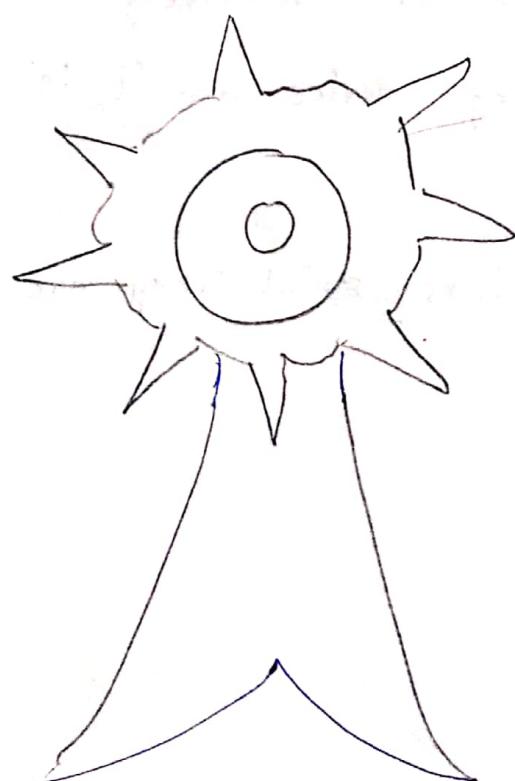

UNIT — ✓

## UNIT - I (Tuned Amplifier)





- ① Introduction
- ② Q-Factor
- ③ Small signal Tuned Amplifiers
- ④ Effect of cascading single Tuned Amplifiers on Bandwidth
- ⑤ " " "
- ⑥ Stagger Tuned
- ⑦ Stability



V - TMU

UNIT-ITuned Amplifiers3) Introduction :-

The amplifier with tuned circuit as a load is known as tuned amplifier. (or) narrow band amplifier.

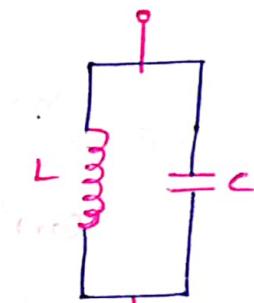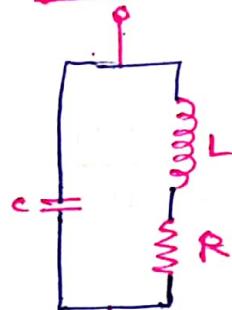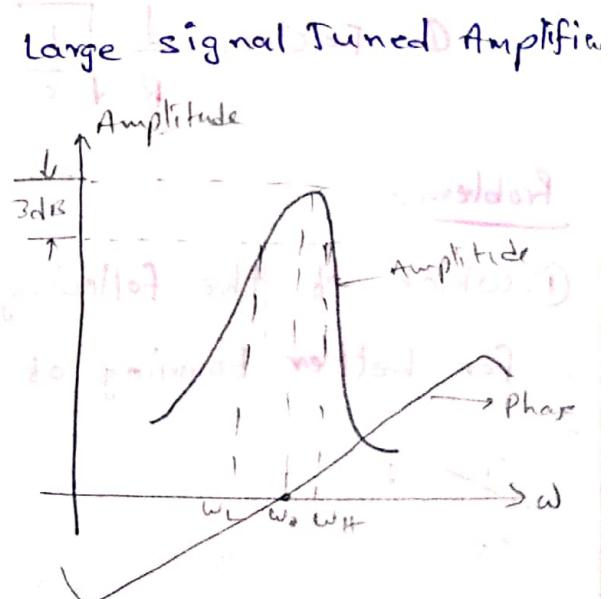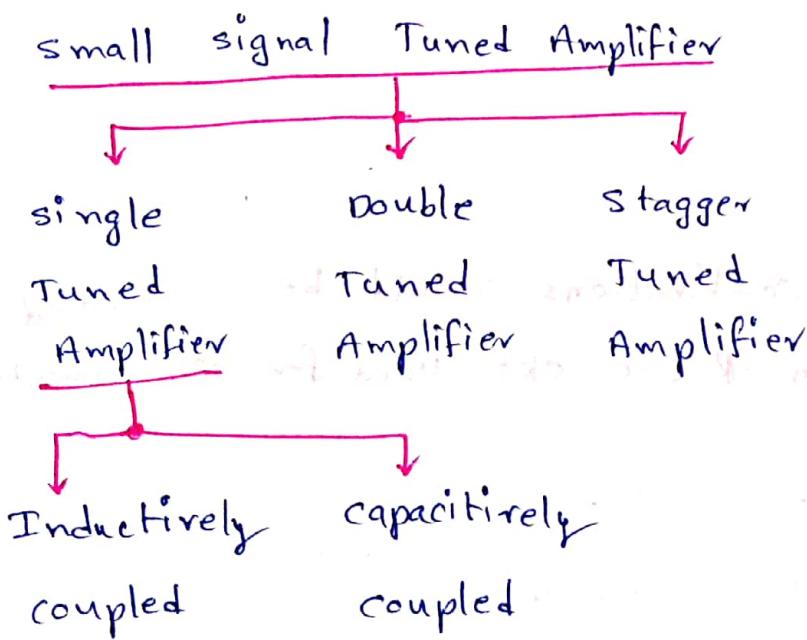Parallel Resonant cktClassification of Tuned Amplifiers :-Tuned cktTuned AmplifierFreq. Response forTuned ckt


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

II Q-Factor :- The characteristic of a series Resonant circuit is determined by the Quality Factor (Q-factor) of the circuit.

→ It defines the sharpness of I-V curves at resonance when Q-factor is large the sharpness of resonance current is more and vice-versa.

$$\hookrightarrow Q = 2\pi \times \frac{\text{Maximum Energy stored}}{\text{Energy dissipation}}$$


(or)

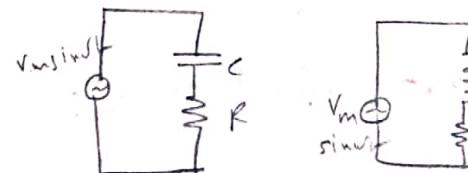

$$Q = \frac{\text{Resonant frequency}}{\text{Band Width}} = \frac{\omega_0}{\Delta\omega}$$

Q-Factor =  $\omega_0 CR$       Q-Factor =  $\frac{\omega_0 L}{R}$
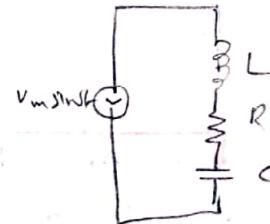
$$Q\text{-Factor} = \frac{V_L}{V_R} (\alpha) \frac{V_C}{V_R} (\alpha) \frac{\omega_0 L}{R} (\alpha) \frac{1}{\omega_0 CR}$$



$$Q\text{-Factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q\text{-Factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

### Problem :- (Gate Question)

① Which of the following combinations should be selected for better tuning of an R-L-C ckt used for communication.


(1)  $R = 20\Omega$ ,  $L = 1.5H$ ,  $C = 35\mu F$

Q value high

(2)  $R = 25\Omega$ ,  $L = 2.5H$ ,  $C = 45\mu F$


(3)  $R = 15\Omega$ ,  $L = 3.5H$ ,  $C = 30\mu F$

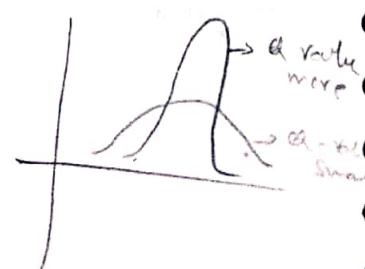(4)  $R = 25\Omega$ ,  $L = 1.5H$ ,  $C = 45\mu F$



Solt :-  $Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{15}$

### III Small signal Tuned Amplifier:-

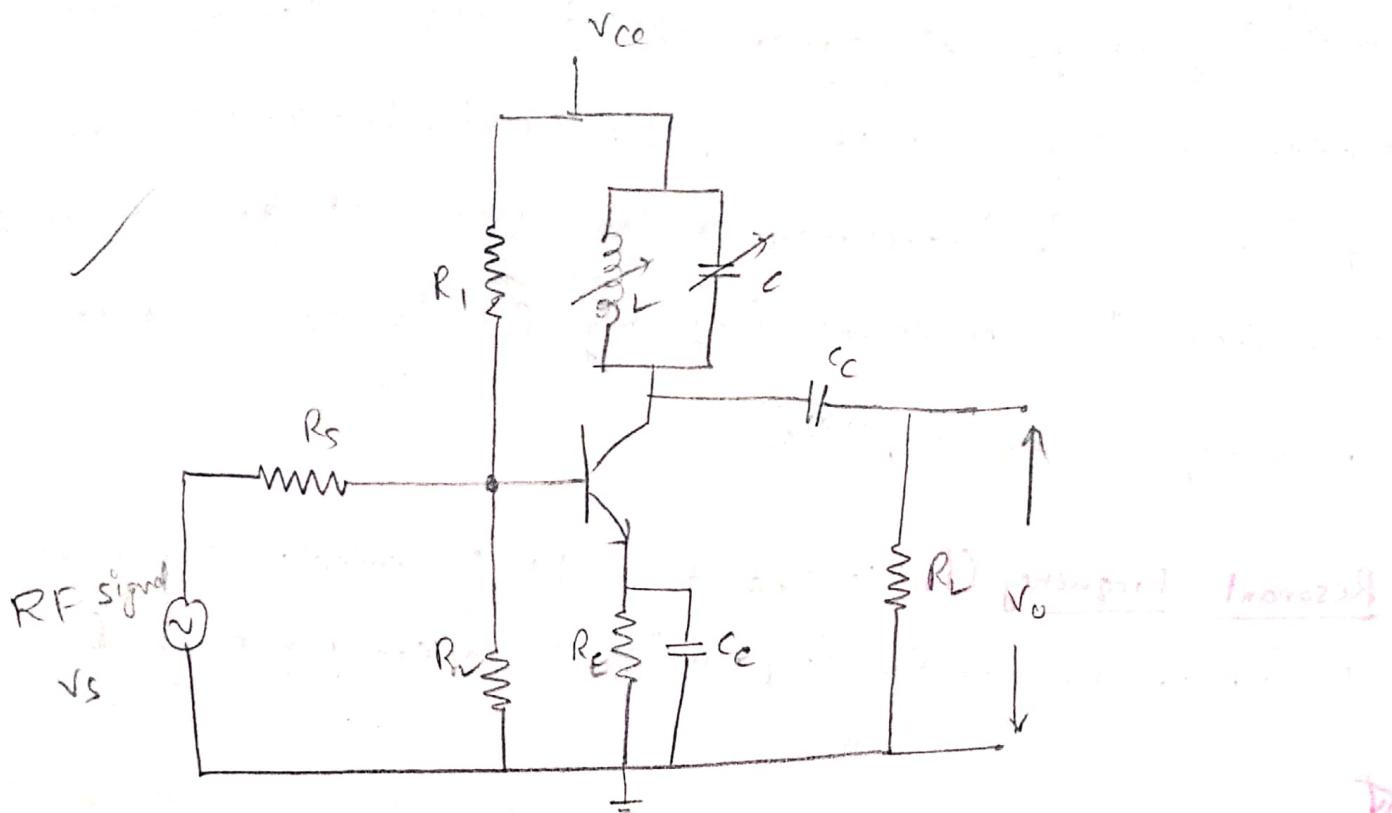

Früher war ein Verstärker mit einem einzigen Transistor ausreichend.

A simple transistor amplifier circuit consisting of parallel tuned ckt in its collector load, makes a single tuned amplifier ckt. The values of capacitance and inductance of the tuned ckt are selected such that its resonant frequency ( $f_r$ ) is equal to the frequency to be amplified.

Resonant Frequency ( $f_r$ ) :- The tank ckt in collector terminal is tuned to certain freq which is called resonant freq.

### Effect of cascading single Tuned Amplifiers on Bandwidth

In order to obtain a high overall gain, several identical stages (or) tuned amplifiers can be used in cascade. The overall voltage gain is the product of the voltage gains of the individual stages. At the same time, the high voltage gain is accompanied by a narrower B.W. than for a single stage.

→ The relative gain of a single tuned amplifier wrt the gain at resonant frequency ( $f_r$ ) is given

$$\left| \frac{A}{A_{res}} \right| = \frac{1}{\sqrt{1 + (28\alpha_e)^2}}$$

where →  $\delta$  = Fractional freq variation

$$= \frac{\omega - \omega_0}{\omega_0}$$

$\alpha_e$  = Effective Q factor

Now, the gain of  $n$  stage cascaded amplifier becomes

$$\left| \frac{A}{A_{res}} \right|^n = \left[ \frac{1}{\sqrt{1 + (28\alpha_e)^2}} \right]^n = \frac{1}{[1 + (28\alpha_e)^2]^{\frac{n}{2}}}$$

The 3dB freq's for the  $n$ -stage cascaded amplifier (3) can be found by equating  $\left| \frac{A_{\text{stage}}}{A_{\text{res}}} \right|^n$  to  $\frac{1}{\sqrt{2}}$

$$\left| \frac{A}{A_{\text{res}}} \right|^n = \frac{1}{\sqrt{1 + (28Q_e)^2}} = \frac{1}{\sqrt{2}}$$

$$\sqrt{1 + (28Q_e)^2} = \sqrt{2}$$

$$1 + (28Q_e)^2 = 2^{\frac{n}{2}}$$

$$1 + (28Q_e)^2 = 2^{1n}$$

for  $28Q_e$  we get  $28Q_e = \pm \sqrt{2^{1n}-1}$

$$28Q_e = \pm \sqrt{2^{1n}-1}$$

Substituting for  $\delta$ , the practical frequency variation

$$\text{i.e., } \delta = \frac{\omega - \omega_0}{\omega_0} = \frac{f - f_0}{f_0}$$

$$2 \left( \frac{f - f_0}{f_0} \right) Q_e = \pm \sqrt{2^{1n}-1}$$

$$2(f - f_0) Q_e = \pm f_0 \sqrt{2^{1n}-1}$$

$$f - f_0 = \pm \frac{f_0}{2Q_e} \sqrt{2^{1n}-1}$$

$$\text{thus, } f_2 - f_0 = + \frac{f_0}{2Q_e} \sqrt{2^{1n}-1}$$

$$\text{similarly, } f_0 - f_1 = + \frac{f_0}{2Q_e} \sqrt{2^{1n}-1}$$

Bandwidth of  $n$  stage identical amplifier is

$$B_{1n} = f_a - f_l = (f_a - f_o) + (f_o - f_l)$$

$$= \frac{f_o}{2Q_e} \sqrt{2^{1/n}-1} + \frac{f_o}{2Q_e} \sqrt{2^{1/n}-1}$$

$$= \frac{f_o}{2Q_e} \sqrt{2^{1/n}-1}$$

$$\boxed{B_{1n} = B_1 \sqrt{2^{1/n}-1}} \quad (\text{or}) \quad \boxed{B_{1n} = B_1 [2^{1/n}-1]^{1/2}}$$

3 dB BW of

the single tuned  
amp

where  $B_{1n} \rightarrow$  B.W at  $n$  stages of  
the cascade amplifier

$B_1 \rightarrow$  B.W for single stage.

→ B.W of  $n$  stages  $B_{1n}$  is equal to  $B_1$  multiplied by  
a factor of  $\sqrt{2^{1/n}-1}$

when.  $n=2 ; \sqrt{2^{1/2}-1} = 0.643$

$$n=3 ; \sqrt{2^{1/3}-1} = 0.510$$

### Effect of Cascading Double Tuned Amplifier on B.W:-

The Problem of Potential instability in single tuned  
amplifier is overcome in Double Tuned amplifier.

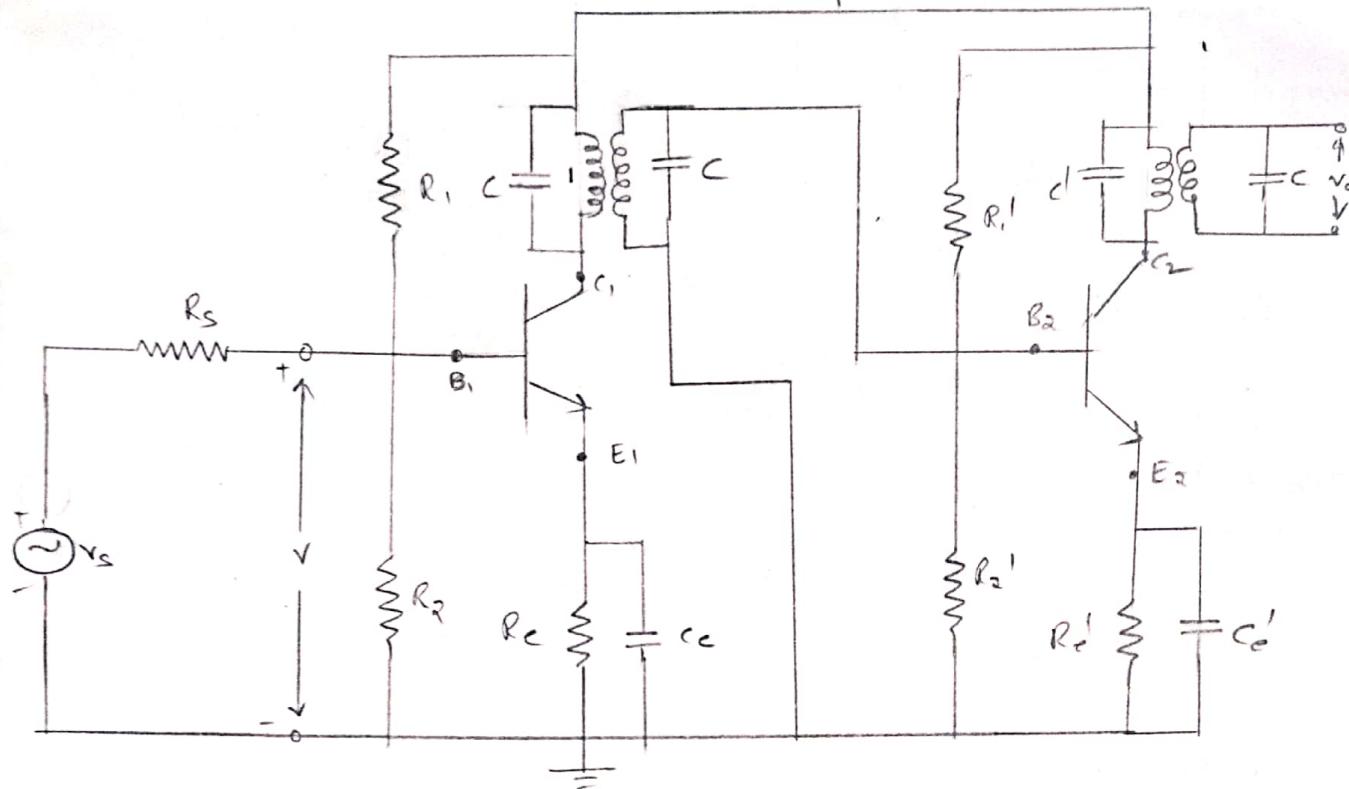



Fig. circuit Diagram for Double Tuned Amplifier

→ The 3 dB Bandwidth of the cascaded double tuned amplifier

$$B_{2n} = B_2 [2^{1/n} - 1]^{1/4}$$

where  $B_2 \rightarrow$  3 dB B.W of the single stage double tuned amplifier

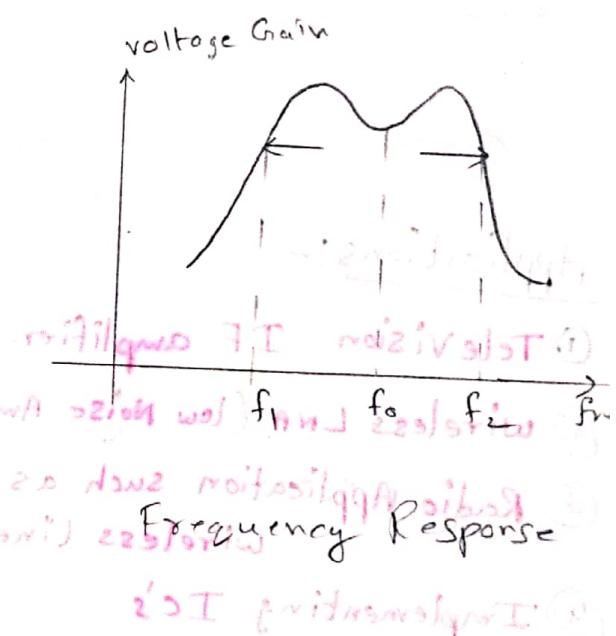(widely spaced between  $f_1$  and  $f_2$ )




so due to loss of quality factor and frequency response is reduced.

2) Frequency Response

is widened.
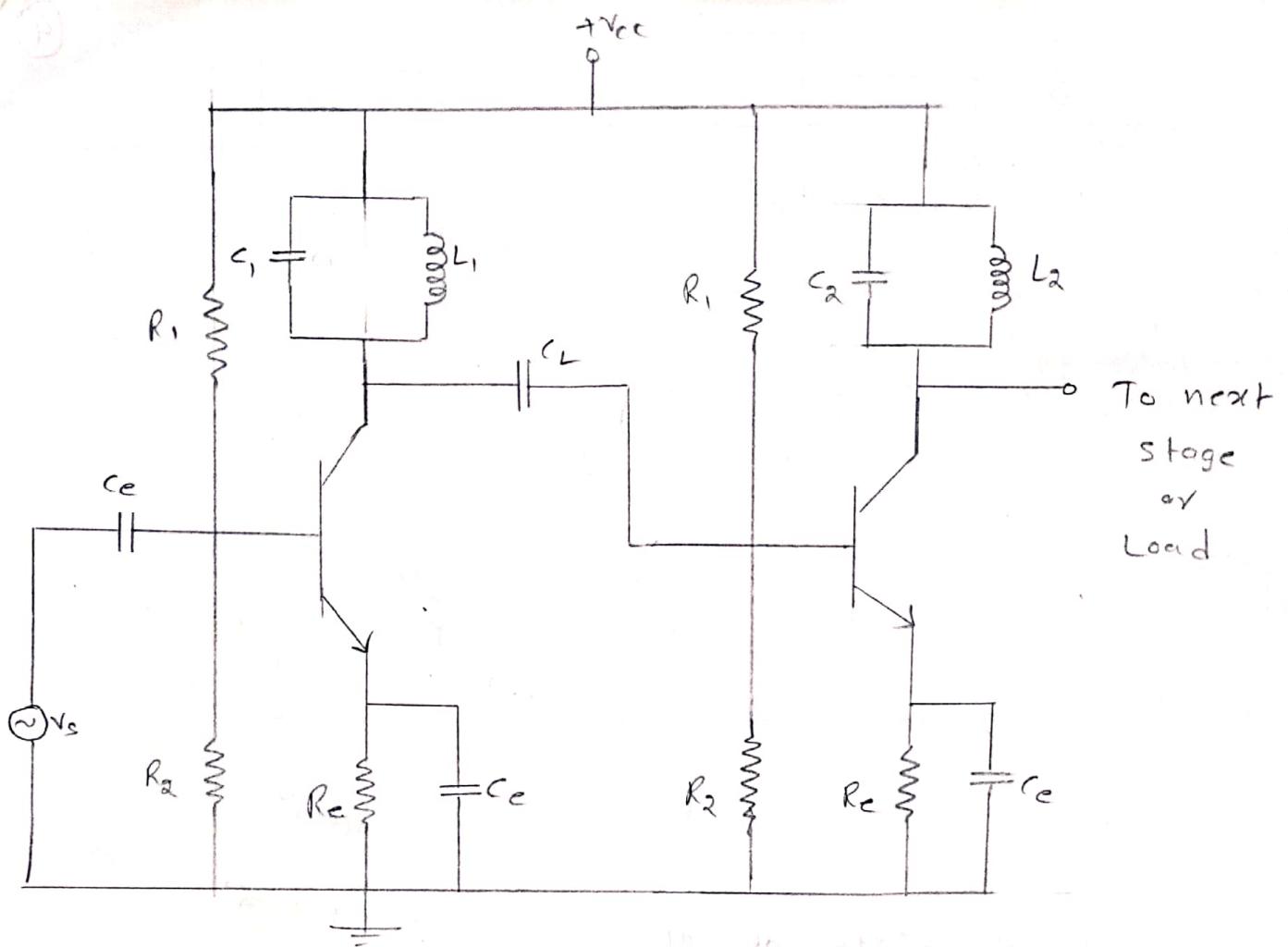
## V) Stagger Tuned Amplifier:-

→ In the double tuned amplifier, it is observed that if two or more tuned circuits are cascaded and tuned to the same freq, the overall B.W reduces. It is known as "synchronous tuning".




## Circuit diagram of Stagger-Tuned Amplifier
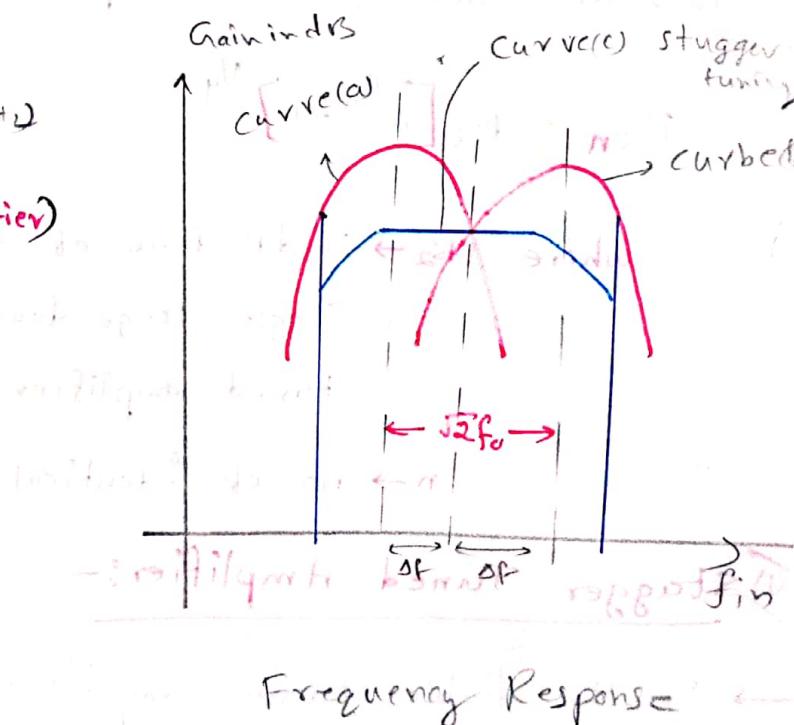
## Applications:-

- Applications

  - ① Television IF amplifier.  $\rightarrow (950\text{MHz} - 2150\text{MHz})$
  - ② wireless LNA (low Noise Amplifier)
  - ③ Radio Application such as wireless line
  - ④ Implementing IC's



curve (a)  $\rightarrow$  gain vs freq response of L/C.

curve (b)  $\rightarrow$   $w_1 = w_2 = w_3 = w_4 = w_5 = L_{2(g)}$

curve (c) → Combined (or) overall response of the Ckt

→ The double tuned amplifier gives wider decrease in B.W with steeper sides and flat top, but alignment of double tuned amplifier is difficult. To overcome this problem stagger tuned amplifier is employed.

→ In this case, two single tuned circuits are connected in a cascade and the resonant frequency of both the stages is different.

The gain of the single tuned amplifier is given by

$$\frac{A}{A_{res}} = \frac{1}{1+j2Qes}$$

$$= \frac{1}{1+jx} \quad \text{where } x \rightarrow 2Qes$$

One stage is tuned to the frequency below  $f_0$ , i.e.,  $f_0 - \delta$  and the other is tuned to a freq above  $f_0 + \delta$

The corresponding selectivity  $f_n$  of the ckt's are,

$$\left( \frac{A}{A_{res}} \right)_1 = \frac{1}{1+j(x-1)} \quad \text{and}$$

$$\left( \frac{A}{A_{res}} \right)_2 = \frac{1}{1+j(x+1)}$$

since, overall Gain,  $A_{ov} = \left( \frac{A}{A_{res}} \right)_1 \left( \frac{A}{A_{res}} \right)_2$

$$\text{Overall gain} = \frac{1}{1+j(x-1)} \cdot \frac{1}{1+j(x+1)}$$


$$= \frac{1}{2-x^2+2jx}$$

$$\left| \left( \frac{A}{A_{res}} \right) \right|_{\text{overall}} = \frac{1}{\sqrt{(2-x)^2 + (2x)^2}}$$

where  $x = 28Q_c$
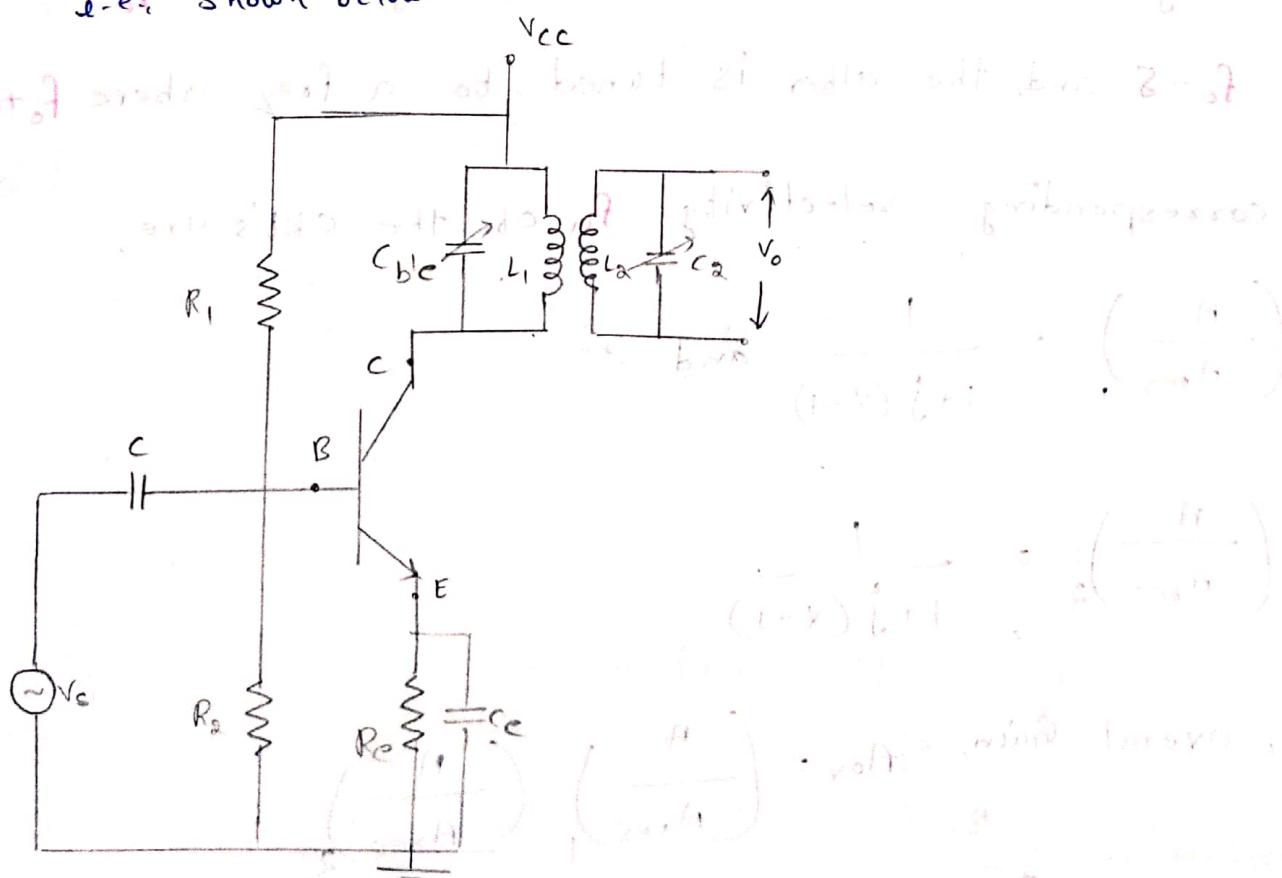
### VII Stability of Tuned Amplifier:-

In Radio frequency tuned amplifiers the transistor used at high frequencies. At that high frequencies inter-junction capacitance are dominated i.e., the reactance of that capacitor value is low. i.e. shown below.




→ In the above CT configuration, the interjunction capacitance from collector to base i.e.,  $C_{bc}$  feedback to the input from the output. This feedback converted the CKT into its open oscillators. (6)

→ This oscillation can stop the working of an amplifier.

→ To overcome the oscillations the gain of amplifier is reduced. The gain of amplifier is reduced then Q-factor (quality factor) is reduced.


→ To overcome this problem the Professor L.A. Hazenlon introduced a CKT called Hazenlon neutralization.

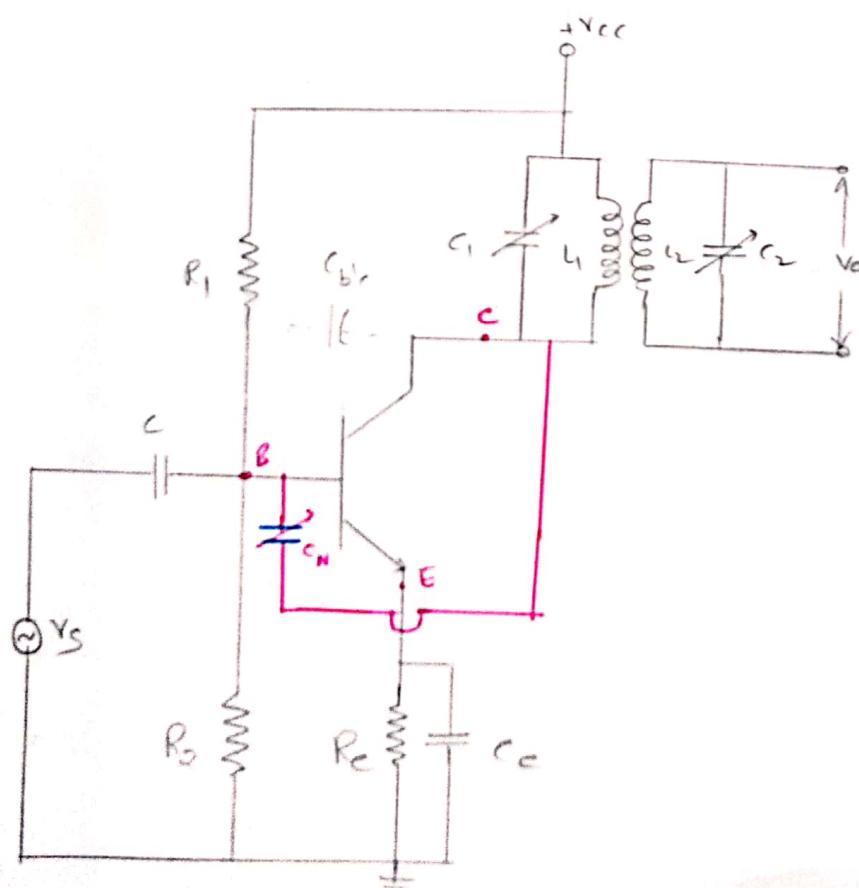→ The Hazenlon neutralization CKT having a small variable capacitance i.e.,  $C_N$  connected between base to the collector of that CKT as shown below.



→ This variable capacitance  $C_N$  is also adjusted so that any feed back signal is cancelled.

The output voltage is fed back and made positive through a matched pair of diodes. This will give different voltage levels at the two outputs of the bridge rectifier. The output voltage with feedback will therefore be given by the equation (eqn 7.37)  $V_o = V_{o0} + \frac{V_{fb}}{2}$ . This will result in both outputs having different magnitudes of voltage. These voltages will then be converted into digital signals. These have to be scaled up to obtain a maximum value of 1023 and must be converted to binary code. This is done by using a digital voltmeter which makes use of the fall time technique.

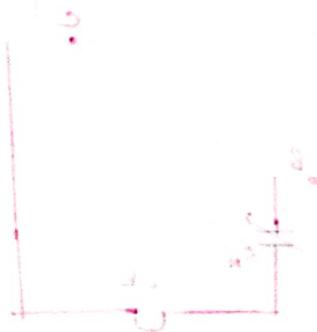

## VIII Multivibrations :-

The word multivibrator is a combination of multi(many) and vibrator(oscillator).

Multivibrator is defined as an electronic circuit that oscillate at many frequencies.

→ Multivibrators are classified based on their output states i.e., stable and Quasi stable states.

### stable state:-

Multivibrators are designed by cross-coupling two inverters, which contain transistors and state indicates the ON (or) OFF condition of the transistor.

→ Stable-state of a multivibrator means, the circuit can remain only in one state permanently. That is, if one transistor is ON and the other transistor is OFF. The circuit remains in that state unless triggered by an external signal to change its state.

## Quasi State :-

Quasi stable-state of multivibrator means, the circuit cannot remain in one state permanently. that is, if one transistor is ON and another transistor is OFF, it remains in that state for a predefined time only. After the completion of predefined time, the ON transistor turns OFF and the OFF transistor turns ON.

→ Multivibrators are categorized as,

① Bistable multivibrator

② Monostable

③ Astable

**Application :** These multivibrators, are used to generate non-sinusoidal waveforms.

**Principle of Working :** Multivibrator is a two stage

amplifier with feedback i.e.,

output of one stage is connected

to the IP of the second stage

and vice versa.

Thus, the active devices are set either in saturation (or) cut-off region as per their requirement.

## ① Bistable Multivibrator:-

- Multivibrators that has two stable states is called bistable multivibrator. This is also referred as Eccles-Jordan circuit, flip-flop, binary, trigger circuit, scale-of-two toggle circuit.
- In this case, the stable state represents the state where Kirchoff's voltage and current laws are satisfied.

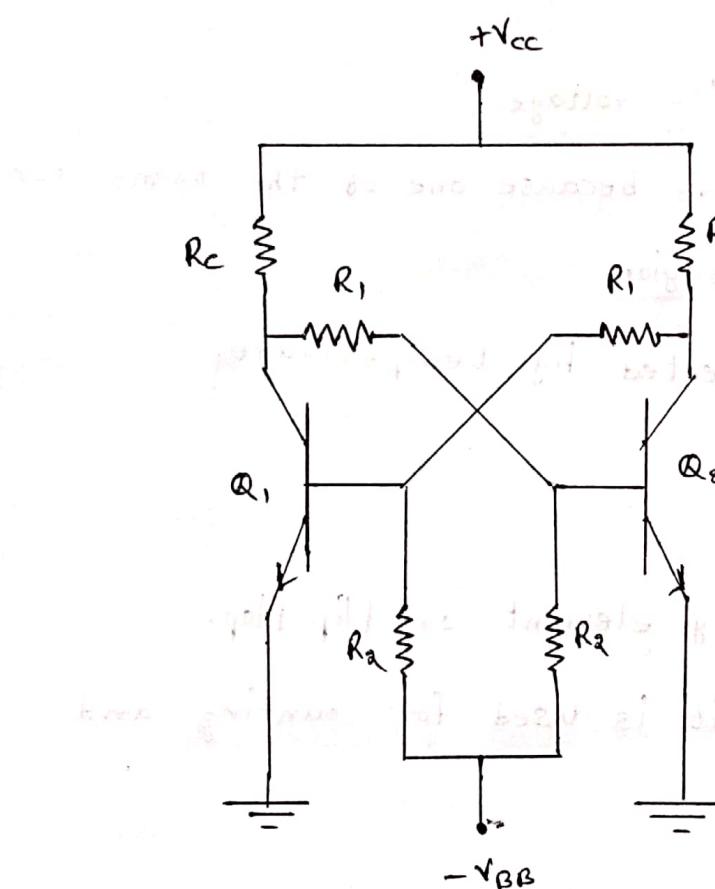


Fig. (1) circuit arrangement of Bistable Multivibrator

- The coupling elements used in this circuit are two resistors i.e., both are d.c. coupled in bistable multivibrator.
- It requires triggering signal to change its state and another trigger for backward transition.

## Merits :-

- ① Bistable multivibrator is simple to design.
- ② Power dissipation is less.
- ③ Transistor with lower breakdown voltage rating are used in circuit.
- ④ Dual voltage supply is not necessary for the operation.

## Limitations :-


- ① It is sensitive to noise voltage.
- ② Its storage time is more because one of the transistor operates in saturation region.
- ③ It can be easily affected by temperature.

## Applications :-

- ① It is used as memory element or flip flop.
- ② In digital operations, it is used for counting and storing binary data.
- ③ It is also used in generation and processing of pulse type waveform.
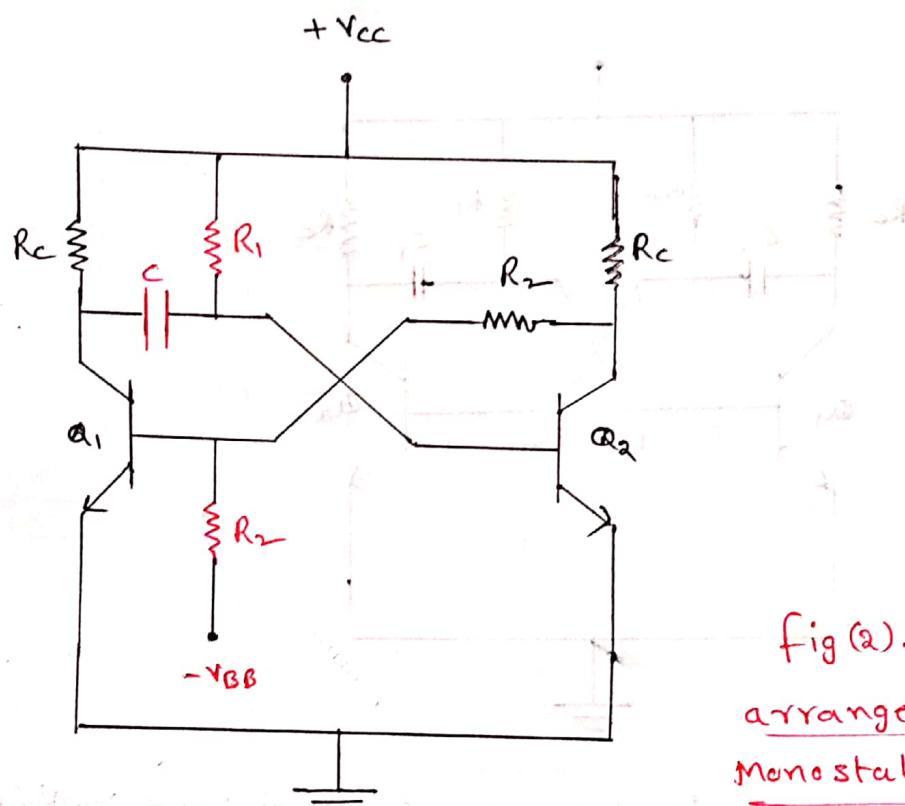
## (2) Monostable Multivibrator :-

→ Monostable multivibrator has one stable state and one quasi state. It is also named as one-shot, single-shot, a single cycle, gating circuit or delay circuit, univibrator.



fig(2). circuit arrangement of monostable multivibrator

- The coupling element used in this ckt are one capacitor and one resistor i.e., one a.c. coupling and one d.c. coupling.  
→ It requires a trigger signal to change stable state to quasi state and no signal for vice versa.

### Applications :-

- ① It is used in pulse circuits.
- ② It is also used as gating circuit as it generates rectangular waveforms.
- ③ It is also be used to introduce delay.

### ③ Astable Multivibrator :-

→ Astable multivibrator has no stable states i.e., both the states are quasi states. It is also called as free-running multivibrator, square wave generator and relaxation oscillator.

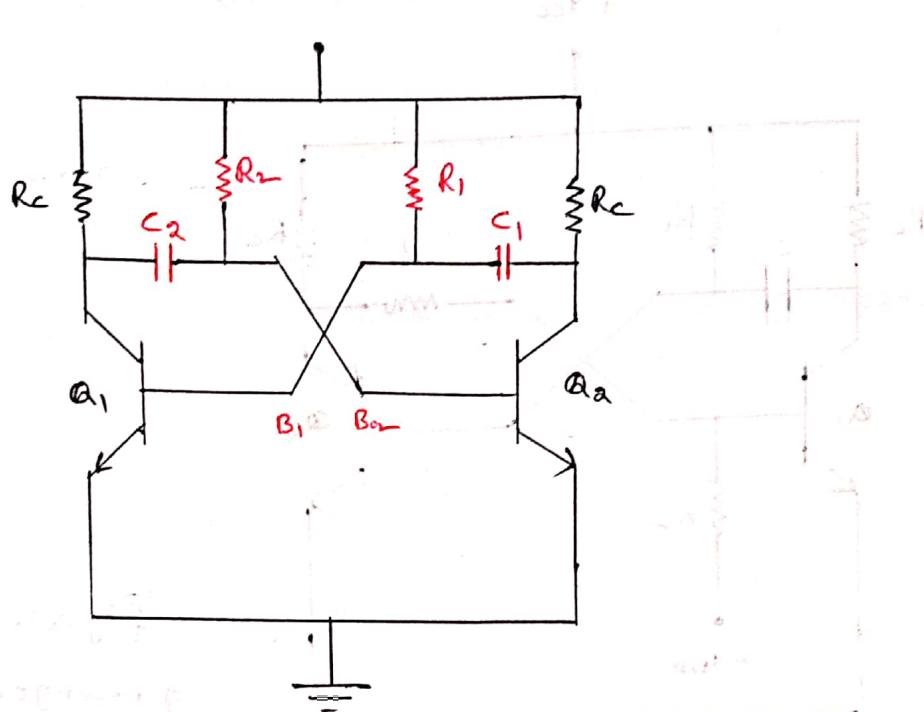


Fig (3). Circuit arrangement of Astable Multivibrator

→ The coupling elements used in this circuit are capacitors i.e., both are ac coupling. It does not require any triggering signal to change its state.


### Applications :-

- ① Used to generate square waveforms.
- ② It is a basic source of fast waveforms.
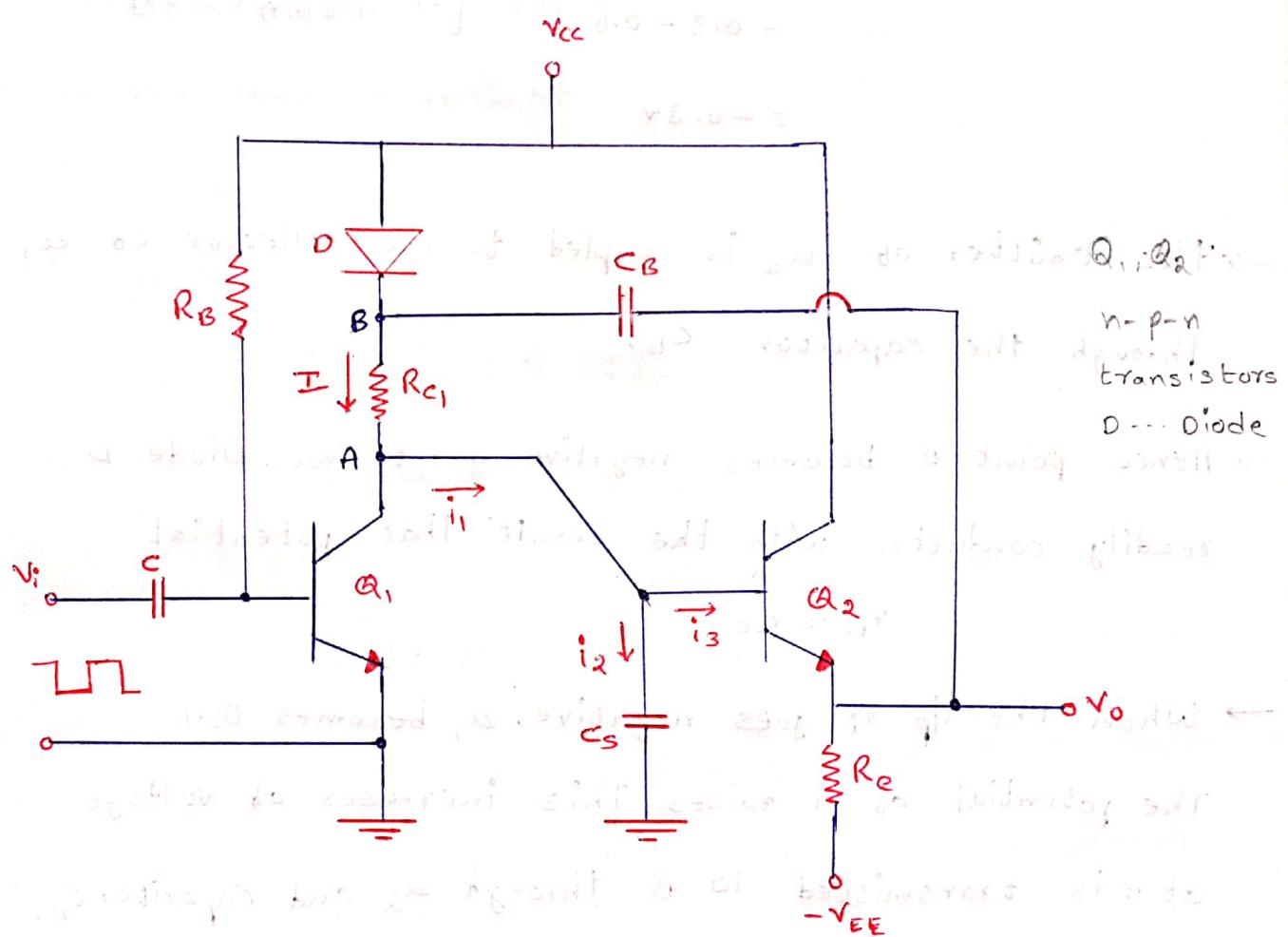
# Boot-strap Generator

The bootstrap sweep circuit

(or) generator uses the Principle in its functioning and generates a ramp voltage.



→ The transistor  $Q_1$  acts as ON-OFF switch, and the transistor  $Q_2$  is an emitter-follower.

→ The i/p  $V_i$  is a pulse voltage, (or) rectangular wave.

→ When the i/p signal  $V_i$  is positive, transistor  $Q_1$  becomes ON i.e., goes into saturation.

$\therefore$  Potential of point A,  $V_A = V_{CE(sat)}$

If  $Q_1$  is silicon transistor,  $V_{CE(sat)} = 0.3V$

∴  $V_A = 0.3V$  (in active region)

Output voltage  $V_o = V_A - V_{BE(Q_2)}$  (in active region)

$$= 0.3 - 0.6 \quad [ \because V_{BE(act)} = 0.6V ]$$

$$= -0.3V$$

→ The emitter of  $Q_2$  is coupled to the collector of  $Q_1$ , through the capacitor  $C_B$ .

→ Hence point B becomes negative w.r.t.  $V_{cc}$ . Diode D readily conducts, with the result that potential

$$V_B \approx V_{cc}$$

→ When the input  $V_i$  goes negative,  $Q_1$  becomes OFF.

The potential of A raises. This increase of voltage at A is transmitted to B through  $Q_2$  and capacitor  $C_B$ .

→ The result is that the potential of B also raises by the same amount. This is the principle of bootstrap.

Thus  $V_B$  raises from  $V_{cc}$  to  $(V_{cc} + V_A)$ .

→ Let I denotes the current through  $R_C$ ,

$$\text{we have } I = \frac{V_B - V_A}{R_C} = \frac{V_{cc}}{R_C} \quad [ \because V_B = V_{cc} + V_A ]$$

→ Since both  $V_{CC}$  and  $R_{C_1}$  are fixed magnitude, the ratio  $\left(\frac{V_{CC}}{R_{C_1}}\right)$  is constant. Hence current  $I$  is of constant magnitude.

→ From the circuit, we have  $I = i_1$ , since  $Q_1$  is now cut off and its collector current is zero. But  $i_1 = i_2 + i_3$ .  $i_3$  is the base current of  $Q_2$ , since  $Q_2$  is an emitter follower, its input impedance is very, very high and hence  $i_3$  is practically zero.

$$\therefore i_1 = i_2 \quad \text{But } i_1 = I$$


$$\therefore i_2 = I, \text{ a constant current.}$$

→ As this current flows through the capacitor  $C_S$ , a ramp voltage develops across it.

→ For an emitter follower, voltage gain is almost unity.

→ Therefore the o/p voltage  $V_o$  is also a ramp voltage.

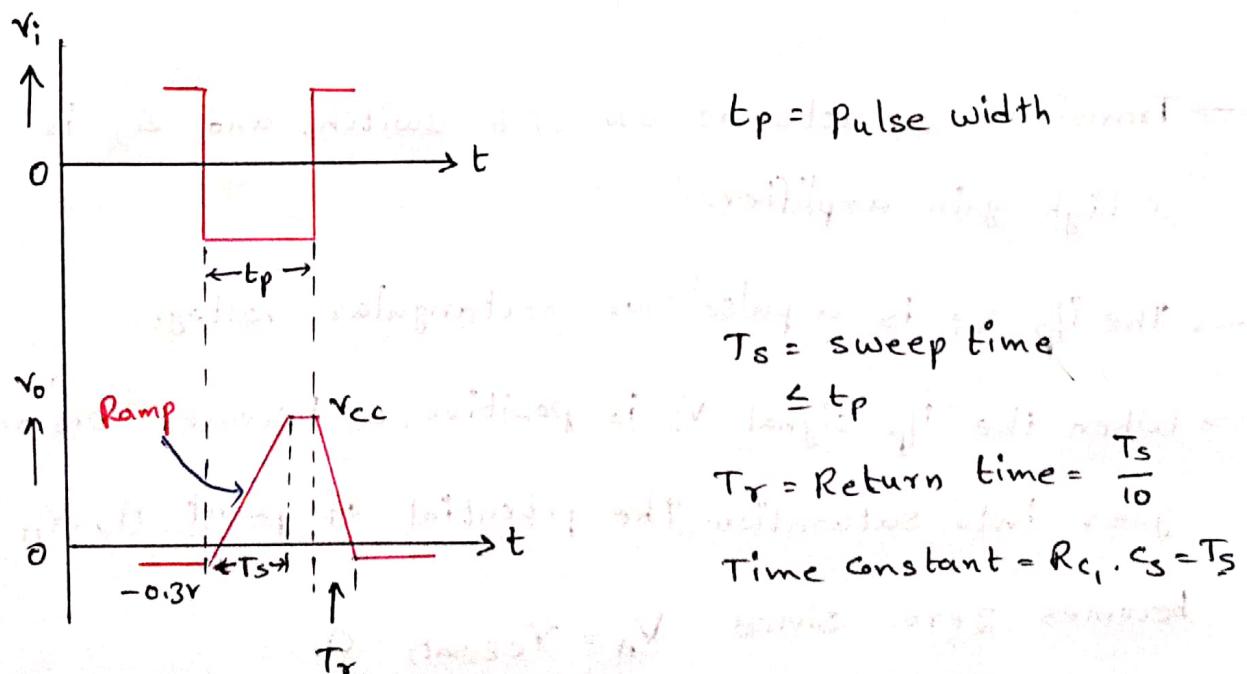Thus the bootstrap ckt generates a ramp voltage.



## X Miller Circuit :-

The Miller sweep circuit also


generates a ramp voltage using the basic principle.

But it differs from the bootstrap sweep circuit

in that it generates a negative ramp. Also it makes

use of a high gain amplifier and it incorporates

negative feedback.

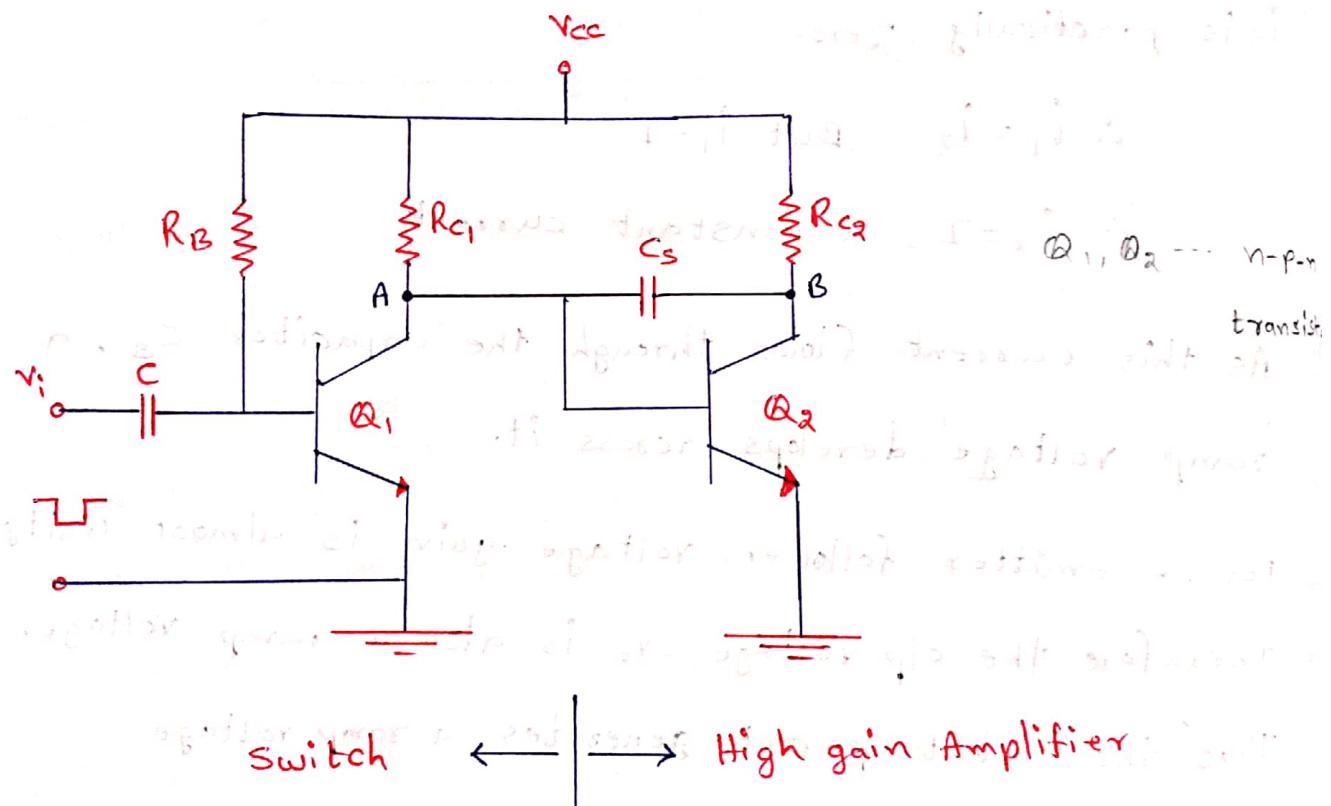

→ Transistor  $Q_1$  acts as ON-OFF switch, and  $Q_2$  is a high gain amplifier.

→ The i/p  $V_i$  is a pulse (or) rectangular voltage.

→ When the i/p signal  $V_i$  is positive,  $Q_1$  becomes ON and goes into saturation. The potential of point A,  $V_A$  becomes zero, since  $V_A = V_{CE(sat)} = 0$ .

→ Transistor  $Q_2$  remains OFF, since it cannot get the necessary base drive. Point B would be at potential  $V_{cc}$

∴ Voltage across the capacitor,  $C_s = V_{cc}$


i.e.,  $V_s = V_{cc}$ .

→ When the flip signal  $V_i$  goes negative,  $Q_1$  cannot obviously conduct. With  $Q_1$  OFF, the potential of point A tends to rise to  $V_{cc}$ . But, due to the capacitor  $C_s$  present in the circuit, potential  $V_A$  cannot rise to  $V_{cc}$  instantaneously. Hence  $V_A$  rises gradually and as a result, the voltage across the capacitor also falls gradually.

[with  $Q_1$  OFF and potential of A going up,  $Q_2$  becomes ON. The potential of B tends to decrease to zero, but because of the capacitor  $C_s$ ,  $V_B$  cannot abruptly come down. As  $V_A$  gradually increases, and  $V_B$  gradually decreases, the voltage across the capacitor progressively falls. The result is that  $C_s$  discharges linearly.]

→ Thus the voltage  $V_s$  across the capacitor  $C_s$  is a decreasing i.e., negative going ramp.

## Wave forms of Input & Output

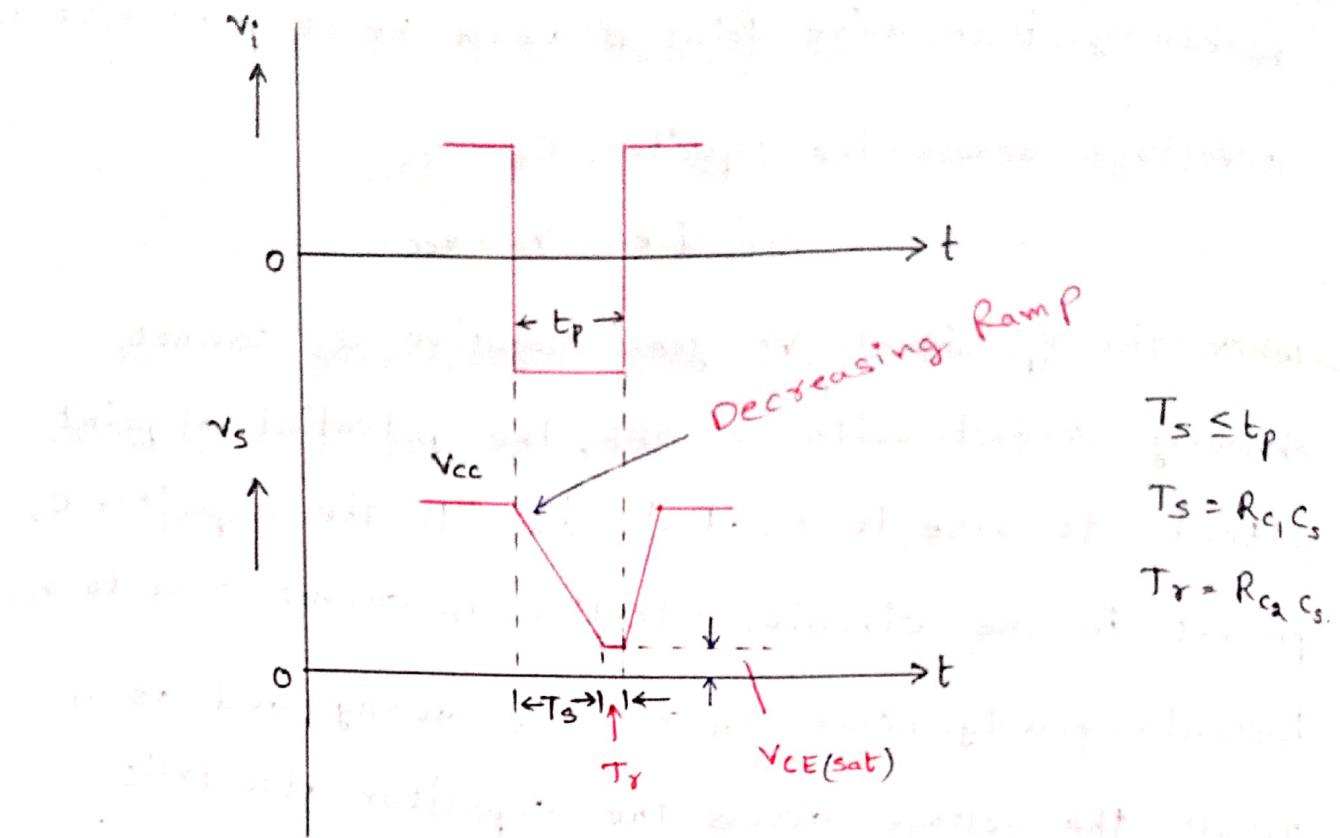

Formation of wave forms due to following three stages and after  
switching off depends on sum of all the different voltages  
at output terminals and resistances left for conduction due  
to breaking of bias resistors and formation of air隙 magnetic  
barrier effect, coupled with reverse operation left after removal  
of current source.

[Current separation]

→ Test of Hysteresis effect of core

→ Effect of leakage field

→ Effect of magnetic saturation

→ Effect of magnetic hysteresis

→ Effect of magnetic core loss

→ Effect of magnetic core saturation

→ Effect of magnetic core loss