

Figure 1 shows a 4-bit parallel adder implemented using a 1:4 decoder and four 2-input AND gates. The decoder has two inputs, D and E, and four outputs, Y0, Y1, Y2, and Y3. The AND gates have inputs D, S1, and S0. The outputs of the AND gates are labeled as follows:

- $Y_0 = D S_1 S_0$
- $Y_1 = D S_1 S_0$
- $Y_2 = D S_1 S_0$
- $Y_3 = D S_1 S_0$

I/II Sem





Sri Indu College of Engineering & Technology :: Sheriguda (V), R.R.Dist

Department of Electronics & Communication Engineering

LAB FILE

Branch: ECE

Class: B.Tech- II Year-I/II sem

Lab : DLD/DE LAB

Code: R22ECE2127/R22ECE2126

Academic Year: 2025-26

Regulation: R22

Core/Elective/H&S: Core

Prepared By

Name: 1. P. MAMATHA, Asst. Professor

2. B. HEMAVATHI, Asst. Professor

3. D.JYOTHI, Asst. Professor

Head of the Department

SRI INDU COLLEGE OF ENGINEERING & TECHNOLOGY

(An Autonomous Institution under UGC, New Delhi)

B.Tech. - II Year – I Semester

L	T	P	C
0	0	2	1

(R22ECE2127) DIGITAL LOGIC DESIGN LABORATORY

Course Outcomes: Upon completing this course, the students will be able to

1. Acquire the knowledge on numerical information in different forms and Boolean Algebra theorems.
2. Define Postulates of Boolean algebra and to minimize combinational functions, and design the combinational circuits.
3. Design and analyze sequential circuits for various cyclic functions.
4. Characterize logic families and analyze them for the purpose of AC and DC parameters.

Course	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
CO1	3	2	3	1	2	1	-	-	1	-	-	2
CO2	3	2	2	1	2	1	-	-	1	-	-	2
CO3	2	3	3	2	2	1	-	-	1	-	-	1
CO4	3	2	1	1	1	-	-	-	-	-	-	-

List of Experiments

1. Realization of Boolean Expressions using Gates
2. Design and realization logic gates using universal gates
3. Design a 4 – bit Adder
4. Design a 4 – bit Subtractor
5. Design and realization a 4 – bit gray to Binary and Binary to Gray Converter
6. Design and realization of a 4-bit pseudo random sequence generator using logic gates.
7. Design and realization of an 8-bit parallel load and serial out shift register using flip-flops.
8. Design and realization Asynchronous and Synchronous counters using flip-flops
9. Design and realization 8x1 using 2x1 mux
10. Design and realization 4-bit comparator
11. Verification of truth tables and excitation tables
12. Realization of logic gates using DTL, TTL, ECL, etc.,

1. Major Equipment required for Laboratories:

1. 5 V Fixed Regulated Power Supply/ 0-5V or more Regulated Power Supply.
2. 20 MHz Oscilloscope with Dual Channel.
3. Bread board and components/ Trainer Kit.
4. Multimeter.

SRI INDU COLLEGE OF ENGINEERING & TECHNOLOGY
(An Autonomous Institution under UGC, New Delhi)**B.Tech. - II Year – I Semester****L T P C**
0 0 2 1**(R22ECE2126) DIGITAL ELECTRONICS LABORATORY****Course Outcomes:** Upon completing this course, the students will be able to

1. Acquire the knowledge on numerical information in different forms and Boolean Algebra theorems.
2. Define Postulates of Boolean algebra and to minimize combinational functions, and design the combinational circuits.
3. Design and analyze sequential circuits for various cyclic functions.
4. Characterize logic families and analyze them for the purpose of AC and DC parameters.

Course	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
CO1	3	2	3	1	2	1	-	-	1	-	-	2
CO2	3	2	2	1	2	1	-	-	1	-	-	2
CO3	2	3	3	2	2	1	-	-	1	-	-	1
CO4	3	2	1	1	1	-	-	-	-	-	-	-

List of Experiments

1. Realization of Boolean Expressions using Gates
2. Design and realization logic gates using universal gates
3. Design a 4 – bit Adder
4. Design a 4 – bit Subtractor
5. Design and realization a 4 – bit gray to Binary and Binary to Gray Converter
6. Design and realization of a 4-bit pseudo random sequence generator using logic gates.
7. Design and realization of an 8-bit parallel load and serial out shift register using flip-flops.
8. Design and realization Asynchronous and Synchronous counters using flip-flops
9. Design and realization 8x1 using 2x1 mux
10. Design and realization 4-bit comparator
11. Verification of truth tables and excitation tables
12. Realization of logic gates using DTL, TTL, ECL, etc.,

1. Major Equipment required for Laboratories:

1. 5 V Fixed Regulated Power Supply/ 0-5V or more Regulated Power Supply.
2. 20 MHz Oscilloscope with Dual Channel.
3. Bread board and components/ Trainer Kit.
4. Multimeter.

SRI INDU COLLEGE OF ENGINEERING & TECHNOLOGY
(An Autonomous Institution under UGC, New Delhi)**B.Tech. - II Year – I Semester****L T P C**
0 0 2 1**(R22ECE2126) DIGITAL ELECTRONICS LAB****Course Outcomes:** Upon completing this course, the students will be able to

1. Acquire the knowledge on numerical information in different forms and Boolean Algebra theorems.
2. Define Postulates of Boolean algebra and to minimize combinational functions, and design the combinational circuits.
3. Design and analyze sequential circuits for various cyclic functions.
4. Characterize logic families and analyze them for the purpose of AC and DC parameters.

Course	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
CO1	3	2	3	1	2	1	-	-	1	-	-	2
CO2	3	2	2	1	2	1	-	-	1	-	-	2
CO3	2	3	3	2	2	1	-	-	1	-	-	1
CO4	3	2	1	1	1	-	-	-	-	-	-	-

List of Experiments

1. Realization of Boolean Expressions using Gates
2. Design and realization logic gates using universal gates
3. Design a 4 – bit Adder
4. Design a 4 – bit Subtractor
5. Design and realization a 4 – bit gray to Binary and Binary to Gray Converter
6. Design and realization of a 4-bit pseudo random sequence generator using logic gates.
7. Design and realization of an 8-bit parallel load and serial out shift register using flip-flops.
8. Design and realization Asynchronous and Synchronous counters using flip-flops
9. Design and realization 8x1 using 2x1 mux
10. Design and realization 4-bit comparator
11. Verification of truth tables and excitation tables
12. Realization of logic gates using DTL, TTL, ECL, etc.,

1. Major Equipment required for Laboratories:

1. 5 V Fixed Regulated Power Supply/ 0-5V or more Regulated Power Supply.
2. 20 MHz Oscilloscope with Dual Channel.
3. Bread board and components/ Trainer Kit.
4. Multimeter.

SRI INDU COLLEGE OF ENGINEERING & TECHNOLOGY**(An Autonomous Institution under UGC, New Delhi)****B.Tech. - II Year – I Semester**

L	T	P	C
0	0	2	1

(R22ECE2126) DIGITAL ELECTRONICS LABORATORY**Course Outcomes:** Upon completing this course, the students will be able to

1. Acquire the knowledge on numerical information in different forms and Boolean Algebra theorems.
2. Define Postulates of Boolean algebra and to minimize combinational functions, and design the combinational circuits.
3. Design and analyze sequential circuits for various cyclic functions.
4. Characterize logic families and analyze them for the purpose of AC and DC parameters.

Course	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
CO1	3	2	3	1	2	1	-	-	1	-	-	2
CO2	3	2	2	1	2	1	-	-	1	-	-	2
CO3	2	3	3	2	2	1	-	-	1	-	-	1
CO4	3	2	1	1	1	-	-	-	-	-	-	-

List of Experiments

1. Realization of Boolean Expressions using Gates
2. Design and realization logic gates using universal gates
3. Design a 4 – bit Adder
4. Design a 4 – bit Subtractor
5. Design and realization a 4 – bit gray to Binary and Binary to Gray Converter
6. Design and realization of a 4-bit pseudo random sequence generator using logic gates.
7. Design and realization of an 8-bit parallel load and serial out shift register using flip-flops.
8. Design and realization Asynchronous and Synchronous counters using flip-flops
9. Design and realization 8x1 using 2x1 mux
10. Design and realization 4-bit comparator
11. Verification of truth tables and excitation tables
12. Realization of logic gates using DTL, TTL, ECL, etc.,

1. Major Equipment required for Laboratories:

1. 5 V Fixed Regulated Power Supply/ 0-5V or more Regulated Power Supply.
2. 20 MHz Oscilloscope with Dual Channel.
3. Bread board and components/ Trainer Kit.
4. Multimeter.

SRI INDU COLLEGE OF ENGINEERING & TECHNOLOGY

(An Autonomous Institution under UGC, New Delhi)

B.Tech. - II Year – II Semester

L	T	P	C
0	0	2	1

(R22ECE2126) DIGITAL ELECTRONICS LABORATORY

Course Outcomes: Upon completing this course, the students will be able to

1. Acquire the knowledge on numerical information in different forms and Boolean Algebra theorems.
2. Define Postulates of Boolean algebra and to minimize combinational functions, and design the combinational circuits.
3. Design and analyze sequential circuits for various cyclic functions.
4. Characterize logic families and analyze them for the purpose of AC and DC parameters.

Course	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
CO1	3	2	3	1	2	1	-	-	1	-	-	2
CO2	3	2	2	1	2	1	-	-	1	-	-	2
CO3	2	3	3	2	2	1	-	-	1	-	-	1
CO4	3	2	1	1	1	-	-	-	-	-	-	-

List of Experiments

1. Realization of Boolean Expressions using Gates
2. Design and realization logic gates using universal gates
3. Design a 4 – bit Adder
4. Design a 4 – bit Subtractor
5. Design and realization a 4 – bit gray to Binary and Binary to Gray Converter
6. Design and realization of a 4-bit pseudo random sequence generator using logic gates.
7. Design and realization of an 8-bit parallel load and serial out shift register using flip-flops.
8. Design and realization Asynchronous and Synchronous counters using flip-flops
9. Design and realization 8x1 using 2x1 mux
10. Design and realization 4-bit comparator
11. Verification of truth tables and excitation tables
12. Realization of logic gates using DTL, TTL, ECL, etc.,

1. Major Equipment required for Laboratories:

1. 5 V Fixed Regulated Power Supply/ 0-5V or more Regulated Power Supply.
2. 20 MHz Oscilloscope with Dual Channel.
3. Bread board and components/ Trainer Kit.
4. Multimeter.

SRI INDU COLLEGE OF ENGINEERING & TECHNOLOGY**(An Autonomous Institution under UGC, New Delhi)****B.Tech. - II Year – II Semester**

L	T	P	C
0	0	2	1

(R22ECE2126) DIGITAL ELECTRONICS LABORATORY**Course Outcomes:** Upon completing this course, the students will be able to

1. Acquire the knowledge on numerical information in different forms and Boolean Algebra theorems.
2. Define Postulates of Boolean algebra and to minimize combinational functions, and design the combinational circuits.
3. Design and analyze sequential circuits for various cyclic functions.
4. Characterize logic families and analyze them for the purpose of AC and DC parameters.

Course	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12
CO1	3	2	3	1	2	1	-	-	1	-	-	2
CO2	3	2	2	1	2	1	-	-	1	-	-	2
CO3	2	3	3	2	2	1	-	-	1	-	-	1
CO4	3	2	1	1	1	-	-	-	-	-	-	-

List of Experiments

1. Realization of Boolean Expressions using Gates
2. Design and realization logic gates using universal gates
3. Design a 4 – bit Adder
4. Design a 4 – bit Subtractor
5. Design and realization a 4 – bit gray to Binary and Binary to Gray Converter
6. Design and realization of a 4-bit pseudo random sequence generator using logic gates.
7. Design and realization of an 8-bit parallel load and serial out shift register using flip-flops.
8. Design and realization Asynchronous and Synchronous counters using flip-flops
9. Design and realization 8x1 using 2x1 mux
10. Design and realization 4-bit comparator
11. Verification of truth tables and excitation tables
12. Realization of logic gates using DTL, TTL, ECL, etc.,

1. Major Equipment required for Laboratories:

1. 5 V Fixed Regulated Power Supply/ 0-5V or more Regulated Power Supply.
2. 20 MHz Oscilloscope with Dual Channel.
3. Bread board and components/ Trainer Kit.
4. Multimeter.

SRI INDU COLLEGE OF ENGINEERING AND TECHNOLOGY

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING



LAB MANUAL

ON

R22ECE2127: DIGITAL LOGIC DESIGN LAB(ECE)

**R22ECE2126: DIGITAL ELECTRONICS LAB
(IT,CSIT,IOT,EEE,AIDS)**

II B. TECH I/II SEMESTER



LIST OF EXPERIMENTS

1. Realization of Boolean Expressions using Gates
2. Design and realization logic gates using universal gates(NAND/NOR)
3. Design a 4 – bit Adder
4. Design a 4 – bit Subtractor
5. Design and realization of a 4 – bit gray to Binary and Binary to Gray Converter
6. Design and realization of 4-bit Pseudo Random sequence generator using logic gates
7. Design and realization of 8-bit parallel load and serial out shift register using flip-flops
8. Design and realization of a Synchronous and Asynchronous counter using flip-flops
9. Design and realization of 8x1 MUX using 2x1 MUX
10. Design and realization of 4-bit comparator
11. Verification of truth tables and excitation tables
12. Realization of logic gates using DTL, TTL, ECL, etc.



Sri Indu College of Engineering & Technology : Sheriguda (V), R.R.Dist

Department of Electronics & Communication Engineering

II Year –I Sem B.Tech ECE/IT/CSIT/IOT

II Year-II Sem B.Tech EEE/AIDS

(R22ECE2127)DIGITAL LOGICDESIGN LAB

(R22ECE2126)DIGITAL ELECTRONICS LAB

List of Experiments:

Expt No	Name of the experiment	COs Mapped
1	Realization of Boolean Expressions using Gates	C212.1
2	Design and realization logic gates using universal gates	C212.1
3	Design a 4 – bit Adder	C212.2
4	Design a 4 – bit Subtractor	C212.2
5	Design and realization a 4 – bit gray to Binary and Binary to Gray Converter	C212.1,2
6	Design and realization of a 4-bit pseudo random sequence generator using logic gates.	C212.2,5
7	Design and realization of an 8-bit parallel load and serial out shift register using flip-flops.	C212.1,5
8	Design and realization Asynchronous and Synchronous counters using flip-flops	C212.3
9	Design and realization 8x1 using 2x1 mux	C212.2
10	Design and realization 4-bit comparator	C212.2
11	Verification of truth tables and excitation tables	C212.4
12	Realization of logic gates using DTL, TTL, ECL, etc.,	C212.6

LIST OF ADDITIONAL EXPERIMENTS

Expt No	Name of the experiment	CO Mapped
1	STUDY OF 7490 BCD COUNTER	C212.3
2	STUDY OF SHIFT REGISTERS	C212.6
3	To generate clock using NAND/NOR gates	C212.2
4	Astable and Monostable multivibrators	C212.6

EXPERIMENT NO:1**Realization of Boolean Expressions using Gates**

Aim: Implementation of the given Boolean function using logic gates in both sop and pos forms.

Apparatus Required: Logic gates trainer kit, logic gates / ICs, patch cords.

Circuit Diagram:

SOP FORM:

SOP: - It is the sum of the Products form in which the terms are taken as 1. It is denoted in the K-Map expression by the Sign summation (Σ)

 


Fig:SOP Form

Truth Table:

A	B	C	AB	AC	BC	X
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	0	0	0
1	0	1	0	1	0	1
1	1	0	1	0	0	1
1	1	1	1	1	1	1

POS FORM:

POS: - It is the product of the sums form in which the terms are taken as 0. It is denoted in the K-Map expression by the Sign pie (π)

 


Fig: POS form


Truth Table:

A	B	C	A+B	B+C	C+A	X
0	0	0	0	0	0	0
0	0	1	0	1	1	0
0	1	0	1	1	0	0
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

Theory: Logic gates are electronic circuits which perform logical functions on one or more inputs to produce one output. There are seven logic gates. When all the input combinations of a logic gate are written in a series and their corresponding outputs written along them, then this input/ output combination is called **Truth Table**. Various gates and their working is explained here.

AND Gate

 AND gate produces an output as 1, when all its inputs are 1; otherwise the output is 0. This gate can have minimum 2 inputs but output is always one. Its output is 0 when any input is 0.




2 Input AND gate		
A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

IC 7408

OR Gate

 OR gate produces an output as 1, when any or all its inputs are 1; otherwise the output is 0. This gate can have minimum 2 inputs but output is always one. Its output is 0 when all input are 0.




2 Input OR gate		
A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

IC 7432

NOT Gate

 NOT gate produces the complement of its input. This gate is also called an INVERTER. It always has one input and one output. Its output is 0 when input is 1 and output is 1 when input is 0.



NOT gate	
A	$\bar{A}$
0	1
1	0

IC 7404

NAND Gate

NAND gate is actually a series of AND gate with NOT gate. If we connect the output of an AND gate to the input of a NOT gate, this combination will work as NOT-AND or NAND gate. Its output is 1 when any or all inputs are 0, otherwise output is 1.



2 Input NAND gate		
A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

IC 7400

NOR Gate

NOR gate is actually a series of OR gate with NOT gate. If we connect the output of an OR gate to the input of a NOT gate, this combination will work as NOT-OR or NOR gate. Its output is 0 when any or all inputs are 1, otherwise output is 1.



2 Input NOR gate		
A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

IC 7402

Exclusive OR (X-OR) Gate

X-OR gate produces an output as 1, when number of 1's at its inputs is **odd**, otherwise output is 0. It has two inputs and one output.




2 Input EXOR gate		
A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

IC 7486

Exclusive NOR (X-NOR) Gate

 X-NOR gate produces an output as 1, when number of 1's at its inputs is **not odd**, otherwise output is 0. It has two inputs and one output.



2 Input EXNOR gate		
A	B	$A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

Procedure:

1. Connect the trainer kit to ac power supply.
2. Connect the inputs of any one logic gate to the logic sources and its output to the logic indicator.
3. Apply various input combinations and observe output for each one.
4. Verify the truth table for each input/ output combination.
5. Repeat the process for all other logic gates.
6. Switch off the ac power supply.

RESULT: Realization of Boolean expressions by using logic gates are verified

VIVA:

1. What is the use of gates?
2. Compare all the gates?
3. Why we need ICs?
4. Define the term digital?
5. Which gate is equal to AND-inverter Gate?
6. What are the logic gates?
7. What is a truth table?
8. What is the maximum number of outputs a logic gate can have?
9. What is an AND gate?
10. What is a NOT gate?

Experiment No: 2**Design and realization of logic gates using universal gates**

Aim:-To study the realization of basic gates using universal gates. Understanding how to construct any combinational logic function using NAND or NOR gates only.

Aparatus Required:

IC 7402(NOR), IC 7400(NAND), 7404(NOT), 7408(AND), 7432(OR), KL 33002,
Power supply, connecting wires and Breadboard etc. or Trainer kit, patch cards.

Theory:

AND, OR, NOT are called basic gates as their logical operation cannot be simplified further.

NAND and NOR are called universal gates as using only NAND or only NOR, any logic function can be implemented. Using NAND and NOR gates and **De Morgan's Theorems** different basic gates & EX-OR gates are realized.

De Morgan's Law:


In formal logic, De Morgan's laws are rules relating the logical operators "AND" and "OR" in terms of each other via negation. With two operands A and B:

1. $A \cdot B = \overline{A + B}$

 2. $A + B = \overline{A \cdot B}$

The NAND gate is equivalent to an OR gate with the bubble at its inputs which are as shown.

The NOR gate is equivalent to an AND gate with the bubble at its inputs which are as shown.




IMPLEMENTING INVERTER USING NAND GATE :

The figure shows two ways in which a NAND gate can be used as an inverter (NOT gate).

 
1. All NAND input pins connect to the input signal A gives an output A' .
2. One NAND input pin is connected to the input signal A while all other input pins are connected to logic 1. The output will be A' .

An AND gate can be replaced by NAND gates as shown in the figure (The AND is replaced by a NAND gate with its output complemented by a NAND gate inverter).




IMPLEMENTING OR USING NAND GATE :

 An OR gate can be replaced by NAND gates as shown in the figure (The OR gate is replaced by a NAND gate with all its inputs complemented by NAND gate inverters).




IMPLEMENTING INVERTER USING NOR GATE:

 - The figure shows two ways in which a NOR gate can be used as an inverter (NOT gate).
- All NOR input pins connect to the input signal A gives an output A'.
- One NOR input pin is connected to the input signal A while all other input pins are connected to logic 0. The output will be A'.




IMPLEMENTING OR USING NOR GATE:

 - An OR gate can be replaced by NOR gates as shown in the figure (The OR is replaced by a NOR gate with its output complemented by a NOR gate inverter)



IMPLEMENTING AND USING NOR GATE:

 - An AND gate can be replaced by NOR gates as shown in the figure (The AND gate is replaced by a NOR gate with all its inputs complemented by NOR gate inverters)



Procedure:

1. Connect the trainer kit to ac power supply.
2. Connect the NAND gates/NOR gates for any of the logic functions to be realized.
3. Connect the inputs of first stage to logic sources and output of the last gate to logic indicator.
4. Apply various input combinations and observe output for each one.
5. Verify the truth table for each input/ output combination.
6. Repeat the process for all logic functions.
7. Switch off the ac power supply.

RESULT: Realization of logic gates with the help of Universal Gates-NAND AND NOR Gates are verified.

VIVA:

1. What do u mean by universal gate?
2. What is truth table?
3. How many AND gates are required to realize the following expression
 $Y = AB + BC$?
4. What is the difference between X-OR and X-Nor Gates?
5. Write properties of X-OR gate?
6. What is universal gates explain?
7. Draw the truth table for NAND?
8. Which is not universal gate?
9. Why it's called universal gates?
10. Draw the truth table for NOR?

Truth table:**ADDITION:**

Inputs								Outputs				
A ₄	A ₃	A ₂	A ₁	B ₄	B ₃	B ₂	B ₁	C ₀	S ₄	S ₃	S ₂	S ₁
1	0	0	0	0	0	1	0	0	1	0	1	0
1	0	0	0	1	0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	0	0	1	0	1	0
1	0	1	0	1	1	0	1	1	0	1	1	1

SUBTRACTION:

Inputs								Outputs				
A ₄	A ₃	A ₂	A ₁	B ₄	B ₃	B ₂	B ₁	B ₀	S ₄	S ₃	S ₂	S ₁
1	0	0	0	0	0	1	0	0	0	1	1	0
1	0	0	0	1	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	1	0	1	0
1	0	1	0	1	1	0	1	1	1	1	0	1

Procedure:

1. Connect the circuit as per circuit diagram.
2. Connect the inputs to the switches and outputs to the logic indicators.
3. Apply the different combinations of inputs and observe the outputs.
4. Apply M=0 for addition operation and M=1 for subtraction operation.
5. Note down the values of c_{out} and sum in addition operation and difference and borrow in subtraction operation.

Result: 4-bit Adder / Subtractor is verified.

VIVA:

1. What is Adder?
2. What is Subtractor?
3. Define Overflow?
4. What is major difference between Half-Adder and Full-Adder?
5. What is the use of 4-bit adder?
6. Which IC is used as 4-bit binary subtractor?
7. How many inputs does a 4-bit adder have?
8. Why adder is used?
9. What is full subtractor formula?
10. What is BCD adder?

Experiment No: 5

Design and realization a 4-bit gray to Binary and Binary to Gray Converter

Aim: To Design and realization of 4-bit gray to Binary and Binary to Gray Converter

Apparatus: binary to gray logic trainer kit, Patch cords

Theory:


Binary to Gray Code Converter

The logical circuit which converts binary code to equivalent gray code is known as **binary to gray code converter**. The gray code is a non weighted code. The successive gray code differs in one bit position only that means it is a unit distance code. It is also referred as cyclic code. It is not suitable for arithmetic operations. It is the most popular of the unit distance codes. It is also a reflective code. An n-bit Gray code can be obtained by reflecting an n-1 bit code about an axis after 2^{n-1} rows, and putting the MSB of 0 above the axis and the MSB of 1 below the axis.

Reflection of Gray codes is shown below.


The 4 bits binary to gray code conversion table is given below

INPUTS				OUTPUTS			
BINARY CODE				GRAY CODE			
A	B	C	D	G1	G2	G3	G4
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

 

Grey to Binary conversion:

INPUTS				OUTPUTS			
BINARY CODE				GRAY CODE			
A	B	C	D	G ₁	G ₂	G ₃	G ₄
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

 **Procedure:**

1. Connect the circuit as per the circuit diagram.
2. Connect the inputs to the switch and outputs to the logic indicators.
3. Apply the different combinations of inputs and observe the outputs.

Result: 4-bit gray to Binary and Binary to Gray Converter is verified.

VIVA:

1. What is a code converter?
2. Give the primary use for Gray code
3. Convert binary number into gray code : 100101
4. Convert gray code into binary : 101010
5. What is GRAY in binary?
6. Which gate converts binary to gray code?
7. How do u convert BCD to GRAY?
8. Why do we use gray code?
9. Which IC is used in gray to binary?
10. Why do we convert gray code to binary?

Experiment No: 6


Design and realization of a 4-bit pseudo random sequence generator using logic gates.

Aim: To Design and realization of a 4-bit pseudo random sequence generator using logic gates.


Apparatus: logic trainer kit, patch cords

Circuit diagram:

Pin Configuration

 

Circuit diagram:

 

Truth Table:

D	Q _A	Q _B	Q _C	Q _D
1	0	0	0	0
1	1	0	0	0
1	1	1	0	0
0	1	1	1	0
1	0	1	1	1
1	1	0	1	1
0	1	1	0	1
0	0	1	1	0
1	0	0	1	1
0	1	0	0	1
1	0	1	0	0
0	1	0	1	0
0	0	1	0	1
0	0	0	1	0
0	0	0	0	1
1	0	0	0	0

Procedure:

1. Connect the circuit as per the circuit diagram.
2. Connect the XNOR gate output to the D input and inputs to XNOR gate are from third and fourth flip flop.
3. Connect outputs of all the flip flops to LED's.
4. Connect the clock and clear inputs as shown in diagram.
5. Observe the output on the LED's.

Result: Designed and realized a 4-bit pseudo random sequence generator using logic gates.

VIVA:

1. What are the 4 types of flip flops?
2. Sequence generator used for?
3. What's the sequence generator?
4. What is the logic gate theory?
5. What is pseudo random sequence?
6. Where is sequence used?
7. Is a sequence generator a type of circuit?
8. What are the 4 types of sequence?
9. What is the sequence formula?
10. Why is sequence important?

Experiment No: 7


8-bit parallel load and serial out shift register using flip-flops.

Aim: To Design and realize an 8-bit parallel load and serial out shift register using flip-flops.


Apparatus: PISO trainer kit, patch cords

Theory:


Parallel-in/ serial-out shift registers do everything that the previous serial-in/ serial-out shift registers do plus input data to all stages simultaneously. The parallel-in/ serial-out shift register stores data, shifts it on a clock by clock basis, and delays it by the number of stages times the clock period. In addition, parallel-in/ serial-out really means that we can load data in parallel into all stages before any shifting ever begins. This is a way to convert data from a *parallel* format to a *serial* format. By parallel format we mean that the data bits are present simultaneously on individual wires, one for each data bit as shown below. By serial format we mean that the data bits are presented sequentially in time on a single wire or circuit as in the case of the “data out” on the block diagram below.

 

 A 4-bit parallel in/serial out shift register.



Timing Diagram:

 

Procedure:

1. Connect the circuit as per circuit diagram.
2. Connect the CLK to CLK I/P as shown above.
3. Connect D₀, D₁, D₂, D₃ and Shift/Load to input switches.
4. If shift/load = 0 inputs are loaded into flipflops and shift/load = 1 shift operation is performed.
5. Observe the serial output at the last flipflop.

Result: 8-bit parallel load and serial out shift register using flip-flops is verified.

VIVA: 1. What is parallel and serial out shift register?

2. What is an 8-bit shift register?
3. What is the principle of Sipo?
4. What is meant by the parallel load of shift register?
5. What are the types of shift register?
6. What is the use of shift register?
7. What is parallel register?
8. What are two functions of a shift register?
9. What are the applications of register?
10. What is the difference b/w register and counter?

Experiment No: 8

Synchronous and Asynchronous counter using flip-flops

Aim: To Design and realization of a Synchronous and Asynchronous counters using flip-flops

Apparatus:


Counters trainer kit, patch cords

Theory:

Since we know that binary count sequences follow a pattern of octave (factor of 2) frequency division, and that J-K flip-flop multivibrators set up for the “toggle” mode are capable of performing this type of frequency division, we can envision a circuit made up of several J-K flip-flops, cascaded to produce four bits of output. The main problem facing us is to determine *how* to connect these flip-flops together so that they toggle at the right times to produce the proper binary sequence.


The **Synchronous Counter**, the external clock signal is connected to the clock input of EVERY individual flip-flop within the counter so that all of the flip-flops are clocked together simultaneously (in parallel) at the same time giving a fixed time relationship. In other words, changes in the output occur in “synchronisation” with the clock signal.

Asynchronous up counter:

 


Asynchronous up counter


Asynchronous Down counter:


 


Synchronous up counter:

 

Synchronous Down counter:

 

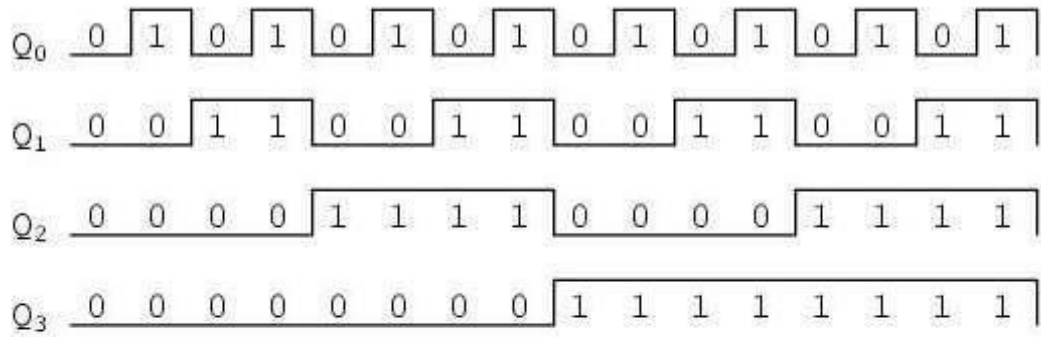 "Up" count sequence*"Down" count sequence***Truth table:****Up Counter:**

Clock Pulse	Decimal No.	Q_3	Q_2	Q_1	Q_0
1 st	0	0	0	0	0
2 nd	1	0	0	0	1
3 rd	2	0	0	1	0
4 th	3	0	0	1	1
5 th	4	0	1	0	0
6 th	5	0	1	0	1
7 th	6	0	1	1	0
8 th	7	0	1	1	1
9 th	8	1	0	0	0
10 th	9	1	0	0	1
11 th	10	1	0	1	0
12 th	11	1	0	1	1
13 th	12	1	1	0	0


14 th	13	1	1	0	1
15 th	14	1	1	1	0
16 th	15	1	1	1	1

Down counter:


Clock Pulse	Decimal No.	Q ₃	Q ₂	Q ₁	Q ₀
1 st	15	1	1	1	1
2 nd	14	1	1	1	0
3 rd	13	1	1	0	1
4 th	12	1	1	0	0
5 th	11	1	0	1	1
6 th	10	1	0	1	0
7 th	9	1	0	0	1
8 th	8	1	0	0	0
9 th	7	0	1	1	1
10 th	6	0	1	1	0
11 th	5	0	1	0	1
12 th	4	0	1	0	0
13 th	3	0	0	1	1
14 th	2	0	0	1	0
15 th	1	0	0	0	1
16 th	0	0	0	0	0

Circuit Diagram:

Asynchronous up counter:

 

Asynchronous down counter:

 

Truth table:

Up Counter:

Clock Pulse	Decimal No.	Q ₃	Q ₂	Q ₁	Q ₀
1 st	0	0	0	0	0
2 nd	1	0	0	0	1
3 rd	2	0	0	1	0
4 th	3	0	0	1	1
5 th	4	0	1	0	0
6 th	5	0	1	0	1
7 th	6	0	1	1	0
8 th	7	0	1	1	1
9 th	8	1	0	0	0
10 th	9	1	0	0	1
11 th	10	1	0	1	0
12 th	11	1	0	1	1
13 th	12	1	1	0	0
14 th	13	1	1	0	1
15 th	14	1	1	1	0
16 th	15	1	1	1	1

Down counter:

Clock Pulse	Decimal No.	Q ₃	Q ₂	Q ₁	Q ₀
1 st	15	1	1	1	1
2 nd	14	1	1	1	0
3 rd	13	1	1	0	1
4 th	12	1	1	0	0
5 th	11	1	0	1	1
6 th	10	1	0	1	0
7 th	9	1	0	0	1
8 th	8	1	0	0	0
9 th	7	0	1	1	1
10 th	6	0	1	1	0
11 th	5	0	1	0	1
12 th	4	0	1	0	0
13 th	3	0	0	1	1
14 th	2	0	0	1	0
15 th	1	0	0	0	1
16 th	0	0	0	0	0

Procedure:

1. Connect the circuit as per circuit diagram.
2. Connect the CLK to CLK I/P as shown in fig.
3. Verify the truth tables.

Result: Design and realization of a Synchronous and Asynchronous counters using flip-flops are verified.

VIVA:

1. Differentiate asynchronous and synchronous counters?
2. Why do we use asynchronous counter?
3. What is another name for asynchronous counter?
4. What are the types of synchronous counter?
5. Draw the 2-bit synchronous counter?
6. What is the principle of Asynchronous counter?
7. Where is asynchronous used?
8. Which is faster synchronous or asynchronous?
9. Draw 2-bit asynchronous counter?
10. Why is it called asynchronous?

Experiment No: 9**8x1 Multiplexer using 2x1 Multiplexer****Aim:**


To Design and realization of 8x1 using 2x1 mux

Apparatus:

Trainer kit, Patch cords

Theory:

This is an 8X1 MUX with inputs d0,d1,d2,d3,d4,d5,d6,d7 , Y as output and S2, S1, S0 as selection lines. The output will depend upon the combination of S2,S1 & S0 as shown in the truth table.

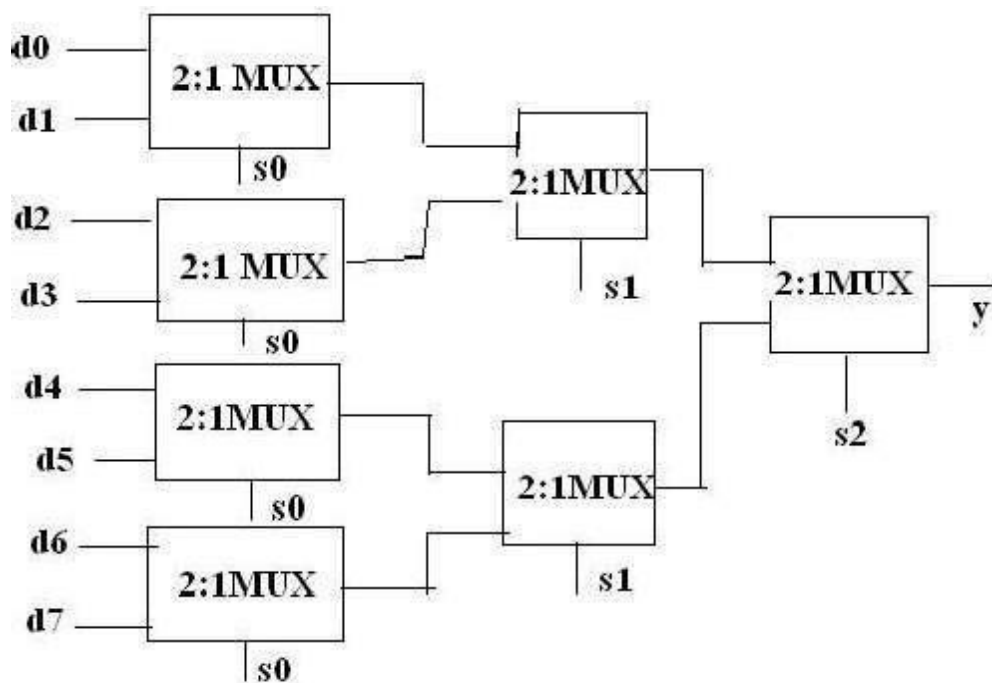Circuit Diagram:

Truth table:

Select Data Inputs			Output
S_2	S_1	S_0	Y
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

Procedure:

1. Connect the circuit as per circuit diagram.
2. Connect D_0 to D_7 to the input switches.
3. Connect selection line inputs to the input switches.
4. Connect the output terminal Y to the output indicator (LED).
5. Verify the truth table given above.

Result: Design and realization of 8x1 using 2x1 mux is done.

VIVA:

1. write the algorithm to implement 8 x 1 multiplexer using 2 x 1 multiplexer?
2. How does a 8X1 multiplexer work?
3. Can we design a 4x1 mux with two 2x1 multiplexers?
4. What is the Boolean function of 8 to 1 multiplexer?
5. What is the Boolean function of 2 to 1 multiplexer?
6. What are the applications of MUX?
7. Why is multiplexer called universal gate?
8. What is the logic function of MUX?
9. What is the full form of MUX?
- 10 Which IC is used for MUX?

Experiment No: 10

Design and realization 4-bit comparator Aim:

To verify the truth table of 4-bit Comparator.

Apparatus: MTS-COMPARATOR KIT,

PATCH CORDS

Theory:


A magnitude digital Comparator is a combinational circuit that compares two digital or binary numbers in order to find out whether one binary number is equal, less than or greater than the other binary number. We logically design a circuit for which we will have two inputs one for A and other for B and have three output terminals, one for $A > B$ condition, one for $A = B$ condition and one for $A < B$ condition.

A comparator used to compare two bits is called a single bit comparator. It consists of two inputs each for two single bit numbers and three outputs to generate less than, equal to and greater than between two binary numbers.

A comparator used to compare two binary numbers each of two bits is called a 2-bit Magnitude comparator. It consists of four inputs and three outputs to generate less than, equal to and greater than between two binary numbers.

A comparator used to compare two binary numbers each of four bits is called a 4-bit magnitude comparator. It consists of eight inputs each for two four bit numbers and three outputs to generate less than, equal to and greater than between two binary numbers.

Pin diagram:

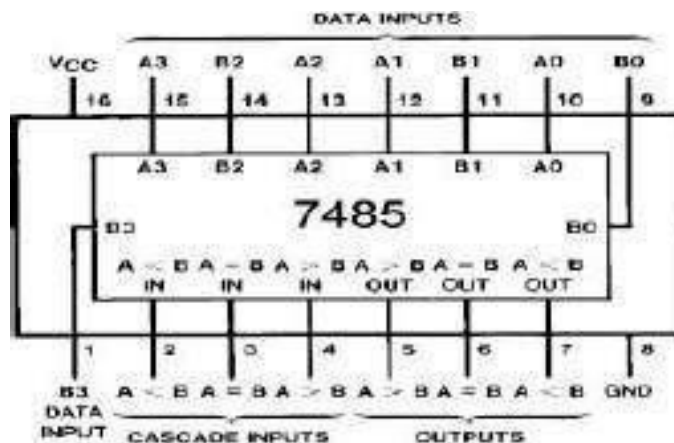

Truth Table:

COMPARING INPUTS				CASCADING INPUTS			OUTPUTS		
A3,B3	A2,B2	A1,B1	A0,B0	A>B	A<B	A=B	A>B	A<B	A=B
A3>B3	X	X	X	X	X	X	H	L	L

A3<B3	X	X	X	X	X	X	L	H	L
A3=B3	A2>B2	X	X	X	X	X	H	L	L
A3=B3	A2<B2	X	X	X	X	X	L	H	L
A3=B3	A2=B2	A1>B1	X	X	X	X	H	L	L
A3=B3	A2=B2	A1<B1	X	X	X	X	L	H	L
A3=B3	A2=B2	A1=B1	A0>B0	X	X	X	H	L	L
A3=B3	A2=B2	A1=B1	A0<B0	X	X	X	L	H	L
A3=B3	A2=B2	A1=B1	A0=B0	H	L	L	H	L	L
A3=B3	A2=B2	A1=B1	A0=B0	L	H	L	L	H	L
A3=B3	A2=B2	A1=B1	A0=B0	L	L	H	L	L	H
A3=B3	A2=B2	A1=B1	A0=B0	X	X	H	L	L	H
A3=B3	A2=B2	A1=B1	A0=B0	H	H	L	L	L	L
A3=B3	A2=B2	A1=B1	A0=B0	L	L	L	H	H	L

Procedure:

1. Connect the trainer kit to ac power supply.
2. Connect Inputs (A0,A1,A2,A3,B0,B1,B2,B3) to Input Switches
3. Connect Cascade Inputs (A<B,A>B,A=B) to Input Switches
4. Connect Outputs (A<B,A>B,A=B) to Output Switches.
5. Connect the inputs of first stage to logic sources and output of the last gate to logic indicator.
6. Apply various input combinations and observe output for each one.
7. Verify the truth table for each input/ output combination.
8. Repeat the process for all logic functions.
9. Switch off the ac power supply.

Result: Truth table of 4-bit Comparator is verified.

VIVA:

1. What is bit comparator?
2. What is 4-bit comparator ?
3. What is the function of comparator?
4. Write an example of a 4-bit comparator?
5. Write 4-bit comparator truth table?
6. Design a 1-bit comparator?
7. Design a 2-bit comparator?
8. Design a 3-bit comparator?
9. Design a 4-bit comparator?
10. Write the Boolean expression of 2-bit comparator?

Experiment No: 11

Verification of truth tables and excitation tables

Aim: Verification of State Tables of Rs, J-k, T and D Flip-Flops using NAND & NOR Gates


APPARATUS REQUIRED: IC S 7400, 7402 Digital Trainer & Connecting leads.

BRIEF THEORY:


RS FLIP-FLOP: There are two inputs to the flip-flop defined as R and S. When I/Ps $R = 0$ and $S = 0$ then O/P remains unchanged. When I/Ps $R = 0$ and $S = 1$ the flip-flop is switches to the stable state where O/P is 1 i.e. SET. The I/P condition is $R = 1$ and $S = 0$ the flip-flop is switched to the stable state where O/P is 0 i.e. RESET. The I/P condition is $R = 1$ and $S = 1$ the flip-flop is switched to the stable state where O/P is forbidden.

- **JK FLIP-FLOP:** For purpose of counting, the JK flip-flop is the ideal element to use. The variable J and K are called control I/Ps because they determine what the flip-flop does when a positive edge arrives. When J and K are both 0s, both AND gates are disabled and Q retains its last value.
- **D FLIP -FLOP:** This kind of flip flop prevents the value of D from reaching the Q output until clock pulses occur. When the clock is low, both AND gates are disabled D can change value without affecting the value of Q. On the other hand, when the clock is high, both AND gates are enabled. In this case, Q is forced to equal the value of D. When the clock again goes low, Q retains or stores the last value of D. a D flip flop is a bistable circuit whose D input is transferred to the output after a clock pulse is received.
- **T FLIP-FLOP:** The T or "toggle" flip-flop changes its output on each clock edge, giving an output which is half the frequency of the signal to the T input. It is useful for constructing binary counters, frequency dividers, and general binary addition devices. It can be made from a J K flip flop by tying both of its inputs high.


CIRCUIT DIAGRAM:
SR Flip Flop

 

D Flip Flop

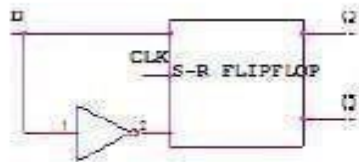

J-k flip-flop using NAND gates

 

PROCEDURE:

1. Connect the circuit as shown in figure.
2. Apply Vcc & ground signal to every IC.
3. Observe the input & output according to the truth table.

TRUTH TABLE:**SR FLIP FLOP:**

CLOCK	S	R	Q_{n+1}
1	0	0	NO CHANGE
1	0	1	0
1	1	0	1
1	1	1	?

D FLIPFLOP:

INPUT	OUTPUT
0	0
1	1

JK FLIPFLOP

CLOCK	S	R	Q_{n+1}
1	0	0	NO CHANGE
1	0	1	0
1	1	0	1
1	1	1	Q_n'

T FLIPFLOP

CLOCK	S	R	Q_{n+1}
1	0	1	NO CHANGE
1	1	0	Q_n'

RESULT: Truth table is verified on digital trainer.

VIVA:

1. What is the main use of flip-flop?
2. What is the aim of flip-flop?
3. What is flip-flop RS?
4. Why is RS flip-flop used?
5. Why is it called flip-flop?
6. Which flip-flop is most important?
7. What is T flip-flop?
8. What is full form of D flip-flop?
9. What is flip-flop clock?
10. What is the full form of JK flip flop?

Experiment No: 12


Realization of logic gates using DTL, TTL, ECL, etc.,


Aim: Realization of logic gates using DTL, TTL, ECL, etc.,

Apparatus: Logic trainer kit, Connecting wires

Theory: Diode- Transistor **Logic**, or **DTL**, refers to the technology for designing and fabricating digital **circuits** wherein **logic gates** employ diodes **in** the input stage and bipolar junction transistors at the output stage. The output BJT switches between its cut-off and saturation regions to create **logic 1** and **0**, respectively.

Circuit Diagram:

 

 

(a) Diode logic (b) resistor transistor logic and (c) diode transistor logic.

Parameter	RTL Logic Family	IIL	DTL	Standard TTL	ECL	MOS	CMOS
Basic Gate	NOR	NOR	NAND	NAND	OR- NAND	NAND	NOR - NAND
Power Dissipation in mW per gate	12	6 nW - 70 uW	8-12	10	40-55	0.2 - 10	1.01
Fan Out	5	Depends on injector current	8	10	25	20	50
Noise Immunity	Normal	Poor	Good	Very Good	Poor	Good	Very Good
Propagation Delay in ns per second	12	25-250	30	10	2	300	70
Speed Power Product	144	< 1	300	100	100	60	d.c. -0.7

Procedure:

1. Connect the trainer kit to ac power supply.
2. Connect the NOR gates for any of the logic functions to be realised.
3. Connect the inputs of first stage to logic sources and output of the last gate to logic indicator.
4. Apply various input combinations and observe output for each one.
5. Verify the truth table for each input/ output combination.
6. Repeat the process for all logic functions.
7. Switch off the ac power supply.

Result: Realization of logic gates using DTL, TTL, ECL truth tables are verified.

VIVA:

1. What is TTL also known as?
2. How many stages does DTL consist?
3. What is a disadvantage of DTL?
4. What TTL is used for?
5. Why is TTL faster than DTL?
6. What is DTL used for?
7. What is the concept of DTL?
8. What are the uses of DTL?
9. How many stages does TTL consist?
10. What are the disadvantage of TTL, ECL?

BEYOND THE SYLLBUS EXPERIMENT 1

DESIGN 450KHZ CLOCK USING NAND/NOR GATES

AIM: To generate 450KHZ clock using nand/nor gates.

APPARATUS : clock generator trainer kit, NAND & NOR IC's, Patch cords

THEORY:

Pulse generator using NAND gate


Pulse generator using NAND gate:

This simple **pulse generator using NAND gate** is very useful and can be used as clock generator for other circuits. The circuit's main element is a 2 input (Schmitt Trigger) NAND gate connected as NOT gate.

Analyzing the circuit diagram and remembering the truth table for a NAND gate, we know that when the two inputs are logic "1", the output will be at logic "0" and when the two inputs are at "0", the output will be a logical "1". Exactly the same behavior that would have a NOT gate.

How the pulse generator using NAND gate works?

 The NAND gate has at its output a square wave whose frequency depends on the values of capacitor C1 and the series combination of the potentiometer P and resistor R1.



When the output of NAND gate is High (logical 1), the capacitor C1 (which has no charge) sends a logical zero (0) at the inputs of the NAND gate. The capacitor begins to charge through the resistor and potentiometer assembly.


Once the capacitor is charged, both inputs of the gate are high (logical 1), causing its output to go low (logic zero). With the low output, capacitor discharge begins through the same set

of resistor and potentiometer in series, returning to its original state. The process is repeated continuously. You can use a 3.0V to 15V power supply.

SQUARE WAVE GENERATOR USING NAND GATE:

Square waves are extensively used in many digital circuits. Many combinational logic circuits require this wave to operate. Here are few methods you can generate simple square wave using NAND, Inverter and Schmitt Trigger gates. These kind of square wave generator fit perfectly for simple oscillator applications with minimum effort required to build.

CIRCUIT DIAGRAM:

 

Procedure :

1. Connect the circuit as per the circuit diagram .
2. Apply the different values of resistors and capacitors and the observe the frequency .
3. Repeat the process for different combinations of resistors and capacitors.
4. Compare the theoretical and practical values of frequencies.

Result: Clock generation using NAND/NOR gates is verified.

BEYOND THE SYLLBUS EXPERIMENT

Design and Realization of a sequence detector-a finite state machine

Aim: To design and realize sequence detector-a finite state machine.

Apparatus: logic gates / ICs

PATCH CORDS

Theory:

A sequence detector is a sequential state machine which takes an input string of bits and generates an output 1 whenever the target sequence has been detected. In a Mealy machine, output depends on the present state and the external input (x). Hence in the diagram, the output is written outside the states, along with inputs. Sequence detector is of two types:

Overlapping


Non-Overlapping

In an overlapping sequence detector the last bit of one sequence becomes the first bit of next sequence. However, in non-overlapping sequence detector the last bit of one sequence does not become the first bit of next sequence. In this post, we'll discuss the design procedure for non-overlapping 101 Mealy sequence detector.

Procedure:

Step 1: Develop the state diagram –

 The state diagram of a Mealy machine for a 101 sequence detector is:



Step 2: Code Assignment –

Rule 1 : States having the same next states for a given input condition should have adjacent assignments.

Rule 2: States that are the next states to a single state must be given adjacent assignments. Rule 1 given preference over Rule 2

Previous States	States	Next States
a,c	a	a,b
b,a	b	b,c
b	c	a

		x	0	1
y	0		a	b
	1		c	

Step3: Make Present State/Next State table – We'll use D-Flip Flops for design purpose.

Present States		I/p	Next States		Flip Flop Excitations		O/P
X	Y		X'	Y'	Dx	Dy	
0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	0
0	1	1	0	0	0	0	1
1	0	0	0	1	0	1	0
1	0	1	1	0	1	0	0
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

Step 4: Draw K-maps for Dx, Dy and output (Z)

XY	00	01	11	10
0	0	0	X	0
1	1	0	X	1

$Dx = \overline{Y}.I$


XY	00	01	11	10
0	0	0	X	1
1	0	0	X	0

$Dy = X.\overline{I}$

XY	00	01	11	10
0	0	0	X	0
1	0	1	X	0

$Z = Y.I$

Step 5: Finally implement the circuit

 

Result: Verified the sequence detector of sequence 101 theoretically and practically.

STUDY OF 7490 BCD COUNTER

AIM: To design IC 7490 as a decade counter with BCD count sequence

COMPONENTS REQUIRED:

IC 7490, Connecting wires& IC Trainer Kit

DECADE COUNTER: TRUTH TABLE:

PROCEDURE:

1. Check the components for their working.

QD	QC	QB	QA
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0

2. Insert the appropriate IC into the IC base.
3. Rig up the circuit as shown in the logic circuit diagram.

4. Apply various input data to the logic circuit via the input logic switches.
5. Note down the corresponding output and verify the truth table.

Note: Write the pin numbers of each gate and also write the intermediate expressions.

RESULT: Verify the respective truth tables.

STUDY OF SHIFT REGISTERS

AIM: Design and verification of SISO shift register.

LEARNING OBJECTIVE:

➤ To Study the Shift registers by using D Flip-Flops.

COMPONENTS REQUIRED: IC 7404, 7408, 7432, 7486, 7474,
Digital kit

THEORY:

SHIFT REGISTER: A register that is used to store binary information is known as a memory register. A register capable of shifting binary information either to the right or to the left is called a shift register. Shift register are classified into the following four types,

1. Serial-in Serial-out (SISO)
2. Serial-in Parallel-out (SIPO)
3. Parallel-in Serial-out (PISO)
4. Parallel-in Parallel-out (PIPO)

Serial-In Serial-Out (SISO):

CLK	Data Input	QA	QB	QC	QD
	1	1	0	0	0
	0	0	1	0	0
	1	1	0	1	0
	1	1	1	0	1
	X	X	1	1	0
	X	X	X	1	1
	X	X	X	X	1

This type of shift register accepts data serially, i.e., one bit at a time on a single input line. It produces the stored information on its single output also in serial output also in serial form. Data may be shifted left (from low to high order bits) using shift-left register or shifted right (from high to low order bits) using shift-right register.

Serial-In Parallel-Out (SIPO): It consists of one serial input, and outputs are taken from all the flip-flop parallelly. In this register, data is shifted in serially but shifted out in parallel. To shift the data out in parallel, it is necessary to have all the data available at the outputs at the same time. Once the data is stored, each bit appears on its respective output line and all the bits are available simultaneously, rather than on a bit-by-bit basis as with the serial output.

Parallel-In Serial-Out (PISO): This type of shift register accepts data parallel, i.e., the bits are entered simultaneously into their respective flip-flops rather than on a bit-by-bit basis on one line.

Parallel-In Parallel-Out (PIPO): In this type of register, data inputs can be shifted either in or out of the register in parallel.

Procedure:

1. Connect the circuit as per the circuit diagram and pin configuration of the ICs.
2. Clear all the flip-flops by applying a high signal to the clear (reset) input.
3. Feed the data into the Serial mode or Parallel mode depends upon the circuit operation.
4. Observe the output through LED's and it's verified with the help of Truth tables.

Application: 1. Used to store binary information

2. Memory register

Result : Thus the shift registers were studied in SISO similarly students can implement PISO and PIPO modes.


MONOSTABLE MULTIVIBRATOR USING IC555

AIM: To construct and study the operation of a monostablemultivibrator using IC555

APPARATUS REQUIRED:

S.no.	Components	Quantity
1.	IC bread board trainer	1
2.	Patch cards and probe	1
3.	IC555	1
4.	Resistor($3.3K\Omega$)	5
5.	Capacitor($0.1\mu f$)	3
6.	CRO	1

CIRCUIT DIAGRAM:

 

THEORY:

Monostablemultivibrator is also known as a triangular wave generator. It has one stable and one quasi stable state. The circuit is useful for generating single output pulse of time duration in response to a triggering signal. The width of the output pulse depends only on external components connected to the op-amp. The diode gives a negative triggering pulse. When the output is $+V_{sat}$, a diode clamps the capacitor voltage to $0.7V$. then, a negative going triggering impulse magnitude V_i passing through RC and the negative triggering pulse is applied to the

positive terminal.

Let us assume that the circuit is in stable state. The output V_0 is at $+V_{sat}$. The diode D_1 conducts and V_c the voltage across the capacitor 'C' gets clamped to 0.7V. the voltage at the positive input terminal through $1R_2$ potentiometer divider is $+\beta V_{sat}$. Now, if a negative trigger of magnitude V_i is applied to the positive terminal so that the effective signal is less than 0.7V. the output of the Op-Amp will switch from $+V_{sat}$ to $-V_{sat}$. The diode will now get reverse biased and the capacitor starts charging exponentially to $-V_{sat}$. When the capacitor charge V_c becomes slightly more negative than $-\beta V_{sat}$, the output of the op-amp switches back to $+V_{sat}$. The capacitor 'C' now starts charging to $+V_{sat}$ through R until V_c is 0.7V.

$$V_0 = V_f + (V_i - V_f) e^{-t/RC}.$$

$$\beta = R_2 / (R_1 + R_2)$$

If $V_{sat} \gg V_p$ and $R_1 = R_2$ and $\beta = 0.5$,

Then, $T = 0.69RC$

PROCEDURE:

1. Connections are made as per the circuit diagram.
2. Negative triggering is applied at the terminal 2.
3. The output voltage is measured by connecting the channel-1 at pin3.
4. The output voltage across capacitor is measured by connecting the channel-2 at the point 'P'.
5. Theoretically the time period is calculated by $T = 1.1R_1C_1$ where $R_1 = 10K\Omega$, $C_1 = 0.1\mu F$.
6. Practically the charging and discharging times are measured and theoretical value of time period is measured with practical value.

OBSERVATION:

Trigger	Output	Capacitor

MODELGRAPH:

 


Fig: (a): Trigger signal (b): Output Voltage (c): Capacitor Voltage

PRECAUTIONS:

1. Make the null adjustment before applying the input signal.
2. Maintain proper vcc levels.

Result: The working of the 555 timer in the monostable mode is studied.


ASTABLE MULTIVIBRATOR USING IC555

AIM: To construct and study the operation of Astablemultivibrator using IC555 Timer.

APPARATUS REQUIRED:

S.no.	Components	Quantity
1.	IC bread board trainer	1
2.	Patch cards and probe	1
3.	IC555	1
4.	Resistor(3.3K Ω)	5
5.	Capacitor(0.1 μ f)	3
6.	CRO	1

CIRCUIT DIAGRAM:

 

Circuit of The Timer 555 as an Astable Multivibrator

THEORY:

A simple OP AMP astablemultivibrator is also called square wave generator and free running oscillator .The principle for the generation of square wave output is to force an OP_AMP to operate in the saturation region $\beta=R2/(R1+R2)$ of the output is feedback to input. The output is also feedback to the negative input terminal after integrating by means of a RC LPF whenever the negative input just exceeds Vref, switching takes place resulting in a square wave output. In astablemultivibrator both states are quasi stable states.

When the output is +Vsat, the capacitor is now starts charging towards +Vsat through resistance R the voltage is held at $+\beta V_{sat}$. This condition continuous until the charge on C just exceed βV_{sat} . Then the capacitor begins to discharge towards -Vsat. Then the capacitor charges more and more negatively until its voltage just- βV_{sat} . The frequency is determined by the time it takes the capacity or to charge from- βV_{sat} and $+\beta V_{sat}$

$$V_c(t)=V_f+(V_i-V_f)e^{-t/RC}$$

$$V_c(t)=V_{sat}-V_{sat}(1+\beta)e^{-t/RC}$$

We get $T1=RC \ln((1+\beta)/(1-\beta))$

$T=2T1=2 RC \ln ((1+\beta)/(1-\beta)), V_o(p-p)=2V_{sat}$

PROCEDURE:

1. Connections are made as per the circuit diagram.
2. Pins 4 and 8 are shorted and connected to power supply $V_{cc}(+5V)$
3. Between pins 8 and 7 resistor $R1$ of $10K\Omega$ is connected and between 7 and 6 resistor $R2$ of $4.7K\Omega$ is connected. Pins 2 and 6 short circuited and Inbetween pins 1 and 5 a Capacitor of $0.01\mu F$ is connected.
4. The output is connected across the pin 3 and GND.
5. In between pins 6 and GND a Capacitor of $0.1\mu F$ is connected.
6. Theoretically with out diode charging time T_c is given by $T_c=0.69(R1+R2) C1$, Discharging time T_d is given by $T_d=0.69R2C1$ The frequency f is given by $f=1.45/(R1+2R2)C1$ %of Duty cycle is $(T_c/(T_c+T_d))*100$
7. Practically T_d and T_c are measured and wave forms are noted and theoretical Values are


verified

8. with practical values
9. Connect diode between pins 7 and 2.
10. Theoretically with diode connected charging time is given by $T_c = 0.69R_1C_1$
11. Discharging time is given by $T_d = 0.69R_2C_1$
12. Practically T_d and T_c are noted and verified with theoretical values

OBSERVATIONS:

With diode		without diode	
etical	al	etical	al

MODEL GRAPH:

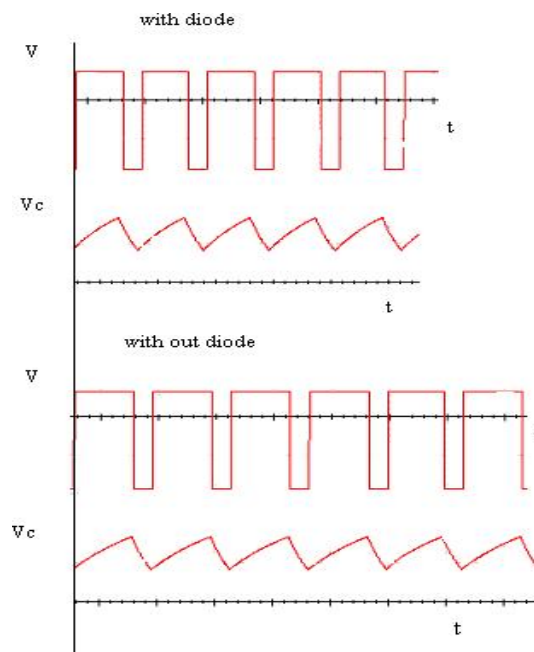

PRECAUTIONS:

1. Make null adjustment before applying the input signal.
2. Maintain proper V_c levels.

RESULT:

The working of the 555 timer in the Astable mode is studied.

Viva Questions

1. What is Multivibrator?
2. Explicate stable and Quasi stable states?
3. What is the other name of astablemultivibrator?
4. Write the expression for time delay in Monostablemultivibrator?
5. What are the applications of Monostablemultivibrator?
6. How does RC controls the pulse width?
7. What are the applications of Astablemultivibrator?
 8. What is the other name of Monostablemultivibrator?
9. How many stable states in monostablemultivibrator?
 10. What is Triggering?